
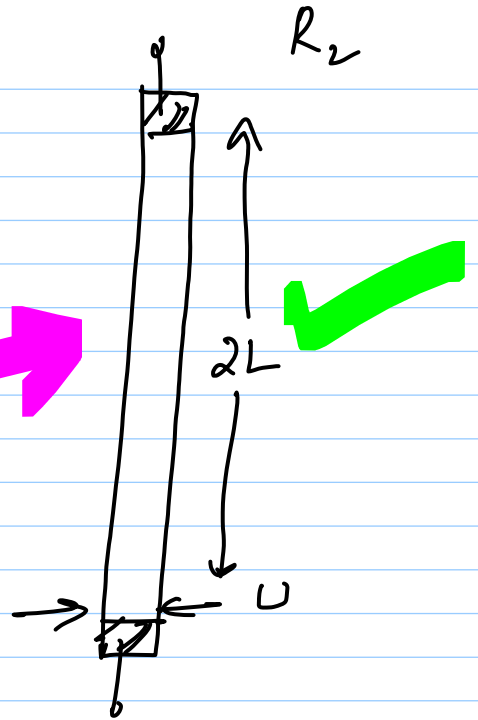
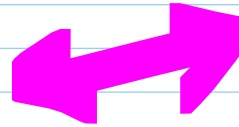


5-2-13

Lec 14




$$\frac{R_2}{R_1} = \frac{2}{1}$$

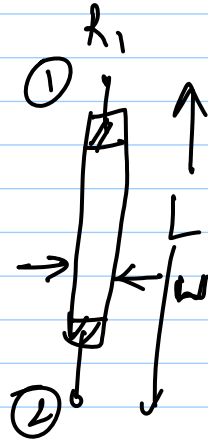

$$R_1 = R_0 + 2R_c$$

$$R_2 = 2R_0 + 2R_c$$


$$R_2' = 2R_0 + 4R_c$$

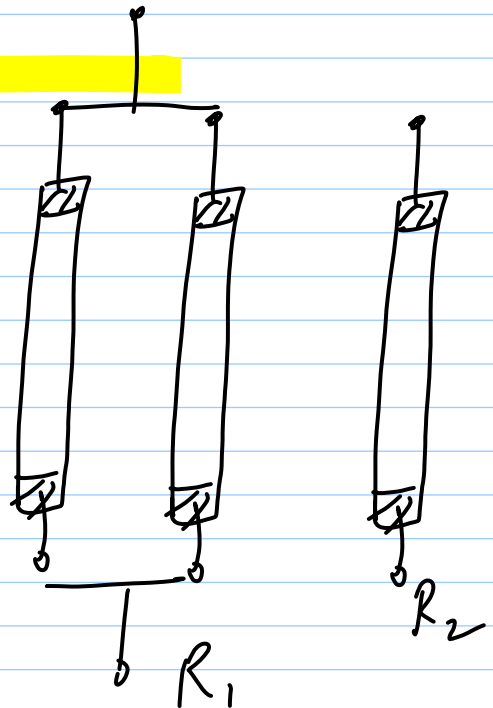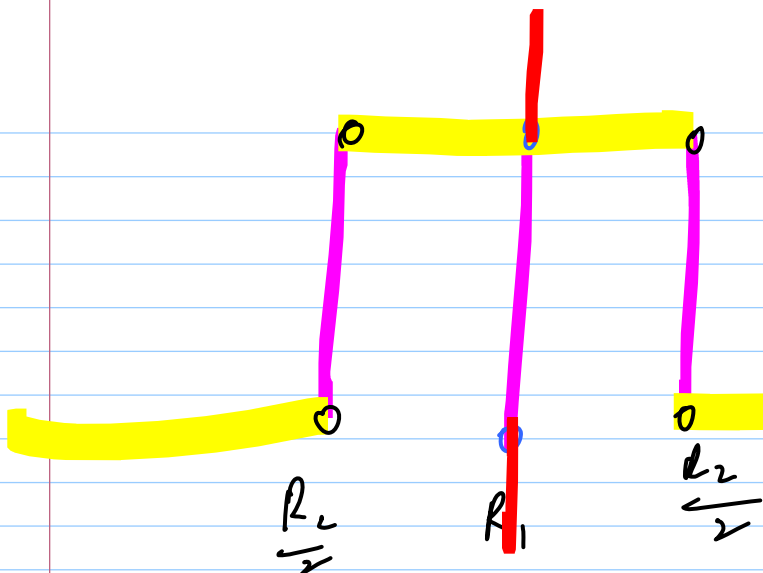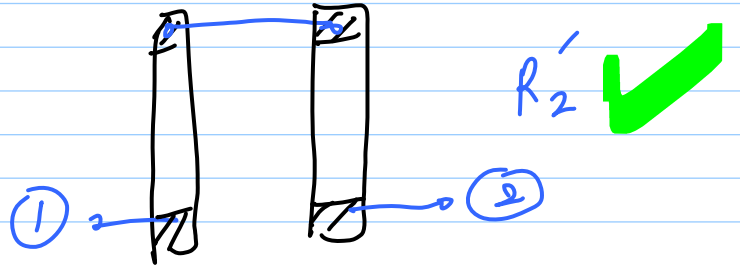


* Use identical units (can use different numbers to get multiples of R, C etc.)

* Use arrays & dummy devices to create identical surroundings

* Same orientation

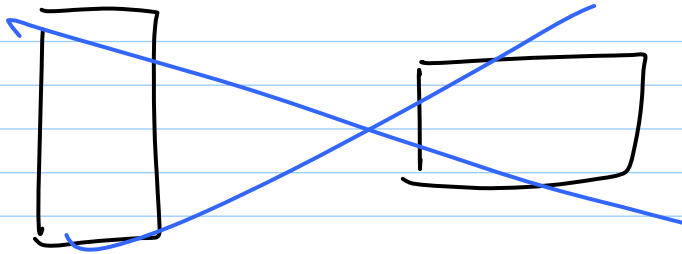

Random Mismatch

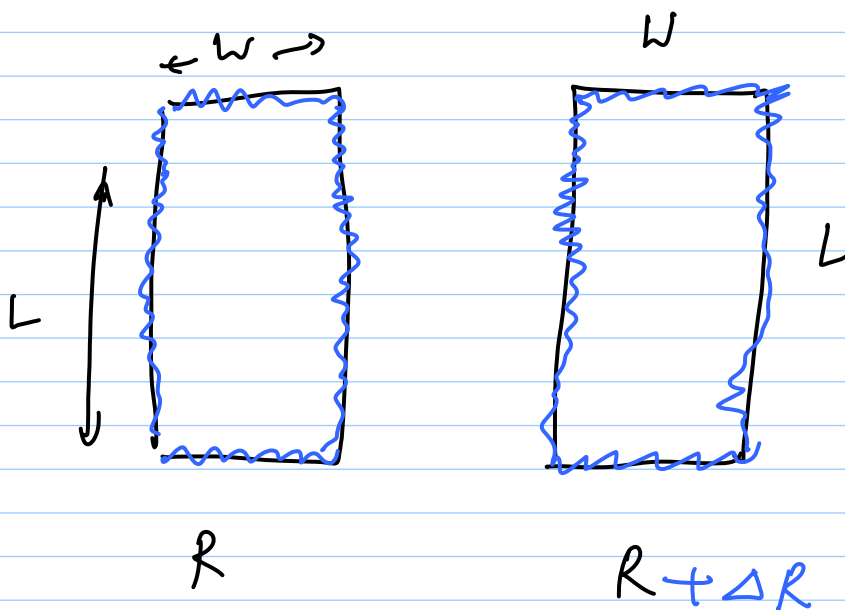

Observations


* As $W \uparrow$ & $L \uparrow \Rightarrow \frac{\Delta W}{W} \downarrow$ & $\frac{\Delta L}{L} \downarrow$
 $\Rightarrow$ larger devices exhibit smaller mismatches

* As $(W \cdot L) \uparrow$,

$$\frac{\Delta W}{W} \downarrow \text{ \& } \frac{\Delta L}{L} \downarrow$$

due to


"averaging" effect

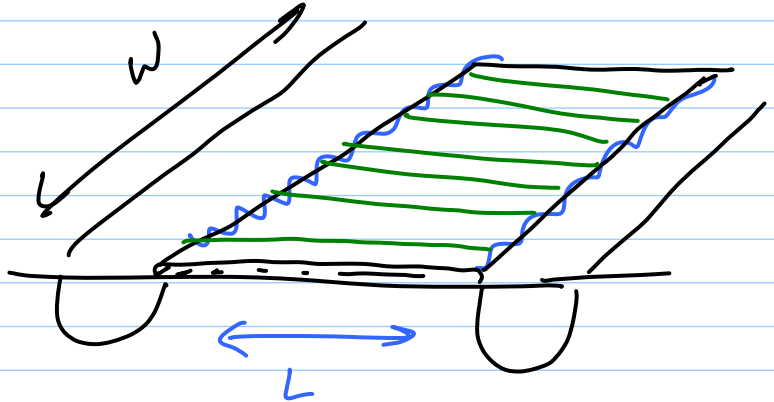

$$\sigma_{V_T} = \frac{A_{V_T}}{\sqrt{W \cdot L}} \quad \text{e.g. } A_{V_T} = 5 \text{ mV} \cdot \mu\text{m}$$

$$\sigma_{\beta} = \frac{A_{\beta}}{\sqrt{W \cdot L}} \quad \beta = \mu C_{ox}$$
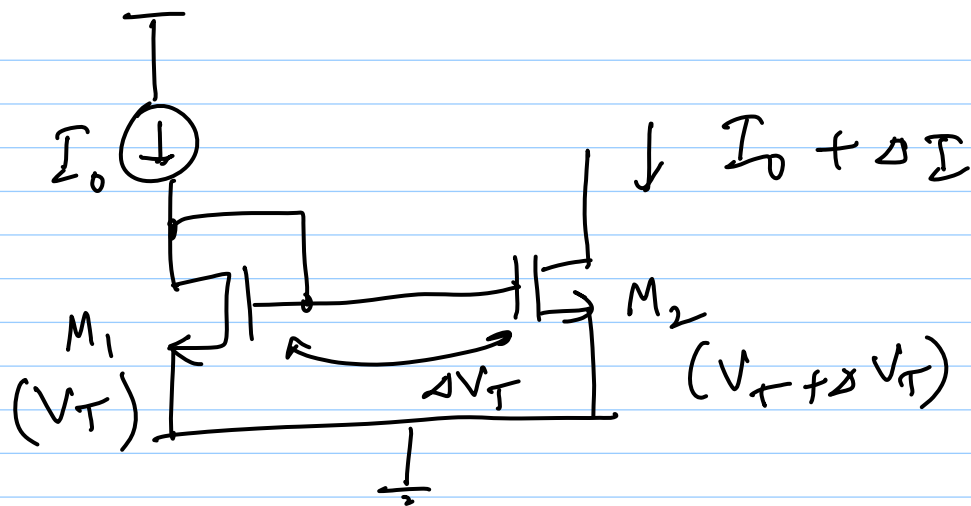
$$\left. \begin{aligned} \sigma_{\frac{\Delta R}{R}} &= \frac{A_R}{\sqrt{W \cdot L}} \\ \sigma_{\frac{\Delta C}{C}} &= \frac{A_C}{\sqrt{W \cdot L}} \end{aligned} \right) \quad \% \cdot \mu\text{m units}$$



$$\Delta I = -g_m \Delta V_T$$

$$\sigma^2(\Delta I) = g_m^2 \sigma_{V_T}^2$$


$$\sigma^2\left(\frac{\Delta I}{I_0}\right) = \frac{g_m^2}{I_0^2} \cdot \sigma_{V_T}^2 = \frac{4\sigma_{V_T}^2}{(V_{GS} - V_T)^2}$$

Mismatch Effects


* DC mismatches (e.g. Current mirror)
 * e.g. Diff. amp.

↳ Common mode gain gets worse

↳ Even order distortion

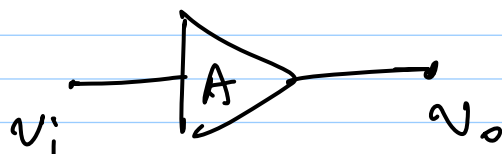
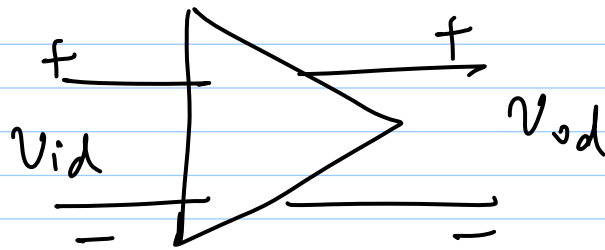
$$V_o = A_0 + A_1 V_i + A_2 V_i^2 + A_3 V_i^3 + \dots$$



$$V_{od} = f(V_{id})$$

no A_o term X

A_1 term ✓

$A_2, A_4, \dots$ X

* If 2 sides are not identical
 $\Rightarrow$ imperfect cancellation of even order terms

