
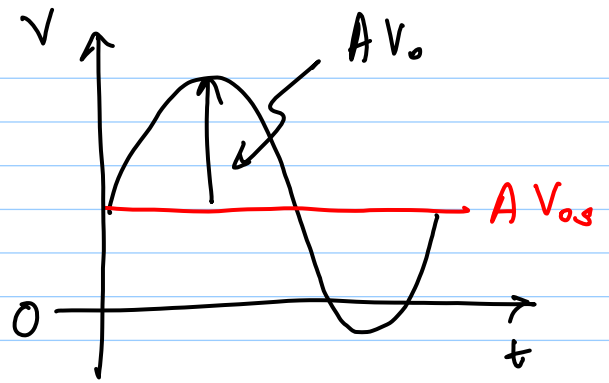



6-2-13

Lec 15

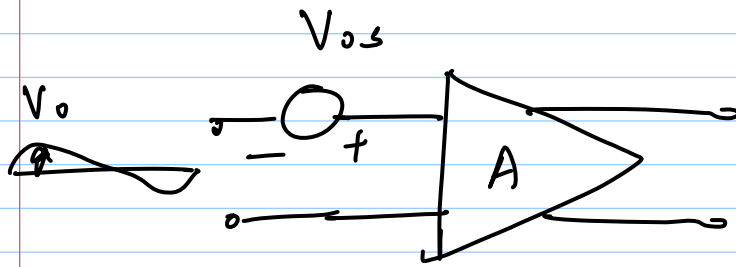


* clipping

* Saturation of gain

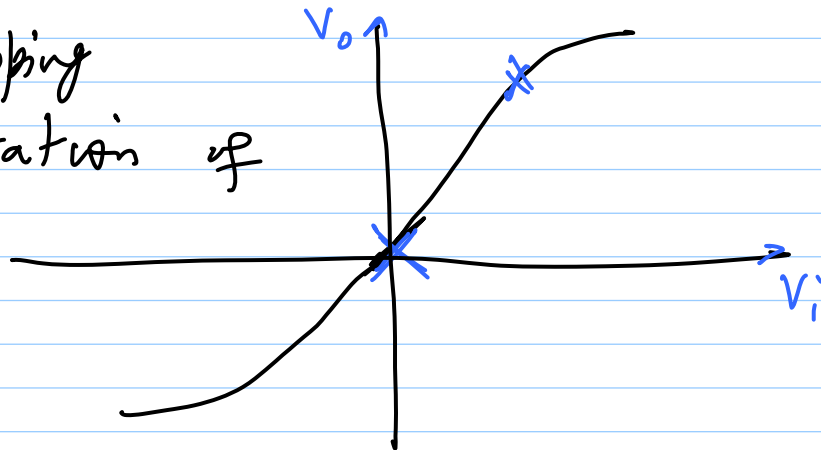

* Desensitisation

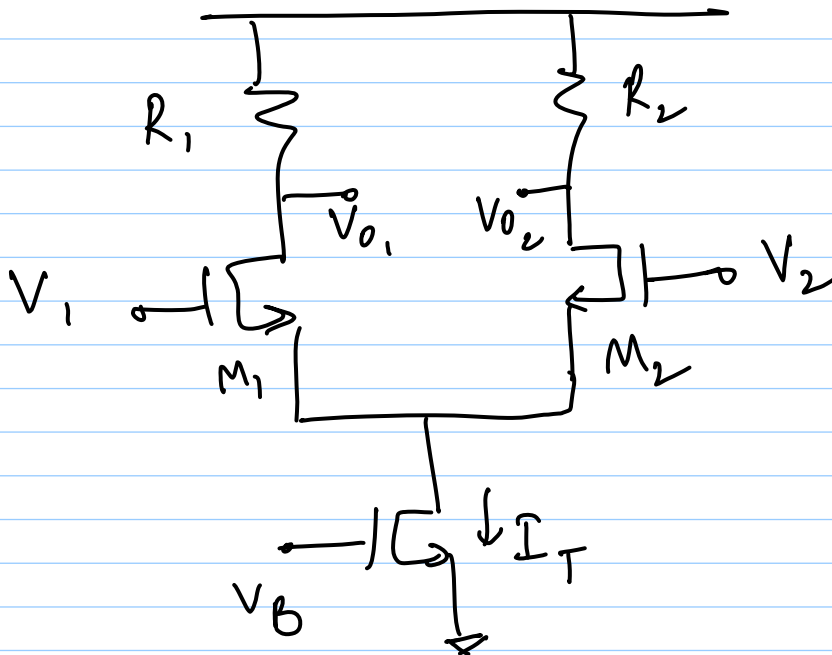

* DC offset is a function of temp. T

* Time-varying DC offsets

$$R = \frac{R_1 + R_2}{2}, \quad R_1 = R + \Delta R, \quad R_2 = R - \Delta R$$

$$\Delta R = (R_1 - R_2)/2$$

$$A \quad I_{OS} = 0$$

$$* \quad \frac{V_{O1} - V_{O2}}{A} = V_{OS}$$

$$V_{ID} = V_{as1} - V_{as2}$$

$$V_{ID} = V_1 - V_2$$

$$\rightarrow V_{ID} = V_{T1} + \sqrt{\frac{2 I_{D1}}{\beta \left(\frac{W}{L}\right)_1}} - V_{T2} - \sqrt{\frac{2 I_{D2}}{\beta \left(\frac{W}{L}\right)_2}}$$

$$= \Delta V_T + \left(\right)$$

$V_{OS} \equiv$ voltage to be applied @
input to drive $V_{OD} = 0$

$$V_{OD} = 0 \Rightarrow V_{O1} = V_{O2}$$

$$I_{D1} R_1 = I_{D2} R_2$$

$$\Delta I_D = I_{D1} - I_{D2} ; I_D = \frac{I_{D1} + I_{D2}}{2}$$

$$(\Delta W/L) = \left(\frac{W}{L}\right)_1 - \left(\frac{W}{L}\right)_2 ; \left(\frac{W}{L}\right) = \frac{(\quad)_1 + (\quad)_2}{2}$$

$$\Delta V_T = V_{T1} - V_{T2} ; V_T = \frac{V_{T1} + V_{T2}}{2}$$

$$\Delta R = R_1 - R_2 ; \quad R = \frac{R_1 + R_2}{2}$$

$$I_{D1} = I_D + \frac{\Delta I_D}{2} ; \dots$$

$$V_{OS} = \Delta V_T + \sqrt{\frac{2(I_D + \Delta I_D/2)}{\beta \left[\left(\frac{W}{L} \right) + \frac{1}{2} \frac{\Delta(W/L)}{L} \right]}}$$

$$- \sqrt{\frac{2(I_D - \Delta I_D/2)}{\beta \left[\left(\frac{W}{L} \right) - \frac{1}{2} \frac{\Delta(W/L)}{L} \right]}}$$

$$(V_{OS} - V_T) = \sqrt{\frac{2I_D}{\beta \left(\frac{W}{L} \right)}}$$

$$= \Delta V_T + (V_{OS} - V_T) \left[\sqrt{\frac{1 + \frac{\Delta I_D}{2I_D}}{1 + \frac{\Delta(W/L)}{2(W/L)}}} - \sqrt{\frac{1 - \frac{\Delta I_D}{2I_D}}{1 - \frac{\Delta(W/L)}{2(W/L)}}} \right]$$

Simplify this to:

$$V_{OS} = \Delta V_T + \frac{(V_{OS} - V_T)}{2} \left[\frac{\Delta I_D}{I_D} - \frac{\Delta(W/L)}{(W/L)} \right]$$

$$I_D, R_1 = I_{D2} R_2$$

$$\left(I_D + \frac{\Delta I_D}{2}\right) \cdot \left(R + \frac{\Delta R}{2}\right) = \left(I_D - \frac{\Delta I_D}{2}\right) \cdot \left(R - \frac{\Delta R}{2}\right)$$

$$\cancel{I_D} \cdot R + \frac{I_D \cdot \Delta R}{2} + \frac{\Delta I_D \cdot R}{2} \approx \cancel{I_D} \cdot R - \frac{\Delta I_D \cdot R}{2} - \frac{\Delta R \cdot I_D}{2}$$


$$\frac{\Delta I_D}{I_D} = -\frac{\Delta R}{R}$$

$$V_{OS} = \Delta V_T + \frac{(V_{DS} - V_T)}{2} \left[\frac{-\Delta R}{R} - \frac{\Delta(W/L)}{W/L} \right]$$

* Minimise $(V_{DS} - V_T)$ to minimise V_{OS}

* ΔV_T of M_1, M_2 directly referred to input

Offset Cancellation

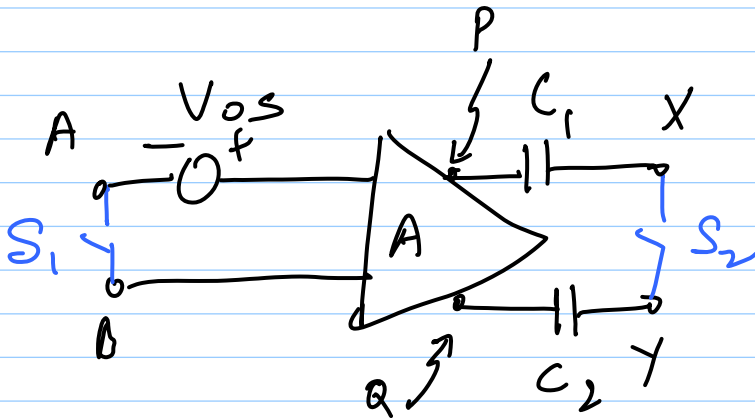

i) S_1 & S_2 are ON

$$V_{IQ} = A V_{OS} = V(C_1, C_2)$$

$$v_{xy} = 0 \quad \text{with} \quad v_{AB} \geq 0$$

2) S_1 & S_2 OFF

* $A \cdot V_{OS}$ gets sampled on C_1, C_2

* Amplifier + $C_1 - C_2$ combination between $A-B$ to $x-y$ looks like an offsetless amplifier

* Problem: saturation & desensitisation issues still exist

→ A.V_{os} exists @ amp. output