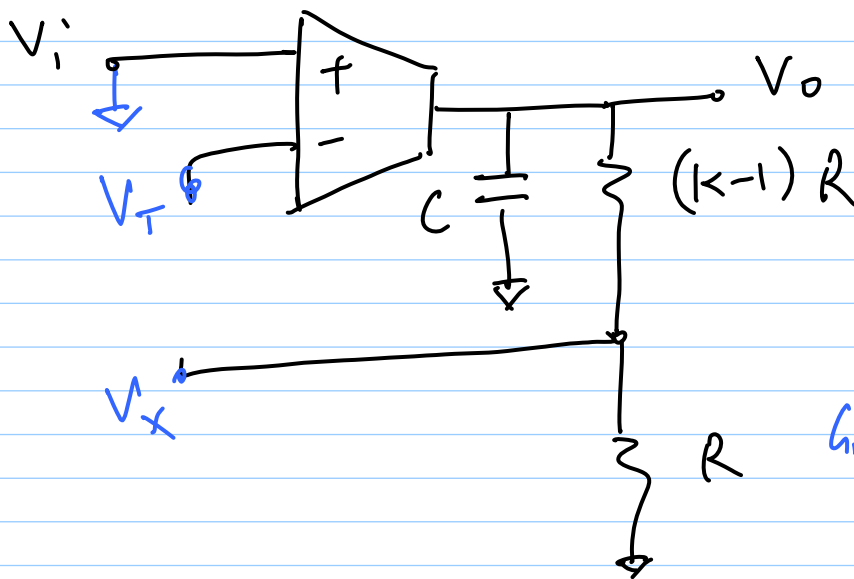


18-2-13



Lec 22



$$\omega_{p1} = \frac{1}{kRC} ; \omega_n = \frac{G_m}{C}$$

DC gain

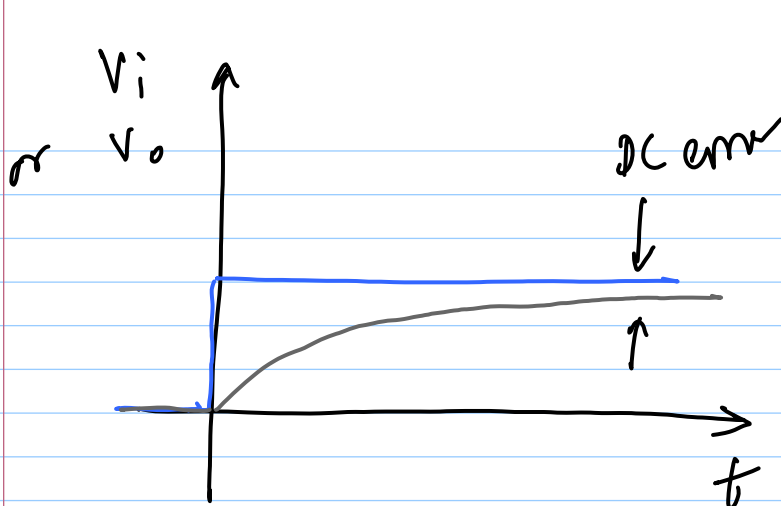
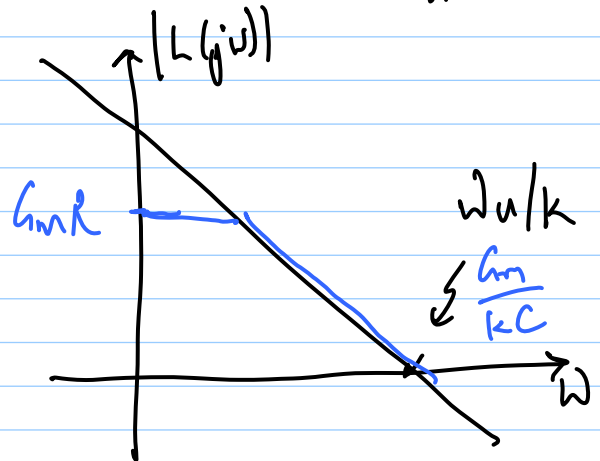
$$= \frac{G_m \cdot (kR)}{k} = G_m \cdot R$$





$\uparrow G_m$ $\rightarrow$ $\uparrow I_X$
 $\uparrow R$ $\rightarrow$ $\uparrow (W/L)$
 or both

$\uparrow (W/L) \Rightarrow \uparrow \text{parasitic cap}$
 $\Rightarrow \text{speed} \downarrow$
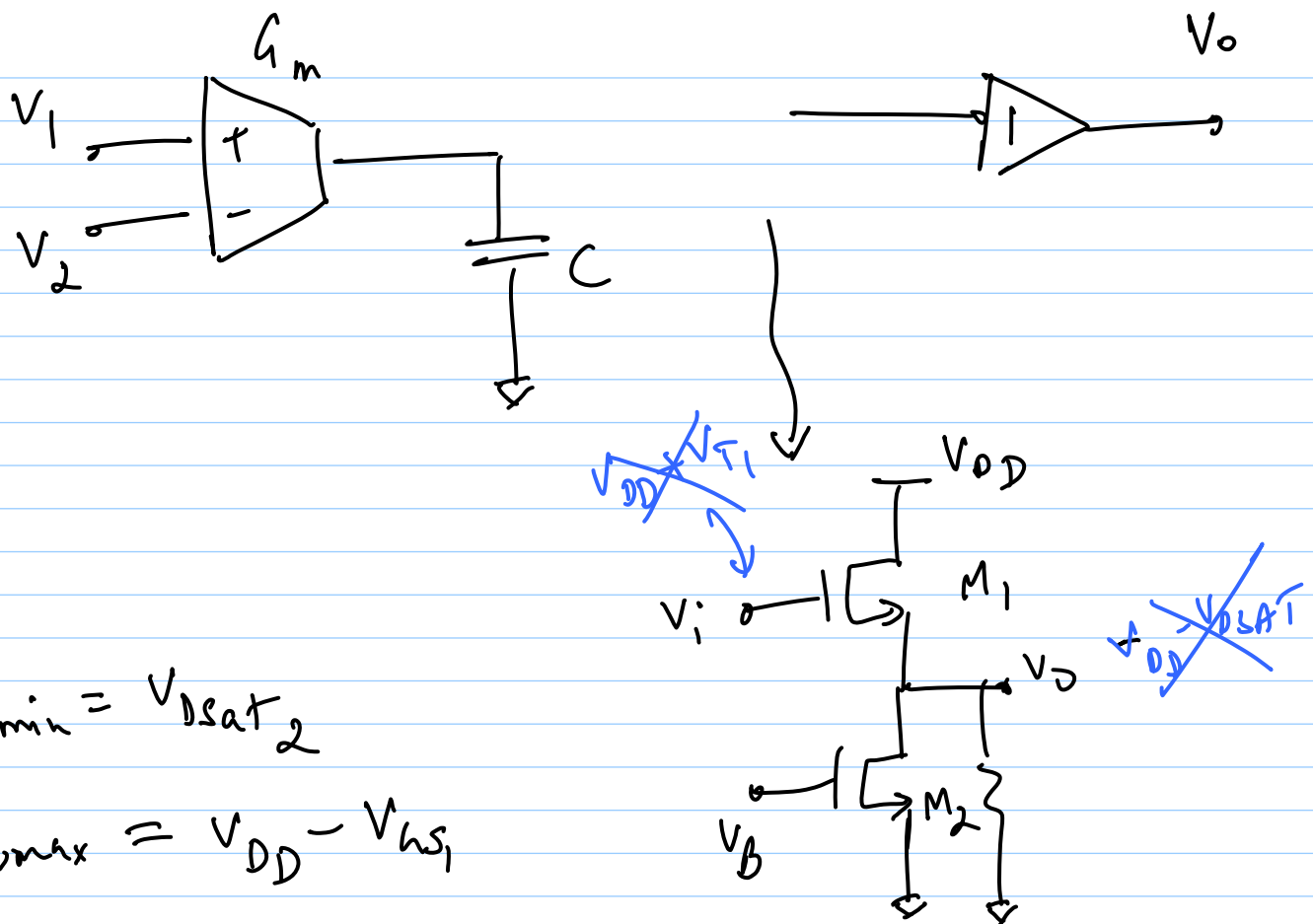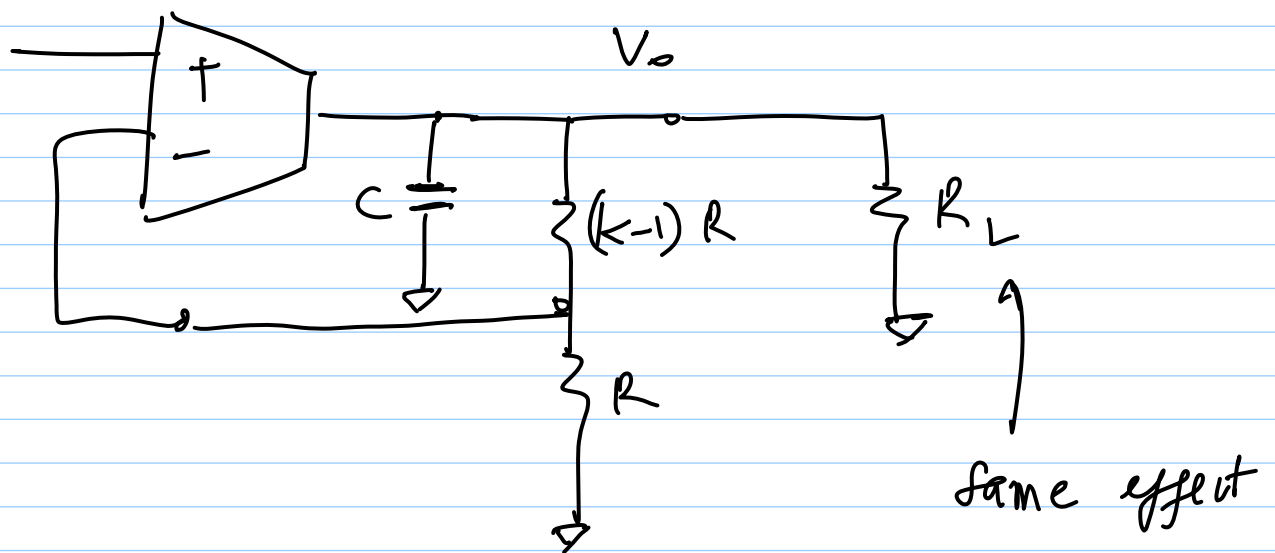
$$\frac{V_o}{V_i}(s) = \frac{G_m R}{1 + G_m R} \cdot k \cdot \frac{1}{1 + \frac{s k R C}{1 + G_m R}} \quad \left. \begin{array}{l} G_m R \gg 1 \\ C_{eq} = k \cdot \frac{1}{1 + \frac{s k R C}{G_m}} \end{array} \right\}$$






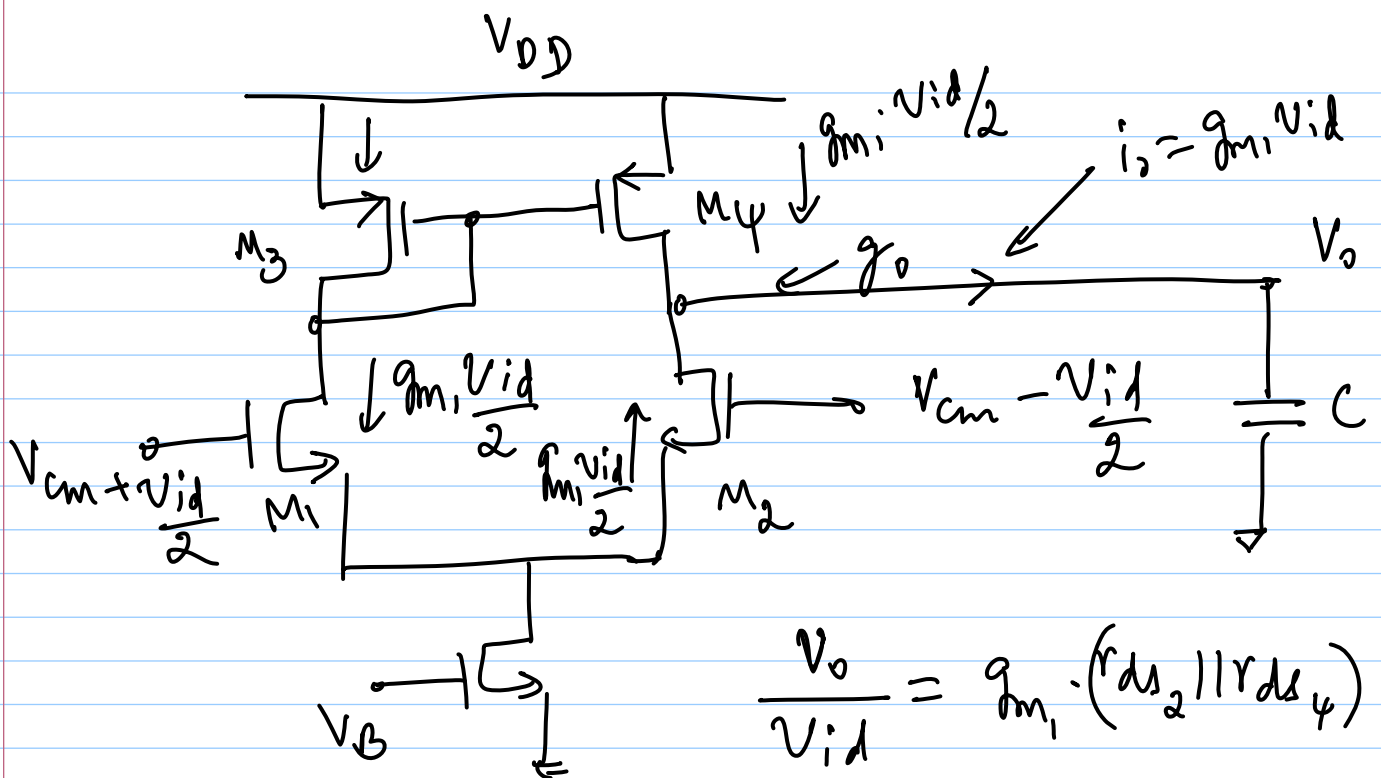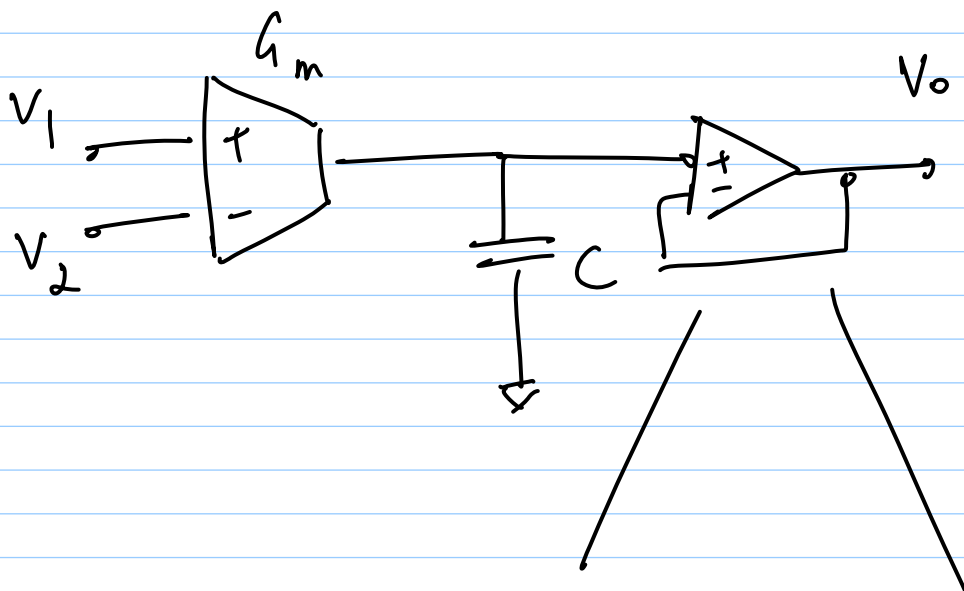

$$\frac{V_o}{V_{id}} = g_{m1} \cdot (r_{ds2} || r_{ds4})$$

w/ cap. $\Rightarrow V_o = \frac{g_m}{sC} \cdot V_{id}$

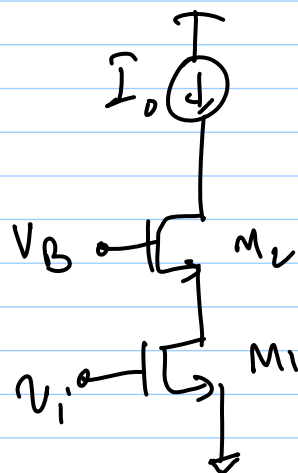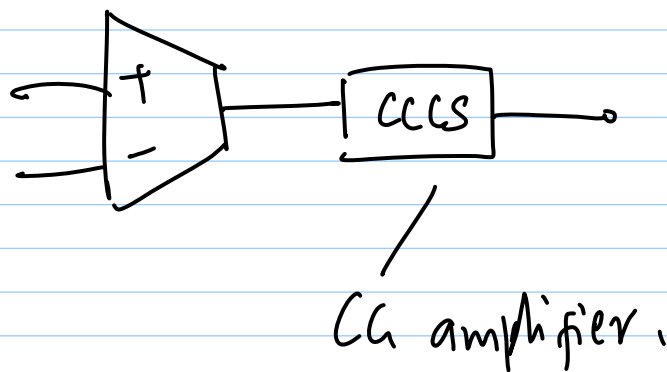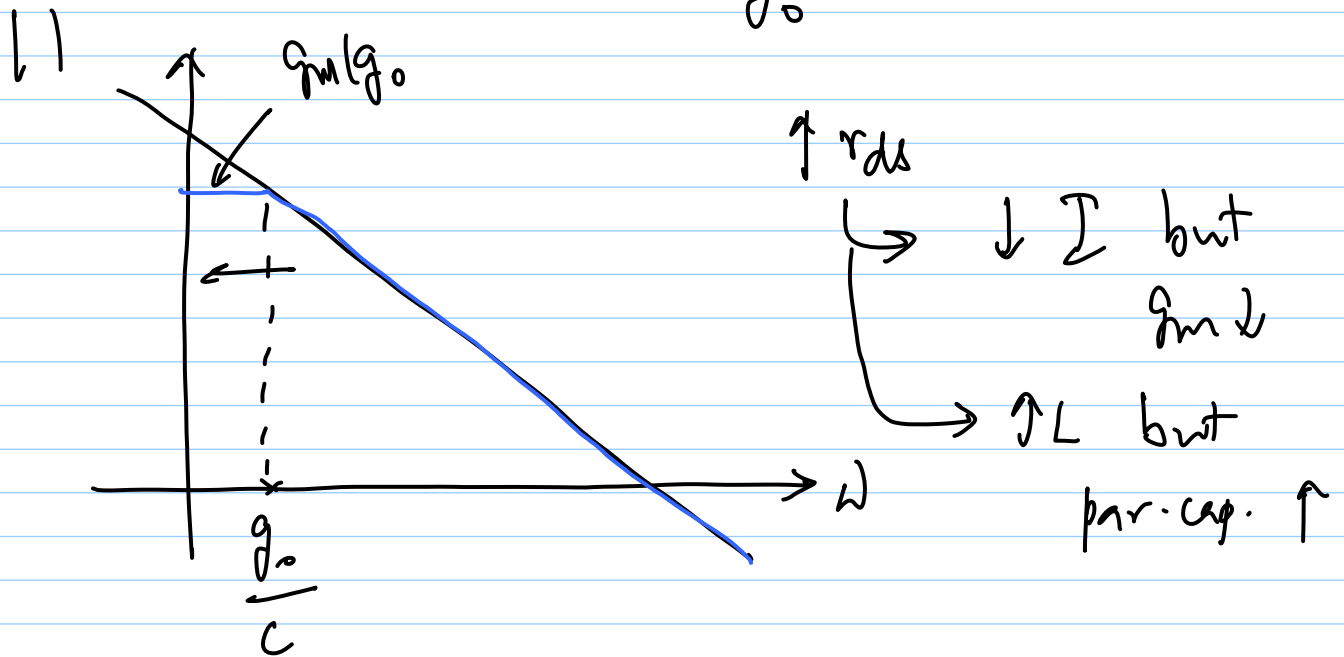
$$\frac{v_o}{v_{id}}(\Delta) = \frac{g_m}{sC + g_o}$$



$\Rightarrow$ use this in
 single stage
 opamp.

Single stage opamps

1) Don't drive resistive loads

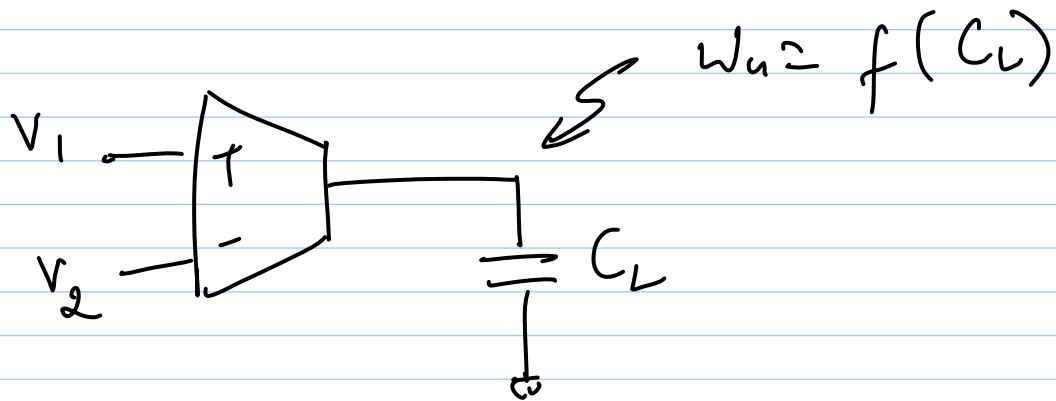

2) 1-stage

- Diff pair (simple)
- telescopic opamp
- folded cascode opamp