

5-3-13

Lec 31

$$C_c \approx \sqrt{\frac{G_{m1}}{G_{m2}} C_1 C_2} \quad \text{for PM } 7, 45^\circ$$

w/ RC pole
cancellation

In the case when $z_1 \rightarrow \infty$, PM is:

$$p_2 \approx \underbrace{A_0}_{\omega_n} p_1 \quad (\text{assume } p_3 \gg p_2)$$




$$\hookrightarrow C'_c \gg \frac{G_{m1}}{G_{m2}} \cdot C_2$$


$$C'_c = \frac{G_{m1}}{G_{m2}} \cdot C_2$$

$$C_c = \sqrt{\frac{G_{m1}}{G_{m2}} \cdot C_1 C_2}$$

$$= \underbrace{\frac{G_{m1}}{G_{m2}} \cdot C_2}_{C'_c} \cdot \underbrace{\sqrt{\frac{G_{m2}}{G_{m1}}}}_{\approx 1} \cdot \underbrace{\sqrt{\frac{C_1}{C_2}}}_{< 1}$$

$$C_c < C'_c$$

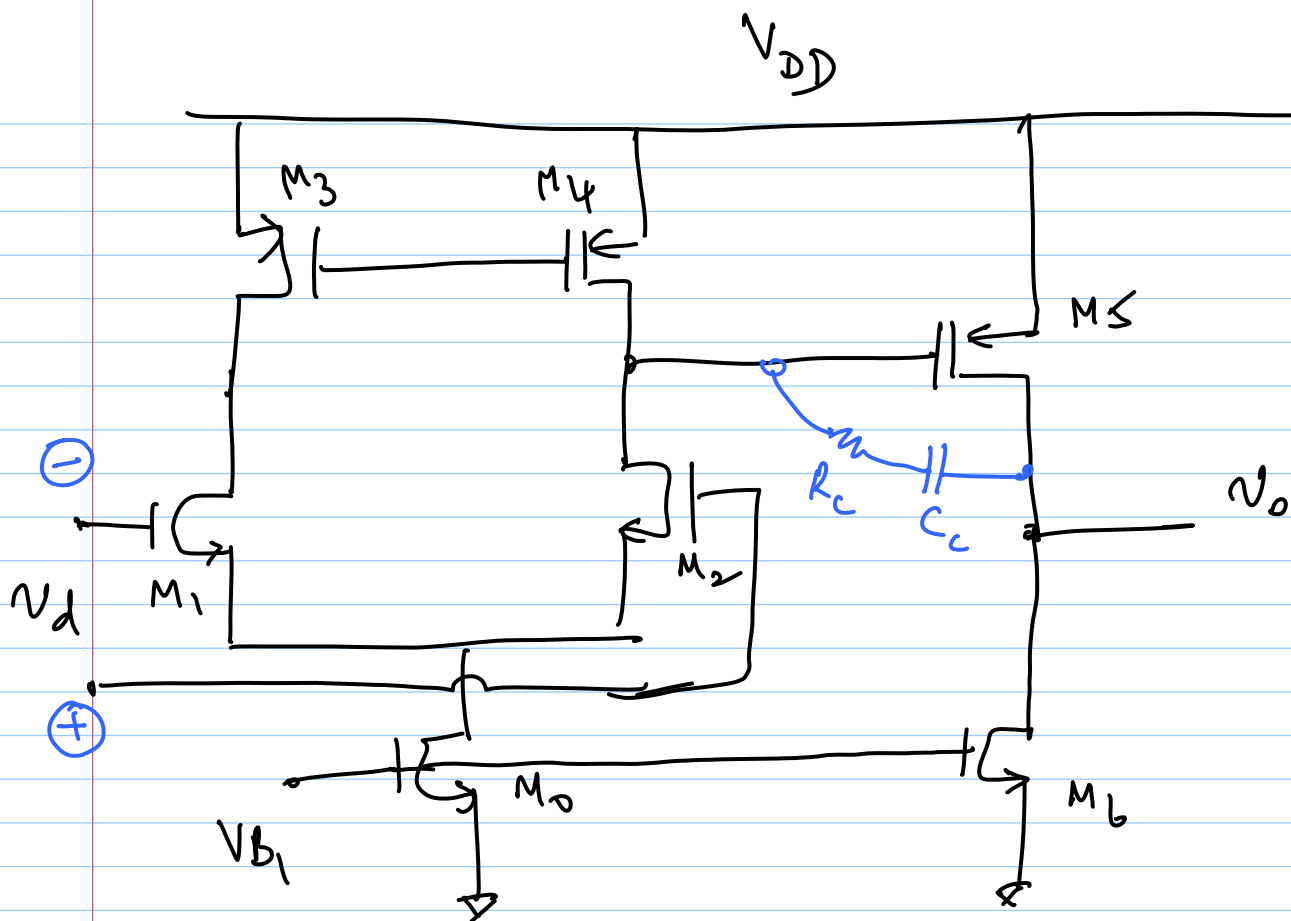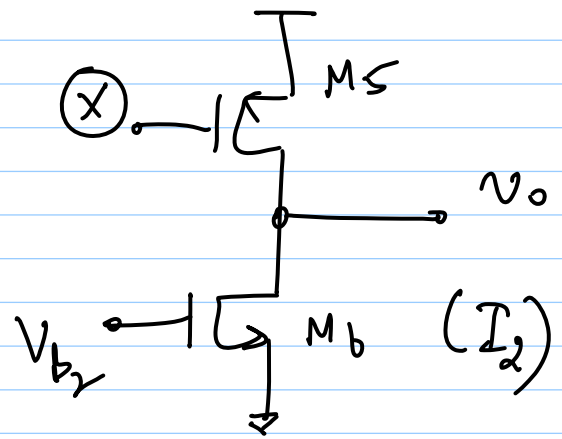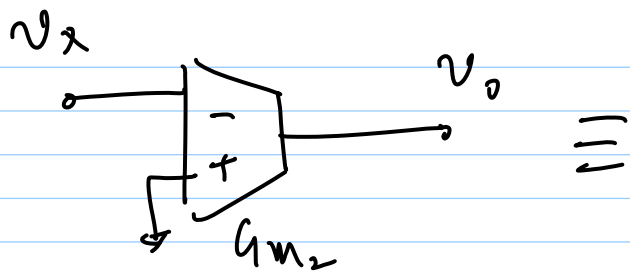

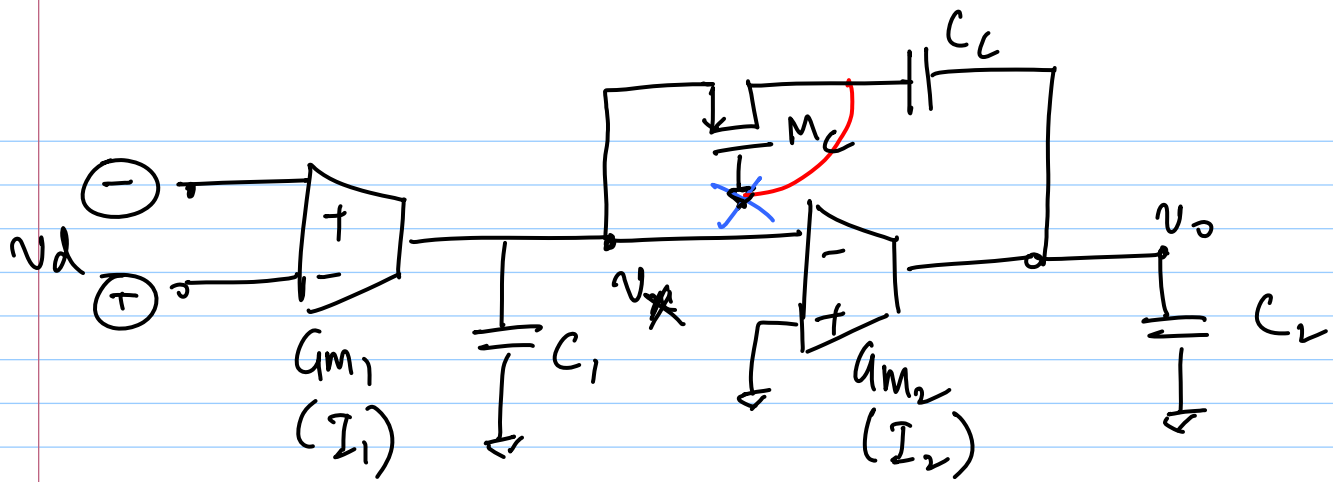


* MOSFET M_c is triode region

→ use PMOS here as $g_{m,c}$ is needed w/ pmos device

$$f_f \quad \underline{I_2} \uparrow \Rightarrow b_2 = \frac{g_{m_2}}{C_2} \uparrow$$

$$z_1 = \frac{1}{\left(R_c - \frac{1}{g_{m_2}}\right) \cdot C_2} \Rightarrow R_c \text{ should } \downarrow$$

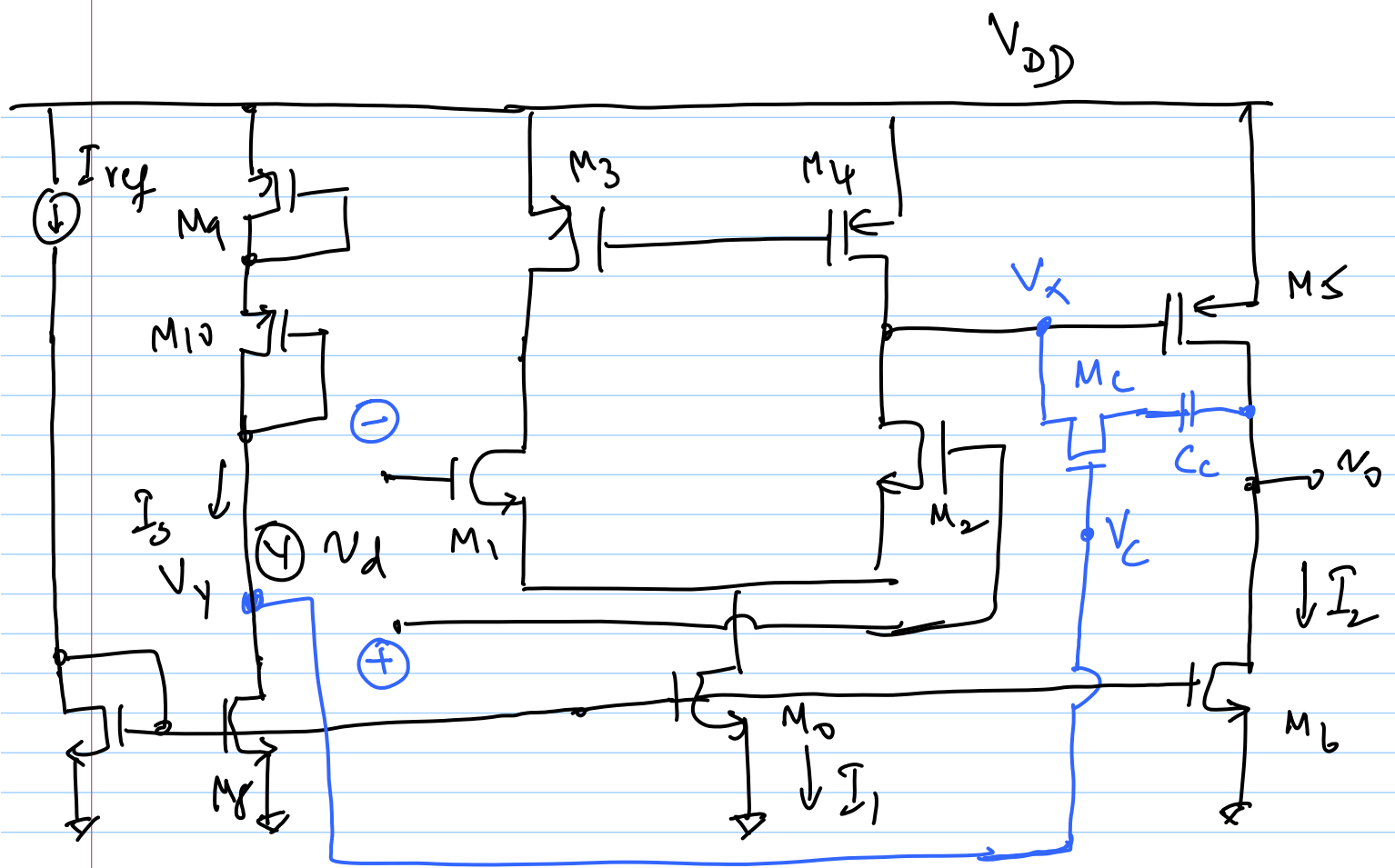→ $V_x \downarrow \Rightarrow R_c \text{ actually } \uparrow$



* 2 identically biased transistors

$$\text{sat. } g_m = \mu C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_T)$$

$$\text{non-sat } g_{de} = g_m(\text{sat.})$$

$$\underline{\text{We want}} : R_c = \frac{1}{g_{m5}} \left[1 + \frac{C_L}{C_c} \right]$$