

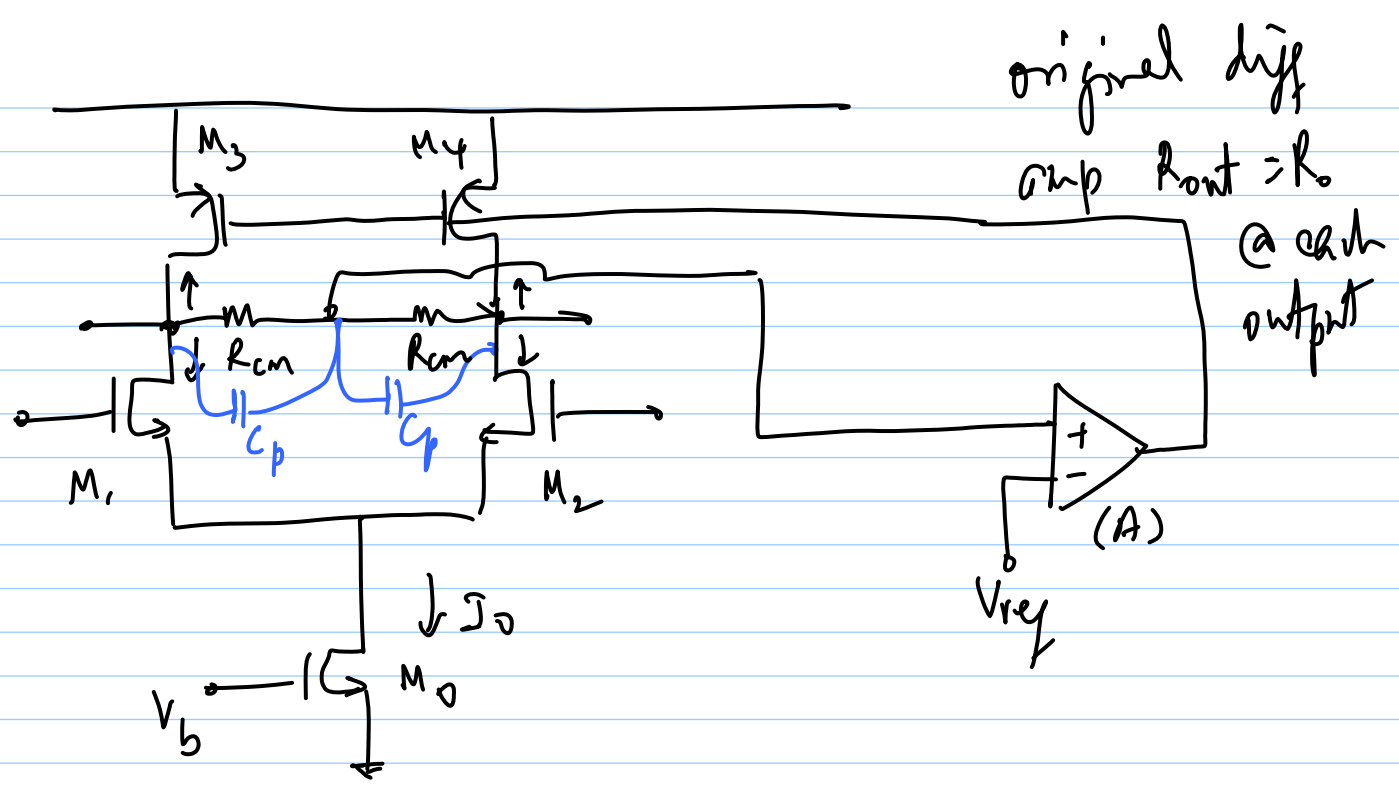
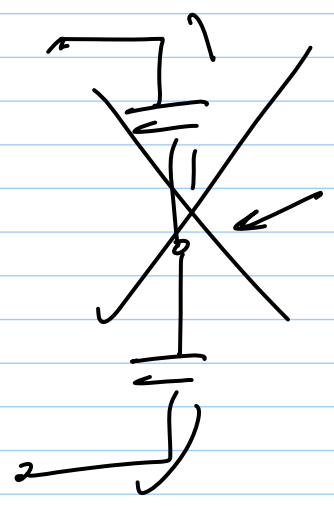


12-3-13


Lec 35


CM detector

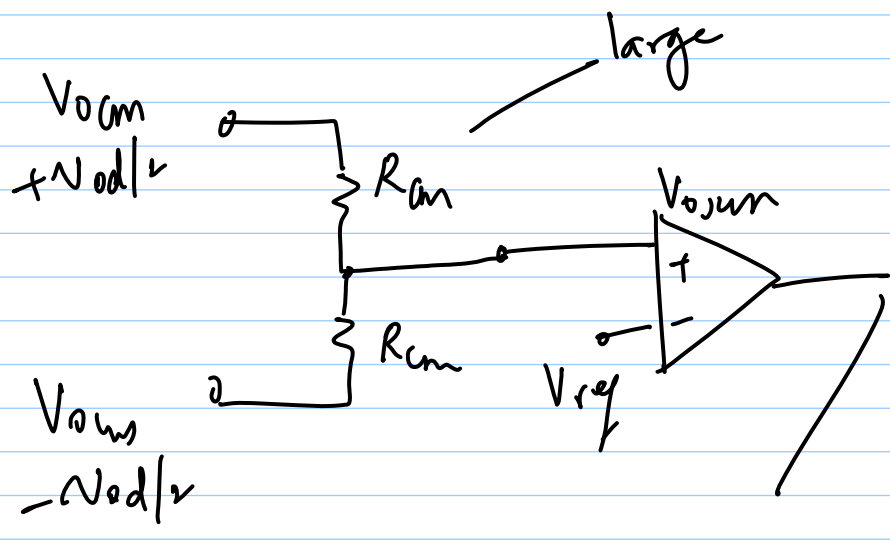

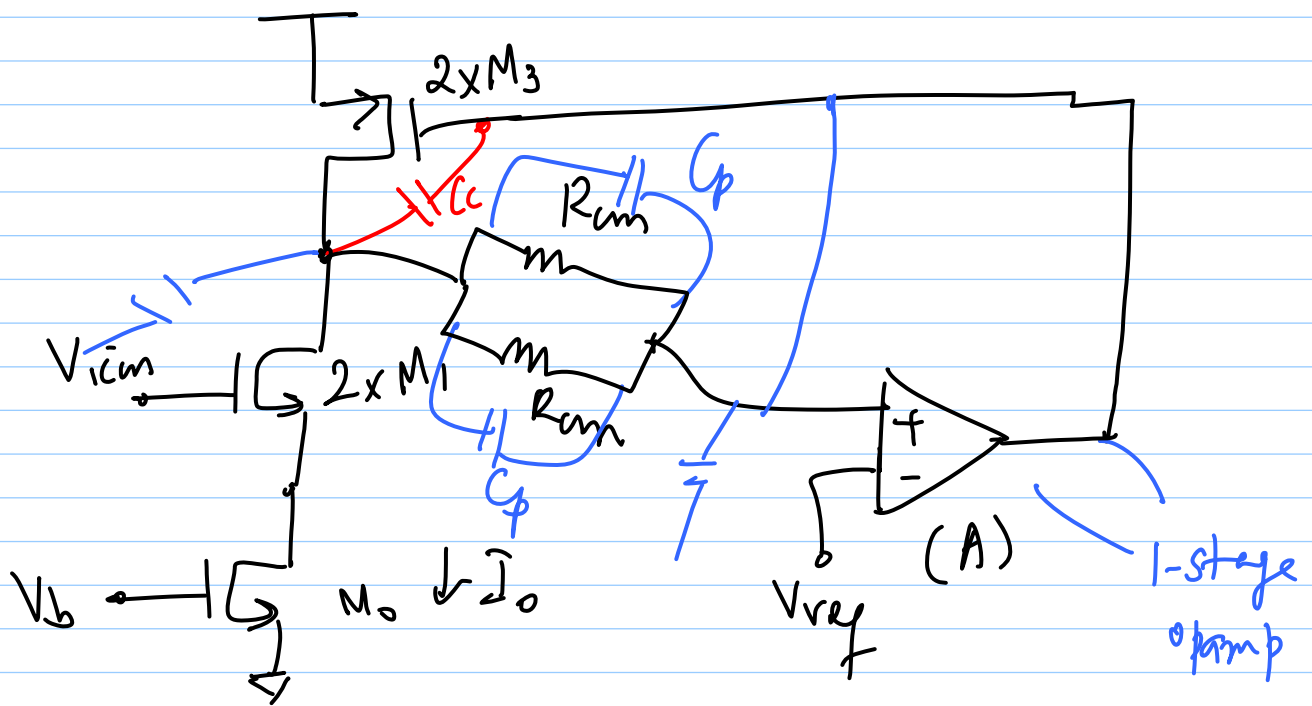
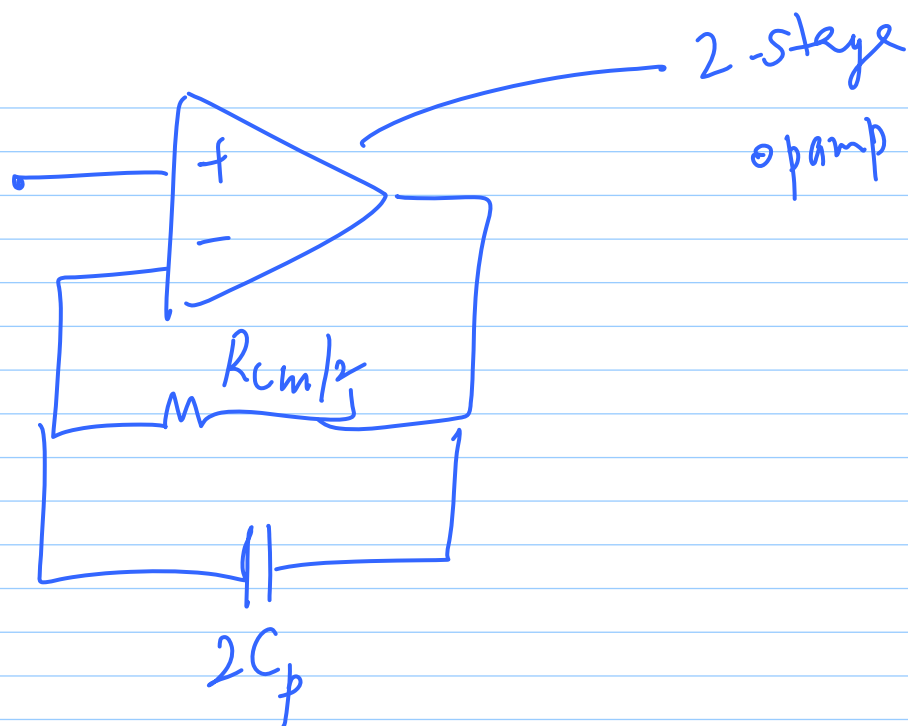
$$L_c \approx A \cdot (2g_{m3}) (R_o/2) = A g_m R_o$$



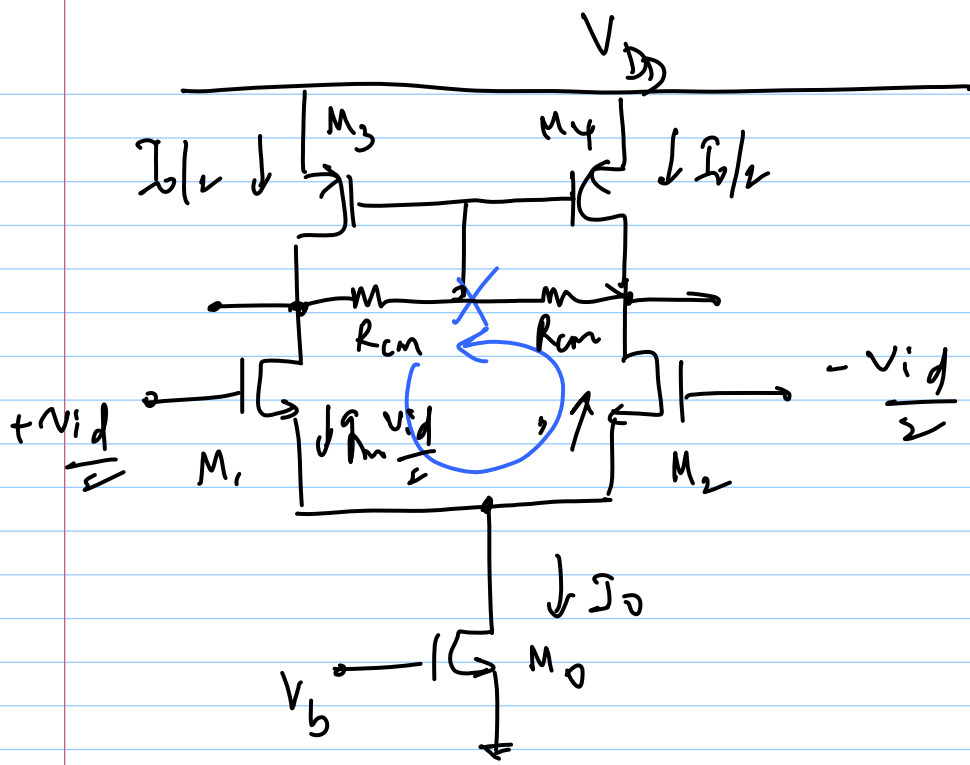

$$V_{o,DC} = V_{DD} - V_{SG3,4}$$