

8/4/13



Lec 39

Next Tuesday - 16/4/13 Quiz 2

3-stage Opamps
Hacker design



$$a = \frac{a_0}{(1+s/\omega_p)}$$

single pole

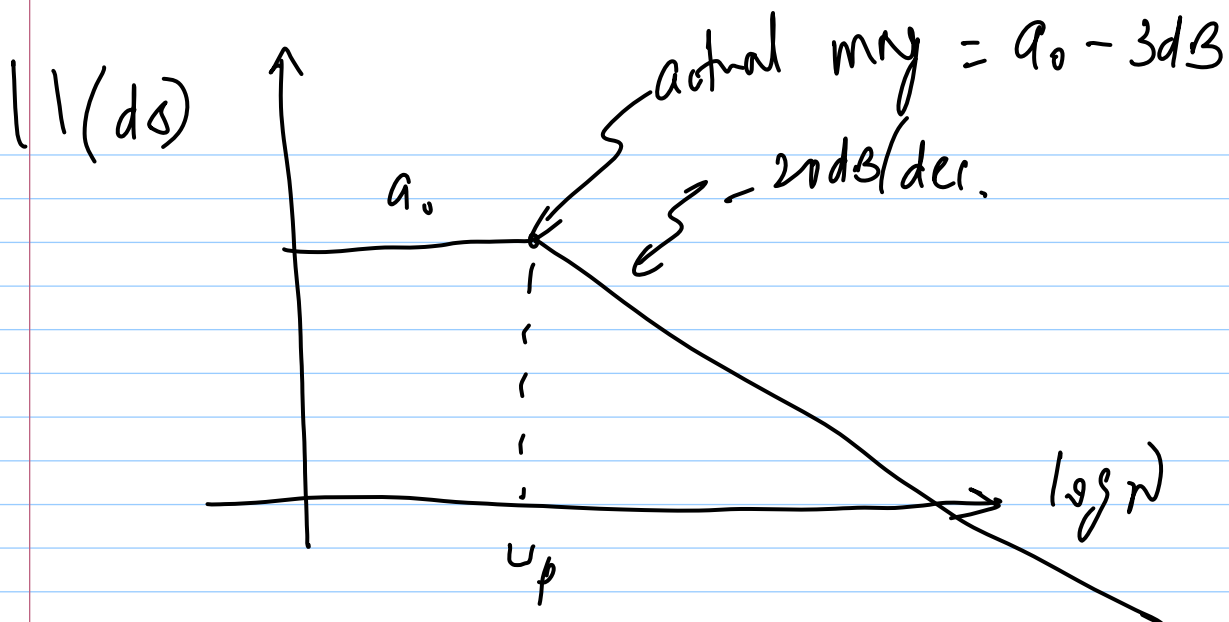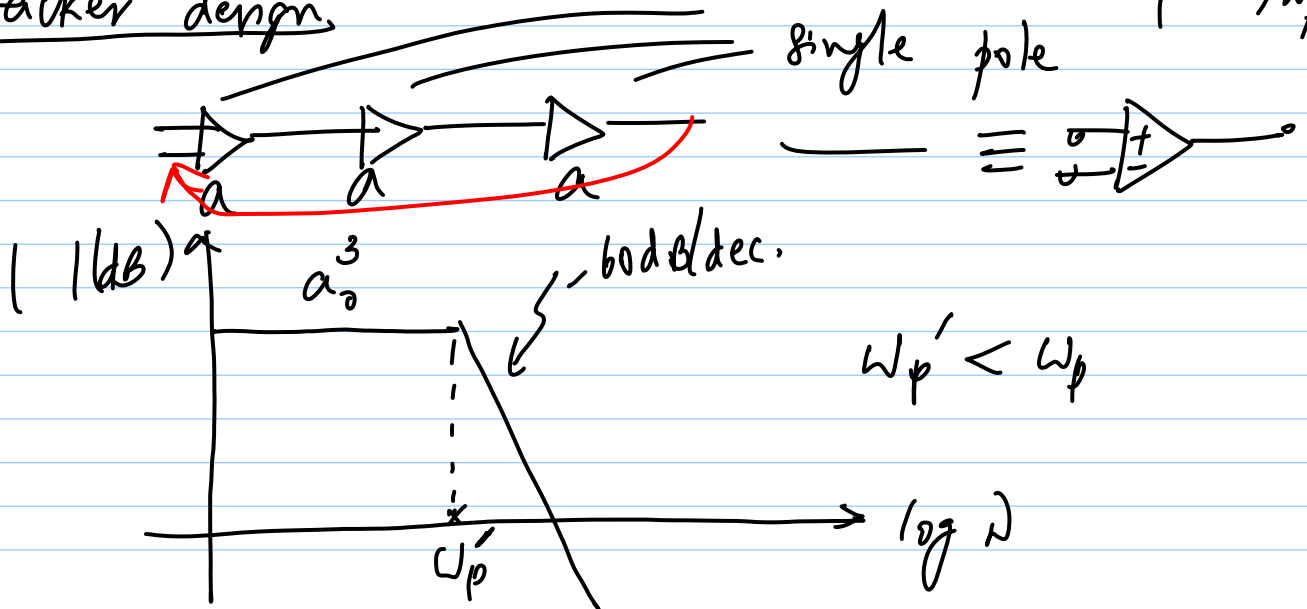


$$A(s) = \frac{A_0}{(1+s/\omega_p)^3}$$

for stable system $A_0 = 8$ ($a_0 = 2$)

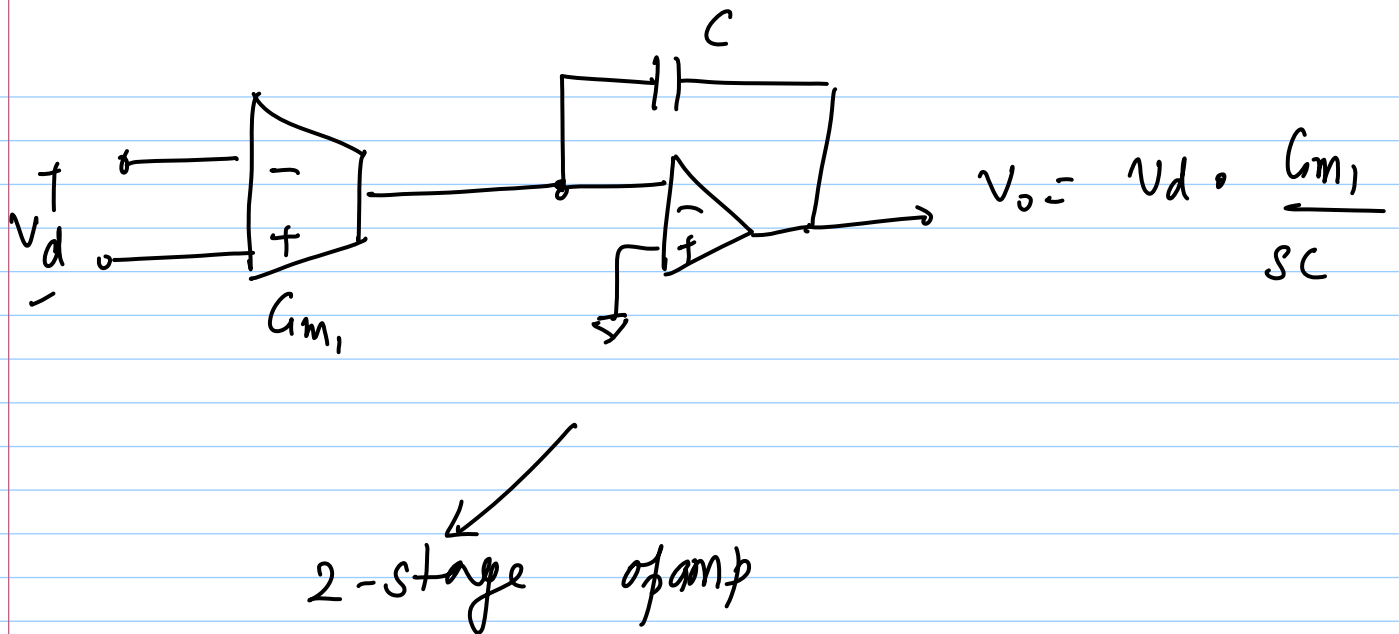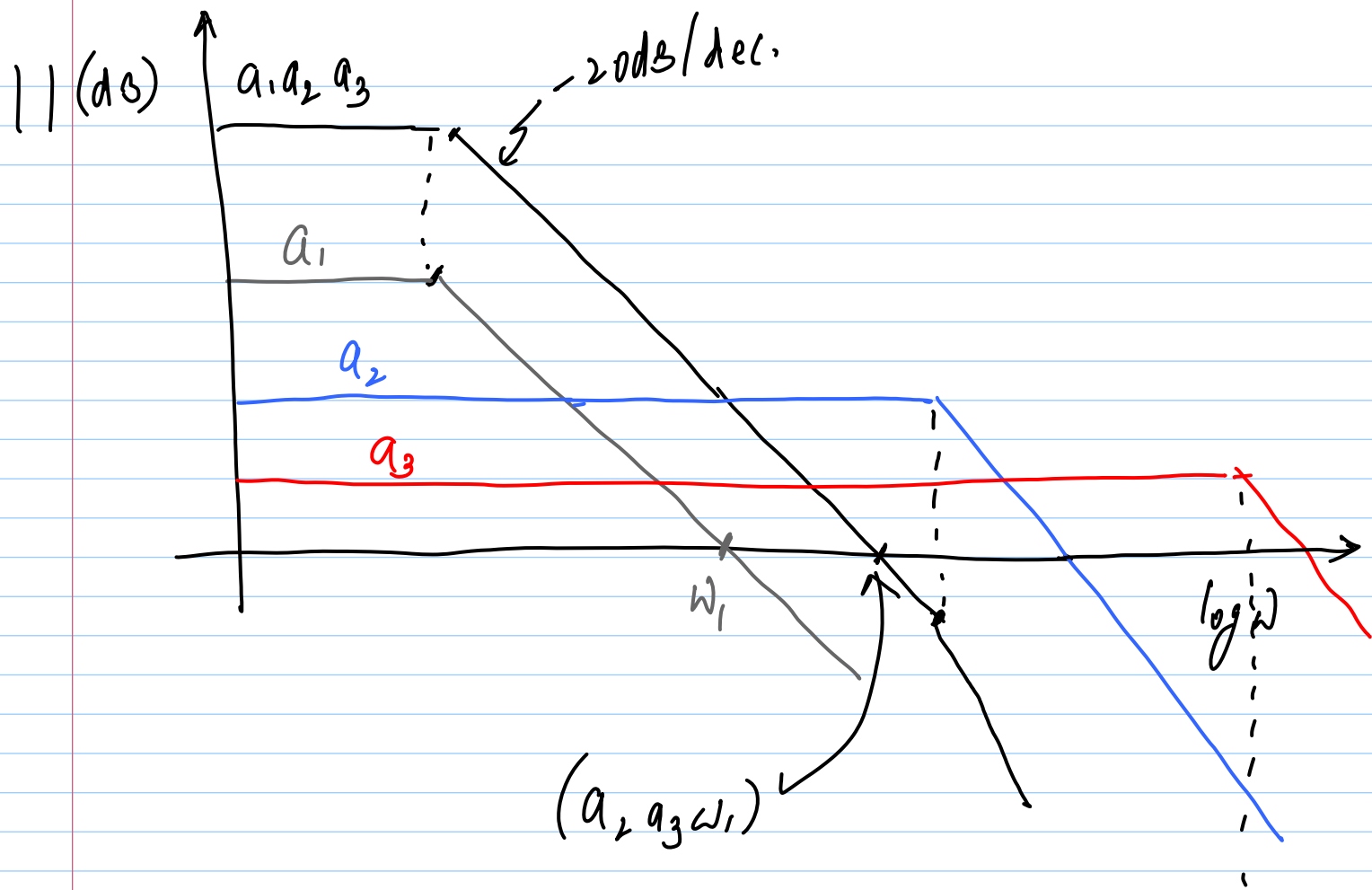

i) Nested Miller

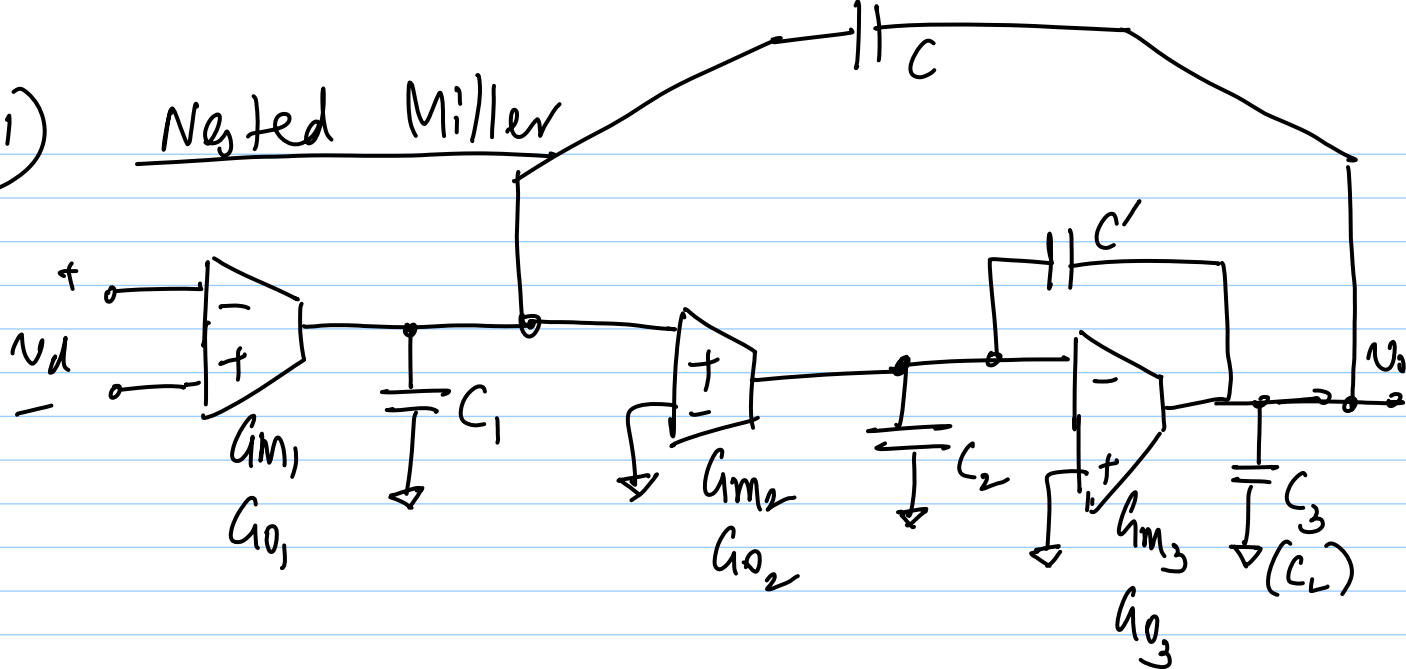

$$\begin{aligned} \text{DC gain } (A_0) &= \frac{G_{m1} G_{m2} G_{m3}}{G_{o1} G_{o2} G_{o3}} \\ \omega_u &= \frac{G_{m1}}{C} ; \omega_d = \omega_u / A_0 \end{aligned} \quad \left. \begin{array}{l} \text{N.D. poles} \\ p'_2 \text{ \& } p'_3 \end{array} \right\}$$

Conditions

$$\star \quad \frac{G_{m1}}{C} < \omega'_u < p'_3 \quad \text{---} \quad \frac{G_{m3} - \frac{C'}{C'+C_2}}{\frac{C' C_2}{C'+C_2} + C_3}$$

$(\omega_u) \qquad \left(\frac{G_{m2}}{C'} \right)$

→ 3-stage opamp is typically slower than 2-stage opamp

2) Multipath NM

