
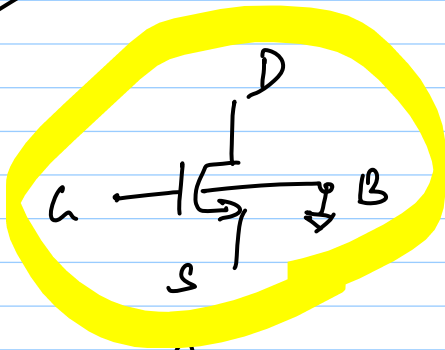


21-1-13

# Lec 4

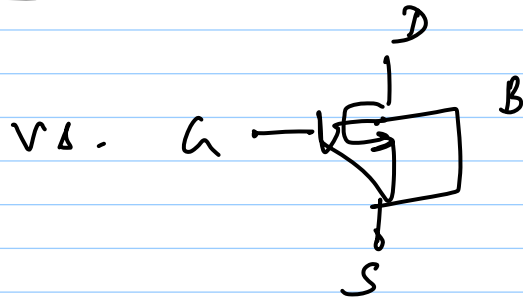

$g_{mbs}$



$$V_T = V_{T0}$$


$$V_T = V_{T0} + \gamma \left[ \sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f} \right] \quad \checkmark$$


$$g_{mb} = \left. \frac{\partial I_D}{\partial V_{SB}} \right|_{V_{DS}, V_{GS} = \text{constant}}$$

$$= \frac{\partial I_D}{\partial V_T} \cdot \frac{\partial V_T}{\partial V_{SB}} = - \frac{\partial I_D}{\partial V_{GS}} \cdot \frac{\partial V_T}{\partial V_{SB}}$$

$$= -g_m \cdot \frac{\gamma}{2\sqrt{2\phi_f + V_{SB}}} = -\eta g_m$$

$$\eta \sim 0.1$$

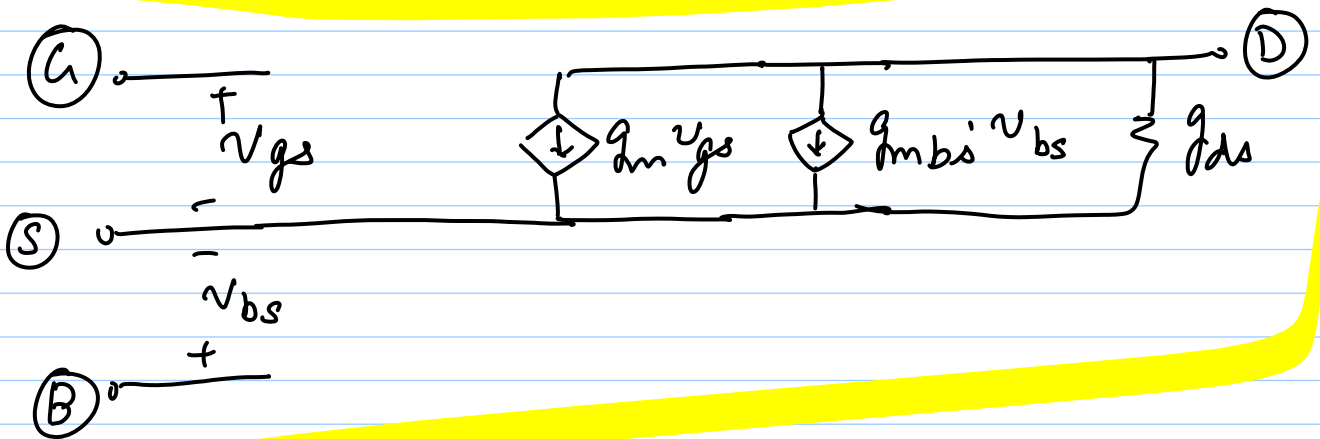

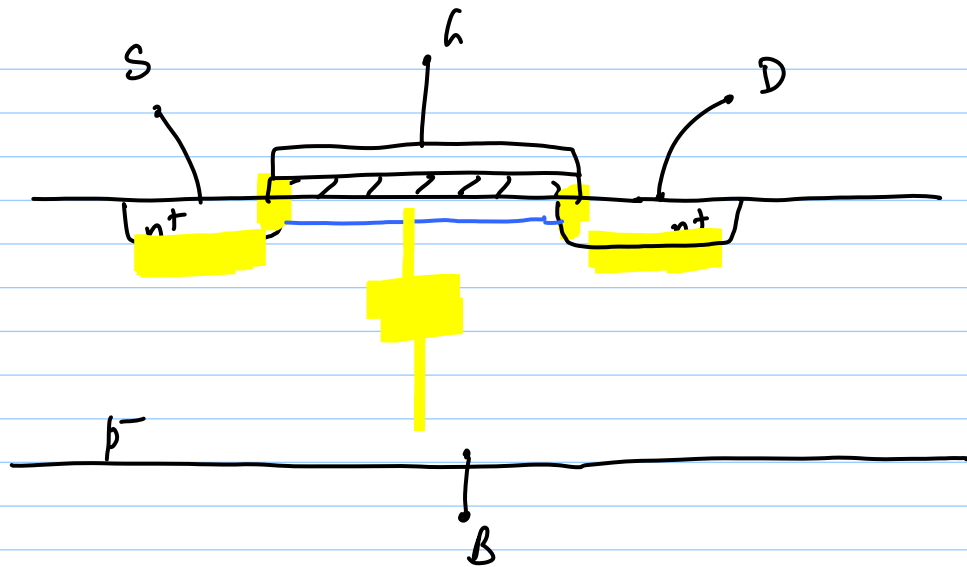

$$C_{ov} = W L_D C_{ox} \quad ; \quad L_D = \text{overlap}$$

$$C_{gc} = W L C_{ox}$$


| $C_{in}$ | OFF             | TRIODE               | SAT                               |
|----------|-----------------|----------------------|-----------------------------------|
| $C_{gs}$ | $C_{ov}$        | $C_{ov} + C_{gc}/2$  | $C_{ov} + \frac{2}{3} W L C_{ox}$ |
| $C_{gd}$ | $C_{ov}$        | $C_{ov} + C_{gc}/2$  | $C_{ov}$                          |
| $C_{gb}$ | range of values | 0                    | 0                                 |
| $C_{sb}$ | $C_{jsb}$       | $C_{jsb} + C_{cb}/2$ | $C_{jsb} + \frac{2}{3} C_{cb}$    |
| $C_{db}$ | $C_{jdb}$       | $C_{jdb} + C_{cb}/2$ | $C_{jdb}$                         |

## Simple Amplifier Ckt analysis

- 1) Visualise the propagation of V & I signals through the ckt.
- 2) Develop insight into ckt performance based on (1)
- 3) Identify relative impedance levels at all nodes in the signal path
- 4) Freq. response: identify relative position of poles & zeroes based on (3) and caps.
- 5) VTC — info on voltage swings.

$$g_m \gg g_{mbs} \gg g_{ds}$$

### Cascode C-S. Amp. (-x)

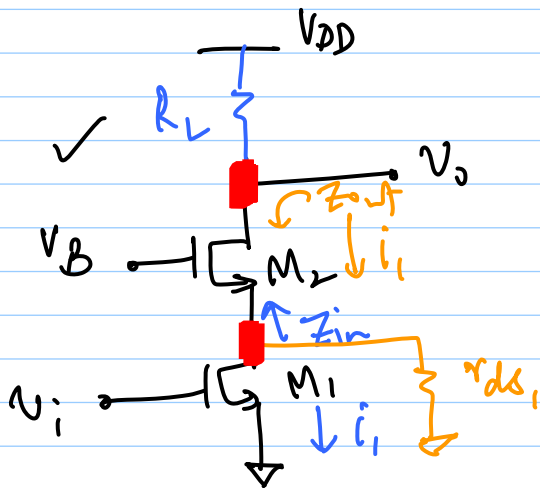


gain

$$Z_{in} \approx 1/g_{m2}$$

$$i_1 = g_{m1} \cdot v_i$$


$$R_{out} = (g_{m2} r_{ds2}) \cdot r_{ds1}$$
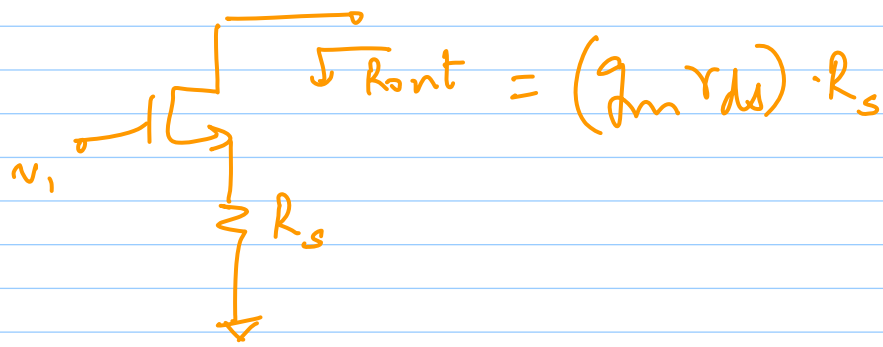
$$a_v = -g_{m1} \cdot [R_L \parallel R_{out}]$$



as  $R_s \rightarrow \infty \Rightarrow a_v \rightarrow -g_m R_{out}$


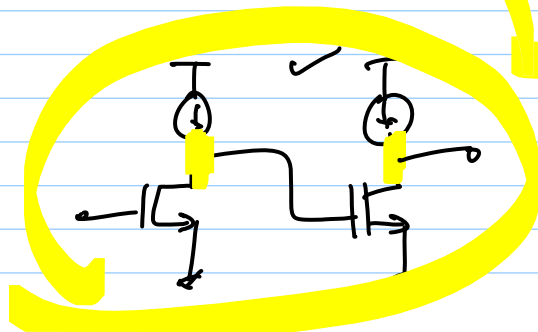
$$a_v = -(g_{m1} r_{ds1}) (g_{m2} r_{ds2})$$



cascode

### Advantage

1)  $V_{th}$  as an ideal current source

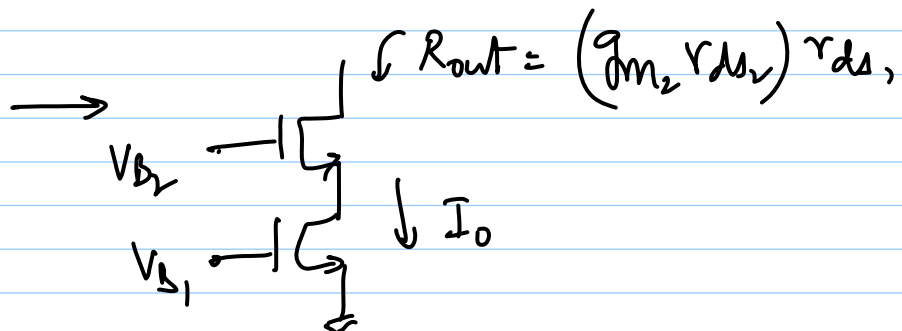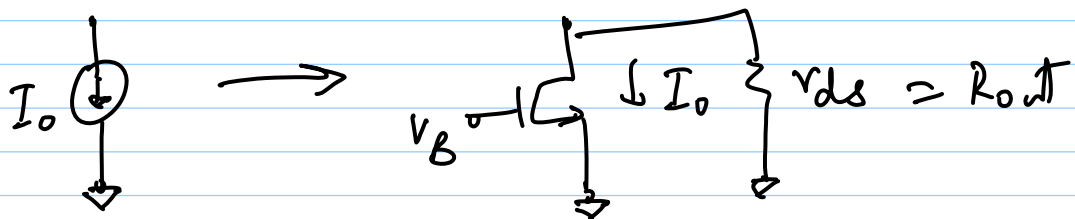

2) Cascade — 2 dominant poles  
cascode — 1 " "

3) Power consumption