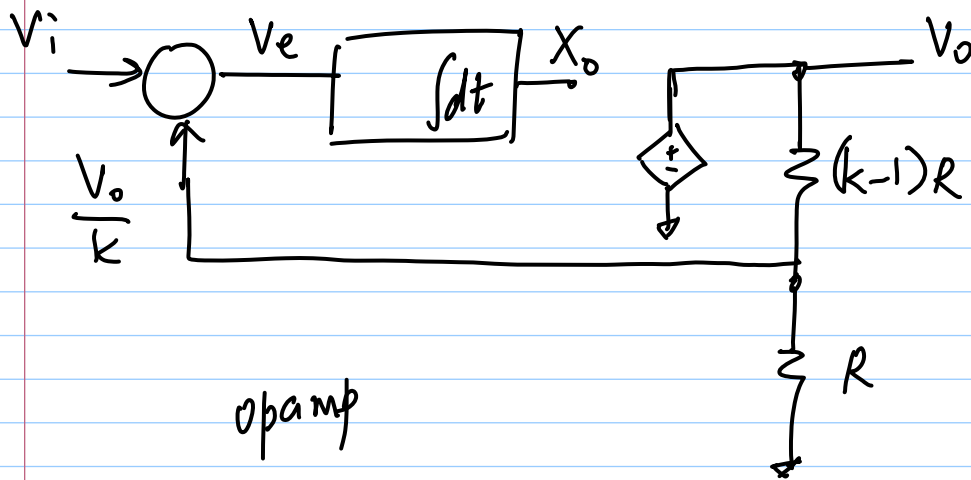


09-04-2013

Lec 40


Voltage Amplifier


$$V_o = k V_i$$




Frequency Multiplier

$$f_{out} = N \cdot f_{in}$$

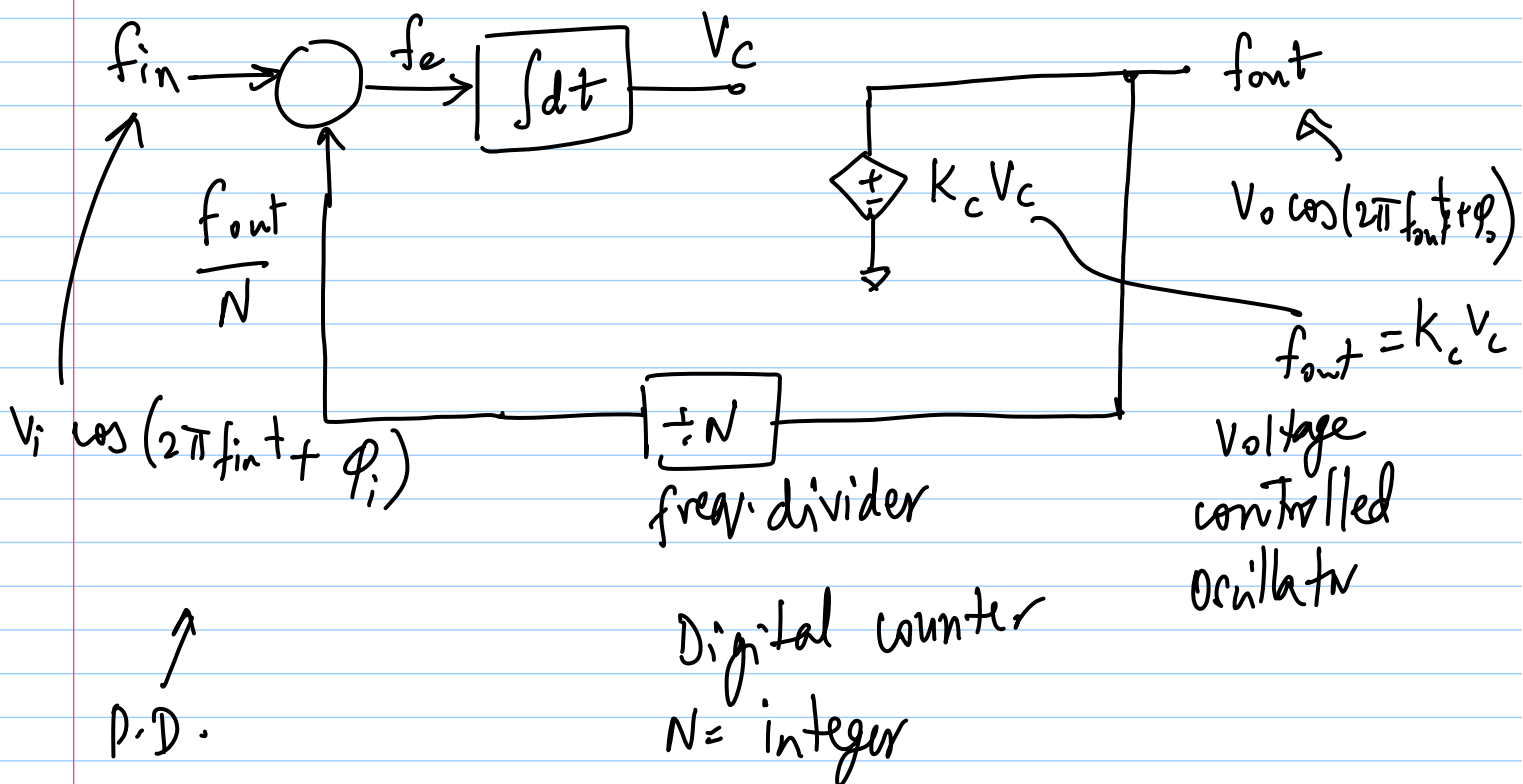


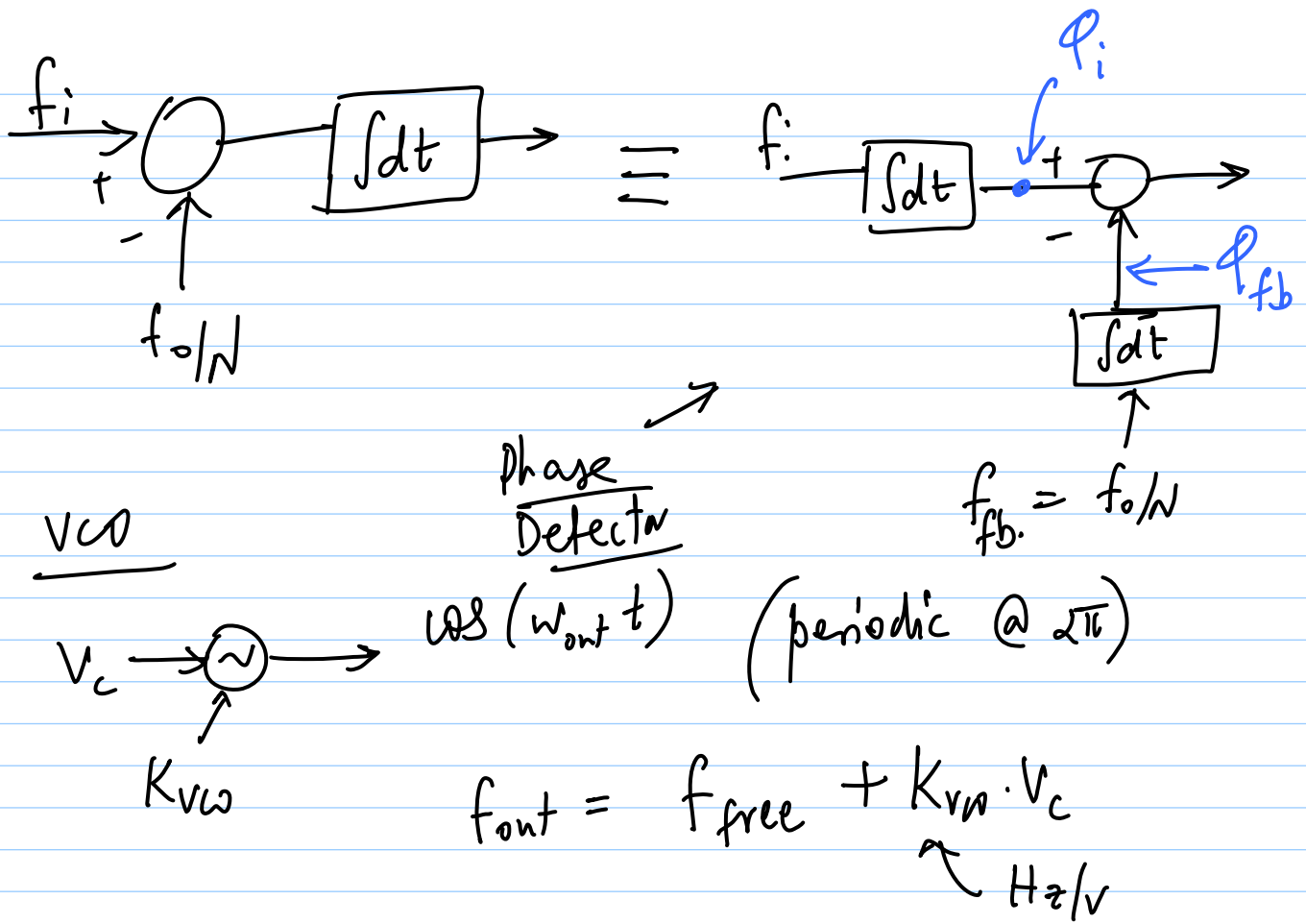

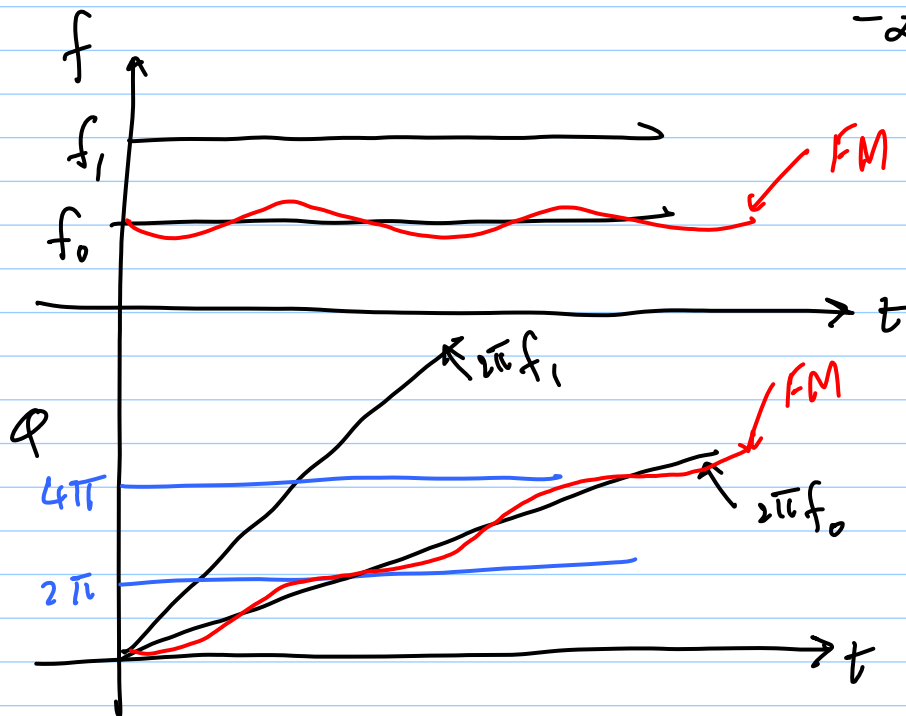
$$\phi_{out} = 2\pi f_{free} t + 2\pi K_{VCO} \int_{-\infty}^t V_c dt + \phi_0$$



Phase Detector

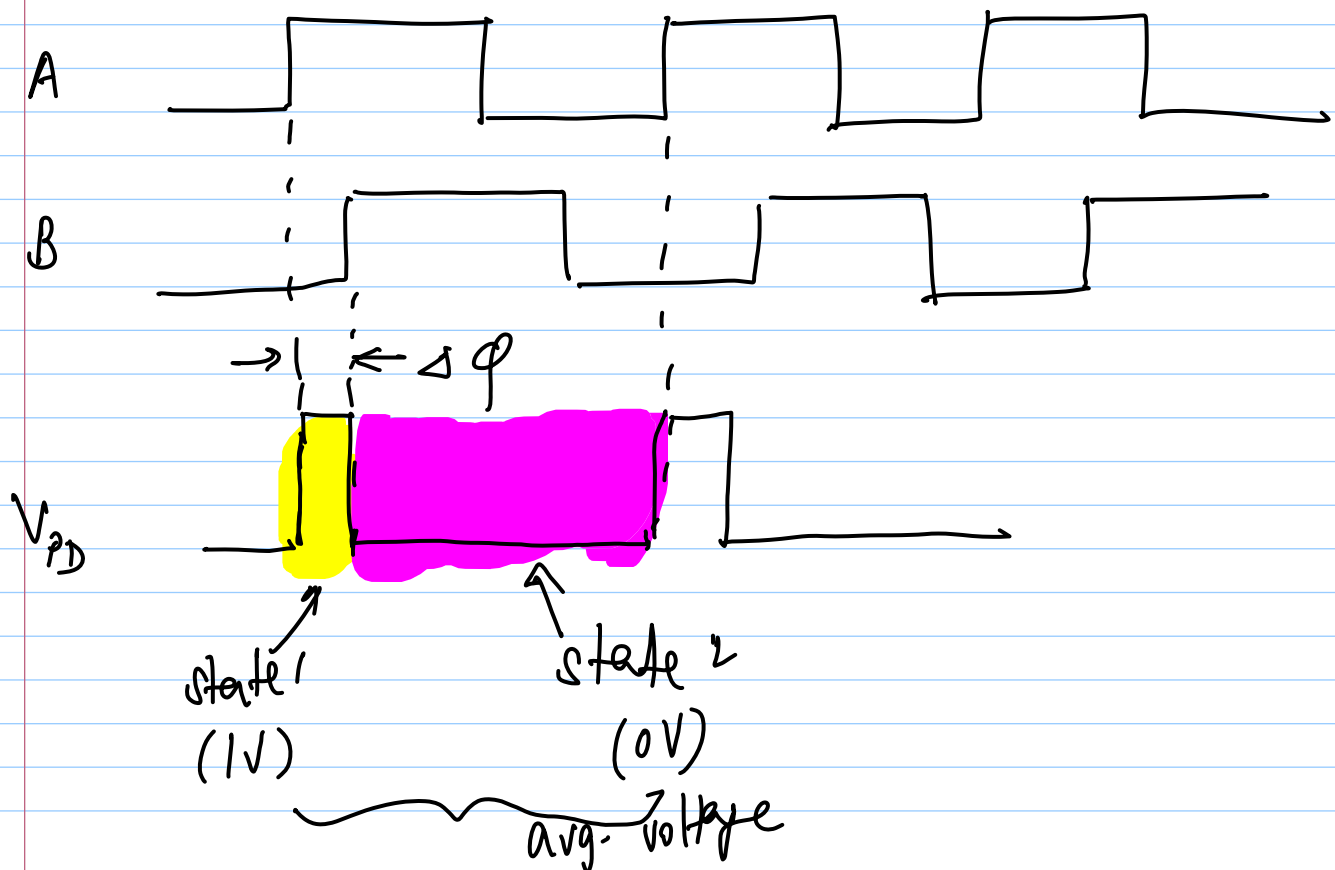

Multiplier PD

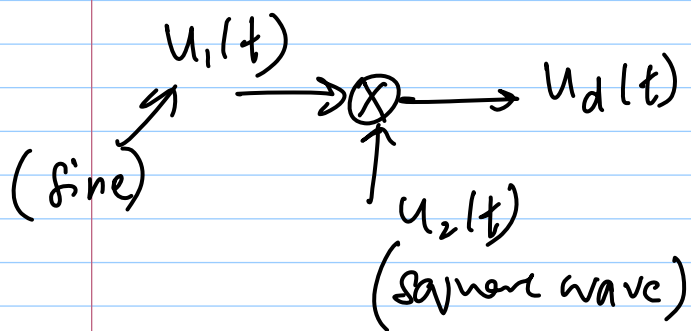

$$u_1(t) = U_{10} \sin(\omega_1 t + \theta_1)$$

$$u_2(t) = U_{20} \left[\frac{4}{\pi} \cos(\omega_2 t + \theta_2) \right.$$

$$+ \frac{4}{3\pi} \cos(3\omega_2 t + \theta_2)$$

$$+ \frac{4}{5\pi} \cos(5\omega_2 t + \theta_2) + \dots \left. \right]$$

$$u_d(t) = u_1(t) \times u_2(t)$$

$$\begin{aligned}
&= u_{10}u_{20} \frac{4}{\pi} \sin(\omega_1 t + \theta_1) \cos(\omega_2 t + \theta_2) \\
&+ u_{10}u_{20} \cdot \frac{4}{3\pi} \sin(\omega_1 t + \theta_1) \cdot \cos(3\omega_2 t + \theta_2) \\
&+ \dots
\end{aligned}$$

$$\begin{aligned}
&= \frac{2}{\pi} u_{10}u_{20} \left[\sin((\omega_1 + \omega_2)t + \theta_1 + \theta_2) \right. \\
&\quad \left. + \sin((\omega_1 - \omega_2)t + \theta_1 - \theta_2) \right] \\
&+ \dots
\end{aligned}$$

LPF gives $(\theta_1 - \theta_2)$ term