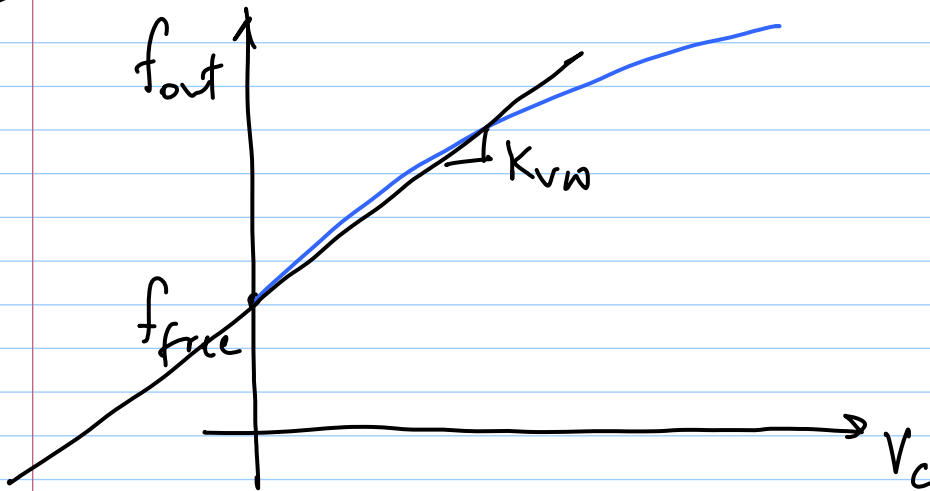


10/4/13


Lec 41



In PLL steady state, $\omega_1 = \omega_2$

$$u_d(t) = \frac{2}{\pi} u_{10} u_{20} \sin \theta_e \quad (\text{Desired term})$$
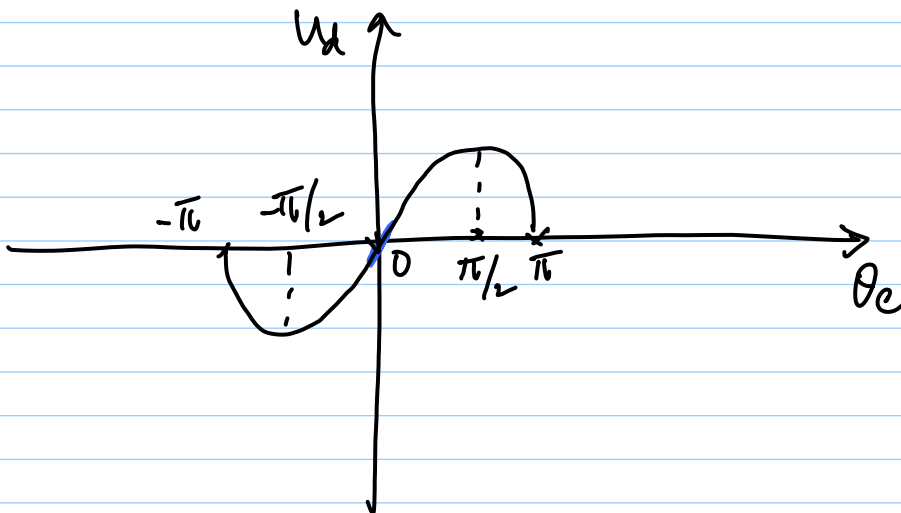
$$\theta_e = \theta_1 - \theta_2 = \text{phase error}$$



$$u_d(t) = K_d \sin \theta_e$$

$$K_d = \frac{2}{\pi} u_{10} u_{20}$$

$\omega_1 \neq \omega_2$ (unlocked state)


$$u_d(t) = \frac{2}{\pi} u_{10} u_{20} \sin[(\omega_1 - \omega_2)t + \theta_e] \\ + \text{higher order terms}$$

* If $u_d(t)$ were truly sinusoidal


average value of sine $= 0$

$\rightarrow u_d(t)$ has to have some distortion
(dc term)

XOR P.D.

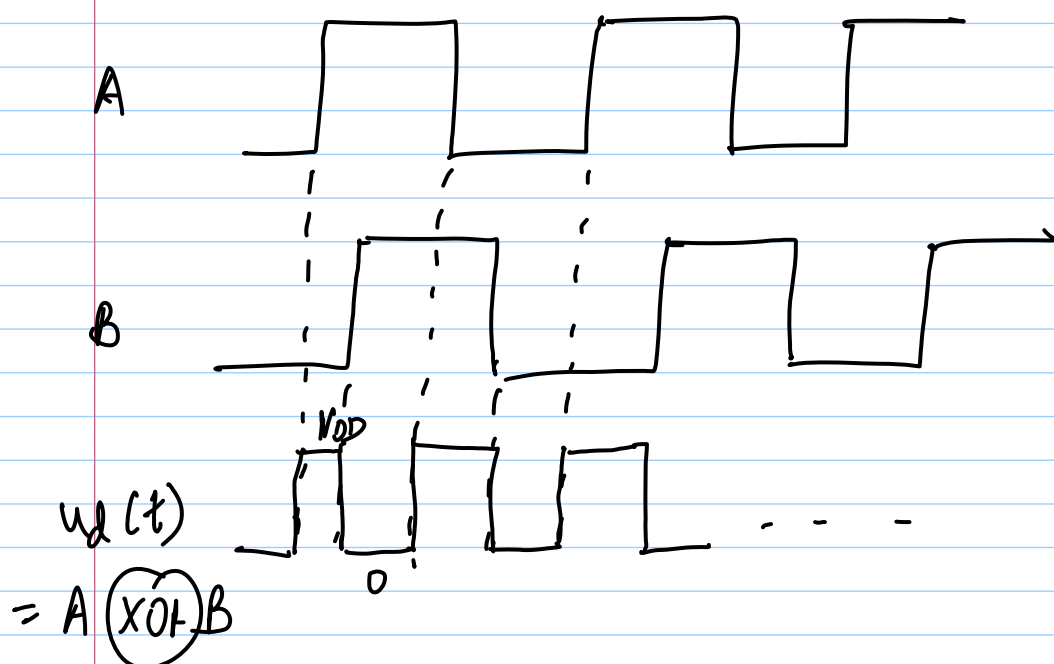

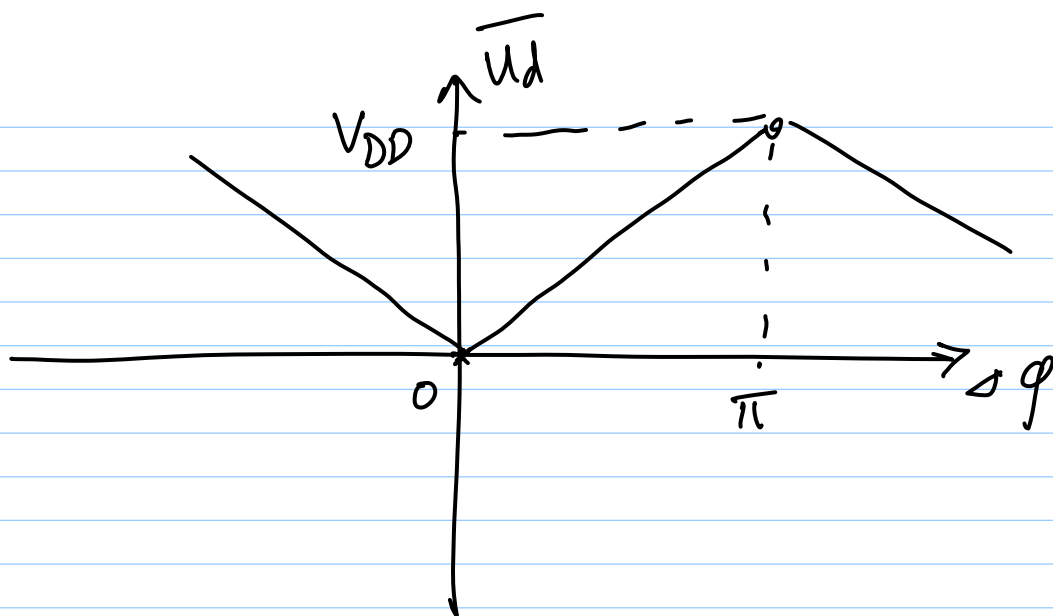
$$\overline{u_d(t)} = 0 \text{ if } \Delta\phi = 0/2\pi$$




③ PFD $\equiv$ phase-frequency detector

$\omega_1 = \omega_2$ no DC term

only DC term comes from distortion

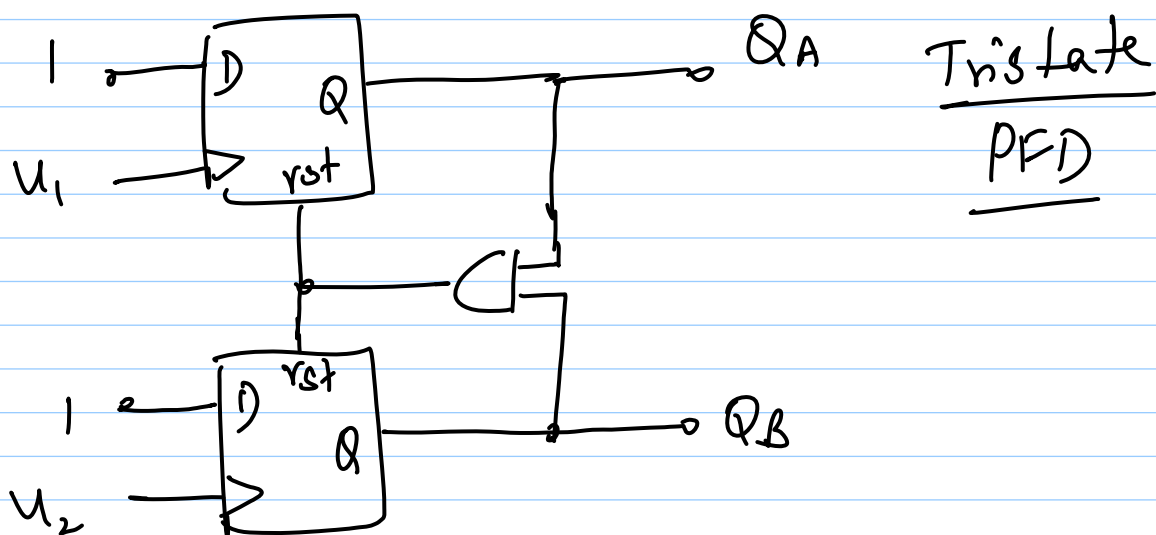


Q_A	Q_B	states
0	0	0
0	1	-1
1	0	+1
1	1	Prohibited (PFD is reset)

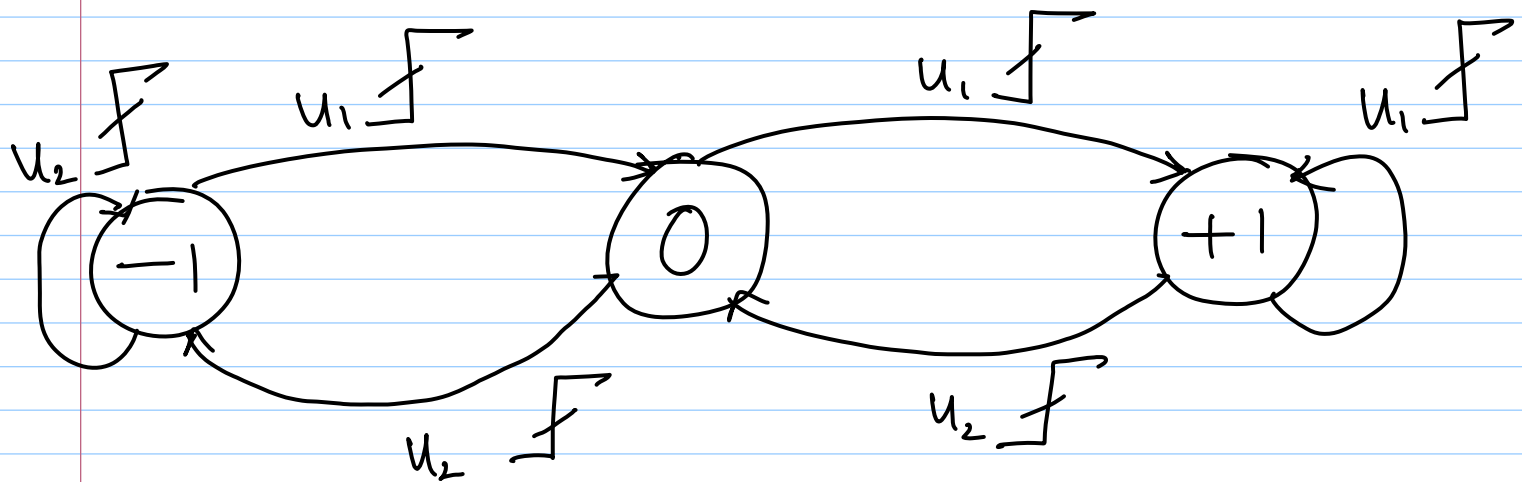

$$Q_e = 0 \Rightarrow \text{avg. } (Q_A - Q_B) = 0$$

$Q_e > 0$

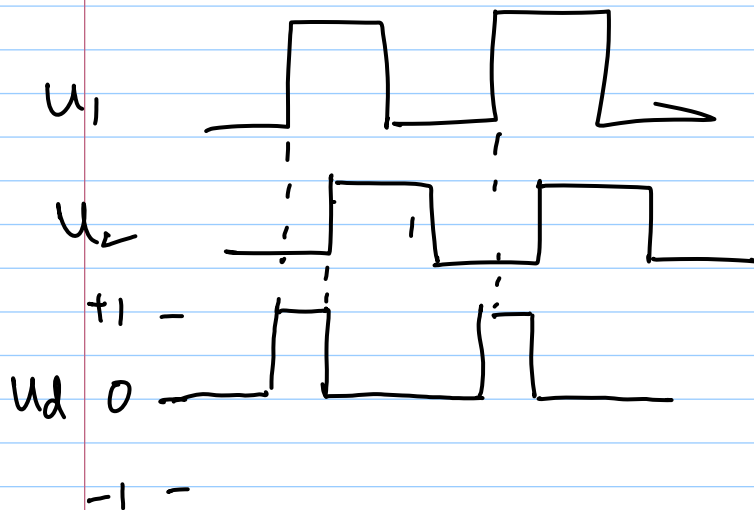

$Q_e < 0$

