
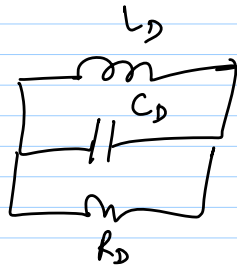



25/9/13

Lec 23


V-C. mixer

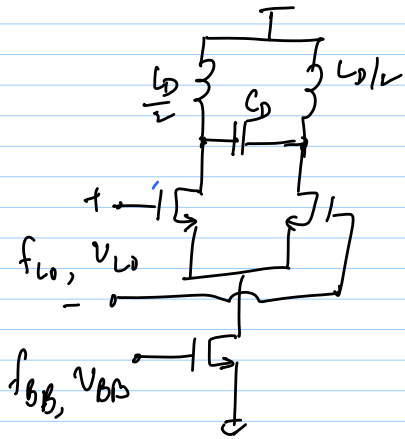

2) Noise from g_m -stage

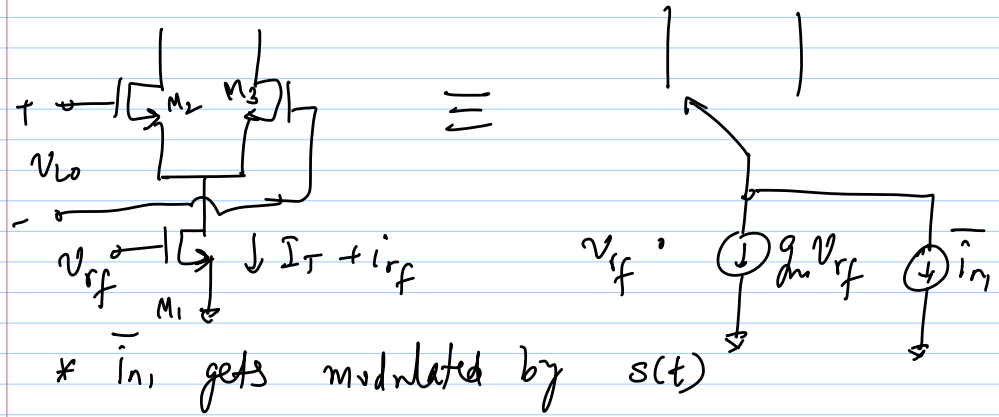

a) thermal noise

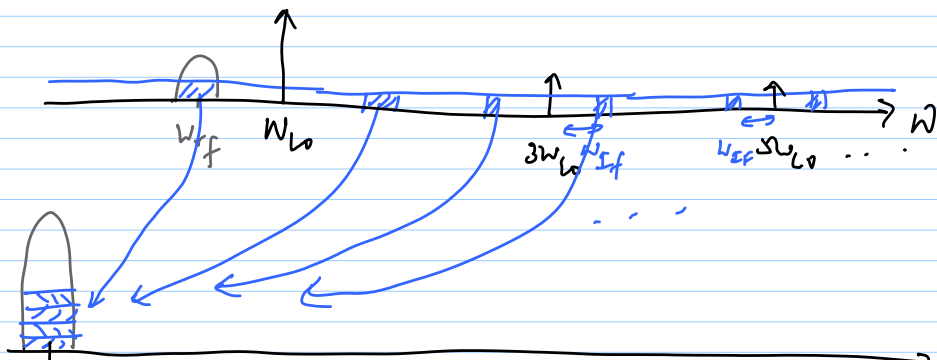


$$\frac{N_{\text{avg}}}{\Delta f} = \frac{4kT\sigma^2}{g_m} \times \left(\frac{2}{\pi} g_m R_L\right)^2 \times \left(1 + \frac{1}{3^2} + \frac{1}{5^2} + \dots\right)$$

$\pi^2/4$

$$\frac{N_{\text{avg}}}{\Delta f} = 4kT\sigma^2 g_m R_L^2$$


b) 1/f noise

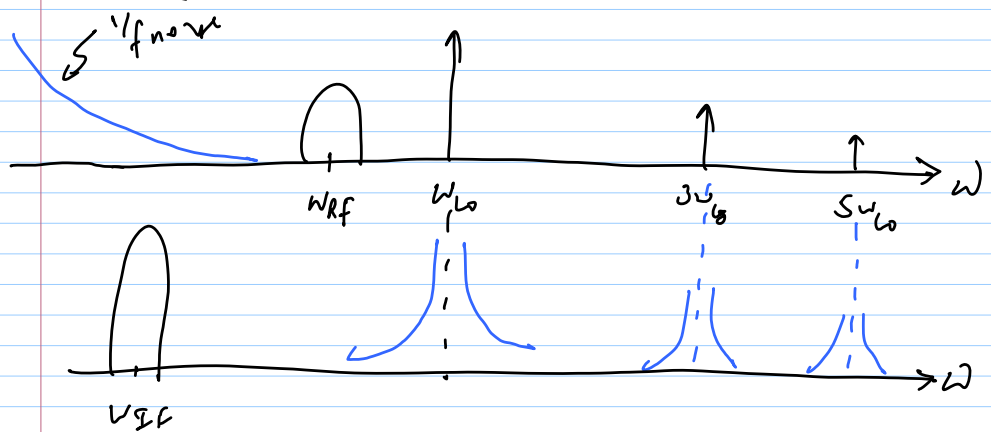


* for Rx mixers - $1/f$ noise is not a big issue as long as symmetry is preserved

* In Tx mixer - $1/f$ noise gets upconverted to RF

3) Noise from switching pair

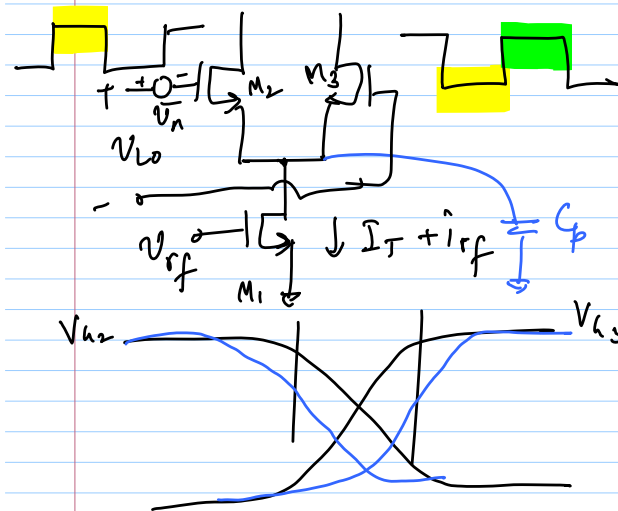

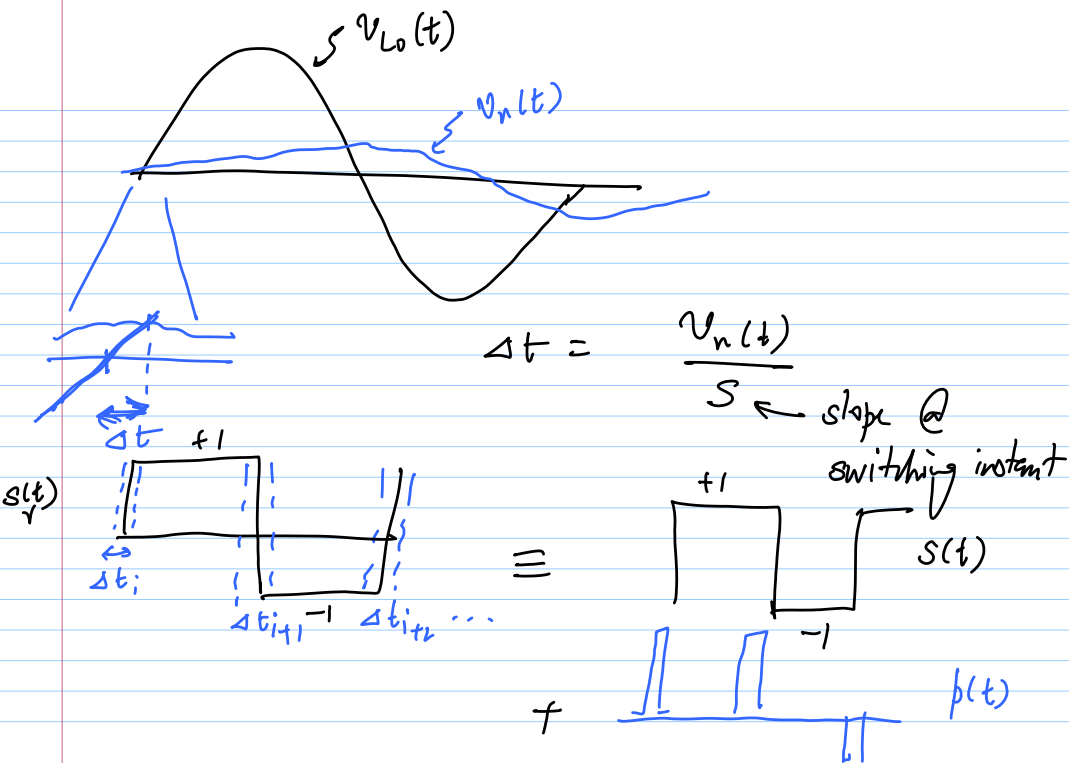\bar{v}_n = noise of M_2/M_3 referred to L_o port



$$s_r(t) = s(t) + p(t)$$

$p_s(t) =$ output current pulse train of height $2I_T$

@ rate $2f_L$
width $\Delta t = \frac{v_n(t)}{S}$

$$v_{L_o}(t) = \pm V_{L_o} \sin \omega_{L_o} t \Rightarrow v_{L_{od}}(t) = 2V_{L_o} \sin \omega_{L_o} t$$

$$\Rightarrow \text{slope} = \frac{dv_{L_{od}}}{dt} = 2V_{L_o} \cdot \omega_{L_o} \cos \omega_{L_o} t$$

$$S = 2V_{L_o} \cdot \omega_{L_o}$$

avg. value of i_{out} over one period:


$$\bar{i}_{on} = \frac{2}{T_L} \times 2I_T \times \Delta t$$

$$= \frac{4I_T \cdot V_n}{8T_L}$$

$$= \frac{4I_T V_n}{4\pi V_{L0}} = \frac{I_T}{\pi V_{L0}} \cdot V_n$$

$$i_{on}(f) = \frac{1}{\pi} \cdot \frac{I_T}{V_{L0}} \cdot V_n(f), \text{ except you have sampled images @ } 2f_{L0}$$

Flicker noise

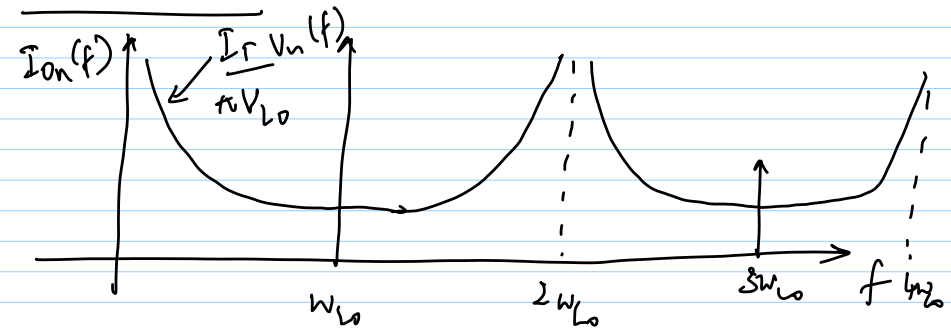

$$i_{out}(t) = \sum_{k=-\infty}^{\infty} \frac{2I_T}{S} V_n(t) \cdot \delta\left(t - k \frac{T_{L0}}{2}\right)$$

$$i_{out}(f) = \frac{4I_T}{S T_{L0}} \sum_{k=-\infty}^{\infty} V_n(f) \delta(f - 2kf_{L0})$$