


30/9/13

Lec 25

Passive Mixer - Refer Razavi 6.2

* use mosfet as a passive switch, no ampl. devices

1) Voltage mode, RF mixer

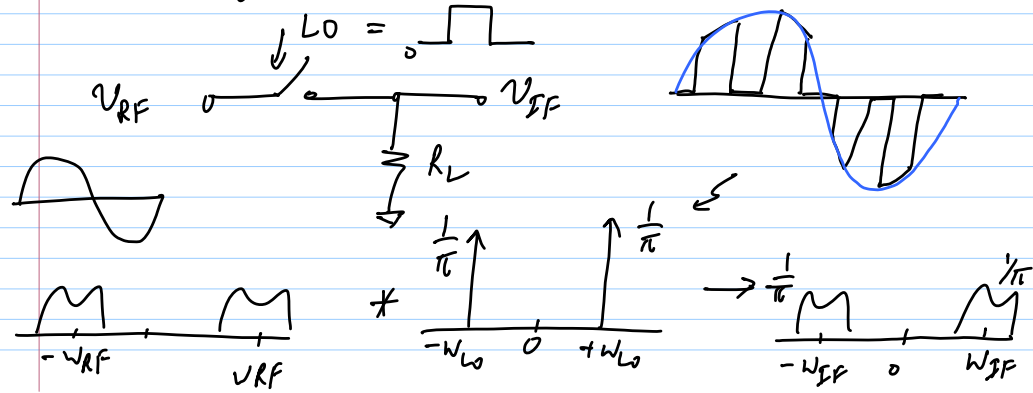


* $s(t) = \frac{2}{\pi} \cos \omega t$

* $G_c = \frac{1}{\pi} \approx -10dB$

* $s_L(t)$ has avg. value = 0.5
 → v_{RF} appears @ IF port with gain = 0.5
 → even-order distortion causes 11Hz


* Single-balanced mixer has twice the gain = $\frac{2}{\pi} \approx -4dB$, & no dc component

2) Sampling Mixer

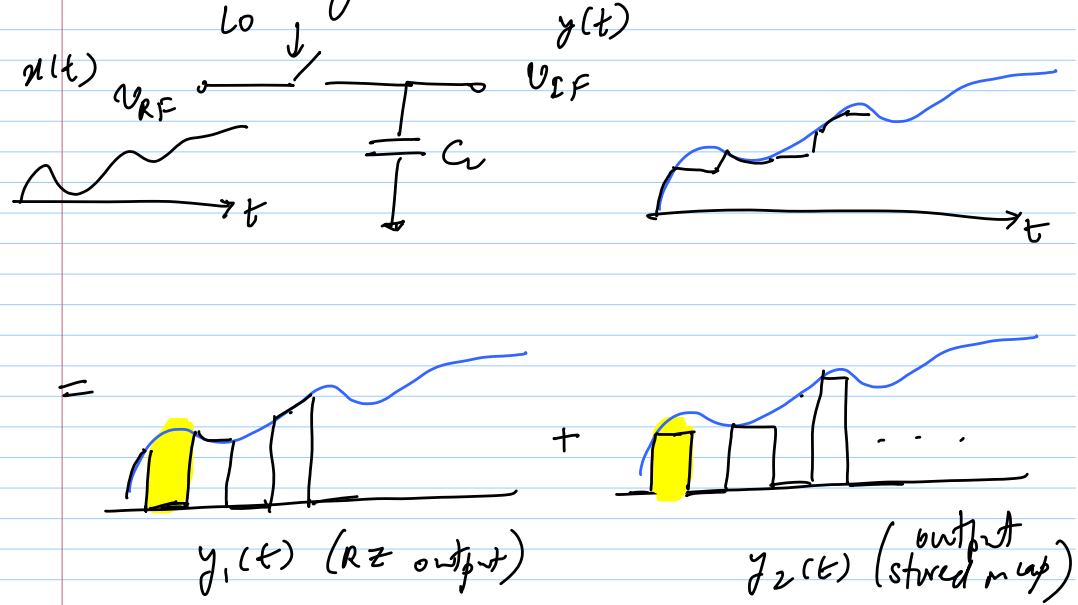

$y(t) = y_1(t) + y_2(t)$

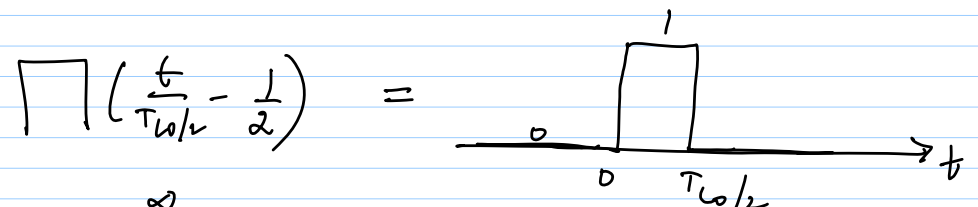$y_1(t) = x(t) \cdot \left[\text{rect} \left(\frac{t}{T_{LO/2}} - \frac{1}{2} \right) * \sum_{k=-\infty}^{\infty} \delta(t - kT_{LO}) \right]$



a) $\sum_{-\infty}^{\infty} \delta(t - kT) \leftrightarrow \frac{1}{T} \sum_{-\infty}^{\infty} \delta(f - \frac{k}{T})$

b) $x(t - T) \leftrightarrow e^{-j\omega T} X(f)$

$$c) \quad \square\left(\frac{t}{T/2} - \frac{1}{2}\right) \longleftrightarrow \frac{1}{j\omega} (1 - e^{-j\omega T/2})$$


$$Y_1(f) = X(f) * \left[\frac{1}{j\omega} (1 - e^{-j\omega T_{L0}/2}) \cdot \frac{1}{T_{L0}} \sum_{k=-\infty}^{\infty} \delta(f - \frac{k}{T_{L0}}) \right]$$

set $k = \pm 1$ gives IF spectrum

$$Y_1(f) \Big|_{IF} = X(f) * \left[\pm \frac{T_{L0}}{j\pi} \cdot \frac{1}{T_{L0}} \delta(f \pm f_{L0}) \right]$$

$$Y_1(f) = \frac{X(f - f_{L0})}{j\pi} - \frac{X(f + f_{L0})}{j\pi}$$

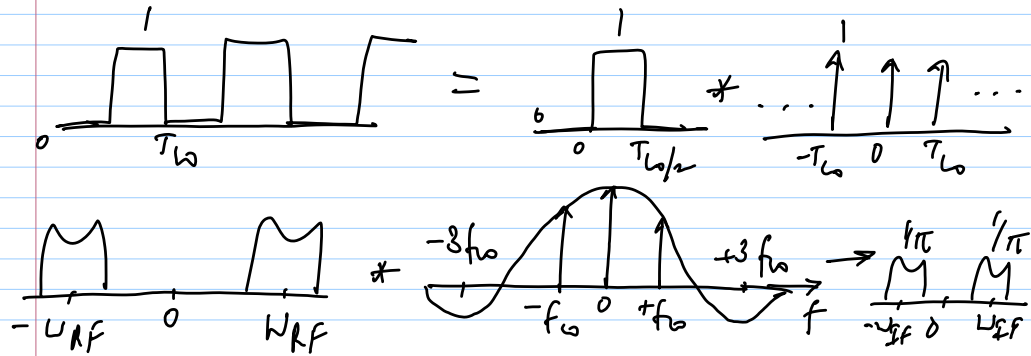as expected $\arg\{Y_1(f)\} = \frac{j\pi}{\omega}$
phase shift of 90°



$y_2(t)$ = impulse train sampling the input convolved with a square pulse

$$= \left[x(t) \cdot \sum_{k=-\infty}^{\infty} \delta(t - kT_{L0} - \frac{T_{L0}}{2}) \right] * \square\left(\frac{t}{T_{L0}/2} - \frac{1}{2}\right)$$

$$\square\left(\frac{t}{T_{L0}/2} - \frac{1}{2}\right)$$

$$Y_2(f) = \left[X(f) * \frac{1}{T_{L0}} \sum_{k=-\infty}^{\infty} e^{-j\omega T_{L0}/2} \cdot \delta(f - k f_{L0}) \right]$$

$$\cdot \frac{1}{j\omega} (1 - e^{-j\omega T_{L0}/2})$$

set $k = \pm 1$ to determine IF output

$$Y_2(f) \Big|_{IF} = \frac{1}{T_{L0}} \left[-X(f - f_{L0}) - X(f + f_{L0}) \right] \cdot \frac{1}{j\omega} [1 - e^{-j\omega T_{L0}/2}] \Big|_{\omega = 2\pi f}$$

If $\omega_{IF} \ll 2\omega_{LO}$,


$$e^{-j\omega_{IF}T_{LO}/2} \approx \left(1 - j\omega_{IF}\frac{T_{LO}}{2}\right)$$

$$Y_2(f)|_{IF} \approx \frac{-X(f-f_{LO}) - X(f+f_{LO})}{2}$$


$$|Y(f)|_{IF} = |Y_1(f) + Y_2(f)|_{IF}$$

$$= \sqrt{\frac{1}{\pi^2} + \frac{1}{4}} \cdot [|X(f-f_{LO})| + |X(f+f_{LO})|]$$

$$G_c = 0.593$$

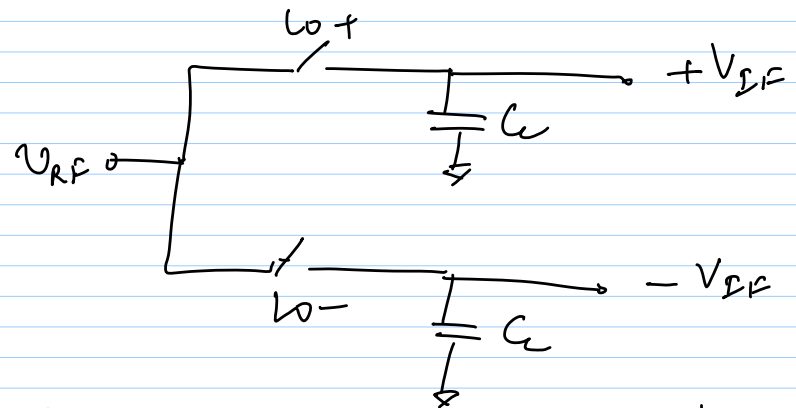

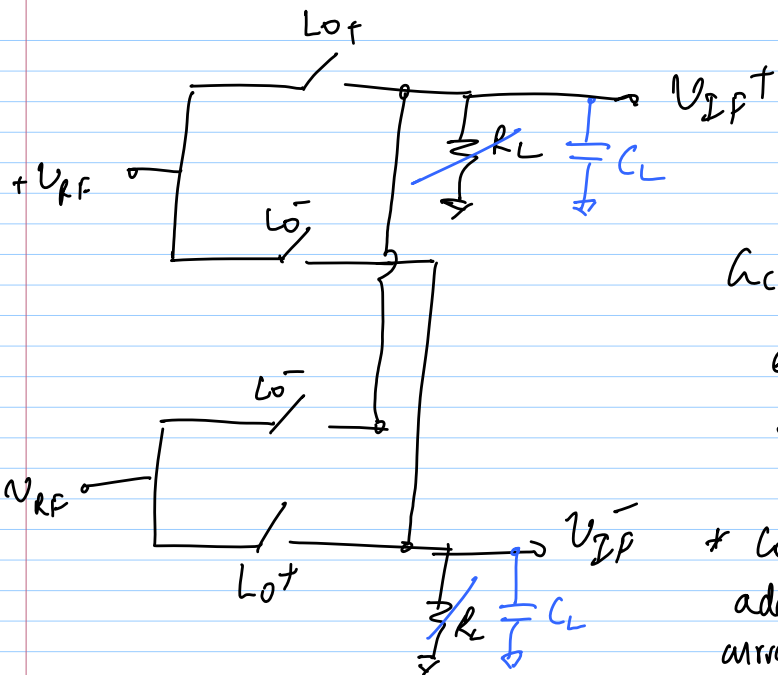Single balanced passive mixer has
 $G_c = 1.186 = 1.48 \text{ dB}$



$$G_c = \frac{2}{\pi}$$

even for
 sampling
 Mixer

* Could choose to
 add o/p as
 currents to keep G_c

