


---

Assignment: #1

Due Date and Time: Feb. 10, 2020, 11:59 PM


---

**PROBLEM 1.** Process Variations

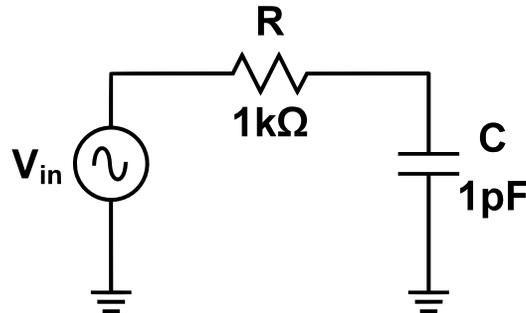

- (a) In the low pass filter shown above, due to process variations, the resistor  $R$  has  $\pm 25\%$  variation and capacitor  $C$  has  $\pm 20\%$  variation across corners. Taking three process corners (MAX, MIN and TYP where TYP is 0%) each for  $R$  and  $C$ , find the percentage variation of the -3dB cut-off frequency w.r.t its typical value for all corners. Identify the critical corners. Suggest a method to correct the error in the -3dB cut-off frequency on-chip.
- (b) If the temperature coefficient( $k$ ) of  $R$  is  $-1000\text{ppm}/^\circ\text{C}$ , find the percentage variation of the cut-off frequency across temperature ( $-40^\circ\text{C}$  to  $125^\circ\text{C}$ ) w.r.t to its value at  $27^\circ\text{C}$  assuming ideal capacitor. Given:  $R(T) = R(T_0) [1 + k (T-T_0)]$ , where  $T_0 = 27^\circ\text{C}$ .


**PROBLEM 2.** Resistor Mismatch

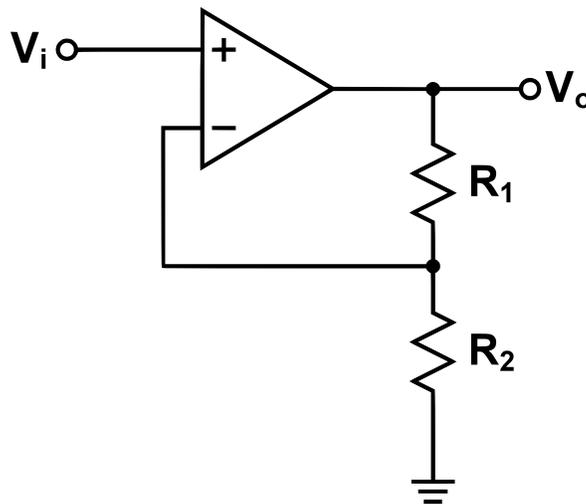

- (a) Assuming the above Opamp to be ideal, find  $R_1$  and  $R_2$  such that voltage gain,  $A_v = V_o/V_i = 2$  and  $R_1 + R_2 = 20\text{k}\Omega$ .
- (b) The resistor value is calculated as  $R = R_{sh}(L/W)$ , where  $L$ ,  $W$  and  $R_{sh}$  are the length, width and sheet resistance of the resistor. If  $R_1$  and  $R_2$  are of the same type and the resistor mismatch is modelled using Gaussian distribution with  $\sigma$  value given, choose  $W$  and  $L$  of  $R_1$  and  $R_2$  such that  $3\sigma$  variation in  $A_v$  is  $\leq 1\%$ . Given:  $R_{sh} = 200\Omega/\square$ . Minimum  $L$  and  $W$  that can be used are  $L_{min} = W_{min} = 500\text{nm}$ . Sigma variation of  $R$  w.r.t. its mean is given by  $\sigma(\Delta R/R) = 0.03/\sqrt{(WL)}$ , where  $W$  and  $L$  are in  $\mu\text{m}$ .

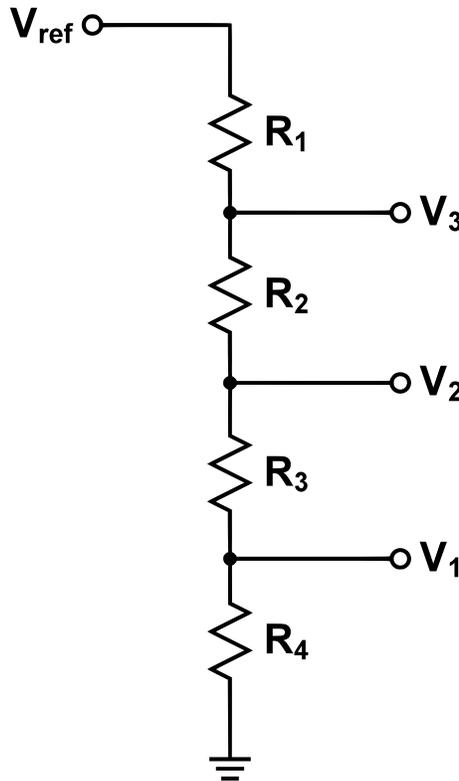**PROBLEM 3.** Mismatch in Resistive Divider

Given:  $V_{ref} = 400\text{mV}$ ;  $V_1 = V_{ref}/4$ ;  $V_2 = V_{ref}/2$ ;  $V_3 = 3V_{ref}/4$ ;  $R_1+R_2+R_3+R_4 = 40\text{k}\Omega$ ; Minimum L and W of resistors,  $L_{min}=W_{min}=500\text{nm}$ ; Sigma variation of R w.r.t. its mean is given by  $\sigma(\Delta R/R) = 0.03/\sqrt{(WL)}$ , where W and L are in  $\mu\text{m}$ .



- (a) For the resistive divider shown above, find the  $3\sigma$  variation in the absolute value of output voltages  $V_1$ ,  $V_2$  and  $V_3$  due to resistor mismatch in terms of  $\sigma(\Delta R/R)$ . Which voltage has the highest  $3\sigma$  variation? Choose W and L of the resistors such that for  $3\sigma(V_i) \leq 1\text{mV}$  for all values of i.
- (b) If the resistive divider is extended to say eight equal resistors, which voltage is expected to have the highest  $3\sigma$  variation?