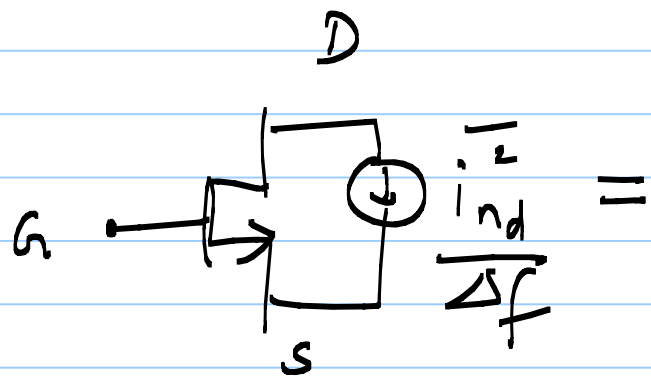


06/02/20

Lec 11




$$i_d / \sqrt{\Delta f} = 4KT \gamma g_m$$


$\gamma = \frac{2}{3}$  for a long channel MOSFET @ low freq.

$\gamma > \frac{2}{3}$  for short channel devices @ high freq.

CG LNA

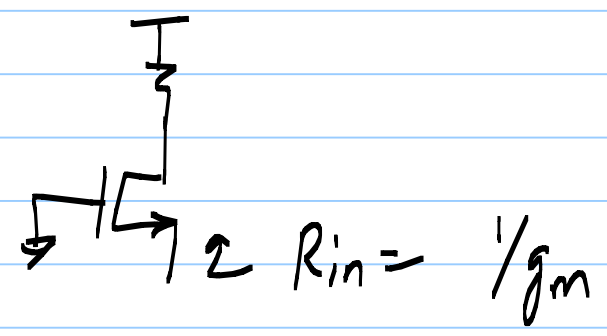

ver 1

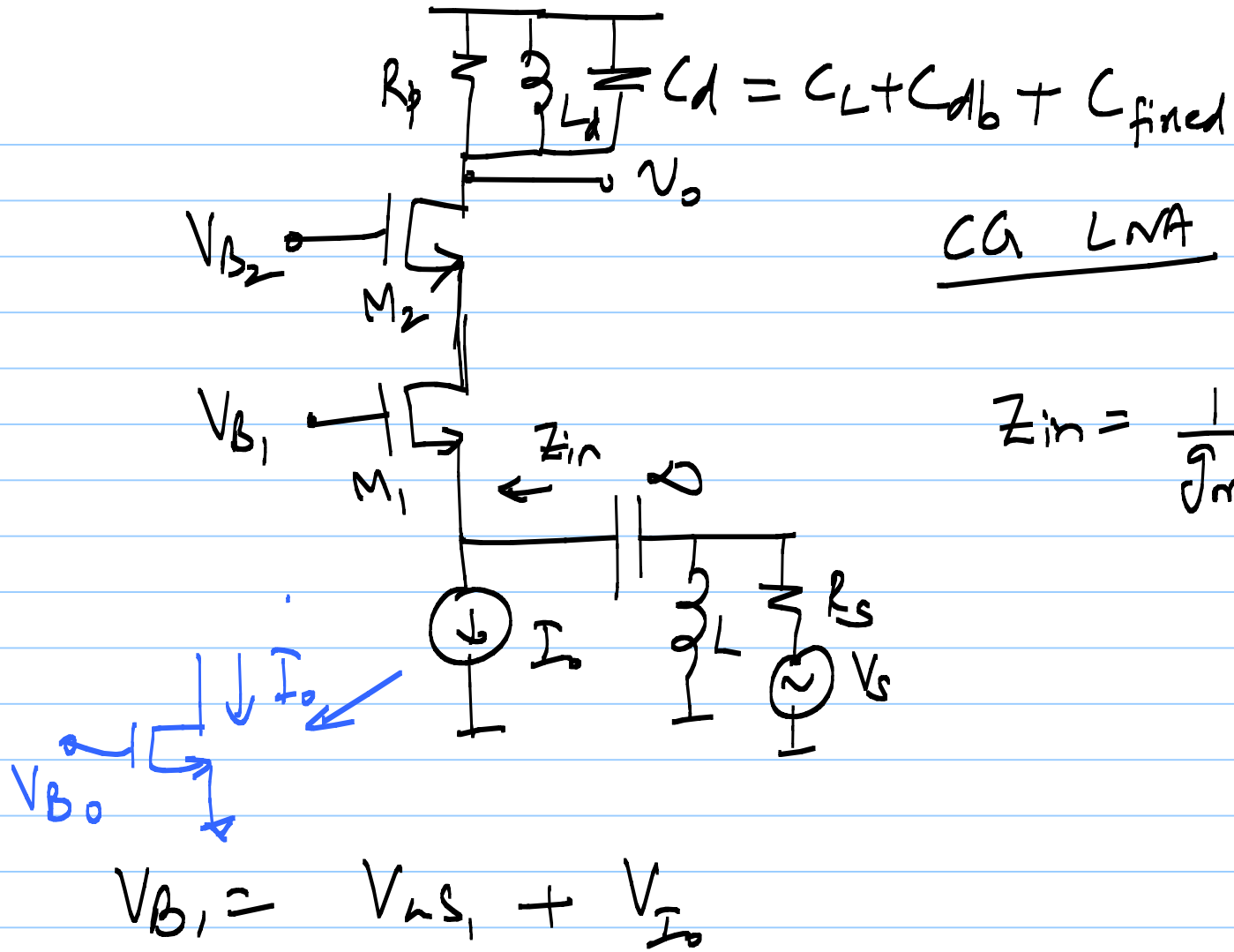

Ver 2

$$V_{B1} = V_{GS1}$$


$$Z_{in} = \frac{1}{g_{m1}}$$

$$\text{set } g_{m1} = 20 \text{ mS}$$

$$M_1 \equiv M_2$$



$$i_{d1} = g_{m1} \cdot \frac{v_s}{2}$$
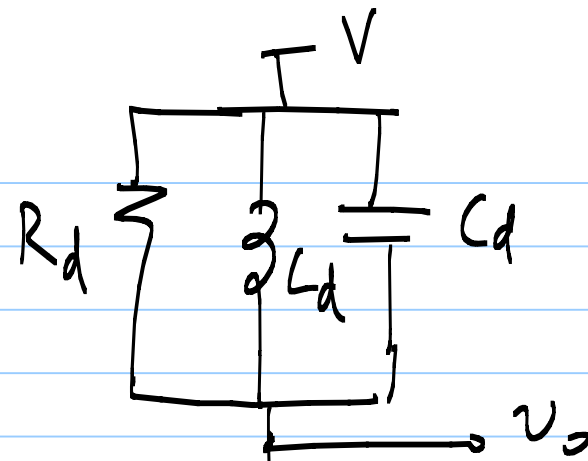
$$v_o = i_{d1} \cdot R_p = g_{m1} R_p \cdot \frac{v_s}{2}$$





$$f_o = \frac{1}{2\pi \sqrt{L C_{gs1}}}$$

$$f_o = \frac{1}{2\pi \sqrt{L_d C_d}}$$

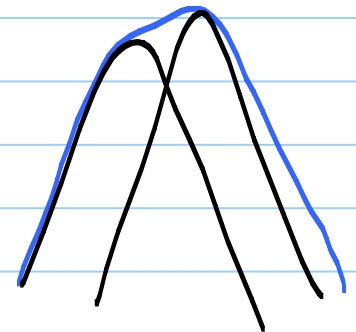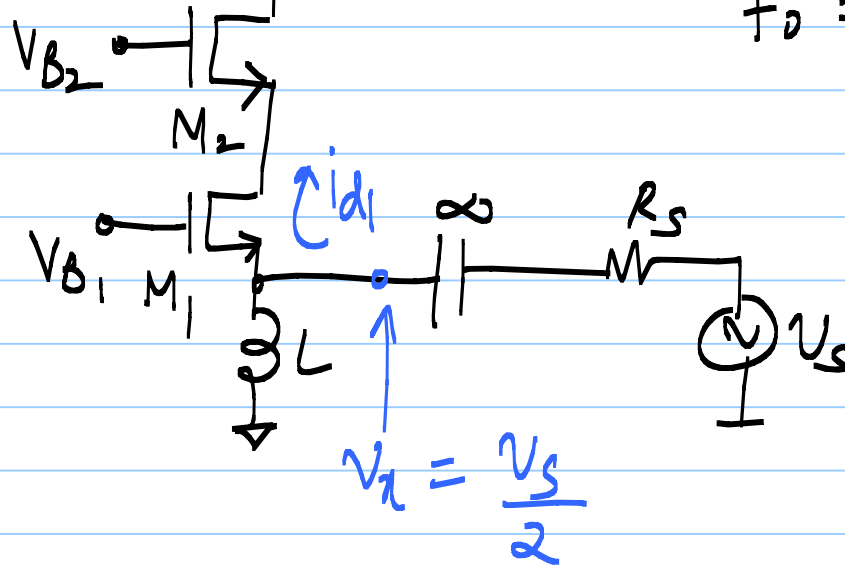

$$\text{gain} = \frac{g_{m1} R_p}{2}$$

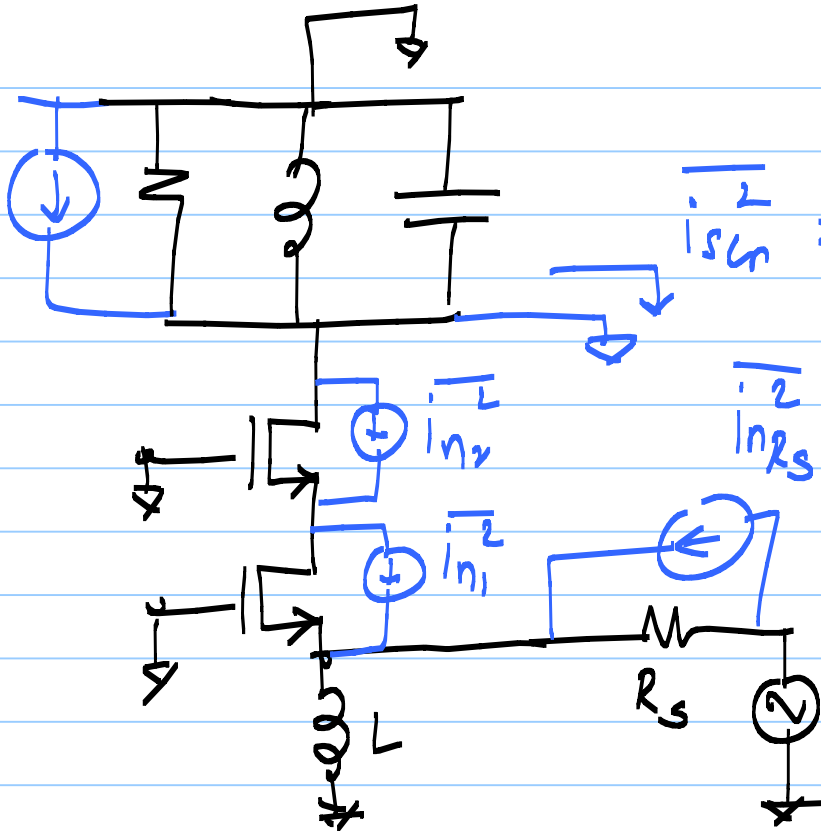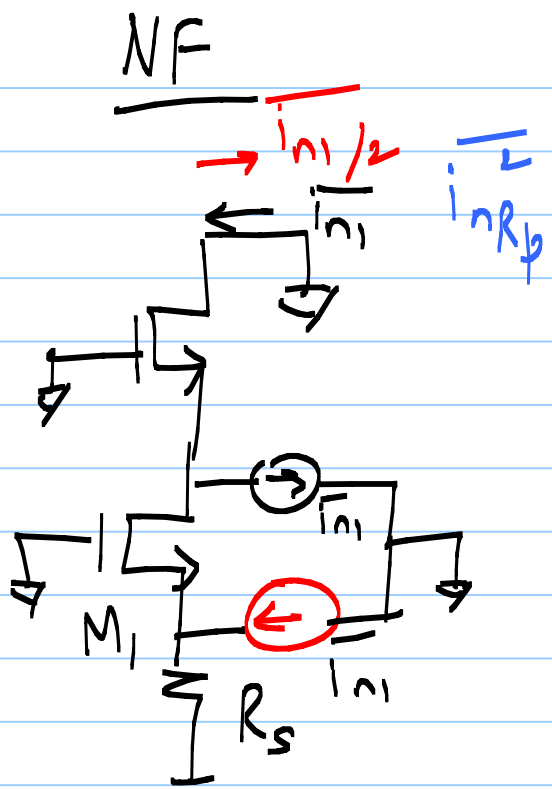

$$i_{scn}^2 = \frac{i_{nR_s}^2}{4} + \frac{i_{n1}^2}{4} + i_{nR_p}^2$$

$$F = \frac{i_{scn}^2}{i_{nR_s}^2/4}$$

$$F = 1 + \frac{\frac{4kT\gamma g_{m1}}{4} + \frac{4kT}{R_p}}{\frac{4kT}{4R_s}} = 1 + \frac{4R_s}{R_p} + \gamma$$

$$F = 1 + \gamma + 4R_s/R_p$$

e.g.  $R_p = \infty$  }  $F = 1.67$   
 $\gamma = 2/3$  }  $NF = 2.2 \text{ dB}$

