
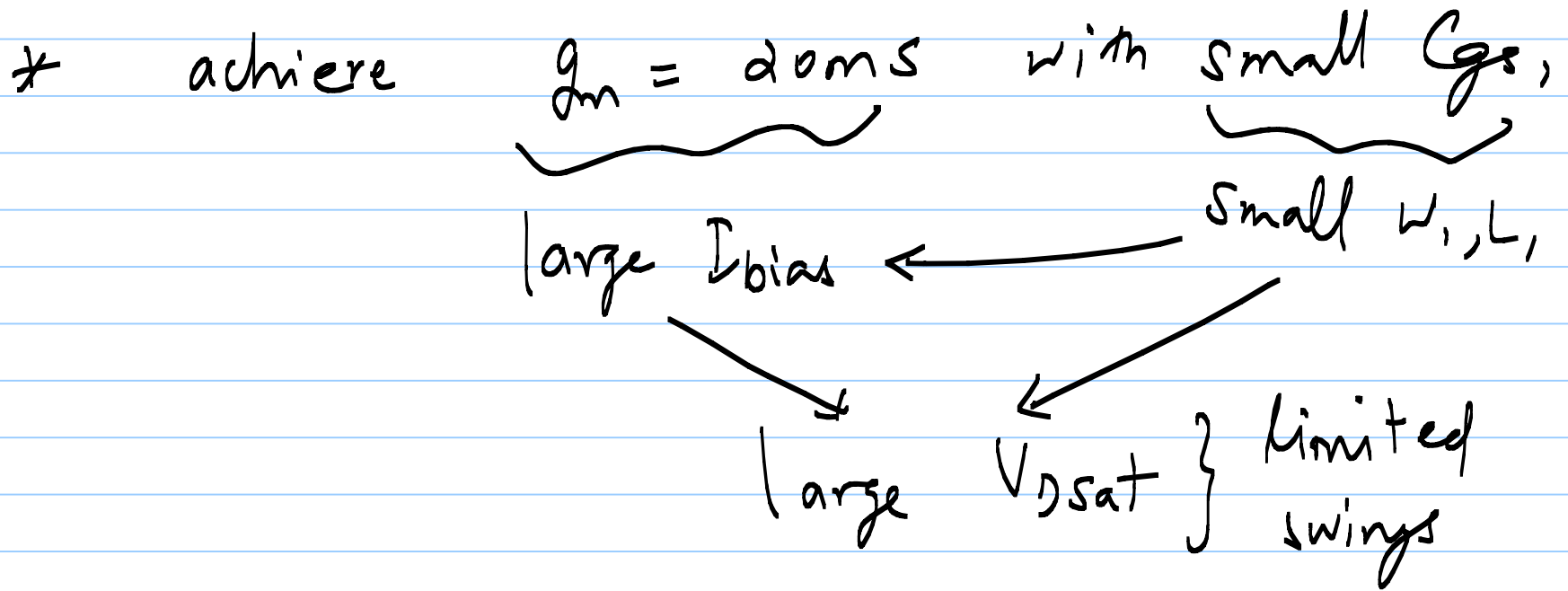


11/2/20

Lec 12

Wide band CG LNA

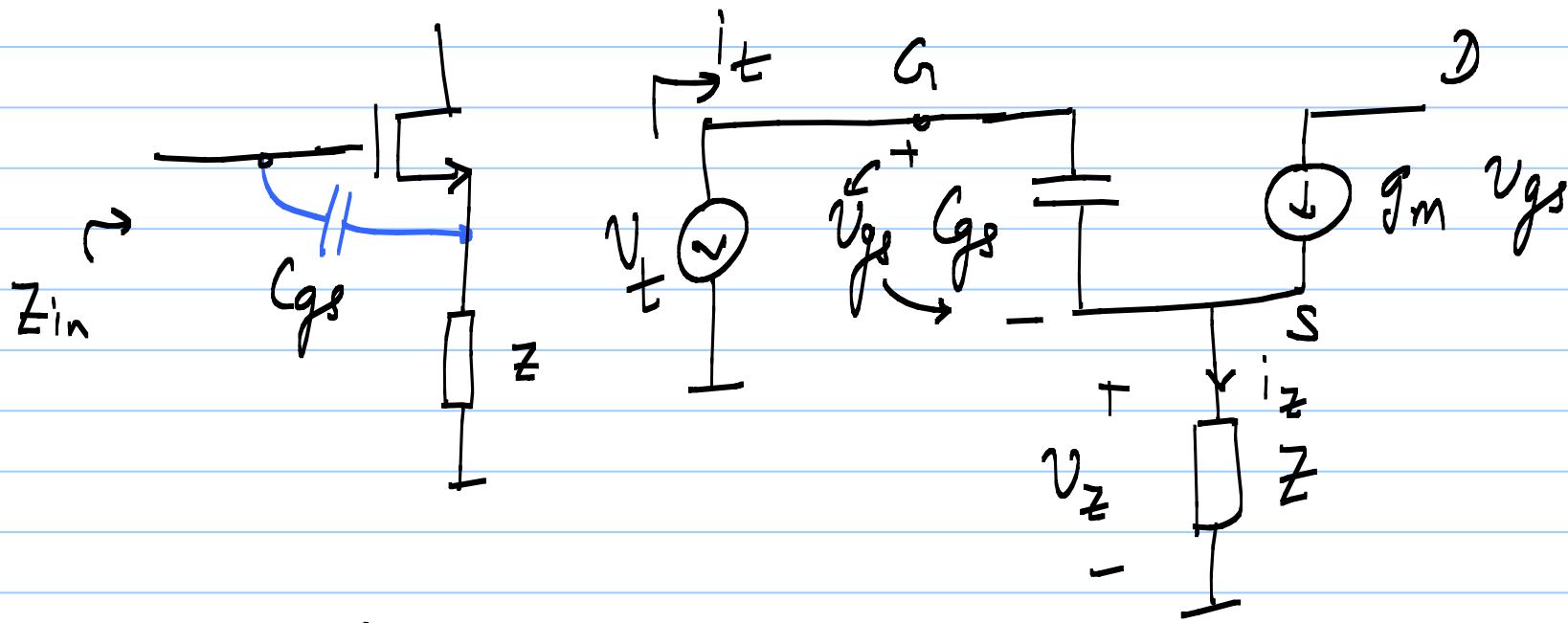



$$Z_{in} = \frac{v_t}{i_t} = ?$$

$$v_{gs} = \frac{i_t \cdot 1}{sC_{gs}} \quad ; \quad i_z = i_t + g_m v_{gs}$$

$$= i_t + \frac{g_m}{sC_{gs}} \cdot i_t$$

$$v_z = i_z \cdot Z = i_t \cdot Z \left( 1 + \frac{g_m}{sC_{gs}} \right)$$

$$v_t = v_{gs} + v_z$$


$$v_t = \frac{i_t}{sC_{gs}} + i_t \cdot Z \left[ 1 + \frac{g_m}{sC_{gs}} \right]$$

$$Z_{in} = \frac{v_t}{i_t} = \underbrace{\frac{1}{sC_{gs}}}_{\text{capacitive}} + \underbrace{Z}_{Z} + \underbrace{\frac{g_m}{sC_{gs}} \cdot Z}$$


$$\frac{g_m}{C_{gs}} \approx \omega_T = 2\pi f_T$$

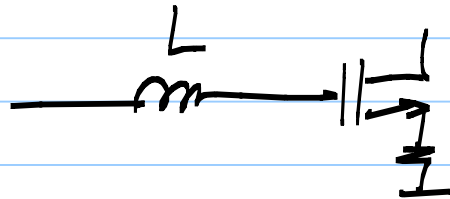1)  $Z = R \Rightarrow Z_{in} = \frac{1}{j\omega C_{gs}} + R + \frac{g_m R}{j\omega C_{gs}}$

add  $\overset{L}{\text{---}} \text{ in series with input}$



HW: noise figure

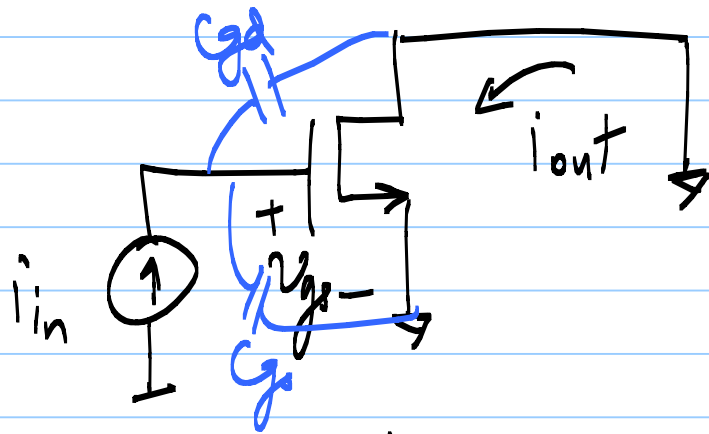

$$\left| \frac{i_{out}}{i_{in}} \right| = 1 \quad \begin{array}{l} @ \omega_T \\ @ f_T \end{array}$$

transition freq.


$$V_{gs} = \frac{i_{in}}{sC_{gs}}$$

$$i_{out} = g_m V_{gs} = \frac{g_m}{sC_{gs}} \cdot i_{in}$$

$$@ \omega = \omega_T = \frac{g_m}{C_{gs}}, \quad \left| \frac{i_{out}}{i_{in}} \right| = 1$$

$$\omega_T = \frac{g_m}{C_{gs} + C_{gd}}$$

HW: NF of following circuit

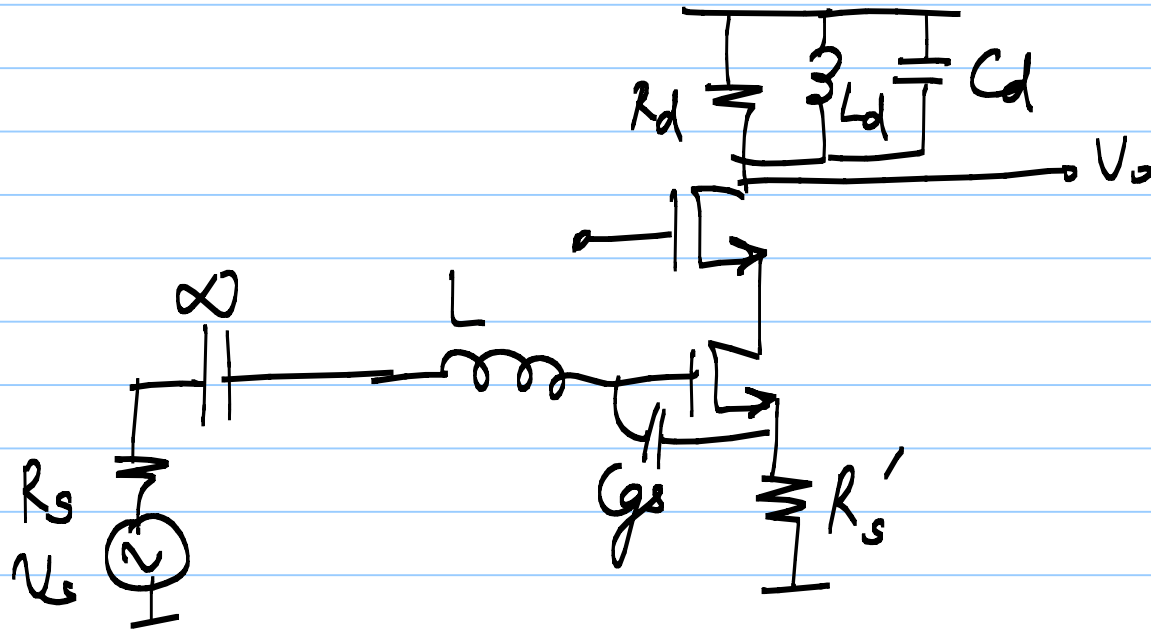

$$2) \quad Z = \text{Capacitance} = \frac{1}{j\omega C_s}$$

$$Z_{in} = \underbrace{\frac{1}{j\omega C_{gs}} + \frac{1}{j\omega C_s}}_{\text{capacitive}} + \underbrace{\frac{g_m}{j\omega C_{gs}} \cdot \frac{1}{j\omega C_s}}_{\frac{-g_m}{\omega^2 C_{gs} C_s}}$$

$$3) \quad Z = \text{---} L_s$$


$$Z_{in} = \underbrace{\frac{1}{j\omega C_{gs}} + j\omega L_s}_{\text{noiseless input match}} + \underbrace{\frac{g_m}{j\omega C_{gs}} \cdot j\omega L_s}_{\leftarrow \frac{g_m}{C_{gs}} \cdot L_s = \omega_T L_s}$$

noiseless  
input match


$$\leftarrow \frac{g_m}{C_{gs}} \cdot L_s = \omega_T L_s$$

\* set  $\omega_T L_s = 50 \Omega$  } does not  
 / } guarantee that  
 $\frac{I_m}{C_g}$  }  $\frac{1}{j\omega C_g} = -j\omega L_s$

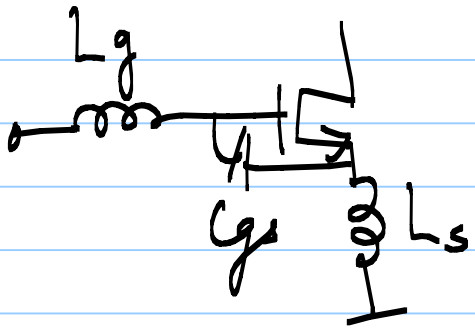If  $\frac{1}{j\omega C_g} > -j\omega L_s \Rightarrow$  use a second ind.  
 $L_g$  to resonate @  
 desired freq.



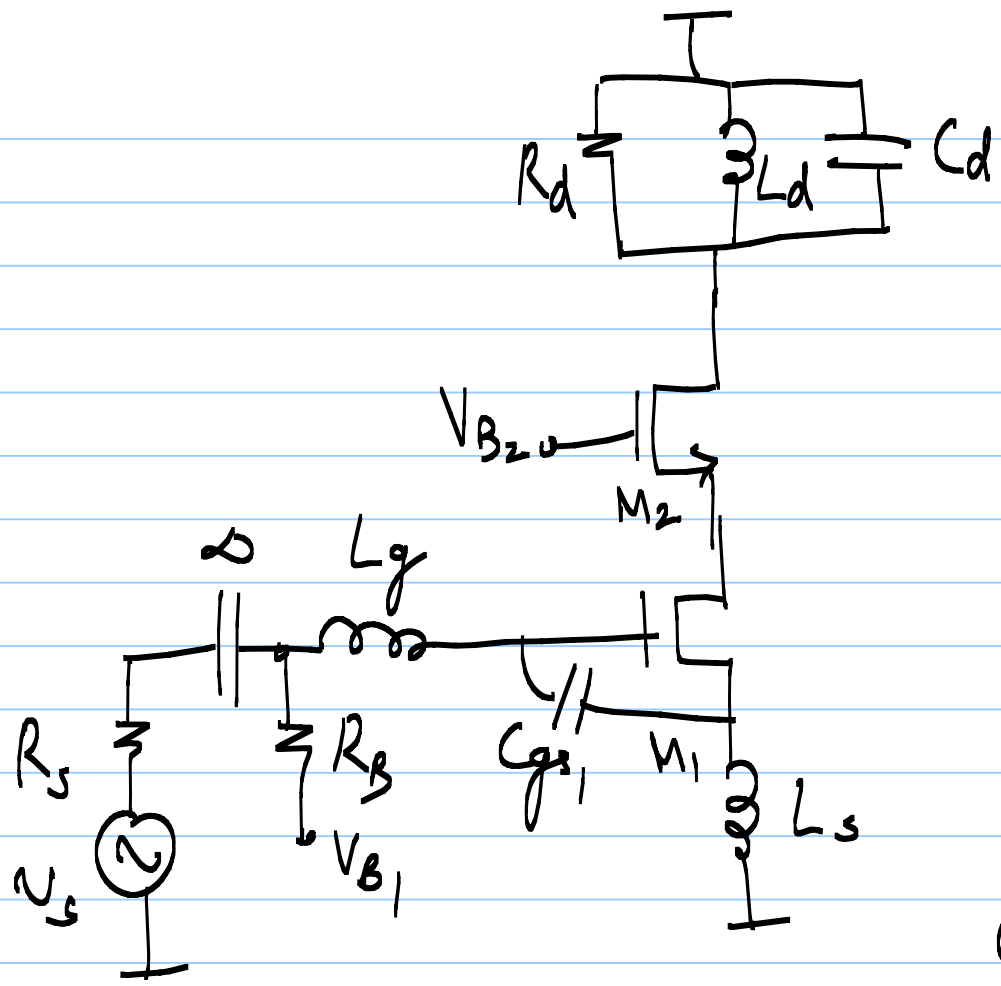\*  $f_0 = \frac{1}{2\pi \sqrt{C_g (L_s + L_g)}}$   
 $\hookrightarrow$  sets  $L_g$



$$f_0 = \frac{1}{2\pi \sqrt{L_d C_d}}$$

Common  
Source  
LNA  
CS LNA