

16/1/20

Lec 2



Resonance

at "resonant" freq.:



$$\omega_0 = \frac{1}{\sqrt{LC}}$$


$$Z_L = -Z_C$$

$Z_{in} = \text{resistive (purely)}$

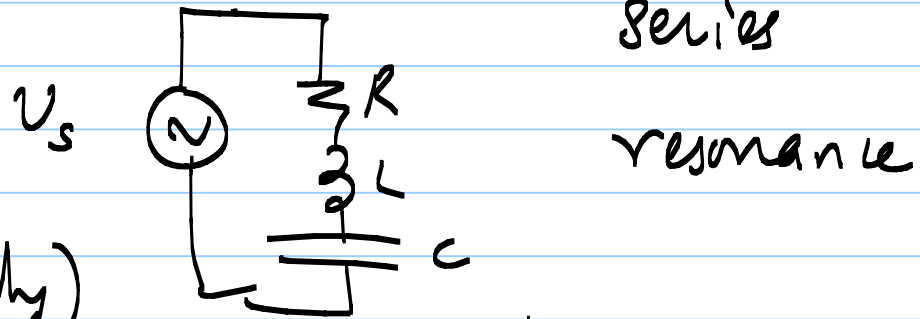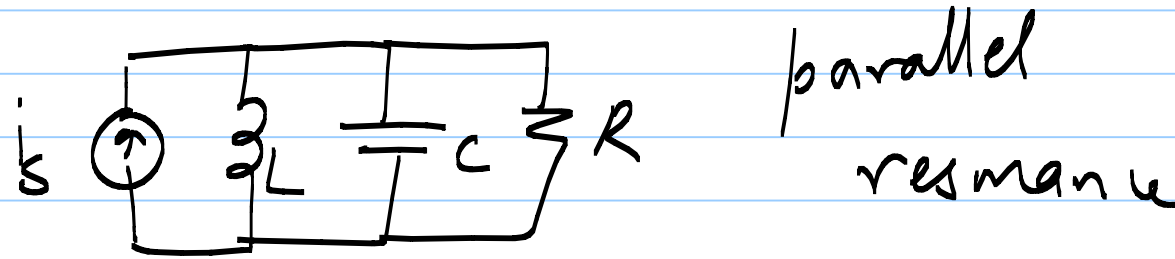

parallel resonance

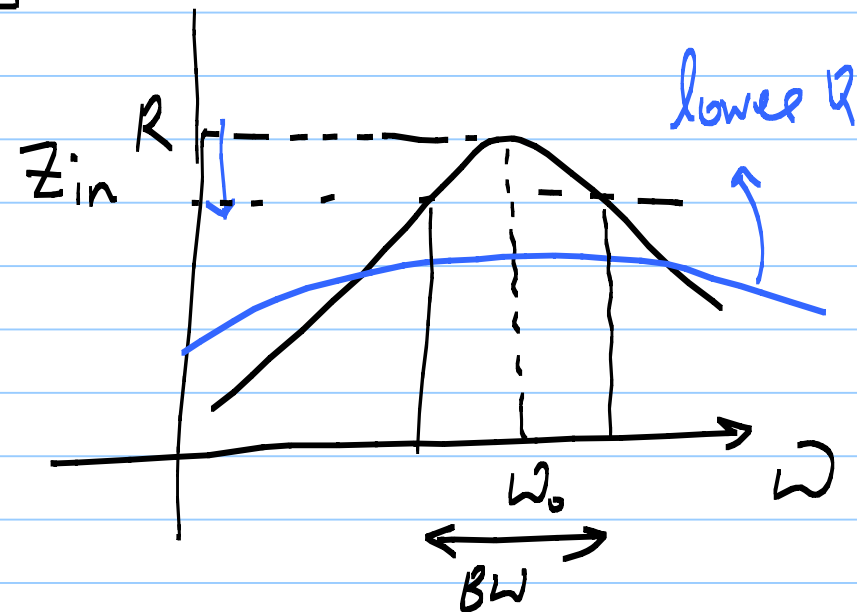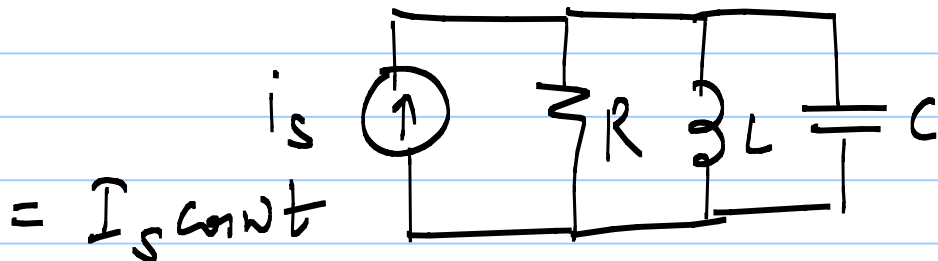

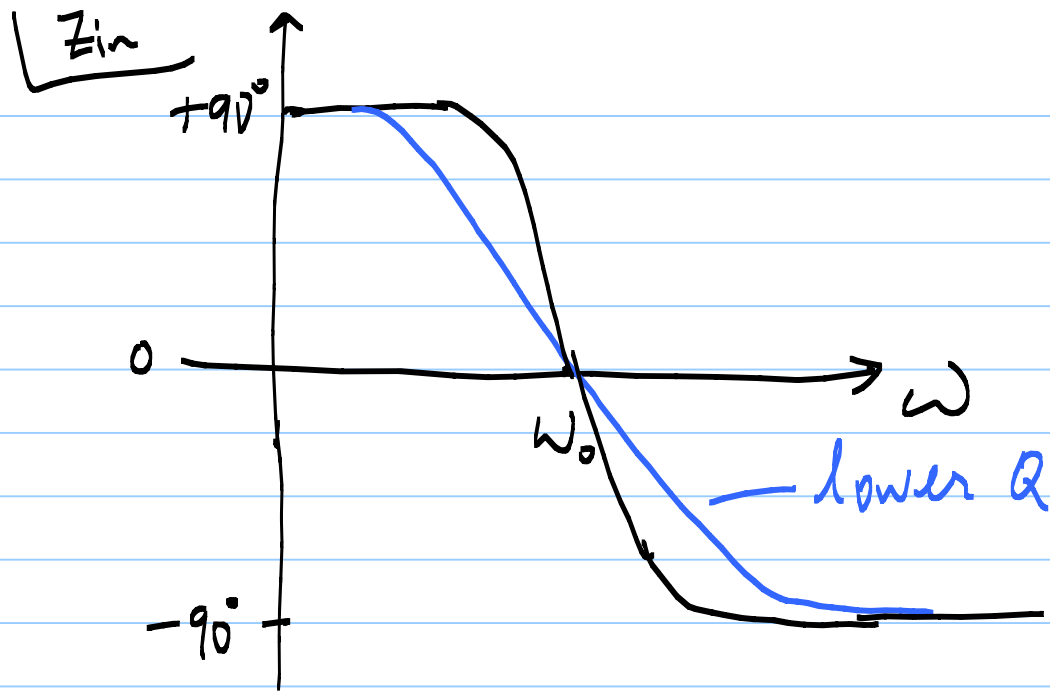

$$Q_3 = -\frac{d\phi_z}{d\omega}$$

$$Q_4 = \frac{\omega_0}{BW}$$

$$\textcircled{a} \quad \omega_0, \quad |I_L| = \frac{I_s \cdot R}{\omega_0 L} = Q \cdot I_s = |I_C|$$

Quality factor:

$$Q_1 = \omega \frac{\text{peak Energy stored}}{\text{Power lost/cycle}}$$

$$Q = R \cdot \sqrt{C/L}$$


$$= \frac{R}{\omega_0 L} \text{ or } \omega_0 R C$$

$$Q_2 = \frac{\text{Re}\{Z\}}{\text{Im}\{Z\}}$$
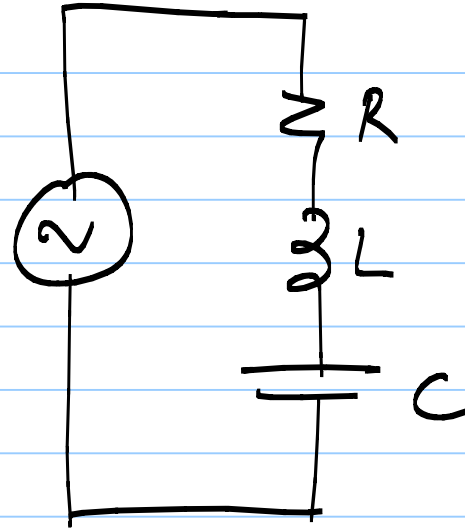
## 2) Series RLC

$$V_s \cos \omega t = v_s$$


$$Q_2 = \frac{\omega_0 L}{R} \quad \omega \frac{1}{\omega_0 RC}$$





@  $\omega_0$ ,


$$|V_L| = |V_C|$$

$$= Q \cdot V_s$$

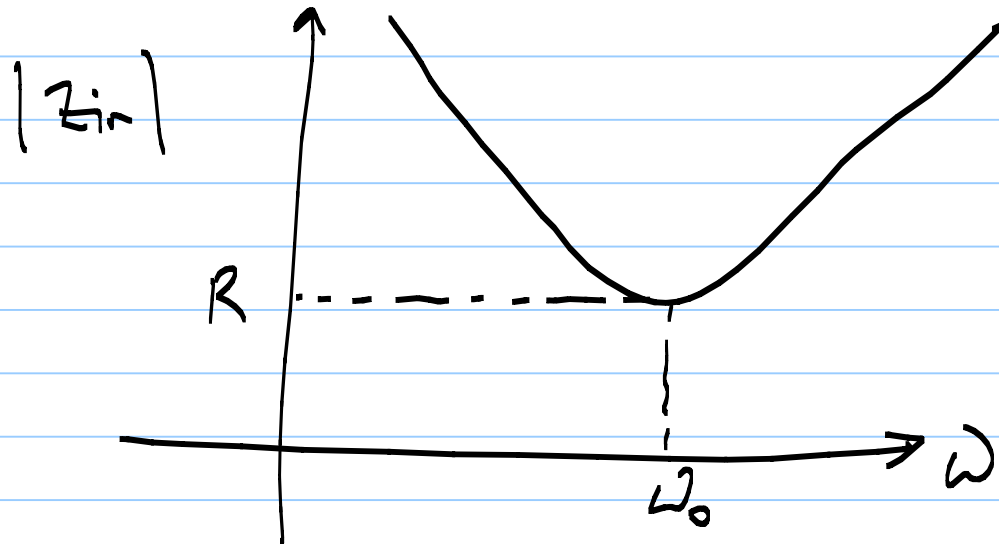

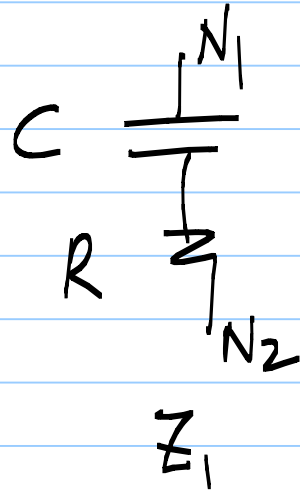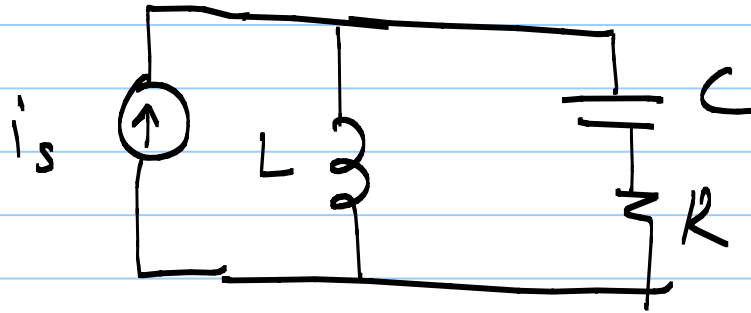

|||

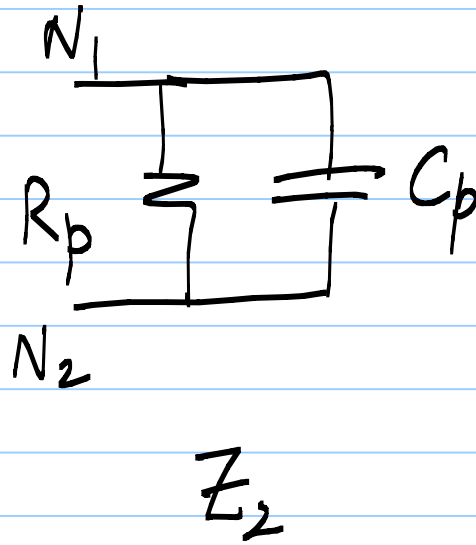

$$Q_2 = Q_1$$

$$L = \omega C_p R_p$$


$$Q_1 = \frac{1}{\omega RC}$$

$$Z_1 = Z_2 \Rightarrow \operatorname{Re}\{Z_1\} = \operatorname{Re}\{Z_2\}$$


$$\operatorname{Im}\{Z_1\} = \operatorname{Im}\{Z_2\}$$

$$C_p = \frac{C}{(\omega RC)^2 + 1} = \frac{C \cdot Q^2}{1 + Q^2}$$
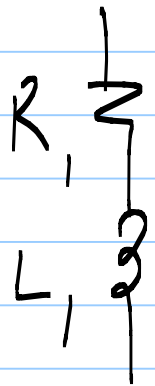
$$R_p = \frac{(\omega CR)^2 + 1}{(\omega CR)^2} \cdot R = R(1 + Q^2)$$



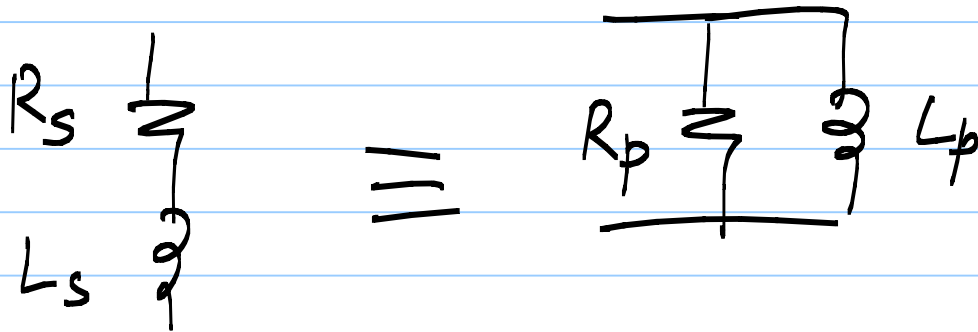
$$Q = \frac{\omega L_1}{R_1} = \frac{\text{Im}(z)}{\text{Re}(z)}$$




$$R_p = R_s (1 + Q^2)$$

$$Q = \frac{\omega L_s}{R_s} = \frac{R_p}{\omega L_p}$$

$$L_p = \frac{L_s (1 + Q^2)}{Q^2}$$

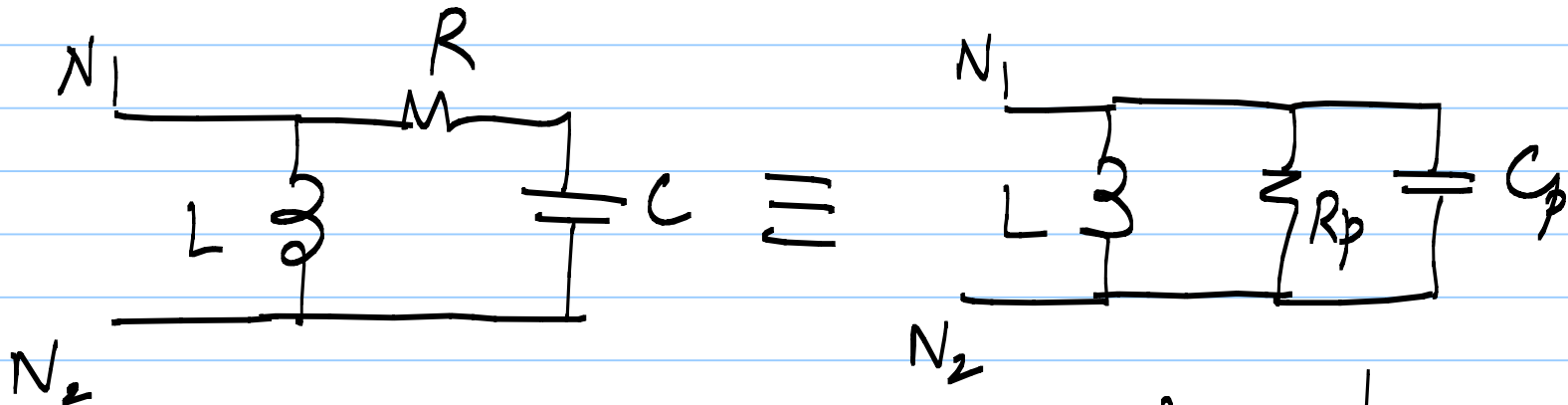

$$\omega = \frac{1}{\sqrt{LCp}}$$

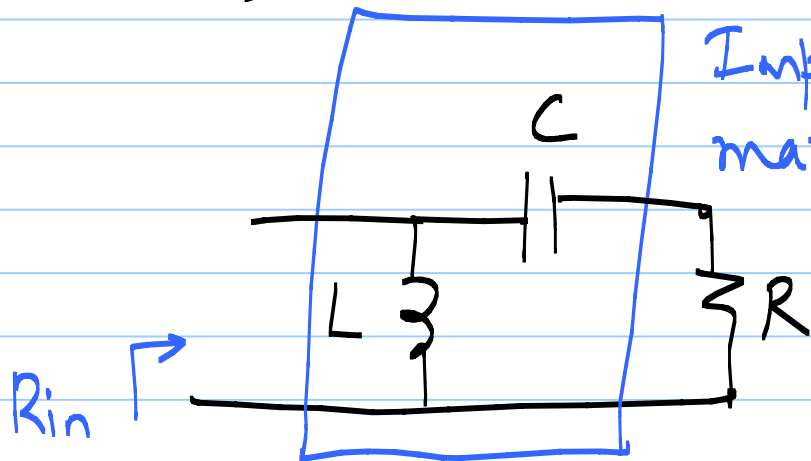

Impedance  
matching  
network

$$R_{in} = R \cdot (1 + Q^2) \text{ @ } \omega$$

$$R_{in} > R$$