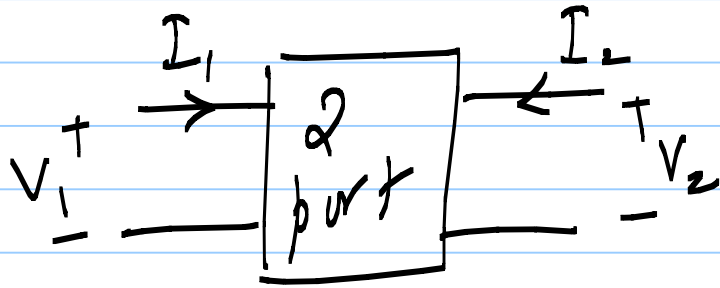


05/3/20

Lec 22


S-parameters




$[Z]$, $[Y]$, $[a]$, $[H]$

$[ABCD]$
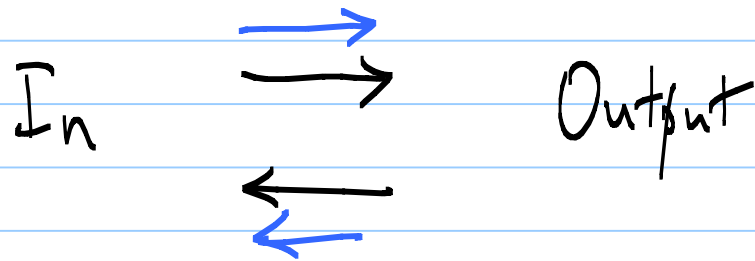
$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$



$[S]$
S-parameters

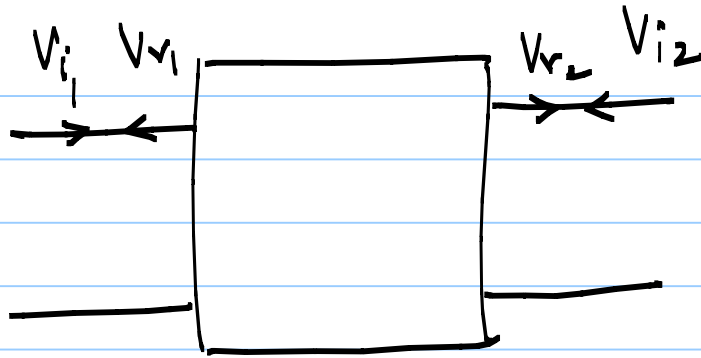

Normalisation
factor of
 $\frac{1}{\sqrt{Z_0}}$


$$\begin{bmatrix} V_{r1}/\sqrt{Z_0} \\ V_{r2}/\sqrt{Z_0} \end{bmatrix} = \underbrace{\begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix}}_{\text{Complex quantities } (x+jy)} \begin{bmatrix} V_{i1}/\sqrt{Z_0} \\ V_{i2}/\sqrt{Z_0} \end{bmatrix}$$

$$a_1 = V_{i1}/\sqrt{Z_0} ; a_2 = V_{i2}/\sqrt{Z_0}$$


$$b_1 = V_{r1}/\sqrt{Z_0} ; b_2 = V_{r2}/\sqrt{Z_0}$$

$$a_1^2 = \text{incident power @ port 1} \dots$$

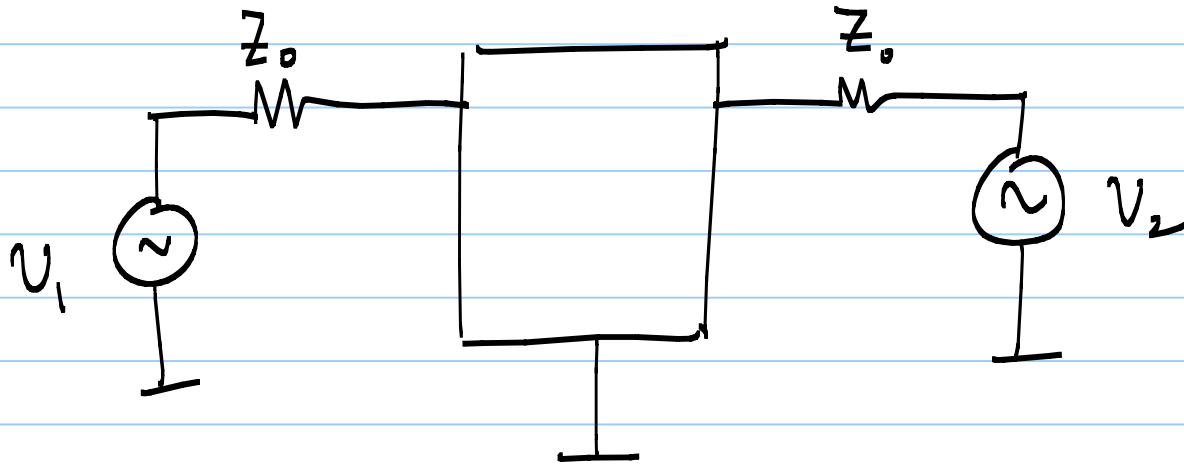$a_1^2, a_2^2, b_1^2, b_2^2$ — power quantities



1-port :

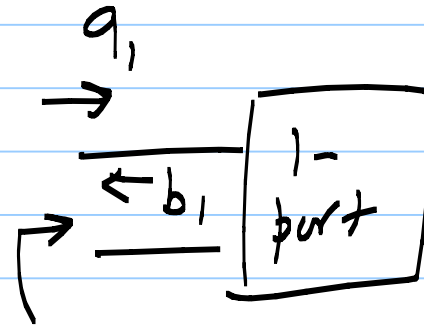


$\frac{b_1}{a_1} = S_{11} = \Gamma$
reflection coefficient

matched impedance : $Z_{in} = Z_0$

$$\Gamma = 0$$

$$|\Gamma| = \left| \frac{Z_{in} - Z_0}{Z_{in} + Z_0} \right|$$

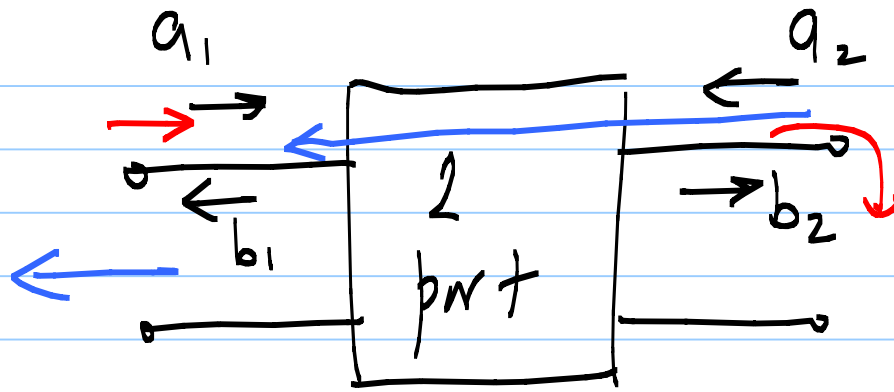

$$\Gamma_f \quad S_{12} = 0$$

$$S_{11} = \frac{b_1}{a_1} = \Gamma$$

$$b_1 = S_{11} a_1 + S_{12} a_2$$




$$b_2 = S_{21} a_1 + S_{22} a_2$$

related
to power
gain


reverse
transmission




S_{11} & S_{22}
decide whether
input & output
ports are matched
to Z_0

(affects stability in active systems)

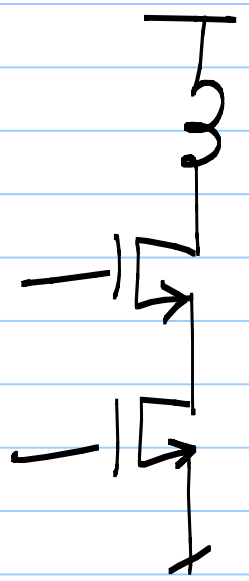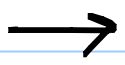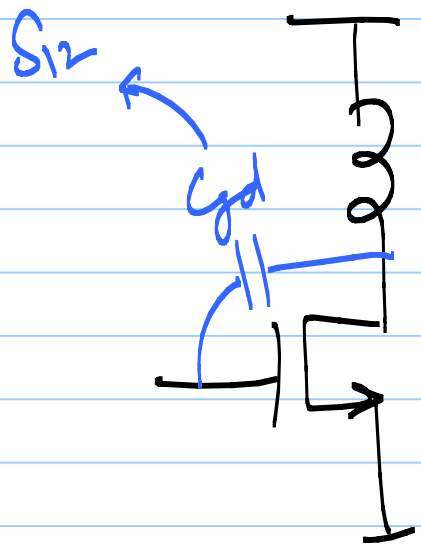


CGLNA

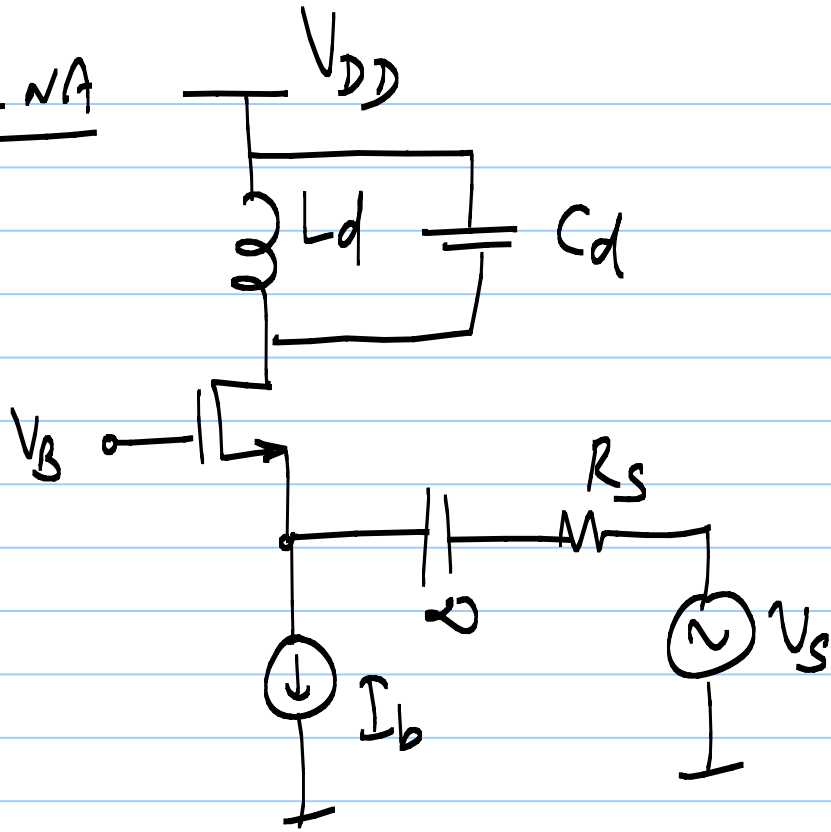

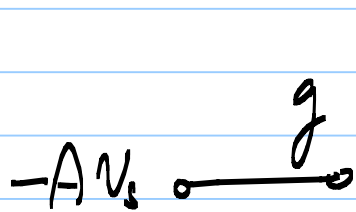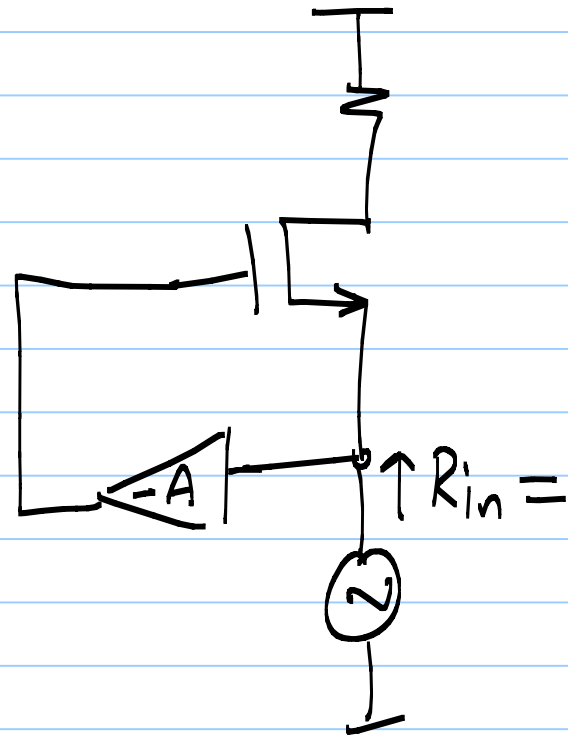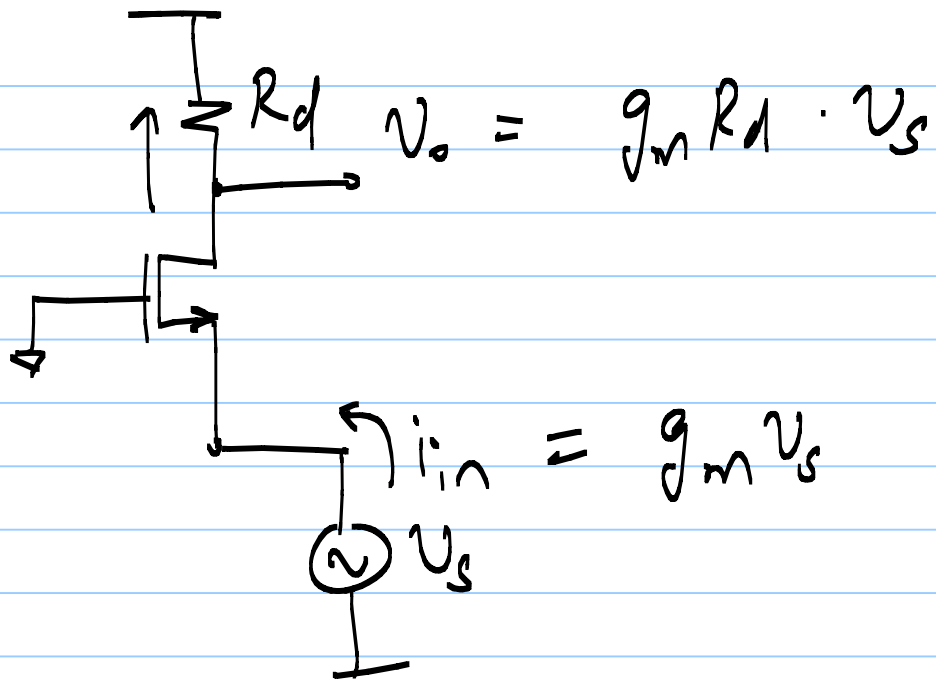

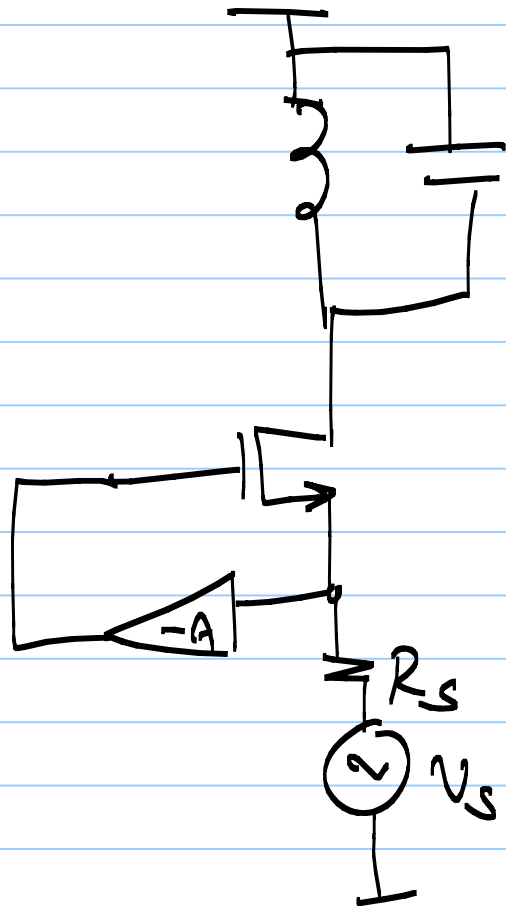$g_m v_{gs} = g_m (-A v_s - v_s)$
 $= -(A+1) g_m \cdot v_s = -i_s$
 $\frac{v_s}{i_s} = \frac{1}{g_m(A+1)}$



* Check for effect on

1) NF, 2) noise of A

3) what does A look like

$$R_{in} = \frac{1}{(A+1)g_m}$$

e.g. $A = 1$

$$R_{in} = \frac{1}{2g_m}$$