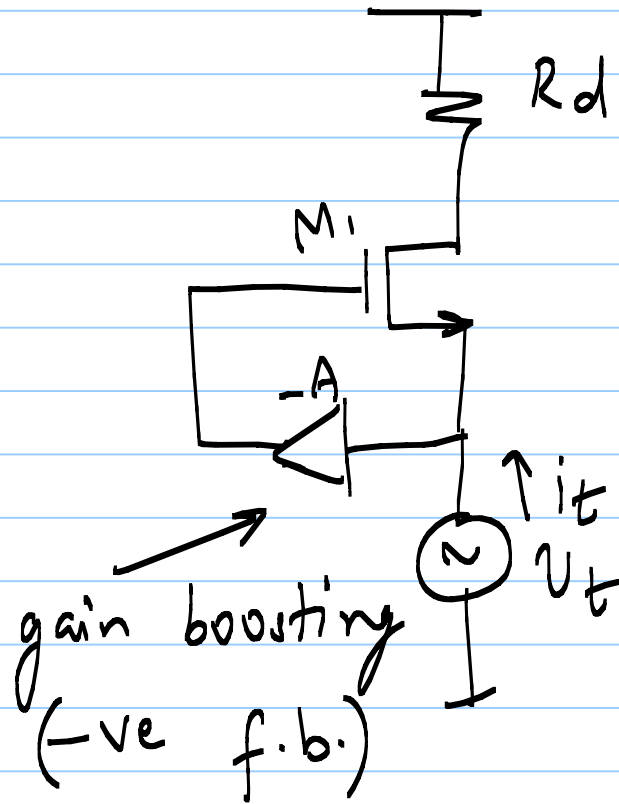


14/3/20

Lec 23




$$Z_{in} = \frac{v_t}{i_t} = \frac{1}{g_m(1+A)}$$

We want  $Z_{in} = 50 \Omega$

for regular c/LNA,  $g_m = 20 \text{ mS}$

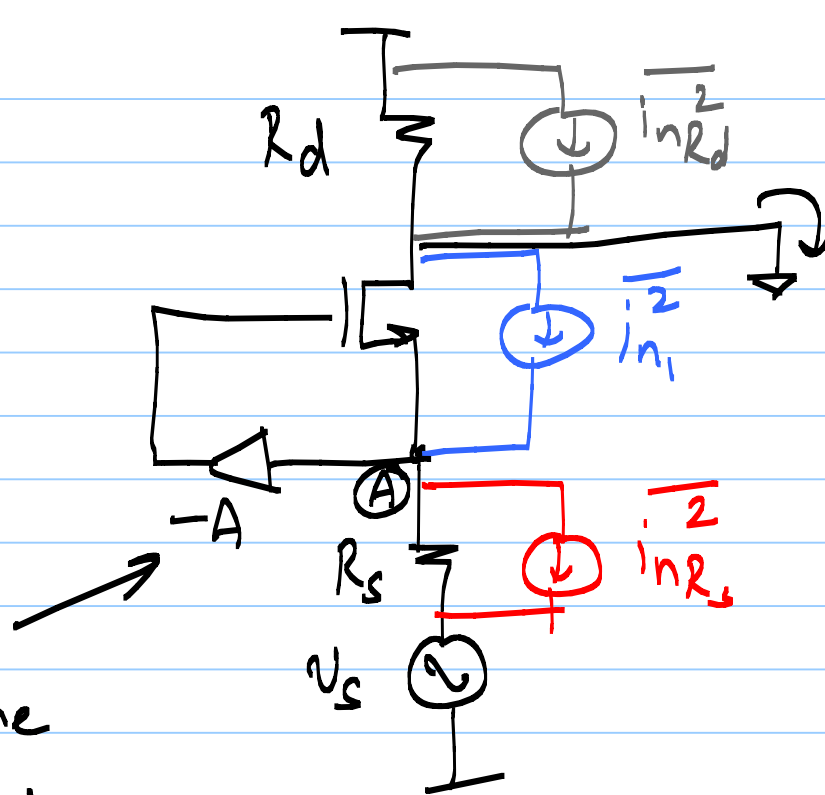here choose  $g_m = \frac{20 \text{ mS}}{1+A}$



$$v_A = \frac{v_s}{2}; \quad g_m = \frac{20 \text{ mS}}{1+A}$$

$$R_{in} = \frac{1}{g_m(1+A)} = 50 \Omega$$

$$\overline{i_{scn R_s}^2} = \left| \frac{i_{nR_s}}{2} \right|^2 = kT/R_s$$

$$\overline{i_{scn R_d}^2} = \overline{i_{nR_d}^2} = \frac{4kT}{R_d}$$

$$\overline{i_{scn M_1}^2} = \left| \frac{i_{nM_1}}{2} \right|^2 = kT \gamma g_m$$

assume  
noiseless A

$$NF = 1 + \frac{4kT/R_d + kT \gamma g_m}{kT/R_s}$$

$$= 1 + \gamma g_m R_s + \frac{4R_s}{R_d} = 1 +$$

Original CALNA:

$$NF = 1 + \gamma + \frac{4R_s}{R_d}$$

$$g_m = \frac{20mS}{1+A} = \frac{1}{R_s(1+A)}$$

$$g_m R_s = \frac{1}{1+A}$$


$$NF_{\text{gain boosted CALNA}} = 1 + \frac{\gamma}{1+A} + \frac{4R_s}{R_d}$$

Ampl. A adds noise

\* A - CS amplifier

\*  $C_{in}$  of A affects high freq.  $S_{11}$

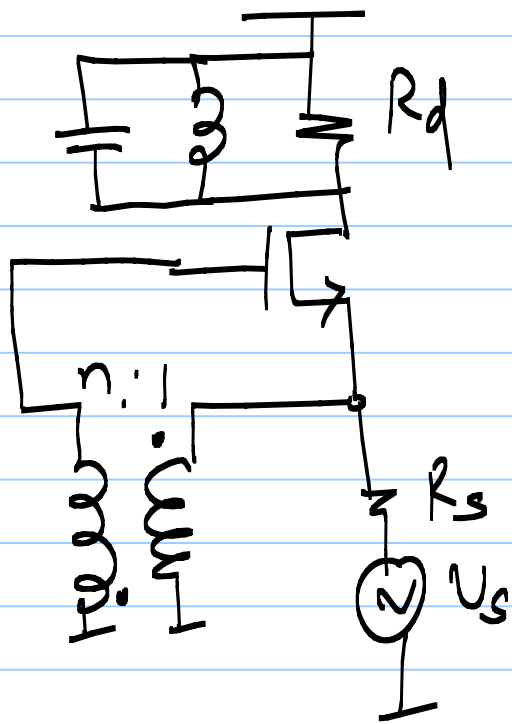- \*  $g_m$  of CSA should be large
  - small device, large current



Use a Xfmr


1:1 Xfmr has  $A=1$

$$NF = 1 + \frac{\gamma}{2} + \frac{4R_s}{R_d}$$



1:n Xfmr can do

much better

$n$  is limited for IC implementations

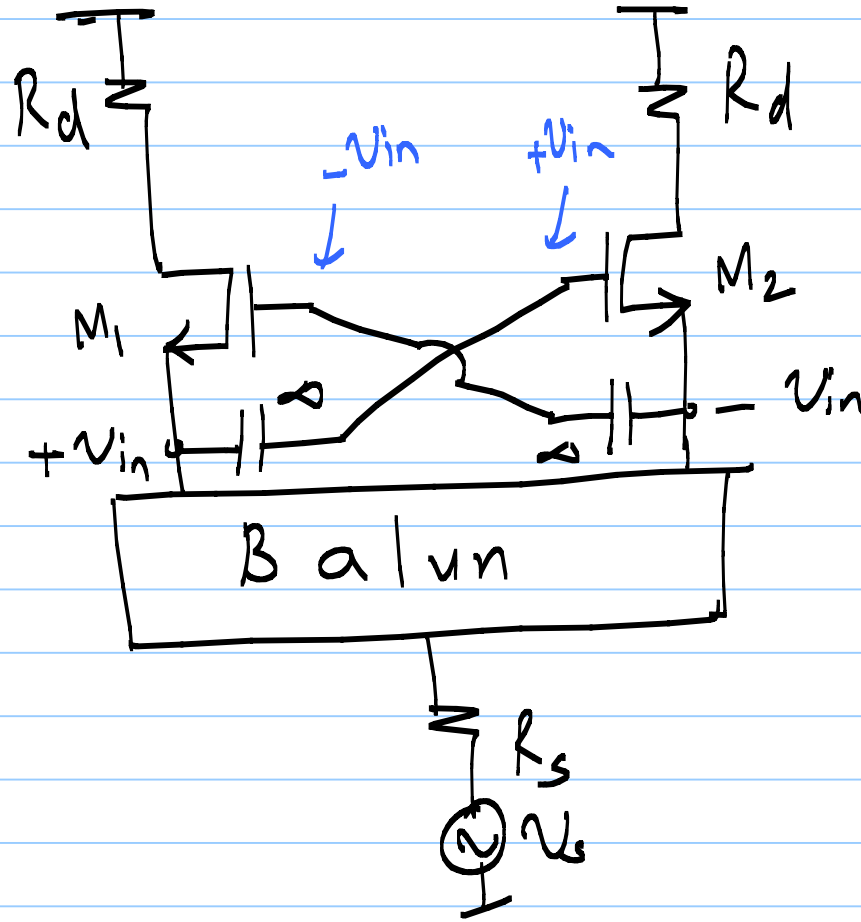

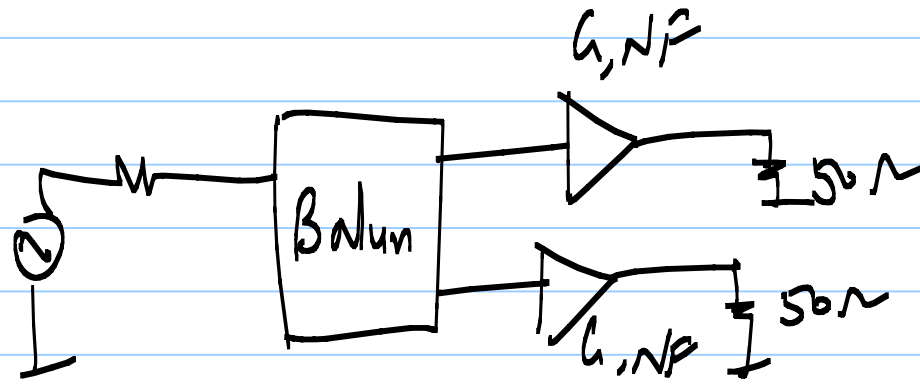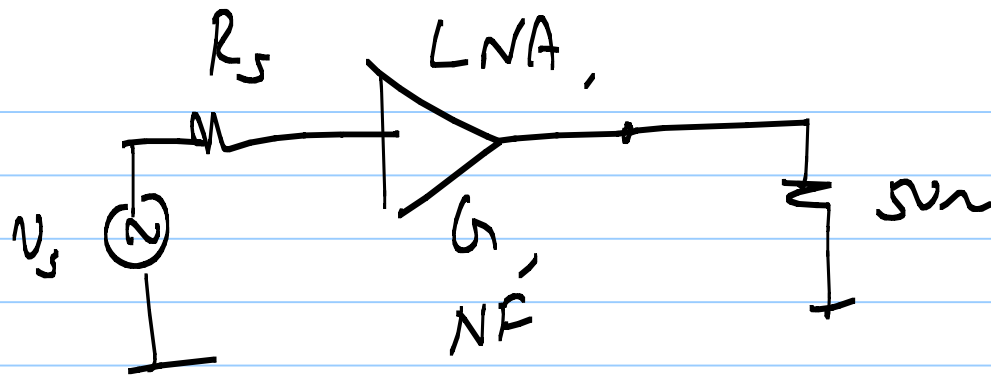\* noise from  $M_1$  &  
 $M_2$  goes down  
 by  $1/2$   
 \* 'Broadband'  
 - balun limits  
 BW



$NF' = ?$

# Ideal Balun

$$[S] = \begin{bmatrix} 0 & 1/2 & 1/2 \\ 1/2 & 0 & 0 \\ 1/2 & 0 & 0 \end{bmatrix}_{3 \times 3}$$

