
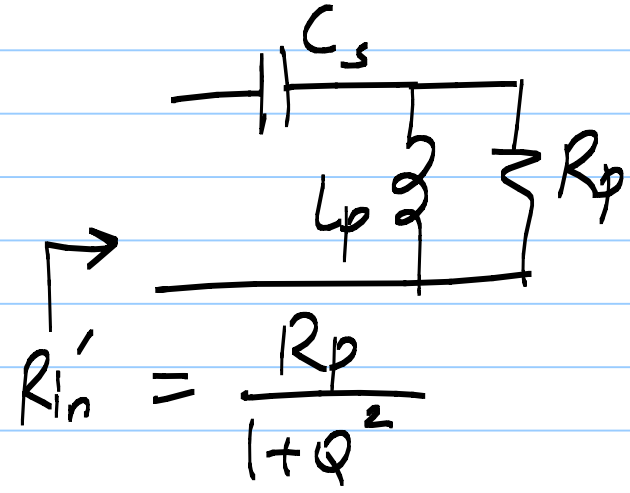


17/1/20



Lec 3

low Q \leftrightarrow wideband MN

high Q \leftrightarrow narrowband MN

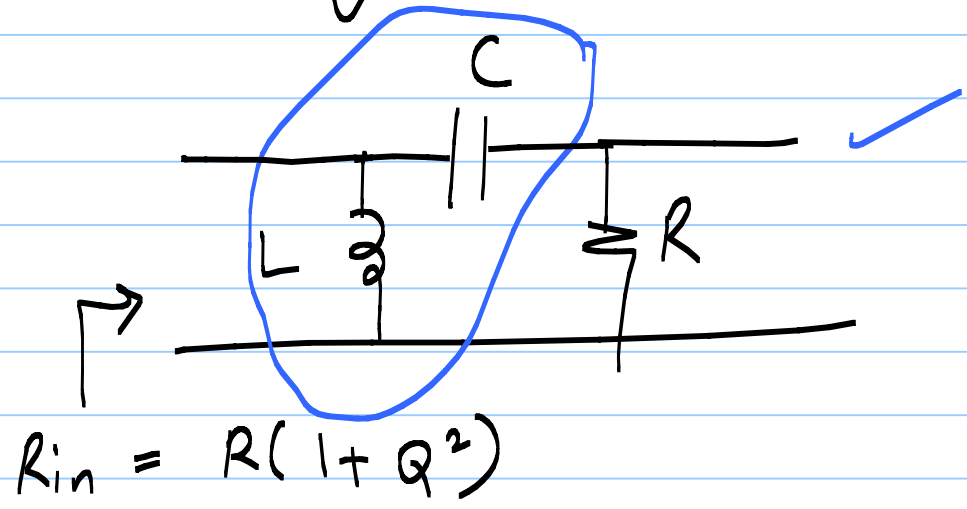

"L-match networks"

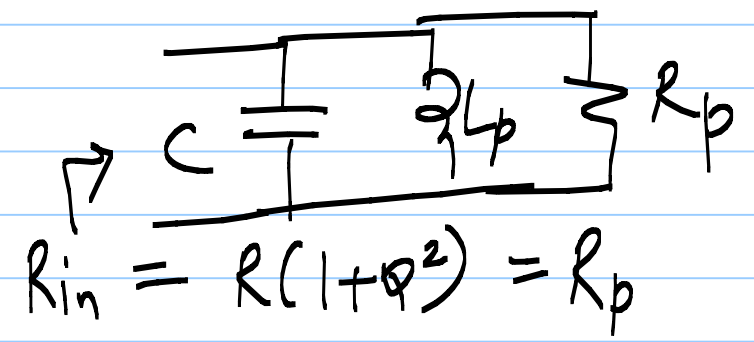
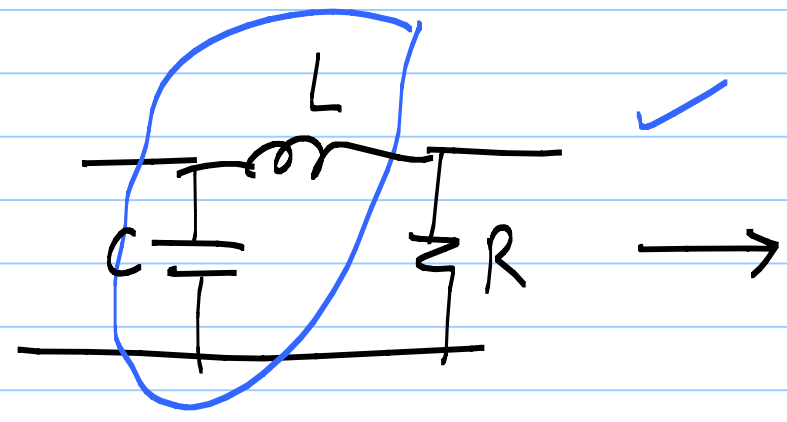


E.g.

R_{in} , R_L , ω
|| || ||
200 Ω 50 Ω 1GHz

$$R_{in} = R_p = R(1 + Q^2)$$


$$Q = \sqrt{\frac{R_p}{R_s} - 1}$$

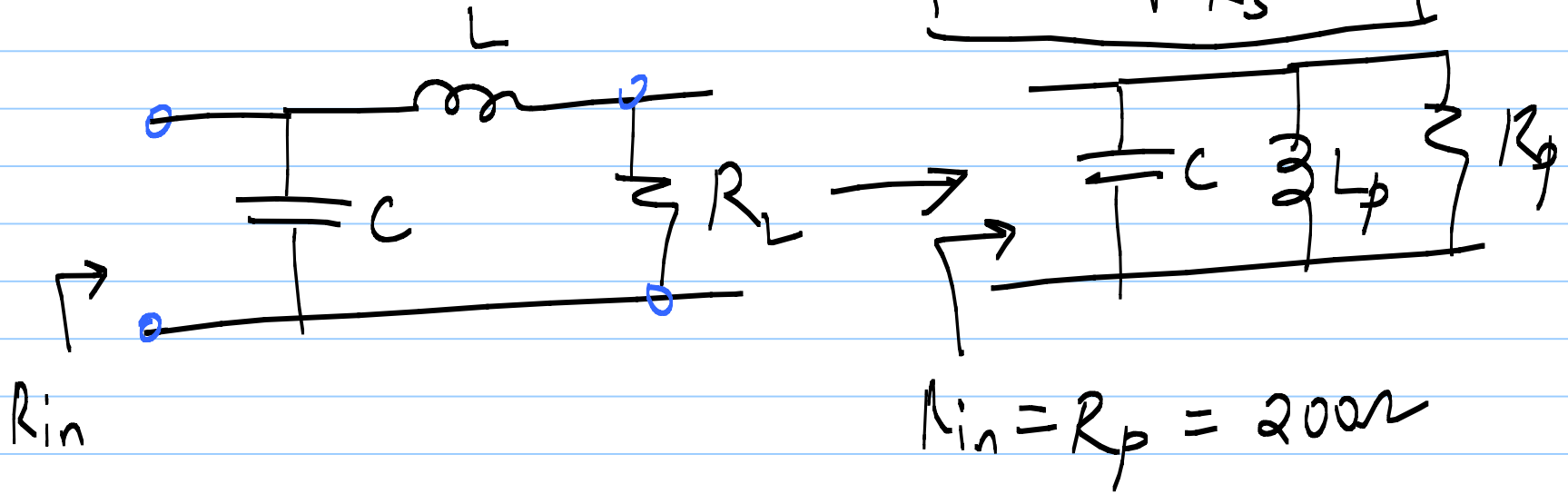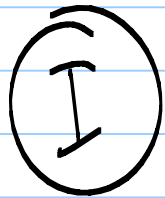

$$Q = \sqrt{3} = 1.732$$

$$Q = \omega C R_p \Rightarrow C = 1.37 \text{ pF}$$
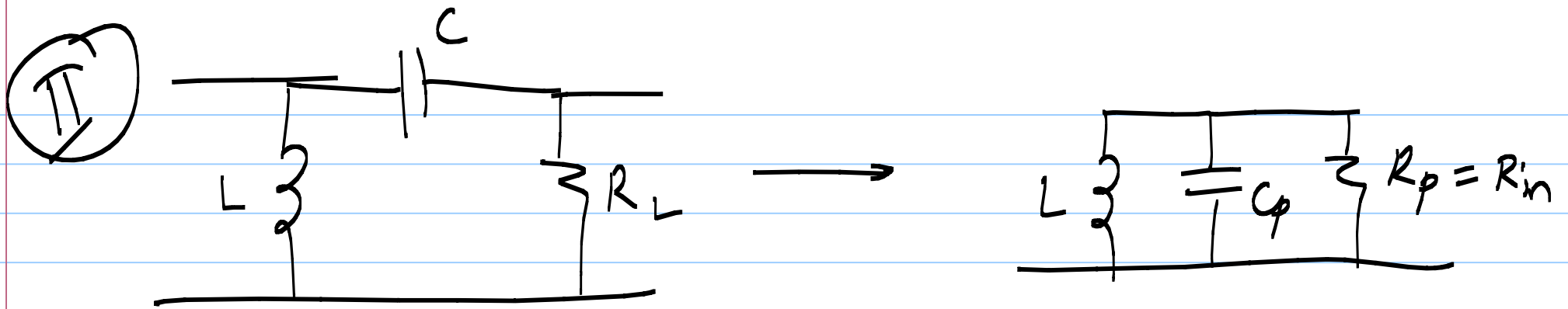
$$Q = \omega L / R_L \Rightarrow L = 13.7 \text{ nH}$$



$$Q = \sqrt{3} = \frac{1}{\omega CR} = \frac{R_p}{\omega L}$$

$$L = 18.4 \text{ nH}$$

$$C = 1.84 \text{ pF}$$




$$\omega = \frac{1}{\sqrt{2} C_p}$$




MN I is better
in terms of area


* 4 types of L-matches $\left\{ \begin{array}{l} \text{up/down match} \\ \text{LP/HP match} \end{array} \right.$

* Π - and T-matches

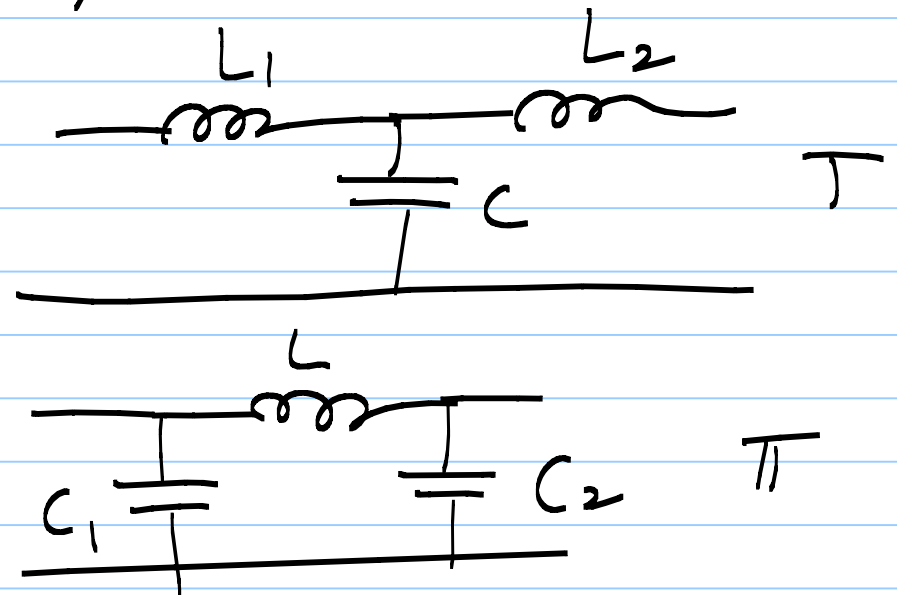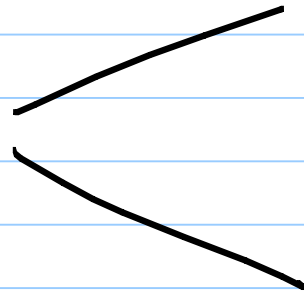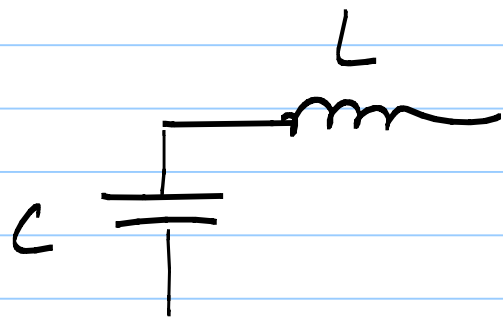
add another degree of freedom to
set Q independent of R_{in}/R_L



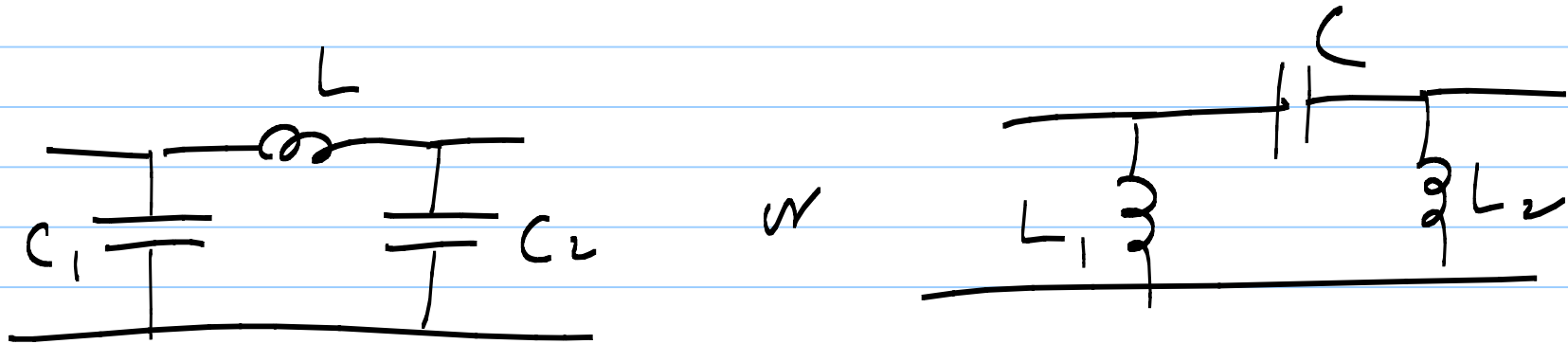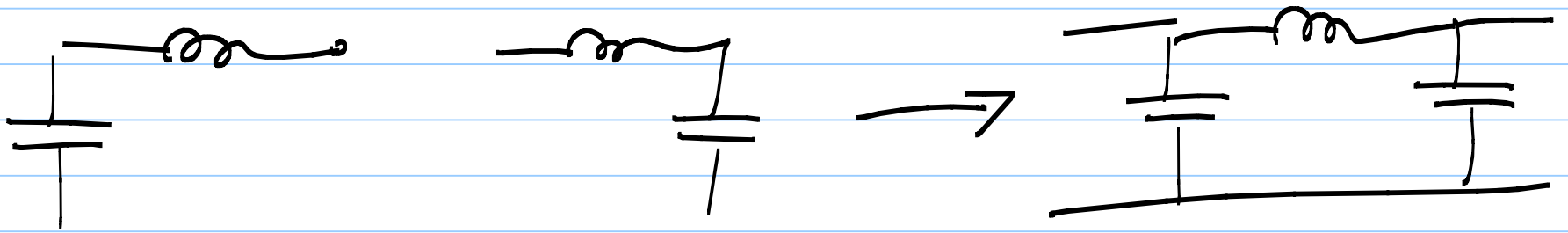
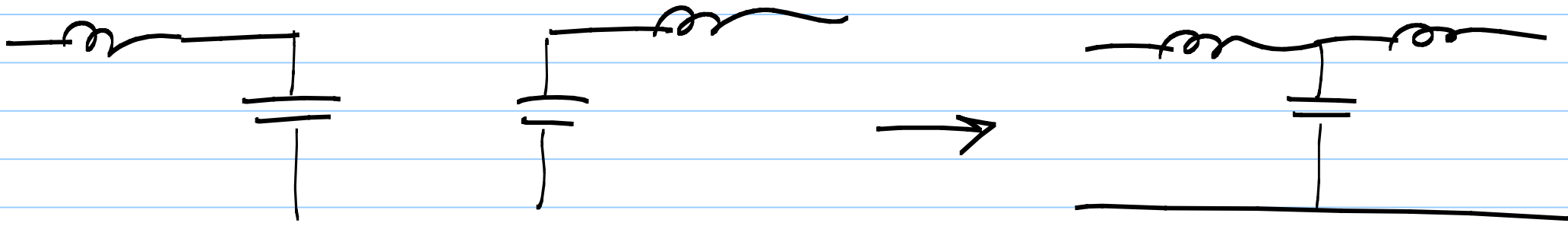


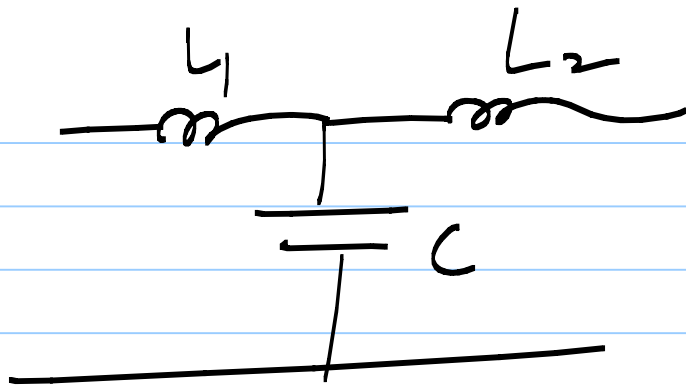


or

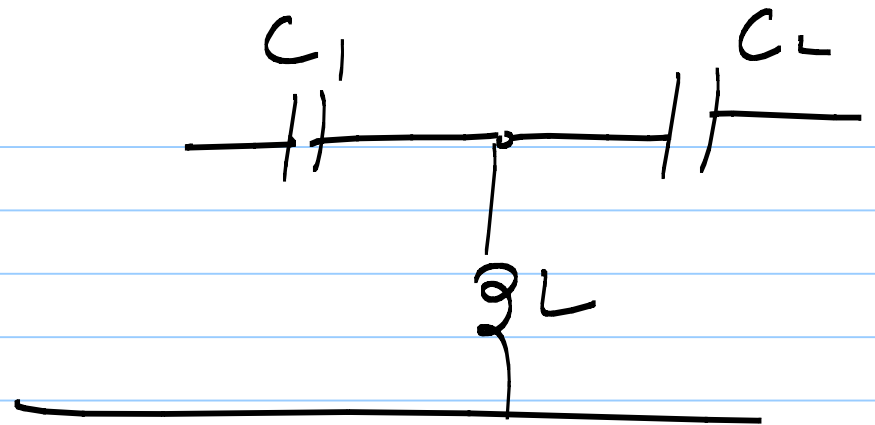

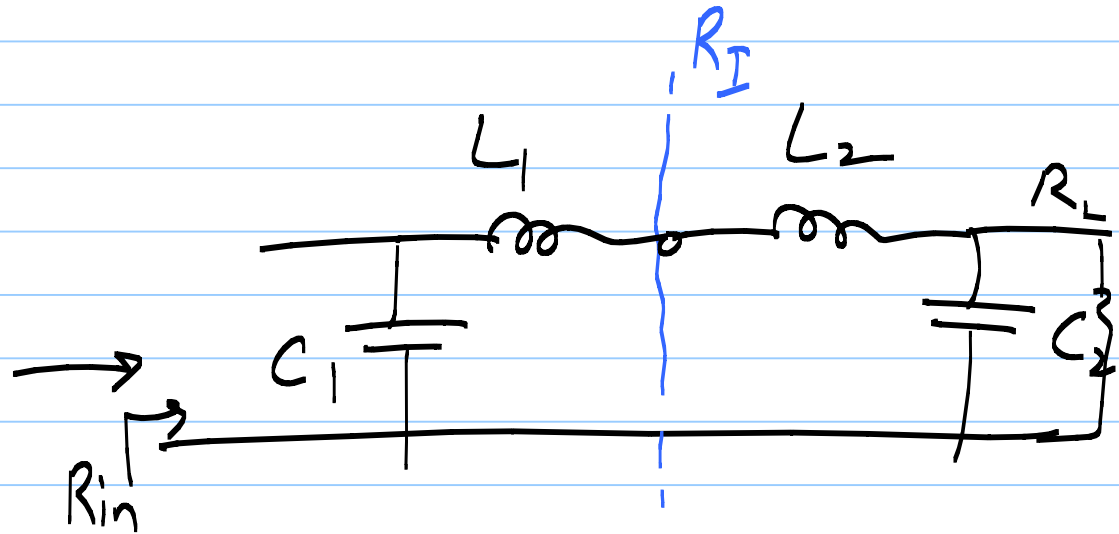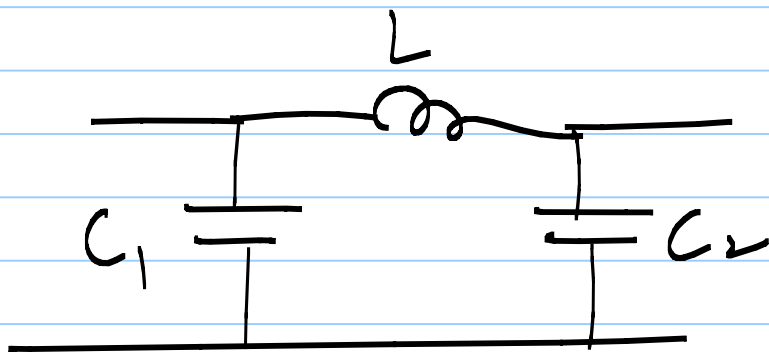Π - & T - matches can set Q independent
of R_L/R_{in}



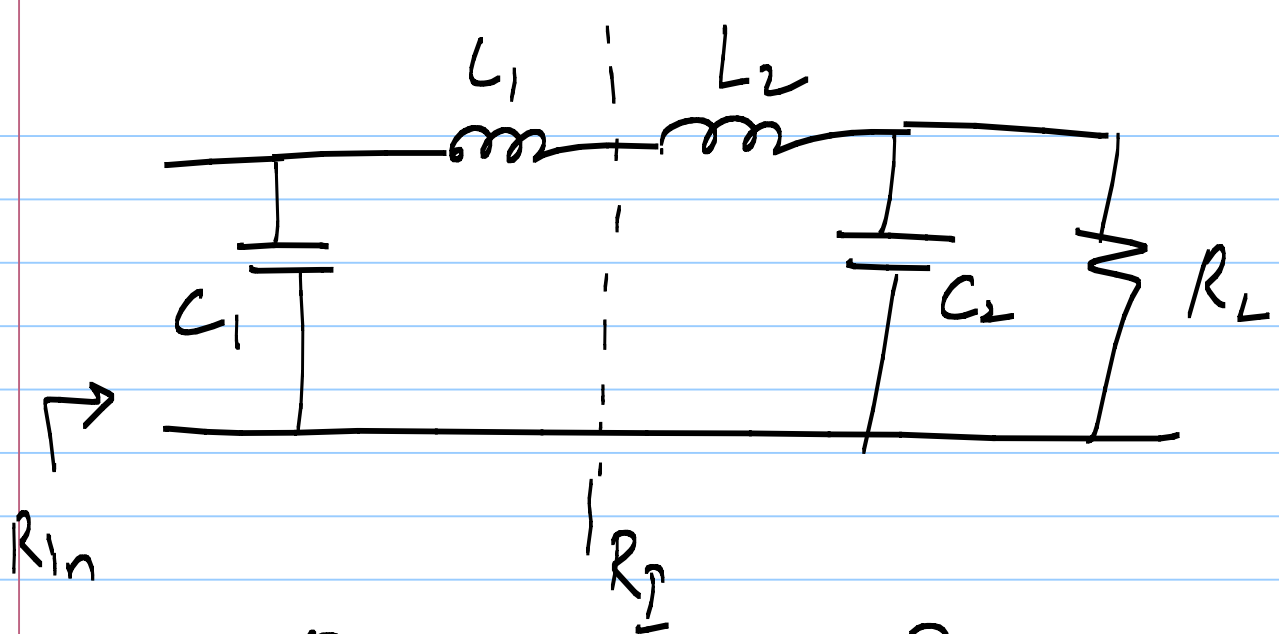

$$Q_R = \sqrt{\frac{R_L}{R_I} - 1}$$

$$R_I < R_L$$

$$Q_L = \sqrt{\frac{R_{in}}{R_I} - 1}$$

$$R_I < R_{in}$$

$$Q_L$$


$$Q_R$$

$$Q = Q_L + Q_R$$

$$Q = \sqrt{\frac{R_{in}}{R_I} - 1} + \sqrt{\frac{R_L}{R_I} - 1}$$

high $Q \leftrightarrow$ small R_I

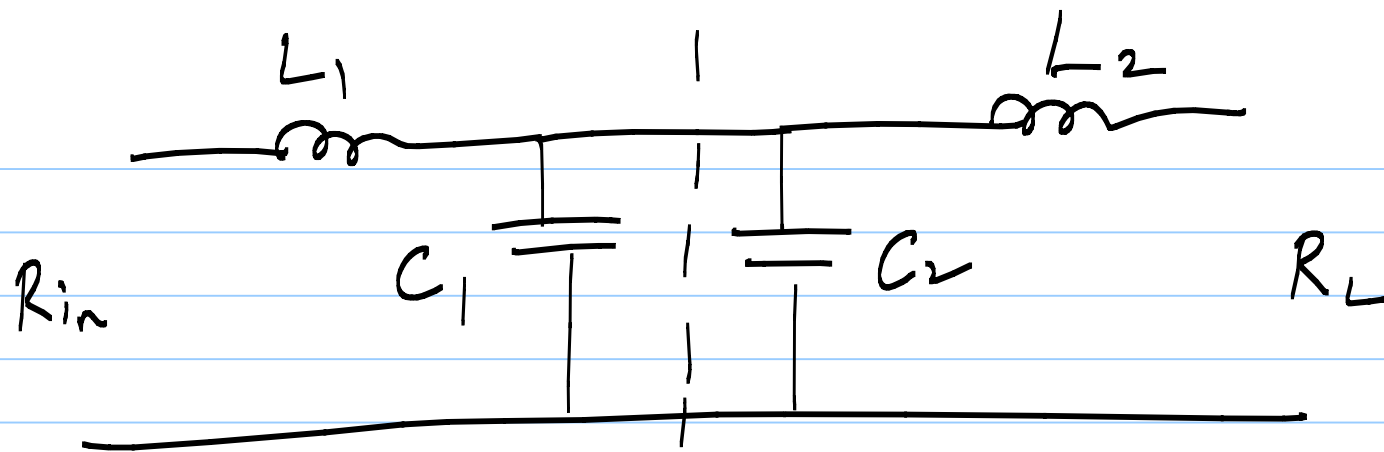* Transformer matching is also possible as a MN



$$R_T > R_{in}, R_L$$

$$Q = \underbrace{\sqrt{\frac{R_T}{R_L} - 1}}_{Q_R} + \underbrace{\sqrt{\frac{R_T}{R_{in}} - 1}}_{Q_L}$$