
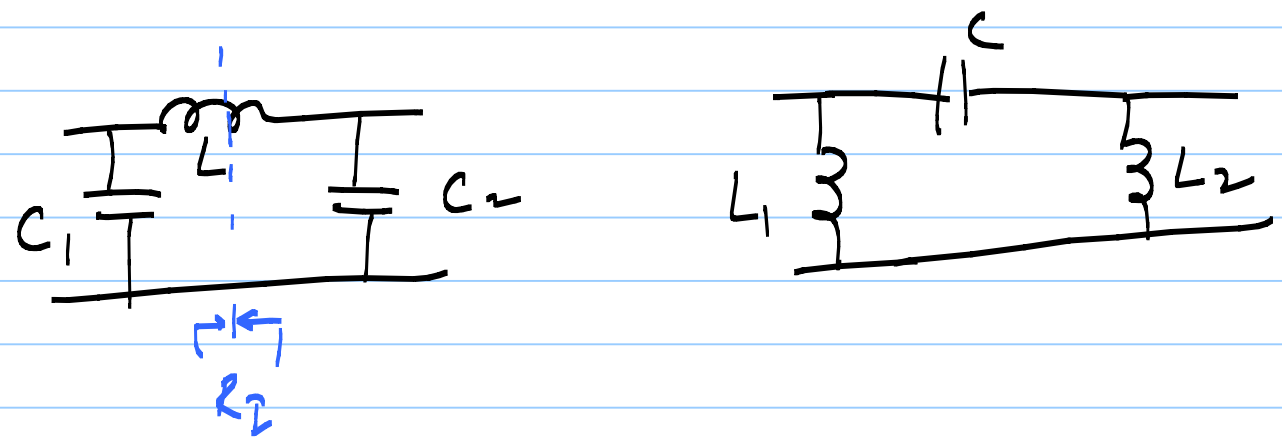


21/1/20

Lec 4

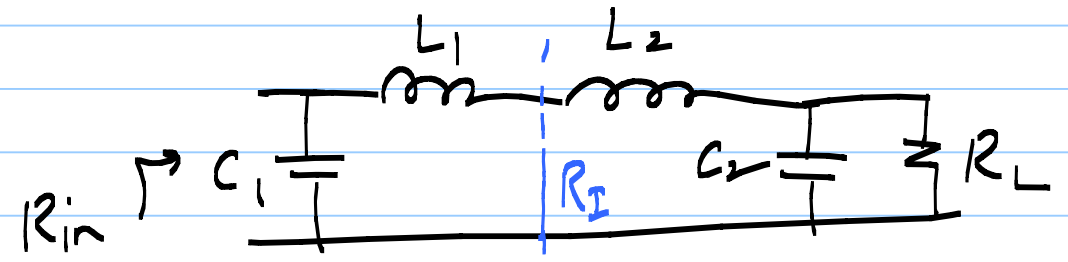

E.g. π match, low pass, $f = 1\text{GHz}$,
 $R_L = 50\Omega$, $R_{in} = 200\Omega$; $Q = 5$




$$Q = Q_L + Q_R = \sqrt{\frac{R_{in}}{R_I} - 1} + \sqrt{\frac{R_L}{R_I} - 1}$$

$$5 = \sqrt{\frac{200}{R_I} - 1} + \sqrt{\frac{50}{R_I} - 1}$$

$$\sqrt{\frac{200}{R_I} - 1} = 5 - \sqrt{\frac{50}{R_I} - 1}$$




$$R_I = 15.2 \Omega$$


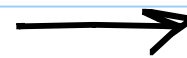


Design the two
L-matches **HW**

Tapped inductor match

{ Tapped C match }

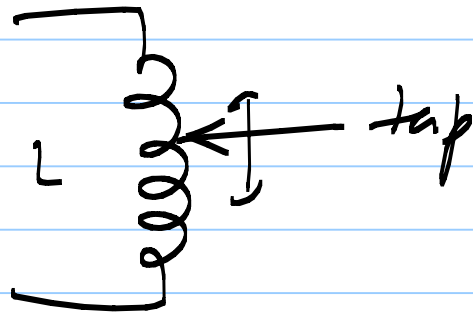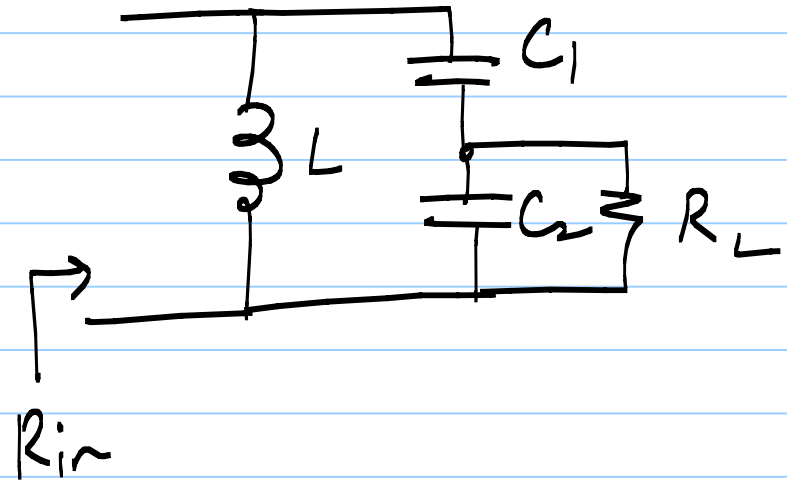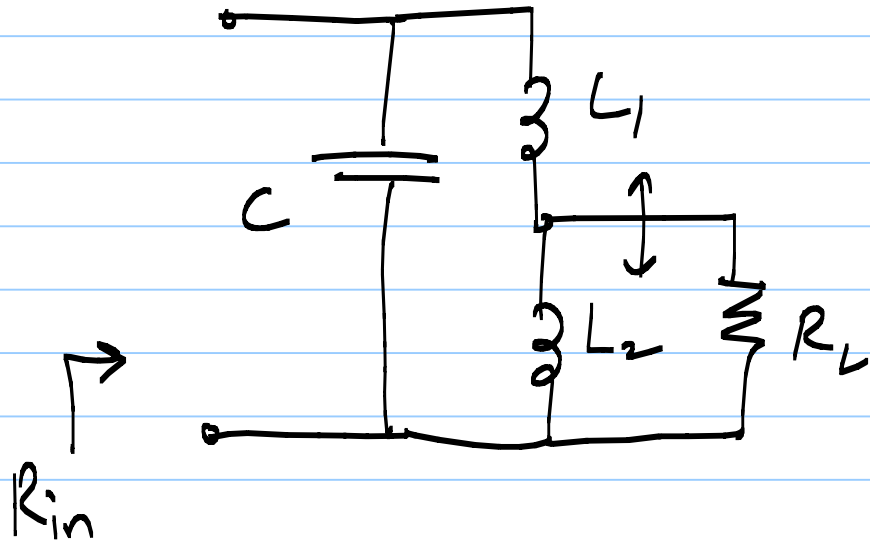


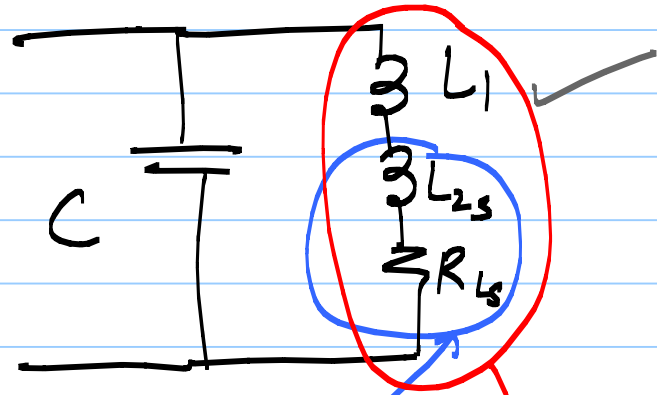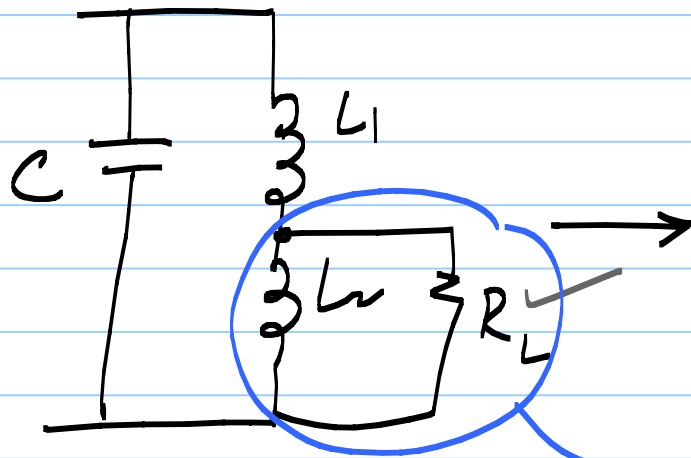

$Q =$

We know $f, Q, \frac{R_{in}}{R_L}$

$R_{in} = R_p \rightarrow$

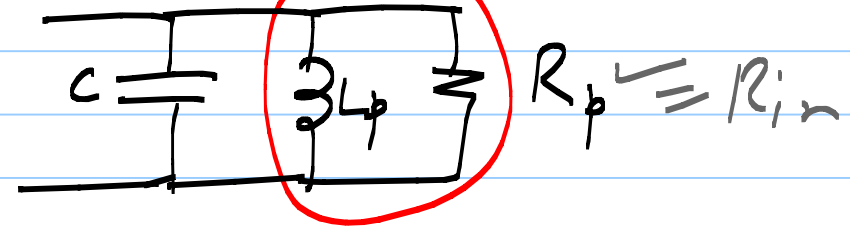


* $R_p = R_{in}$

* find C & L_p from Q


* find $(L_1 + L_{2s})$ & R_{Ls}

* Calculate $Q' = \sqrt{\frac{R_L}{R_{Ls}} - 1}$



* Calculate L_2, L_{2s}, L_1

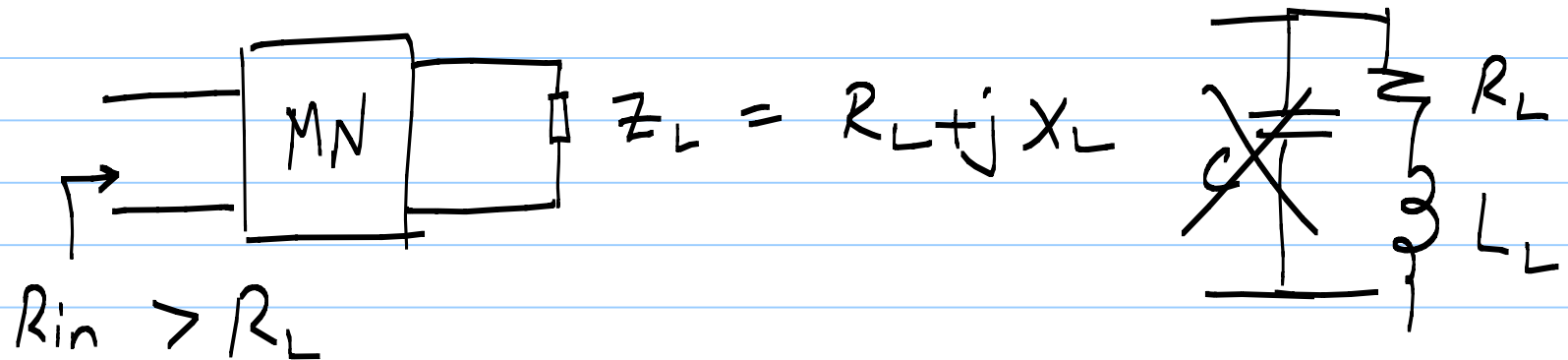



eg. X_L is positive

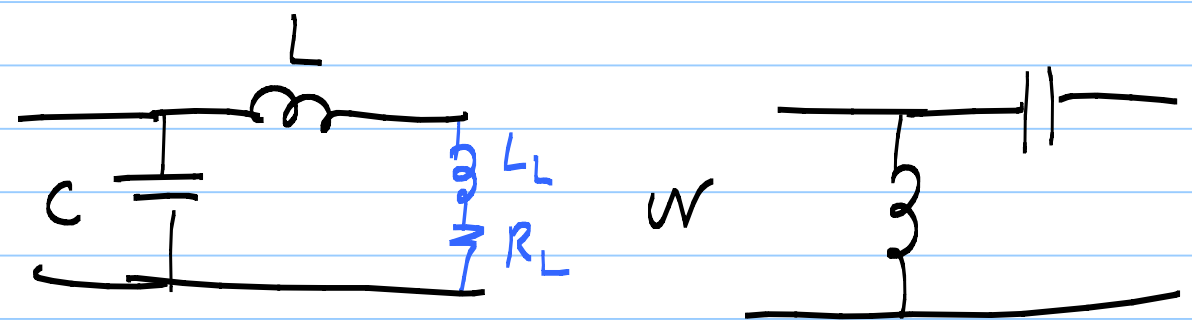


①

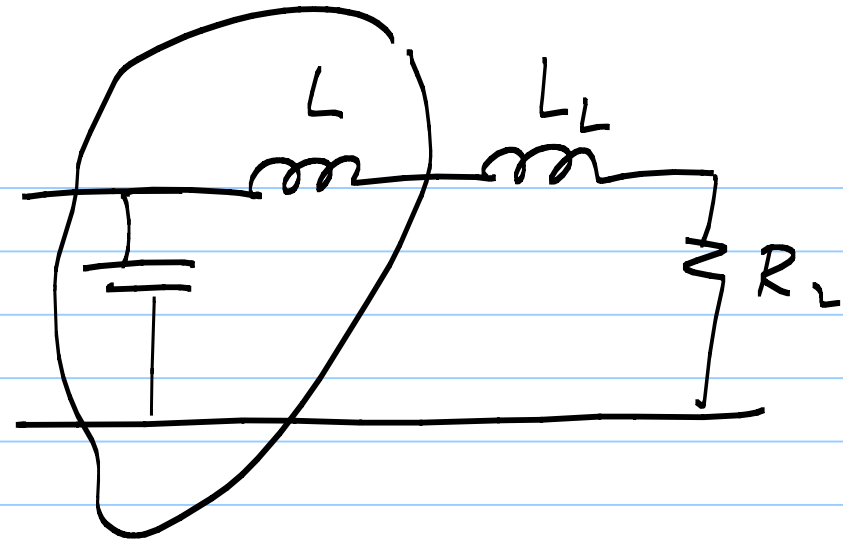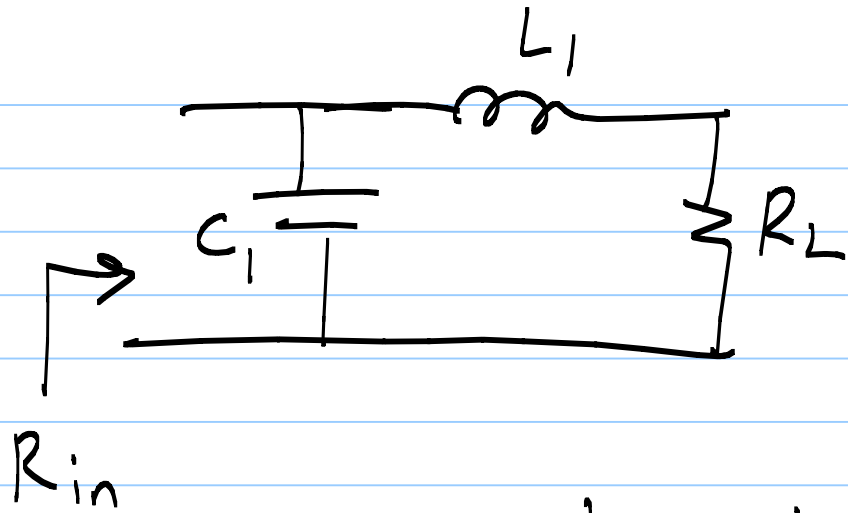


$$L_1 > L_L$$

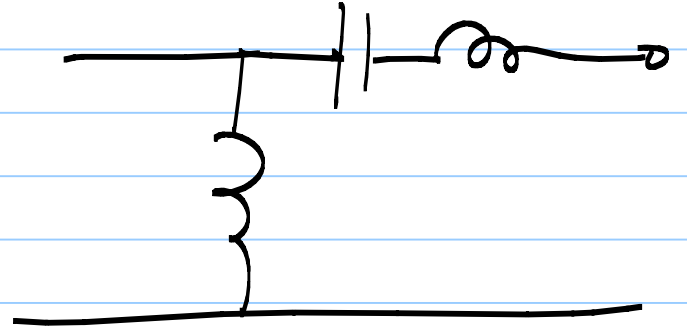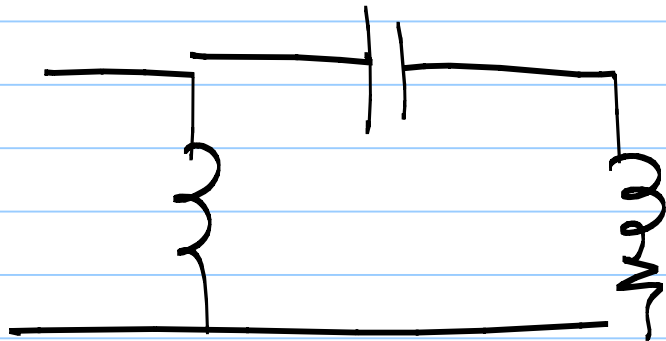


2

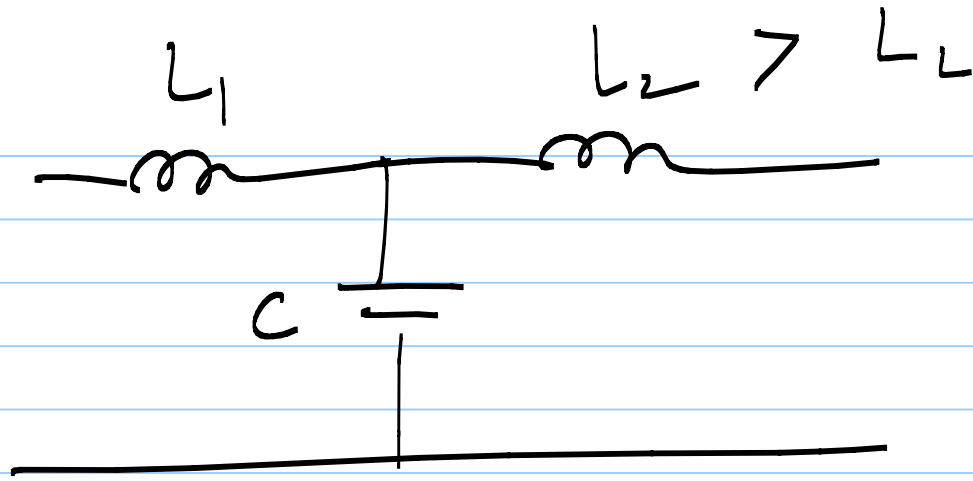

3

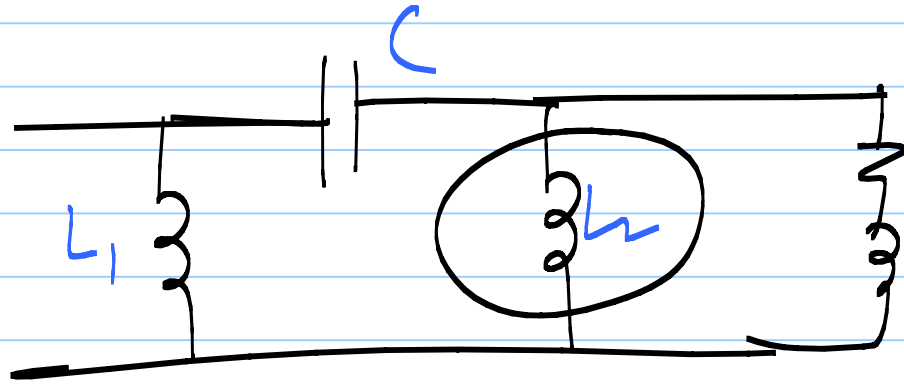

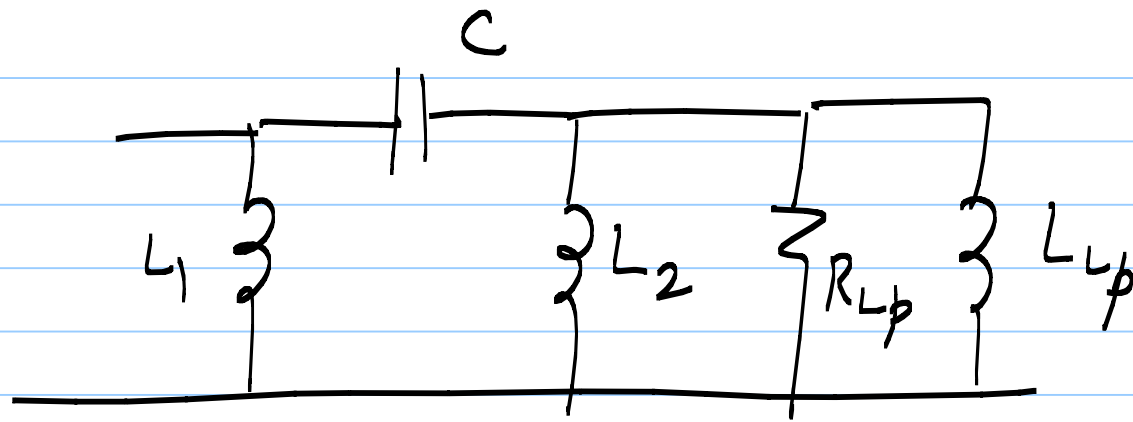

$$L_3 = L_2 // L_{lp}$$

