




4/2/20




Lec 9

Low Noise Amplifier

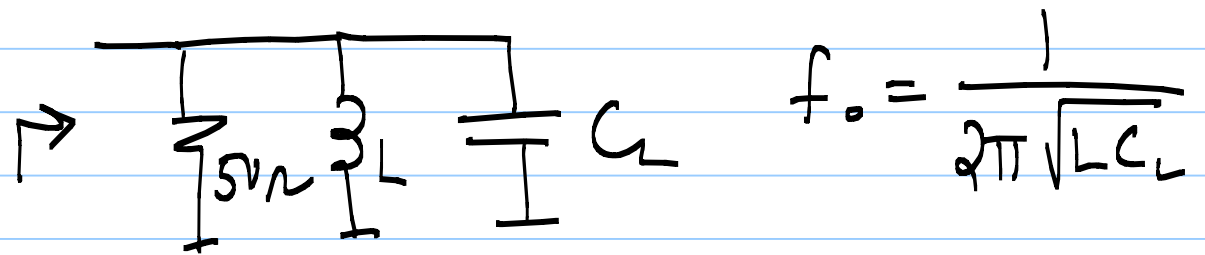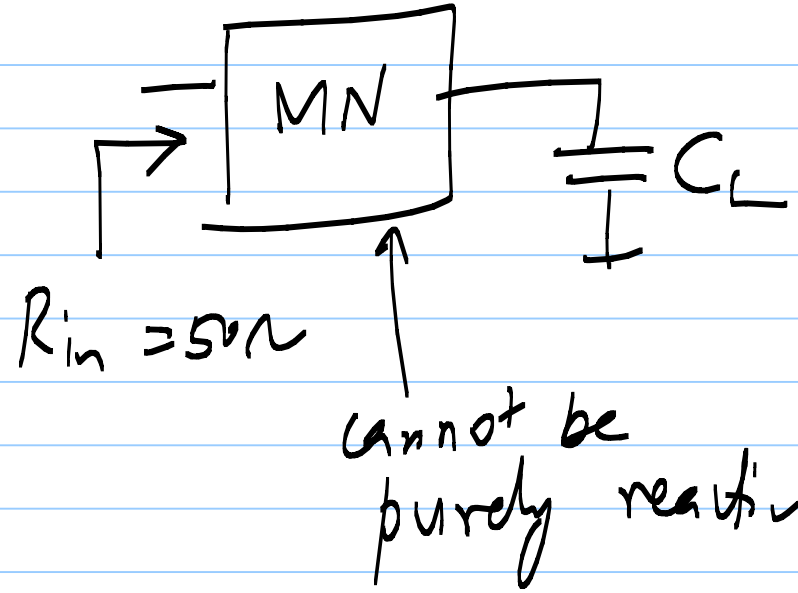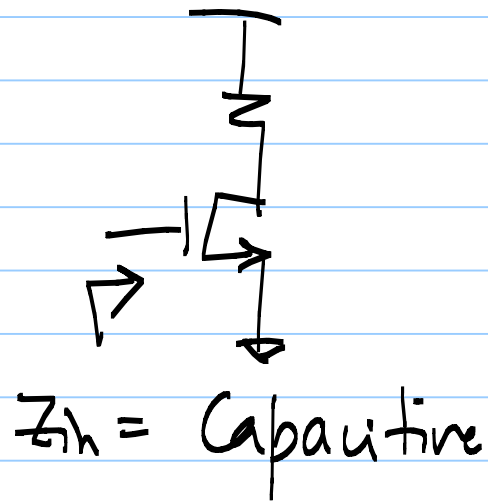- high gain
- low noise
- $Z_{in} = 50\Omega$
- high  $IP_3$
- low Power consumption






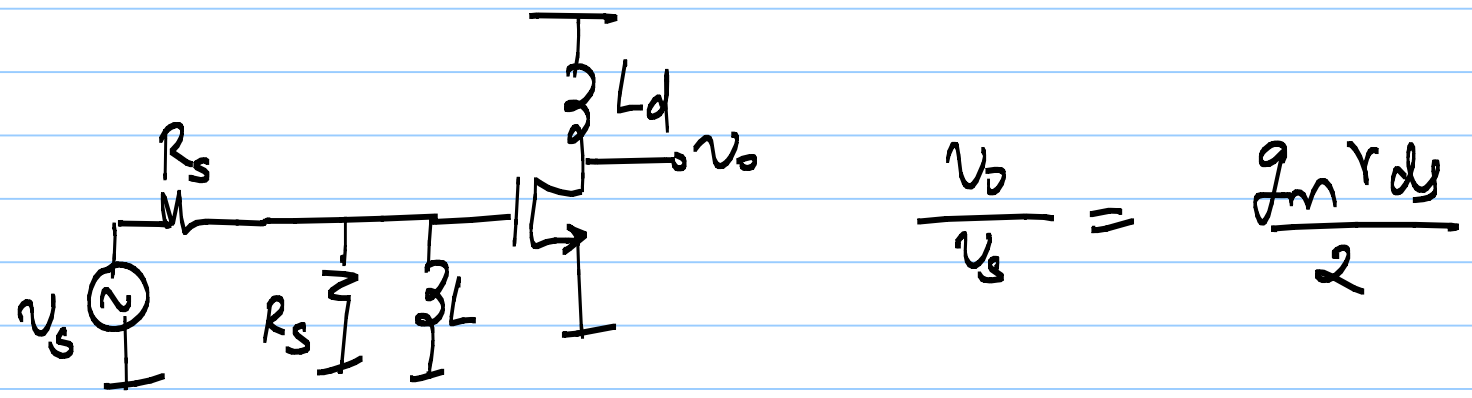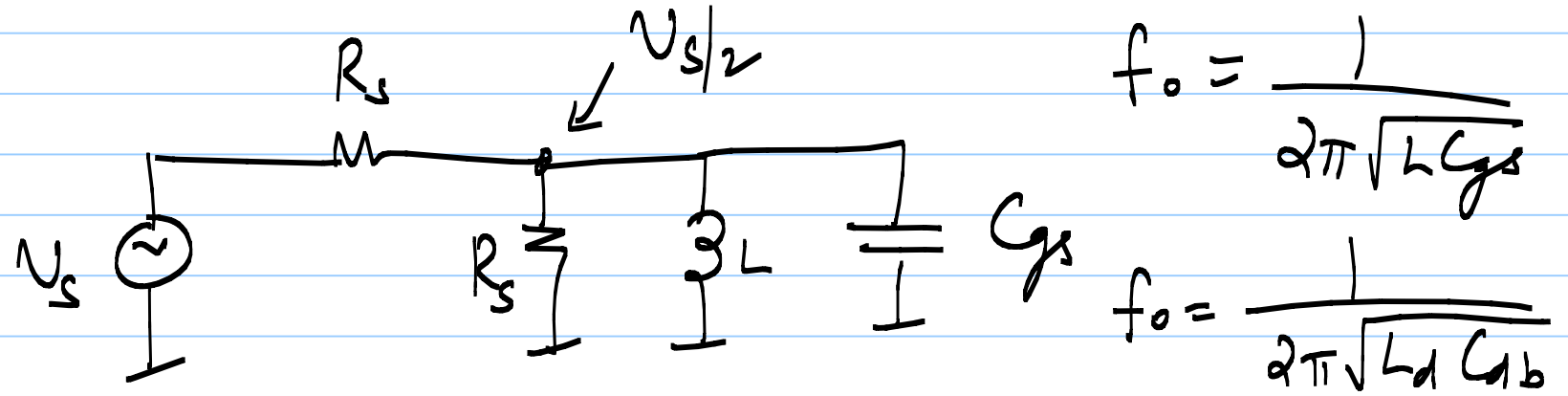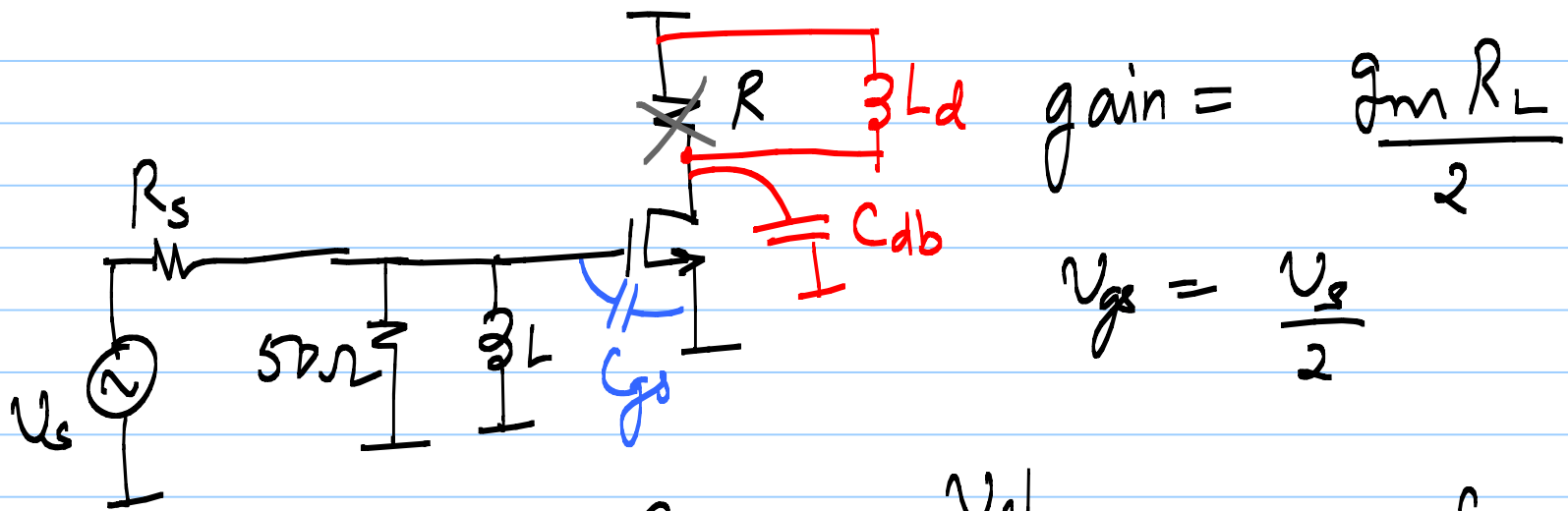

$$Z_{out} = ?$$



1) stand alone LNA

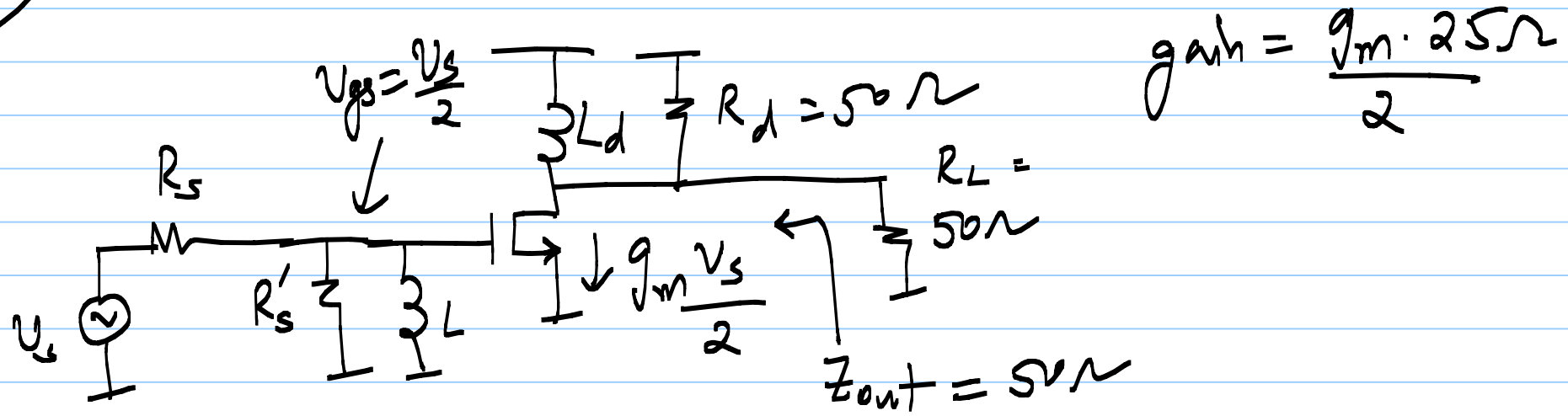


2) LNA driving  $C_L$  ;  $f_0 =$  desired operating freq.  
 (on IC)  
 $\Rightarrow$  Choose  $L_d$  such that

$$f_0 = \frac{1}{2\pi \sqrt{L_d (C_{db} + C_L)}}$$


1)

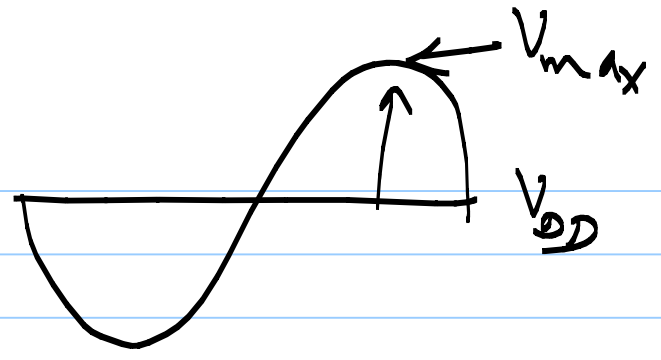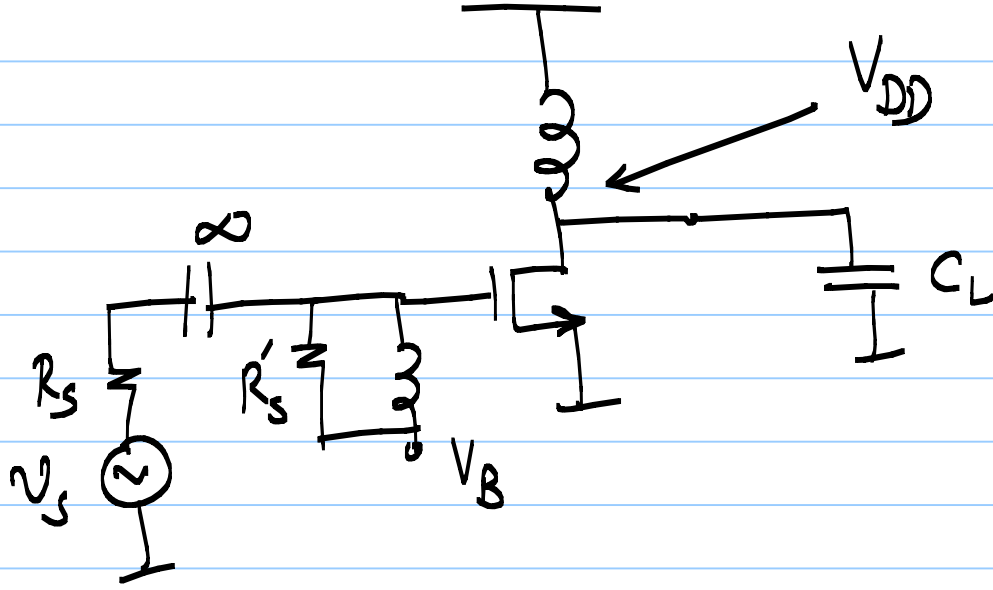


2)

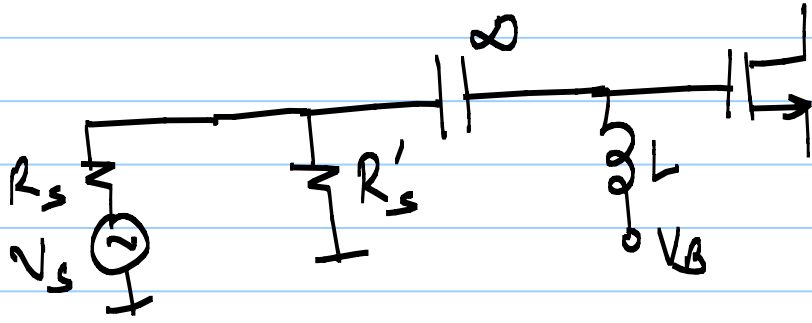

3)

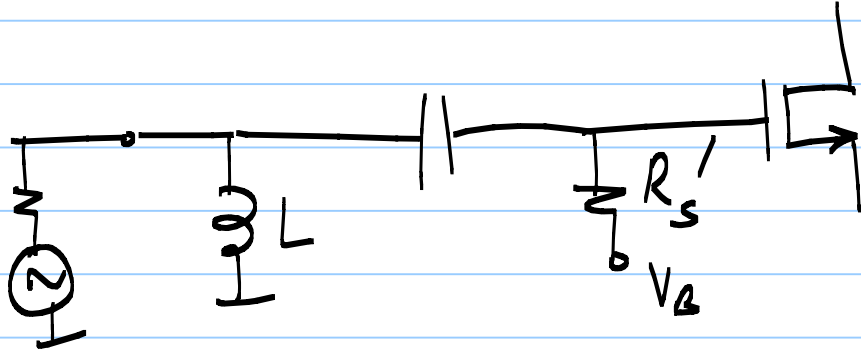

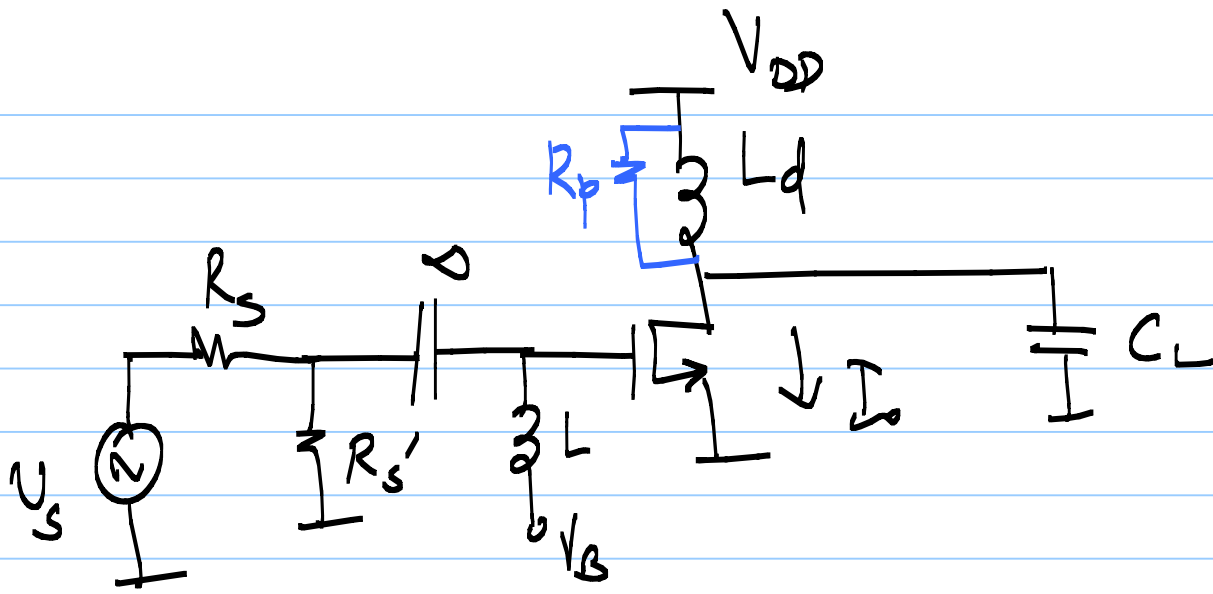

$$\text{gain} = \frac{g_m (r_{ds} \parallel R_p)}{2}$$

Set  $I_D, W, L$   
 $\parallel$   
 $L_{\min}$ .

