

# EE5311- Digital IC Design

## Module 2 - Interconnects

Janakiraman V

Assistant Professor  
Department of Electrical Engineering  
Indian Institute of Technology Madras  
Chennai

October 28, 2017

# Learning Objectives

- ▶ Estimate the wire parasitics given the sheet resistance and the capacitance per unit length
- ▶ Derive the Elmore delay for a given RC tree
- ▶ Estimate the wire RC delay by applying the Elmore delay model to a distributed RC network

# Outline

- ▶ Capacitance
- ▶ Resistance
  - ▶ Sheet Resistance
  - ▶ Skin depth
- ▶ Resistance Models
- ▶ Lumped model (C and RC)
- ▶ Propagating delay and rise time
- ▶ Elmore delay model
- ▶ Example - Time constant of a rc-wire model

# Capacitance

 


Figure: Wire capacitance

$$C_{int} = \frac{\epsilon_{di}}{t_{di}} WL$$

# Capacitance

 


Figure: Thin wire capacitance

 


Figure: Thin wire capacitance model

$$C_{wire} = \frac{\epsilon_{di}}{t_{di}} W + \frac{2\pi\epsilon_{di}}{\log(t_{di}/H)}$$

# Resistance

$$R = \frac{\rho L}{HW}$$

$$R = R_{\square} \frac{L}{W}$$

$$R_{\square} = \frac{\rho}{H}$$

- ▶  $R_{\square}$  - Sheet resistance ( $\Omega/\square$ ) - Technology Parameter
- ▶ To obtain resistance of a wire just multiply with  $L/W$

# Skin Effect

$$\delta = \sqrt{\frac{\rho}{\pi f \mu}}$$

- ▶ At high frequencies current tends to flow only in the outer surface confined to a depth of  $\delta$
- ▶ Area of current flow is  $\approx 2(H + W)\delta$

$$r(f) = \frac{\sqrt{\pi \rho f \mu}}{2(H + W)}$$

# Lumped Model

 


Figure: Lumped Capacitance model

$$C_{lumped} = L \times c_{wire}$$



# Lumped RC Model

 


Figure: Lumped RC model

Assumptions:

- ▶ The network has a single input node
- ▶ All capacitors are between the node and ground
- ▶ The network does not contain any resistive loops (tree)

# Lumped RC Model

 


Figure: Lumped RC model

- ▶ Path resistance ( $R_{ij}$ ) is the net resistance from the source node to node  $i$  ( $R_{44} = R_1 + R_2 + R_4$ )
- ▶ Shared path resistance: Sum of resistance shared between two paths

$$R_{ik} = \sum R_j : [R_j \in (\text{path}(s \rightarrow i) \cap \text{path}(s \rightarrow k))]$$

# Elmore Delay Model

 



Figure: Elmore delay

$$\tau_{Di} = \sum_{k=1}^N C_k R_{ik}$$

Delay is affected by:

- ▶ All capacitances ( $C_k : k \in 1, 2 \dots N$ ) - Loading
- ▶ Path resistances

# Elmore Delay Model Example

 

## Assumption

- ▶ Input is an ideal step function.
- ▶ All capacitances charge up to  $V_{DD}$  as  $V_k \approx V_{DD}(1 - e^{-t/\tau_k})$  - Second order effects are negligible

# Elmore Delay Model Example

$$V_{in} - V_3 = (i_1 + i_2 + i_3)R_1 + i_3R_3$$

$$i_k = C_k \frac{dV_k}{dt}$$

$$\int_0^{\infty} (V_{in} - V_3)dt = \int_0^{V_{DD}} R_1(C_1dV_1 + C_2dV_2 + C_3dV_3) + R_3C_3dV_3$$

Substituting  $V_3 \approx V_{DD}(1 - e^{-t/\tau_3})$  and integrating we get

$$\tau_3 = C_1R_1 + C_2R_1 + C_3(R_1 + R_3)$$

Clearly shows that off path resistances don't affect delay (to a first order) but all capacitances do

# Elmore Delay Model

 


Figure: RC Ladder

Delay is the **first order** time constant of the transfer function

$$\frac{V_N(s)}{V_{in}(s)} = \frac{H(s)}{G(s)}$$

General expression for the delay of an RC-ladder is

$$\tau_{DN} = \sum_{k=1}^N C_k \sum_{i=1}^k R_i$$

# Delay of RC wire model

 


Figure: RC wire delay model.

Delay of an RC-wire model is

$$\tau_{DN} = \left(\frac{L}{N}\right)^2 (rc + 2rc + \dots + Nrc) = (rcL)^2 \frac{N+1}{2N} \approx \frac{rcL^2}{2} = \frac{RC}{2}$$

- ▶  $r$  = resistance per unit length ( $\Omega/m$ )
- ▶  $c$  = capacitance per unit length ( $F/m$ )
- ▶ Delay of a wire is a quadratic function of its length
- ▶ The delay of the distributed rc line is half that of the lumped RC model

# Design Thumb Rules

rc delay should be considered only when

- ▶ wire delay is larger or comparable to the gate delays

$$(L_{crit} = \sqrt{\frac{2t_{pgate}}{rc}})$$

- ▶ rise/ fall delay at the source is smaller than rise/ fall time of the line ( $t_{rise} < rcL^2$ )

When the wire delay is comparable to the total delay, consider RC models. Else lumped C model will do



## Example

| Material | $R_{\square}(\Omega/\square)$ | $c(aF/\mu m)$ |
|----------|-------------------------------|---------------|
| Poly     | 150                           | 196           |
| Al       | 0.075                         | 110           |

Calculate the propagation delay of 10cm long,  $1\mu m$  wide Al wire. Compare the delay with that of a Polysilicon wire.

# References

The material presented here is based on the following books/  
lecture notes

1. Digital Integrated Circuits Jan M. Rabaey, Anantha Chandrakasan and Borivoje Nikolic 2nd Edition, Prentice Hall India