

EE5311- Digital IC Design

Module 4 - Combinational Circuit Design

Janakiraman V

Assistant Professor
Department of Electrical Engineering
Indian Institute of Technology Madras
Chennai

October 16, 2018

Learning Objectives

- ▶ Explain logical effort (LE) and electrical effort (EE)
- ▶ Derive the optimum number of buffers with their sizes to drive a load.
- ▶ Implement any arbitrary boolean function in Static CMOS logic
- ▶ Derive logical effort for any gate built in any style of logic
- ▶ Optimize the path delay of arbitrary gates driving a load capacitance
- ▶ Implement logic functions using ratio'd logic and dynamic logic
- ▶ Use the pass transistor to implement simple gates like MUX and XORs 8. Explain basic domino logic

Outline

- ▶ CMOS gates
- ▶ Gate sizing
- ▶ Capacitance estimation
- ▶ Delay estimation
- ▶ Logical effort
- ▶ Path delay optimization
- ▶ Buffer insertion
- ▶ Circuit Families
 - ▶ Static CMOS
 - ▶ Ratioed gates
 - ▶ Cascode Voltage Switch Logic (CVSL)
 - ▶ Dynamic circuits
 - ▶ Pass Transistor circuits

CMOS Gates

 


Figure: A CMOS Gate

- ▶ Pull down to GND with NMOS
- ▶ Pull up to V_{DD} with PMOS

CMOS Gates

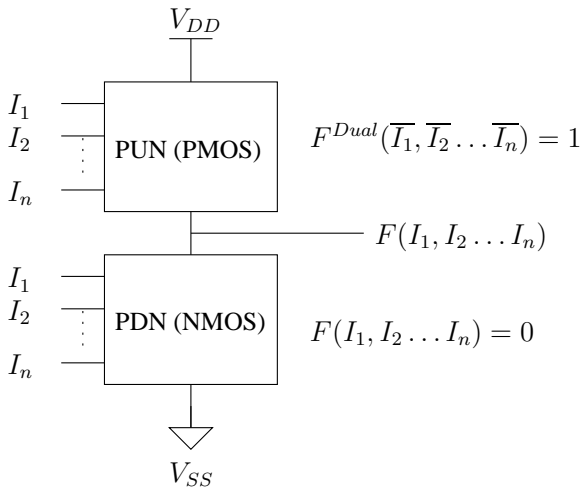


Figure: A CMOS Gate

CMOS Gates

- ▶ Pull up network (PUN) - PMOS only
- ▶ Pull down network (PDN) - NMOS only
- ▶ Series transistors provide an AND logic
- ▶ Parallel transistors provide an OR logic
- ▶ Use the SOP form to obtain the PDN
- ▶ Use De Morgan's laws to obtain the dual PUN
- ▶ CMOS gates are naturally inverting.
- ▶ N-input logic gate requires $2N$ transistors

Examples

- ▶ $Y = \overline{AB}$
- ▶ $Y = \overline{A + B}$
- ▶ $Y = \overline{A + BC}$
- ▶ $Y = \overline{D + A.(B + C)}$

Simple CMOS Gates - Gate Sizing

 


Figure: NOR2 and NAND2 Gate

- ▶ Transistor size is chosen so that rise and fall propagation delays are equal to that of a unit inverter

CMOS Gates - Capacitance


 


Figure: Inverter Capacitance Approximation

Useful Approximations

- ▶ Capacitance at all three terminals are equal (C)
- ▶ Capacitances are between the terminal and ground

Shared Diffusion - Capacitance

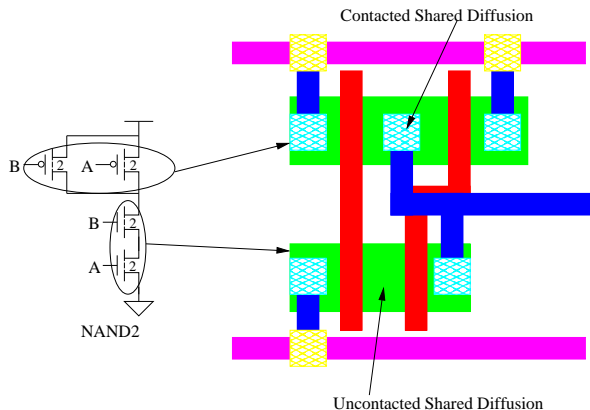

- ▶ Contacted shared diffusions need to be larger - Higher cap
- ▶ Uncontacted shared diffusions are smaller - Lower cap

NAND3 - Capacitance

 


Figure: Uncontacted shared diffusion cap counted only once

Parasitic Delay

 


Figure: Parasitic delay for an n input NAND

$$t_{pd} = 3RC + \sum_{i=1}^{n-1} \frac{iR}{n} nC = \left(\frac{n^2}{2} + \frac{5n}{2}\right)RC$$

- ▶ Delay grows quadratically as the number of inputs
- ▶ Keep the number of inputs down to 4

Parasitic Delay - Approximation

Gate Type	No. of Inputs				
	1	2	3	4	n
Inverter	1				
NAND		2	3	4	n
NOR		2	3	4	n
Tristate Mux	2	4	6	8	2n

$$p_{inv} = 3RC$$

- ▶ Count diffusion capacitance only on output node
- ▶ Normalize to parasitic delay of an inverter
- ▶ Parasitic delay is independent of gate size to a first order

NAND2 - Delay

 


Figure: NAND2 gate driving an arbitrary load capacitance

- ▶ Rise Time Propagation Delay = $R(6C + C_L)$
- ▶ Fall Time Propagation Delay = $(R/2)(2C) + R(6C + C_L)$
- ▶ Rise Time Contamination Delay = $(R/2)(6C + C_L)$
- ▶ Fall Time Contamination Delay = $R(6C + C_L)$

NAND2 Upsized - Delay

 


Figure: NAND2 Upsized by a factor of k

- ▶ Rise Time Propagation Delay = $(6RC + RC_L/k)$
- ▶ Fall Time Propagation Delay = $(7RC + (RC_L/k))$

NAND2 Delay - Observations

$$t_{pdr} = (6RC + RC_L/k)$$



$$t_{pdf} = (7RC + (RC_L/k))$$

$$k = C_{GATE}/4C$$

$$t_{pd} = t_{par} + 4RC \left(\frac{C_L}{C_{GATE}} \right)$$

- ▶ Parasitic delay = $t_{par} = 6RC$ or $7RC$ - Independent of k
- ▶ Effort delay = $4RC \left(\frac{C_L}{C_{GATE}} \right)$ Depends on
 - ▶ $h = \left(\frac{C_L}{C_{GATE}} \right)$ - Ratio of load capacitance to input gate capacitance - Size dependent (Electrical Effort)
 - ▶ Gate capacitance of the unit gate ($4C$) - Decided purely by the logic complexity of the gate (Logical Effort)

Logical Effort Intuition

  

- ▶ A reference gate is placed in a circuit such its load capacitance is C_L and it offers a gate capacitance of C_{GATE}
- ▶ If the reference gate is swapped by another logically equivalent gate that is *sized to offer exactly the same* gate capacitance C_{GATE}
- ▶ The delay will be lesser for the gate with lesser logical effort

NAND2 - Normalized Delay


$$t_{pd} = 6RC + 4RC \left(\frac{C_L}{C_{GATE}} \right)$$

- ▶ Good to have a process independent representation
- ▶ Ideal unit inverter driving a FO1 load with no parasitic capacitance = $\tau = 3RC$

$$d = t_{pd}/\tau$$

$$d = ((4/3)h + 2)$$

Linear Delay Model

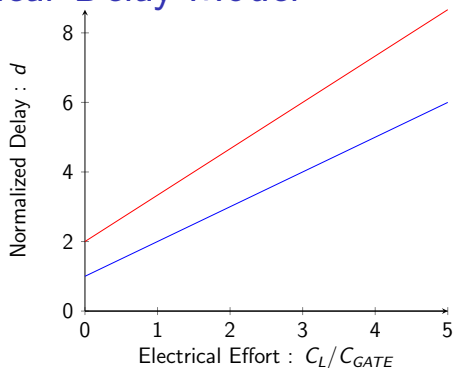

$$d = h + 1$$

$$d = (4/3)h + 2$$

$$d = gh + p$$

$$h = \frac{C_L}{C_{GATE}}$$

Logical Effort

Def: Ratio of input gate capacitance of the gate to that of an inverter that can deliver the same output current

Gate Type	No. of Inputs				
	1	2	3	4	n
Inverter	1				
NAND		$4/3$	$5/3$	$6/3$	$(n+2)/3$
NOR		$5/3$	$7/3$	$9/3$	$(2n+1)/3$
Tristate Mux	2	2	2	2	2
X(N)OR		4,4	6,12,6,	8, 16, 16, 8	

Gate Delay Estimation Examples

- ▶ Estimate the delay of an FO4 inverter
 - ▶ $d = 4 + 1 = 5$
 - ▶ $\tau = 0.2T_{FO4}$
 - ▶ FO4 delay of a process $\approx 2\lambda/3 - 2\lambda/2$ ps
 - ▶ 180nm Process - FO4 delay $\approx 60 - 90$ ps
- ▶ Estimate the delay of an Ring Oscillator
 - ▶ $d = 2N$
 - ▶ $T_{period} = 2 * 2N$
 - ▶ $f_{RO} = 1/4N\tau$

Gate Sizing

 


Figure: Gate Sizing

$$t_{pd} = \sum_{i=1}^N g_i h_i + p_i$$

$$\prod_{i=1}^N g_i = G$$

$$\prod_{i=1}^N h_i = H = \frac{C_{out}}{C_{in}}$$

Gate Sizing

 


Figure: Gate Sizing

- ▶ $P = \sum_{i=1}^N p_i$ - Independent of gate size
- ▶ G - Path logical effort
- ▶ H - Path electrical effort - Constant
- ▶ $F = GH$ - Path effort - Constant
- ▶ Minimize $\sum_{i=1}^N g_i h_i$;
- ▶ Use $\frac{\sum_{i=1}^N g_i h_i}{N} \geq (\prod_{i=1}^N g_i h_i)^{\frac{1}{N}} = (F)^{\frac{1}{N}}$ (AM \geq GM)
- ▶ Optimal delay = $NF^{1/N} + P$

Gate Sizing

 


Figure: Gate Sizing - Large Caps

$$G = 4/3 \times 5/3$$

$$H = 4500/1$$

$$F = 10000$$

$$\tau_{opt} = NF^{1/N} + \sum_{i=1}^4 p_i = 4 * 10 + \sum_{i=1}^4 p_i$$

Can we do better?

Buffer Insertion

- ▶ Inserting inverters does not alter the logical effort.
- ▶ Useful to change the electrical effort
- ▶ Can potentially reduce the path delay
- ▶ Beware of the inversion

Buffer Insertion

 


Figure: Buffer Insertion

$$D = NF^{1/N} + \sum_{i=1}^{n_1} p_i + (N - n_1)p_{inv}$$

$$\frac{\partial D}{\partial N} = -F^{1/N} \ln(F^{1/N}) + F^{1/N} + p_{inv} = 0$$

$$p_{inv} + \rho(1 - \ln(\rho)) = 0$$

Buffer Insertion


 


Figure: Buffer Insertion

$$\rho = F^{1/N}$$

$$p_{inv} = 1$$

$$p_{inv} + \rho(1 - \ln(\rho)) = 0$$

 

- ▶ Solving we get $\rho_{opt} = 3.59$
- ▶ $\hat{N} = \log_{\rho} F$
- ▶ Fan out of 4 is a practical and near optimum choice

Buffer Sizing

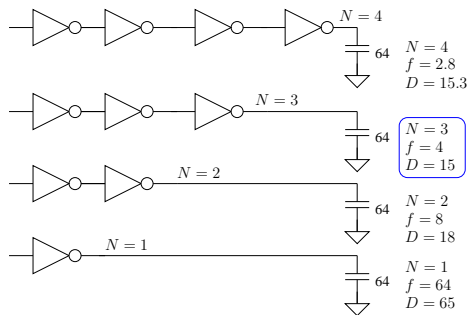


Figure: Buffer Sizing

- ▶ $D = NF^{1/N} + N$
- ▶ $F = 64$
- ▶ Optimal stage effort ≈ 4

Sizing - Summary

- ▶ Gate sizing (N is fixed)
 - ▶ Stage delay is made equal for all gates
 - ▶ $\tau_{opt} = NF^{1/N} + p$
- ▶ Buffer insertion (N is variable)
 - ▶ Reduce $NF^{1/N}$ by increasing N
 - ▶ Optimal stage delay ≈ 4
 - ▶ $\hat{N} = \log_4(F)$
 - ▶ $\tau_{opt} = \hat{N}F^{1/\hat{N}} + p$
- ▶ How do you reduce $F = GH$?
 - ▶ $H = C_{out}/C_{in}$ - Fixed
 - ▶ $G = \prod_{i=1}^N g_i$ - Can we reduce g_i ?

Circuit Families

- ▶ Static CMOS
- ▶ Ratioed gates
- ▶ Cascode Voltage Switch Logic (CVSL)
- ▶ Dynamic circuits
- ▶ Pass Transistor circuits

Static CMOS

- ▶ Good noise margins
- ▶ Fast
- ▶ Low power
- ▶ Insensitive to device variations
- ▶ Easy to design
- ▶ Supported by CAD tools
- ▶ Available in all standard cell libraries

Static CMOS

- ▶ Fundamentally inverting gates in nature
- ▶ Think NAND-NOR instead of AND-OR
- ▶ Use Demorgan's laws

 
 


Figure: $F = AB + CD$

Complex Static CMOS

Sizing

- ▶ Worst case PU and PD drive strength of the gate must be similar to that of the unit inverter


 
 
 
 
 
 
 


Figure: $F = \overline{AB + C}$

Complex Static CMOS - Logical Effort

 - ▶ Logical effort of complex gates can be different for different inputs
- ▶ $g_A = g_B = 6/3$
- ▶ $g_C = 5/3$
- ▶ $p = 7/3$



Complex Static CMOS

Draw the Static CMOS circuit that implements $Y = \overline{A(B + C)} + DE$ indicating the sizes and the logical effort each input

Special Functions

<i>A</i>	<i>B</i>	<i>C</i>		<i>Y</i>
0	0	0		0
0	0	1		0
0	1	0		0
0	1	1		1
1	0	0		0
1	0	1		1
1	1	0		1
1	1	1		1

$$Y = AB + BC + CA$$

Special Functions

 


Figure: Full Adder Carry Circuit

$$Y = AB + BC + CA$$

Special Functions

Logic functions are written in SoP form (Sum of minterms)

$$Y = \sum m(3, 5, 6, 7)$$

$$\bar{Y} = \sum m(0, 1, 2, 4)$$

Inverting Property - **IF**

$$Y = F(A, B, C)$$

$$\bar{Y} = F(\bar{A}, \bar{B}, \bar{C})$$

The PMOS dual n/w *can be* identical to the NMOS network

Full Adder

Inverting property valid for both SUM and CARRY

A	B	C_i		S	C_o
0	0	0		0	0
0	0	1		1	0
0	1	0		1	0
0	1	1		0	1
1	0	0		1	0
1	0	1		0	1
1	1	0		0	1
1	1	1		1	1

Table: Full Adder: $S = \sum m(1, 2, 4, 7)$, $C_o = \sum m(3, 5, 6, 7)$

$$\bar{S} = \sum m(0, 3, 5, 6)$$

$$\bar{C}_o = \sum m(0, 1, 2, 4)$$

Input Ordering

- ▶ Delay when B rises last =
 $(R/2)2C + R(6C) = 7RC = 2.33\tau$
- ▶ Delay when A rises last = $R(6C) = 6RC = 2\tau$
- ▶ Outer input is close to the supply/ ground rail
- ▶ Inner input is close to the output
- ▶ Input that arrives last is connected to the inner input

 


Figure: Outer input (B) and inner input (A)

Asymmetric Gates

- ▶ Intentionally skew the sizes to favour more important inputs
- ▶ Reset is not a high priority signal
- ▶ Pull down resistance = $R/4 + 3R/4 = R$
- ▶ Logical effort for input A is $g_A = 10/9 < 4/3$
- ▶ In the limit $g_A = 1$ - Large RESET transistor

 


Figure: Input A preferred over *RESET*

Skewed Gates

- ▶ Intentionally skew the sizes to favour more important transition
- ▶ Logical Effort : Ratio of input capacitance of the gate to that of an unskewed inverter of same drive current
- ▶ Logical effort for rise $g_u = 2.5/3$
- ▶ Logical effort for fall $g_d = 2.5/1.5$
- ▶ For least average delay $W_P = \sqrt{2} \implies g_u = 1.15, g_d = 0.81$


 
 
 





Figure: Logical effort for a HI Skew inverter

Skewed Gates




UNSKWEWED

 

HI-SKEW

   

LOW-SKEW

   

Ratioed Circuits

- ▶ Static CMOS requires $2N$ transistors, where N is the number of inputs
- ▶ N transistors are PMOS - Each is at least twice the width of the NMOS
- ▶ Ratioed logic mitigates this problem


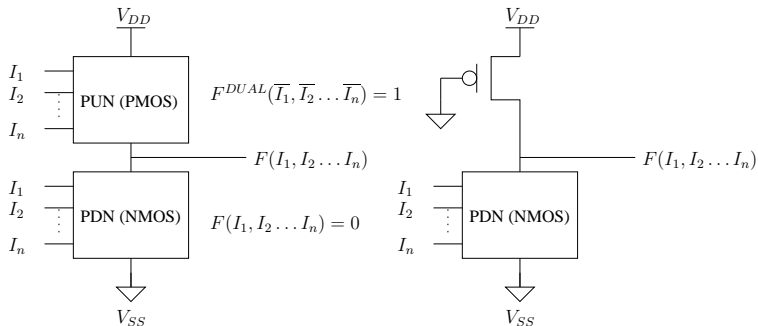


Figure: Pseudo NMOS Circuit

Pseudo NMOS Gate - V_{OL}

 - ▶ Pull up PMOS is always ON
- ▶ $A = 0 \implies V_{OH} = V_{DD}$
- ▶ $A = V_{DD} \implies Y = V_{OL}$? - NMOS and PMOS fight
- ▶ NMOS in Linear Region
- ▶ PMOS in Velocity Saturation



Pseudo NMOS Gate - V_{OL}

$$I_{DSn} = \frac{k'_n W_n}{L} V_{OL} \left(V_{DD} - V_{Tn} - \frac{V_{OL}}{2} \right)$$
$$I_{DSp} = \frac{k'_p W_p}{L} V_{DSATp} \left(-V_{DD} - V_{Tp} - \frac{V_{DSATp}}{2} \right)$$
$$I_{DSn} = -I_{DSp}$$
$$V_{OL} = \frac{k'_p W_p}{k'_n W_n} \left(\frac{V_{DD} + V_{Tp} + \frac{V_{DSATp}}{2}}{V_{DD} - V_{Tn}} \right) V_{DSATp}$$
$$V_{OL} \approx \frac{\mu_p W_p}{\mu_n W_n} |V_{DSATp}|$$

- ▶ W_p/W_n should be as small as possible
- ▶ Rise delay severely affected if W_p is very small

Ratioed Circuits - Pseudo NMOS Gates

 


Figure: Pseudo NMOS Gates INV, NAND2 and NOR2

Pseudo NMOS Gates- Logical Effort

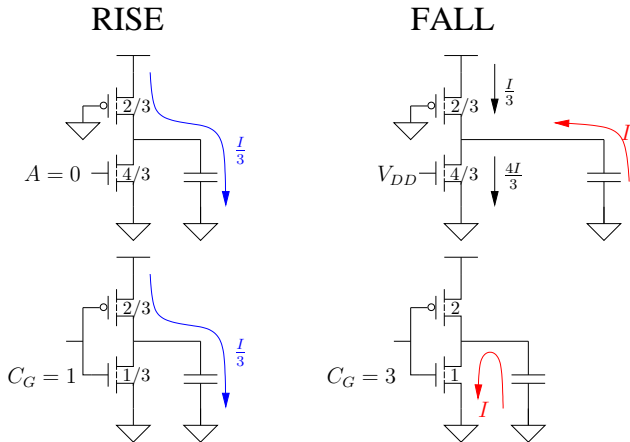


Figure: Logical Effort : Reference symmetric inverter

Pseudo NMOS - Logical Effort

Gate	g_u	g_d	g_{avg}	p_u	p_d	p_{avg}
INV	4/3	4/9	8/9	18/9	6/9	12/9
NAND2	8/3	8/9	16/9	30/9	10/9	20/9
NOR2	4/3	4/9	8/9	30/9	10/9	20/9

- ▶ Average delay for NAND2 is larger than Static CMOS
- ▶ Works well for fast-wide NORs - Logical effort is independent of number of inputs
- ▶ Beware of SF process corner - Slow NMOS and Fast PMOS

Dynamic Circuits

Ratioed circuits suffer from

- ▶ Weak pull up transistor
- ▶ Contention on a falling transition
- ▶ Significant static power
- ▶ Non-zero V_{OL}
- ▶ Dynamic Circuits circumvent these problems by using a clocked Pull up

 


Figure: Dynamic Circuits

Dynamic Circuits - Evaluate and Precharge

Dynamic circuits function in two phases

- ▶ Pre-charge
- ▶ Evaluate
- ▶ In precharge phase, A should NOT be HIGH
- ▶ Add a footer device as well


 
 
 





Figure: Two phases

Dynamic Circuits - Footed and Unfooted

UNFOOTED

 

FOOTED

   

Dynamic Circuits - Monotonicity

During Evaluate

- ▶ Input should be monotonically rising
- ▶ Input CANNOT start HIGH and fall LOW

 



Figure: Input Monotonicity

Dynamic Circuits - Domino Logic

During Evaluate


- ▶ Insert a static CMOS INVERTER in between
- ▶ All dynamic gates evaluate and fall like a Domino
- ▶ All inverters rise - Skew HI inverter

DOMINO AND

 


Dynamic Circuits - Keeper Transistors

 - ▶ Dynamic gates suffer from charge leakage
- ▶ In evaluate mode the dynamic node is FLOATING
- ▶ Leakage current can cause it to drift and discharge




Dynamic Circuits - Keeper Transistors

 - ▶ Weak keeper keeps the
- ▶ In evaluate mode the dynamic node is FLOATING
- ▶ Leakage current can cause it to drift and discharge




Dynamic Circuits - Weak Keepers

 - ▶ Keeper size is critical
- ▶ Typically as small as possible
- ▶ Can increase L instead of decreasing W - $C \uparrow$
- ▶ Weak keeper helps solve the problem



Cascode Voltage Switch Logic

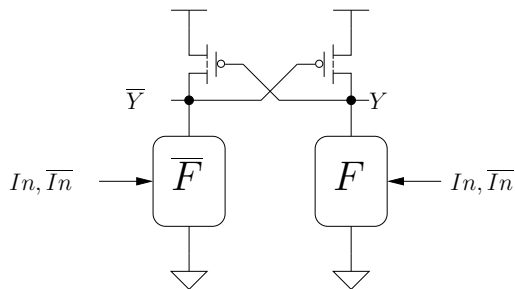
- ▶ Performance of ratioed circuits
- ▶ Avoid static leakage at the same time
- ▶ Cross coupling helps turn off the leaking side
- ▶ Needs true and complement versions of the inputs
- ▶ Output is true and complement form



Dynamic version is dual rail domino logic


Level Translators

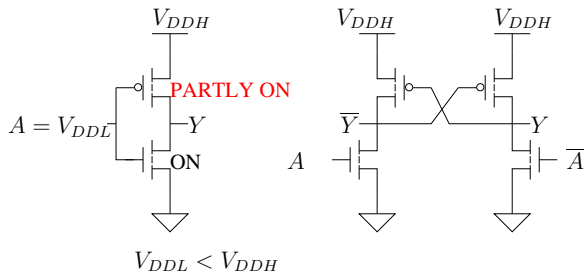- ▶ Low voltage domain (V_{DDL}) driving high voltage domain (V_{DDH})- Static leakage problem
- ▶ PMOS partially turned ON when NMOS is fully ON
- ▶ Cross coupling the PMOS eliminates the issue
- ▶ High voltage driving low voltage is not an issue



Chip IO Pads

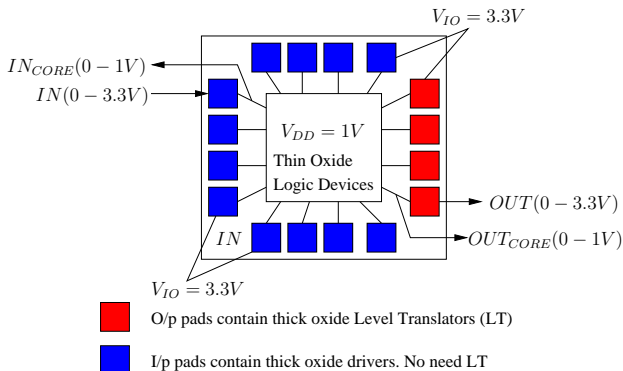- ▶ Withstands larger voltage swing - Protects core
- ▶ IO pads use thick oxide devices \implies Larger V_{TH}
- ▶ Requires larger supply voltage (V_{IO}) to overcome V_{TH}
- ▶ Typically $V_{IO} = 3.3V$ and logic $V_{DD} = 1.0V$
- ▶ Pads also contain ESD protect diodes



Transmission Gates

- ▶ Usually input is fed to the GATE terminal
- ▶ In some, they can be fed to the DRAIN/ SOURCE
- ▶ NMOS can pass ZERO and PMOS can pass ONE
- ▶ Combine the two - Pass gate or Transmission gate
- ▶ Typically used in implementing
 - ▶ XOR2
 - ▶ MUX-2
 - ▶ MUX-N

Multiplexer Implementation

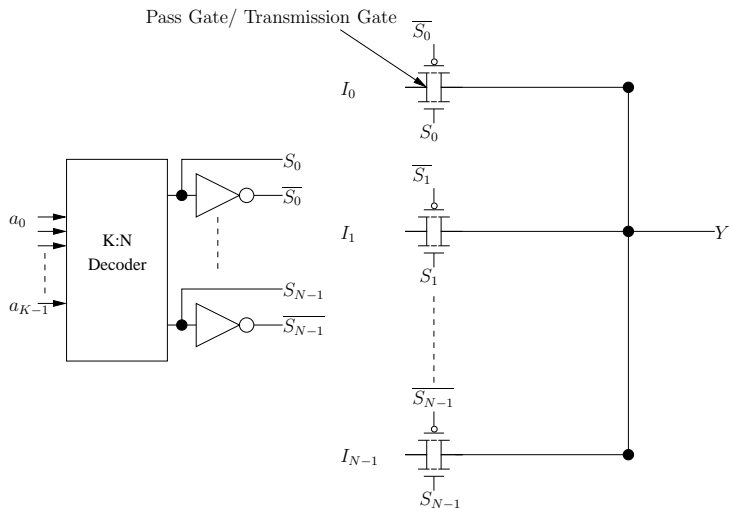


Figure: $N : 1$ Mux. $N \leq 2^K$

Transmission Gate Mux 2

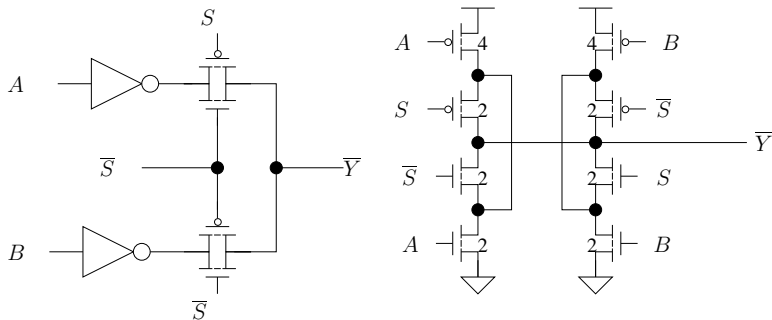


Figure: TG sizing

- ▶ NMOS and PMOS size is the same in the TG - They turn ON in parallel
- ▶ Delay of the TG gate depends on the driving gate's strength

Tri-State Inverter


 
 


Figure: Tri State Inverter

Circuit Sizing

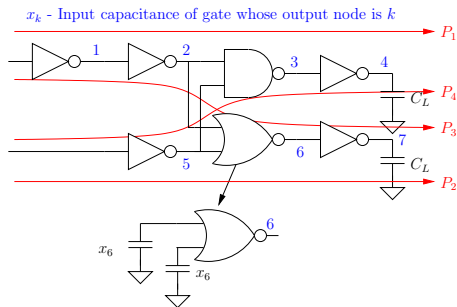

- ▶ Find x_k 's such that all outputs settle within a time T_{Spec}
- ▶ Path P_3 is potentially the longest path - Optimize the path
- ▶ Optimizing P_3 can increase delay of P_4 and cause a timing violation
- ▶ How do we ensure timing across all paths?

Node Based Timing

- ▶ Need to move away from path analysis
- ▶ Need to formulate a node based optimization problem

Define arrival time a_{jk} at the output of a gate due to input j


$$a_{jk} = a_j + d_{jk}$$

$$a_k = \max(a_1, a_2 \dots a_j) \dots j \in INPUTS(Gate_k)$$

$$a_k = 0 \dots k \in PI$$

- ▶ The arrival time (a_k) at the output of gate k is maximum of the a_{jk} 's across all inputs
- ▶ The arrival time at the primary inputs (PI) is zero.

Circuit Arrival Times

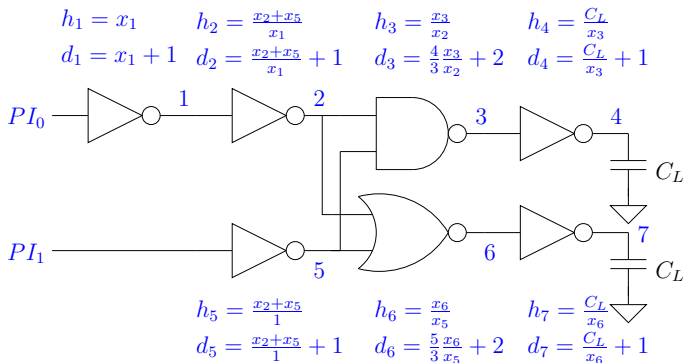

$$\begin{aligned}
 a_1 &= d_1 \\
 a_2 &= a_1 + d_2 \\
 a_3 &= \max(a_2 + d_3, a_5 + d_3) \\
 a_4 &= a_3 + d_4
 \end{aligned}$$

$$\begin{aligned}
 a_5 &= d_5 \\
 a_6 &= \max(a_2 + d_6, a_5 + d_6) \\
 a_7 &= a_6 + d_7 \\
 \max(a_4, a_7) &\leq T_{Spec}
 \end{aligned}$$

Handling MAX operation

- ▶ MAX is not good for optimization problem
- ▶ Equalities in the constraints are also not good
- ▶ The arrival time constraints are modified as shown below

Old	Modified
$a_3 = \max(a_2 + d_3, a_5 + d_3)$	$a_2 + d_3 \leq a_3$ and $a_5 + d_3 \leq a_3$
$a_6 = \max(a_2 + d_6, a_5 + d_6)$	$a_2 + d_6 \leq a_6$ and $a_5 + d_6 \leq a_6$
$\max(a_4, a_7) \leq T_{Spec}$	$a_4 \leq T_{Spec}$ and $a_7 \leq T_{Spec}$

Similarly, the equality constraints of remaining arrival times are converted to inequalities.

Formulation : Sizing for Minimum Delay

Objective Function : $minimize(T_{Spec})$

Subject to:

$$\begin{array}{lll} d_1 \leq a_1 & a_2 + d_3 \leq a_3 & a_5 + d_3 \leq a_3 \\ a_1 + d_1 \leq a_2 & a_2 + d_6 \leq a_6 & a_5 + d_6 \leq a_6 \\ d_5 \leq a_5 & a_4 \leq T_{Spec} & a_7 \leq T_{Spec} \end{array}$$

- ▶ This is a convex problem and hence the solution obtained is a *Global Optimum*
- ▶ For a circuit with N gates the number of constraints is $O(N)$

Formulation : Minimum Area for a given T_{spec}

Objective Function : $minimize(\sum_{k=1}^6 x_k)$

Subject to:

$$\begin{array}{lll} d_1 \leq a_1 & a_2 + d_3 \leq a_3 & a_5 + d_3 \leq a_3 \\ a_1 + d_1 \leq a_2 & a_2 + d_6 \leq a_6 & a_5 + d_6 \leq a_6 \\ d_5 \leq a_5 & a_4 \leq T_{Spec} & a_7 \leq T_{Spec} \end{array}$$

This is a convex problem and hence the solution obtained is a *Global Optimum*

References

Most of the material presented here is based on the first reference [Weste]. The circuit sizing alone is based on references 2 and 3 [Boyd].

1. CMOS VLSI Design, Neil H.E. Weste, David Harris and Ayan Banerjee, 3rd Edition, Pearson Education
2. S. Boyd, S.-J. Kim, D. D. Patil, M. A. Horowitz, "Digital circuit optimization via geometric programming", Operations Research, vol. 53, no. 6, pp. 899-932, Nov. 2005.
3. <http://web.stanford.edu/boyd/papers/pdf/date05.pdf>