

# E4215: Analog Filter Synthesis and Design: HW7

Nagendra Krishnapura (nkrishnapura@mltc.com)

due on 25 Mar. 2003

For 1-5, give the schematic of the passive filter with all the element values. For 1-3, give the the transfer function in the normalized form which is

$$\frac{b_0 + b_1(s/Q/\omega_n) + b_2(s/\omega_n)^2}{1 + s/Q/\omega_n + (s/\omega_n)^2}$$

where  $\omega_n$  is a convenient normalizing frequency. For 3-5, give the expression for the frequency transformation along with the numerical values for the parameters in the transformation. For 6, give the final schematic and explain very briefly the purpose of each feedforward component<sup>1</sup>.

1. (1 pt.) Design a second order passive low-

 


Figure 1:

pass RLC notch filter with  $Q = 1/\sqrt{2}$ ,  $\omega_p = 1$  Mrad/s and a transmission zero at  $\omega_z = 10$  Mrad/s. Use the topology in Fig. 1 with  $C_1 + C_2 = 10$  nF. What is the attenuation in dB at 1 Mrad/s? Call this  $A_p$ .

2. (2 pts.) Scale the filter in (1) so that it uses  $R = 1 \Omega$  and has a notch at 10 rad/s. What

<sup>1</sup>Elements from the input to various opamps.

is the frequency  $\Omega_p$  at which the attenuation is  $A_p$ ? What is the smallest frequency<sup>2</sup> at which the attenuation is  $A_s = -20$  dB? Call this  $\Omega_s$ .

3. (3 pts.) Transform the prototype in (2) to a passive RLC highpass filter with an attenuation  $A_p$  (determined in (1)) at 10 Mrad/s and a termination impedance 10 k $\Omega$ . What is the frequency of the notch in this filter? Draw the schematic replacing the inductors with capacitively terminated gyrators whose gyration resistance is 10 k $\Omega$ .
4. (4 pts.) Transform the prototype in (2) to a passive RLC bandpass filter whose attenuation is  $A_p$  at  $\omega_{p1} = 10$  Mrad/s and  $\omega_{p2} = 12.1$  Mrad/s. The termination impedance should be 10 k $\Omega$ . What are the “stopband” edges  $\omega_{s1}$  and  $\omega_{s2}$  where the attenuation is  $A_s$ ? What is the gain of the filter at 11 Mrad/s? If one of the notches of the filter is at 4.7 Mrad/s, where is the other notch?

5. (4 pts.) Transform the prototype in (2) to a passive RLC bandstop filter whose attenuation is at least  $A_s$  in the range  $81$  Mrad/s  $\leq \omega \leq 100$  Mrad/s. Use a termination impedance of 1 k $\Omega$ . What are the “passband” edges  $\omega_{p1}$  and

<sup>2</sup>You can calculate this analytically-you’ll get a 2<sup>nd</sup> order equation in  $\Omega^2$ ; or determine it using simulation-be sure to use a sufficiently small frequency step.

$\omega_{p2}$  where the attenuation is  $A_p$ ? What is the filter's attenuation at 90 Mrad/s?

6. (2 pts.) Realize an opamp-RC version of the highpass filter in (3). Use the Tow-Thomas biquad with feedforward technique to realize the zeros at the output of the first opamp. Use  $R = 10\text{ k}\Omega$  in the resonator core.
7. (1 pt.) Realize a bandpass filter whose attenuation is  $A_p$  at  $f_{p1} = 10\text{ MHz}$  and  $f_{p2} = 12.1\text{ MHz}$ . (Hint: You don't have to go through the whole synthesis again. Use the result from (4)).
8. (2 pt.) Simulate the magnitude response of the passive circuits in 1, 3 (not the part with the gyrator), 4, 5. (Plot all 4 magnitude responses in 4 subwindows of the same plot for submission. Use appropriate ranges for x and y axes to show all points of interest). In each, mark the frequency of the notch(es).
9. (1 pt.) Simulate the magnitude response of the opamp-RC filter in 6. For the opamps use ideal voltage controlled voltage sources with  $\text{gain}=10^6$ .