

# E4215: Analog Filter Synthesis and Design: Midterm

Nagendra Krishnapura (nkrishnapura@mltc.com)

11 Mar. 2003

90 minutes; 3 problems; 25 pts.; Closed book; No calculators;

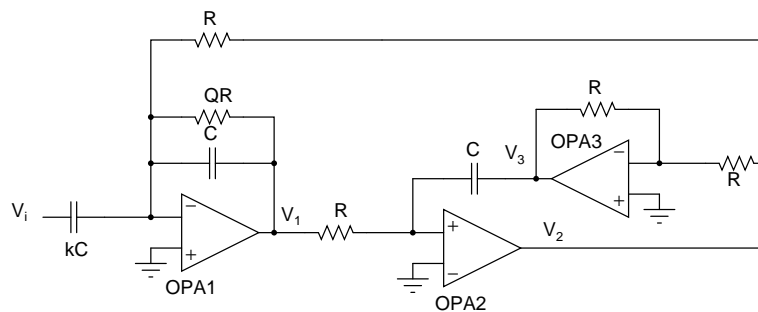


Figure 1: Circuit for problem 1.

1. (a) (4 pts.) Derive the transfer functions  $V_1(s)/V_i(s)$  and  $V_2(s)/V_i(s)$  for the circuit in Fig. 1. Assume ideal opamps.
- (b) (3 pts.) Sketch the magnitude and phase responses of  $V_1(s)/V_i(s)$  and  $V_2(s)/V_i(s)$  for  $Q = 5, k = 2$ .
- (c) (3 pts.) How would you modify the circuit so that a second order low pass filter with dc gain=1 is realized between  $V_i$  and  $V_3$ ? What is the transfer function  $V_3(s)/V_i(s)$  for this modified circuit?
2. A filter with an input  $V_{in}(t) = \cos(1 \text{ Grad/s } t) + \cos(10 \text{ Grad/s } t) + \cos(100 \text{ Grad/s } t)$  should have an output  $V_{out}(t) = a_1 \cos(1 \text{ Grad/s } t + \phi_1) + a_{10} \cos(10 \text{ Grad/s } t + \phi_{10}) + a_{100} \cos(100 \text{ Grad/s } t + \phi_{100})$  where  $a_1 \ll a_{10}, a_{100} \ll a_{10}$ .
  - (a) (1 pt.) What is the required type of filter?
  - (b) (1 pt.) Give a second order transfer function (with general parameters) which realizes a filter of the required type.
  - (c) (2 pts.) Choose the parameter(s) of the transfer function such that  $a_1/a_{10} = 10^{-2}$ .
  - (d) (4 pts.) Using a 2 nH inductor, design a passive second order filter which realizes the transfer function determined above. Assume that the voltage source driving this filter has an output resistance of  $50 \Omega$ .

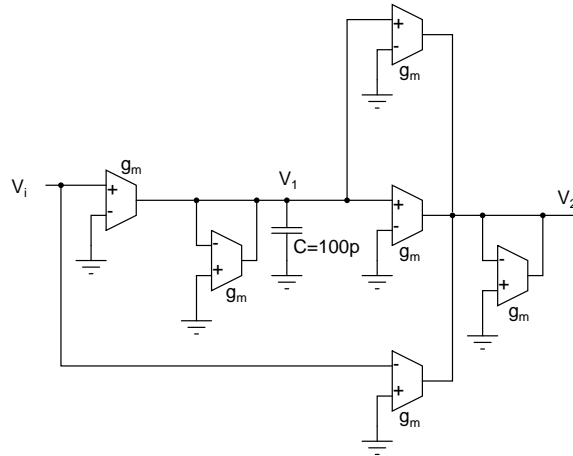


Figure 2: Circuit for problem 3. All transconductances are of an identical value;  $g_m=1$  mS.

- (e) (2 pts.) What is the ratio  $a_{100}/a_{10}$  with the filter designed above?
3. (a) (3 pts.) Derive the transfer functions  $V_1(s)/V_i(s)$  and  $V_2(s)/V_i(s)$  for the circuit in Fig. 2. All transconductances are of an identical value;  $g_m=1$  mS.
- (b) (2 pts.) Where are the poles and zeros of  $V_2(s)/V_i(s)$  (give the correct signs)? Sketch the magnitude and phase responses of  $V_2(s)/V_i(s)$ .

Notes:

- It is generally less confusing to carry out the calculations analytically and to substitute the numerical values at the end.
- Use judicious approximations to simplify numerical calculations. e.g.  $1 + \delta \approx 1$  if  $\delta$  is small, say 0.01. You can then verify if the approximation is valid by substituting back the answer so obtained.