

E4215: Analog Filter Synthesis and Design

Transfer functions realizable in a biquad

Nagendra Krishnapura (nkrishnapura@mltc.com)

18 Feb. 2003

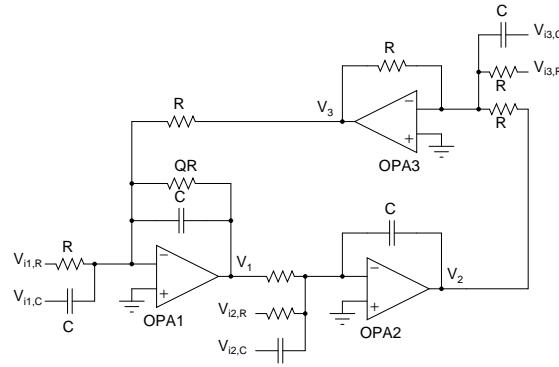


Figure 1: Tow-Thomas biquad with various possible inputs

Table 1: Transfer function between different inputs and outputs in Fig. 1. $D(s) = 1 + \frac{sCR}{Q} + (sCR)^2$

	V_1	V_2	V_3
$V_{i1,R}$	$-\frac{sCR}{D(s)}$	$\frac{1}{D(s)}$	$-\frac{1}{D(s)}$
$V_{i2,R}$	$-\frac{1}{D(s)}$	$-\frac{1/Q + sCR}{D(s)}$	$\frac{1/Q + sCR}{D(s)}$
$V_{i3,R}$	$\frac{sCR}{D(s)}$	$-\frac{1}{D(s)}$	$-\frac{sCR/Q + (sCR)^2}{D(s)}$
$V_{i1,C}$	$-\frac{(sCR)^2}{D(s)}$	$\frac{sCR}{D(s)}$	$-\frac{sCR}{D(s)}$
$V_{i2,C}$	$-\frac{sCR}{D(s)}$	$-\frac{sCR/Q + (sCR)^2}{D(s)}$	$\frac{sCR/Q + (sCR)^2}{D(s)}$
$V_{i3,C}$	$\frac{(sCR)^2}{D(s)}$	$-\frac{sCR}{D(s)}$	$-\frac{(sCR)^2/Q + (sCR)^3}{D(s)}$

The last row in Table 1 using the capacitive input $V_{i3,C}$ is not practical because it introduces an extra pole in the feedback around opamp OPA3, degrading stability (as in an opamp differentiator).