

## Problem 2

DC gain = 2

$$\omega_z = \sqrt{10} \times 10^6 \times 2\pi$$

$$\omega_p = 1 \times 10^6 \times 2\pi$$

$$\omega_z = \sqrt{10} \omega_p$$

$$H(s) = \frac{2 \left[ 1 + \frac{s^2}{(\sqrt{10}\omega_p)^2} \right]}{1 + \frac{s}{\omega_p Q} + \left( \frac{s}{\omega_p} \right)^2} = \frac{2 + \frac{1}{5} \left[ \frac{s}{\omega_p} \right]^2}{1 + \frac{s}{\omega_p Q} + \left( \frac{s}{\omega_p} \right)^2}$$

If we use same filter as designed in Part 1  
 Denominator remains same ( $\omega = 1.59 \text{ k}\Omega$ )  
 $C = 100 \text{ pF}$


(a) At  $V_1$

To get  $\frac{1}{5} \frac{s^2}{\omega_p^2}$  or  $\frac{1}{5} s^2 RC^2$  term in numerator

use  $V_{11}, C$  with capacitor =  $\frac{C}{5}$

To get DC gain 2

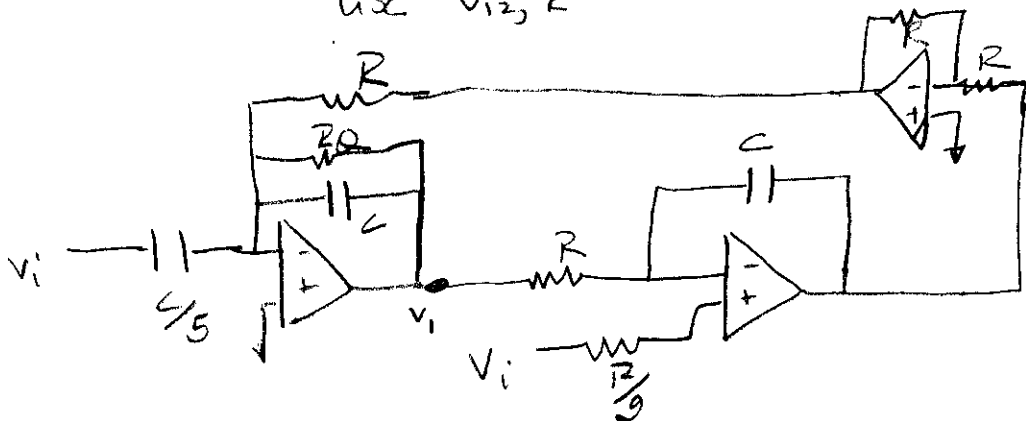use  $V_{12}, R$  with a resistance =  $\frac{R}{9}$



(b) At  $V_2$

To get  $s^2$  term in the numerator

- Use  $V_{i2}, C$  with capacitor value  $\frac{C}{\sqrt{5}}$  to get  $-\left[\frac{1}{5}s^2R^2 + \frac{1}{5} \frac{SCR}{R}\right]$  term in the numerator.


- Use  $V_{i1}, C$  with capacitor value  $\frac{C}{5} \times \frac{1}{R} \left[\frac{\sqrt{5}}{5} C\right]$  to get  $\frac{1}{5} \frac{SCR}{R}$  term in the numerator to cancel out  $-\frac{1}{5} \frac{SCR}{R}$  term due to  $V_{i2}, C$ .

- Use  $V_{i3}, R$  with resistance  $\frac{R}{g}$  to set DC gain  $g$


$$H(s) = \frac{-\frac{SCR}{5R} + \frac{1}{5} (sCR)^2}{D(s)} + \frac{\frac{SCR}{5R}}{D(s)} - \frac{g}{D(s)}$$

$\uparrow$  due to  $V_{i1}, C$                        $\uparrow$  due to  $V_{i2}, C$                        $\uparrow$  due to  $V_{i3}, R$

$$= \frac{g + \frac{1}{5} (sCR)^2}{D(s)}$$

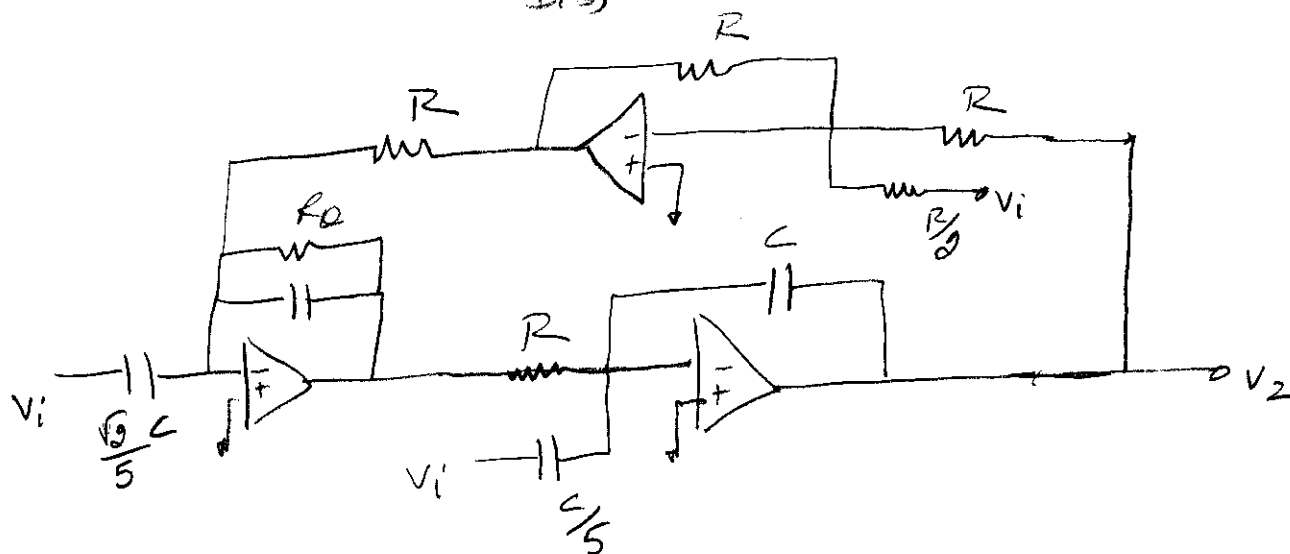

Problem 3

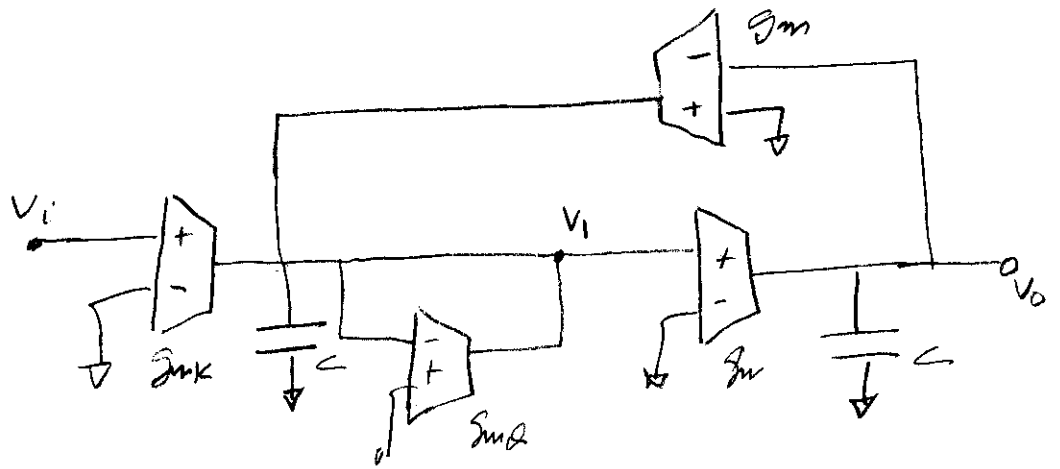

$$\frac{V_o}{V_i} = \frac{g_{mK}}{g_m} \frac{1}{\left(\frac{sC}{g_m}\right)^2 + \frac{g_{mQ}}{g_m} + 1}$$

DC gain =  $\frac{g_{mK}}{g_m} = 10$

$Q = \frac{g_m}{g_{mQ}} = \frac{1}{\sqrt{2}}$  (Butterworth filter)

$\therefore g_m$  is the smallest conductance.

$g_m = 10 \mu S$      $g_{mQ} = 10\sqrt{2} \mu S$      $g_{mK} = 100 \mu S$

Also  $\omega_p = 3 \times 10^6 \times 2\pi \text{ rad/s}$  [For Butterworth filter 3dB bandwidth =  $\omega_p$ ]  
 $= \frac{g_m}{C}$


$\therefore C = 0.153 \text{ pF}$

(b)  $\omega_z = 10 \text{ MHz}$      $\omega_p = 3 \text{ MHz}$   
 $\times 2\pi$                        $\times 2\pi$

$\omega_z = \frac{10}{3} \omega_p$

$$H(s) = \frac{10 \left[ 1 + \frac{s^2}{\omega_z^2} \right]}{1 + \frac{s}{Q\omega_p} + \left(\frac{s}{\omega_p}\right)^2} = \frac{10 + \frac{9}{10} \frac{s^2}{\omega_p^2}}{1 + \frac{s}{\omega_p Q} + \left(\frac{s}{\omega_p}\right)^2}$$

# Voltage Summing Technique

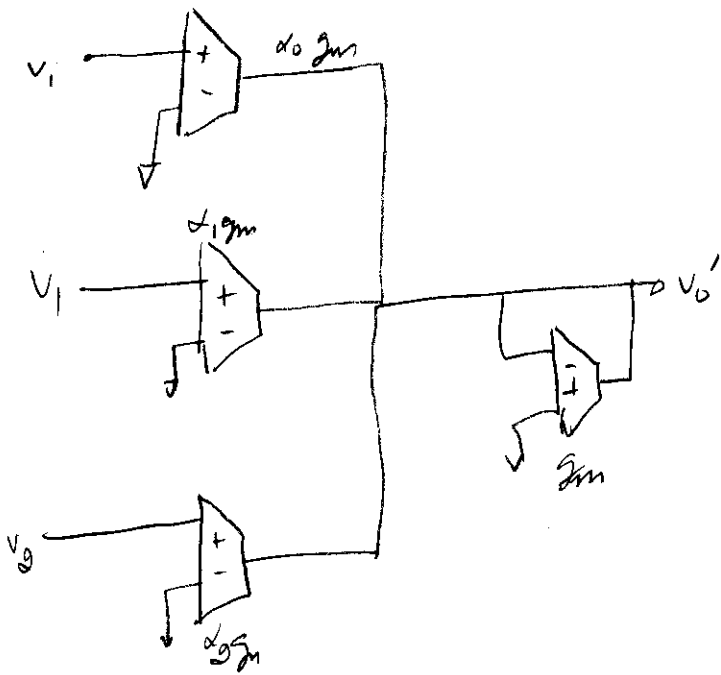

$$\frac{V_0'(s)}{V_L'(s)} = \frac{(\alpha_0 + K\alpha_2) + (\alpha_0 + \alpha_1 K\theta) \frac{s}{\omega_p} + \alpha_0 \left(\frac{s}{\omega_p}\right)^2}{1 + \frac{s}{\omega_p} + \left(\frac{s}{\omega_p}\right)^2}$$

$$\alpha_0 + K\alpha_2 = 10$$

$$\alpha_0 + K\alpha_1 = 0$$


$$\alpha_0 = \frac{9}{10}$$

$$\alpha_0 = \frac{9}{10}$$

$$\alpha_1 = -\frac{9}{100} \sqrt{2}$$


$$\alpha_2 = \frac{91}{100}$$

[So apply  $V_1$  to inverting terminal of  $\alpha_1 g_m$ ]

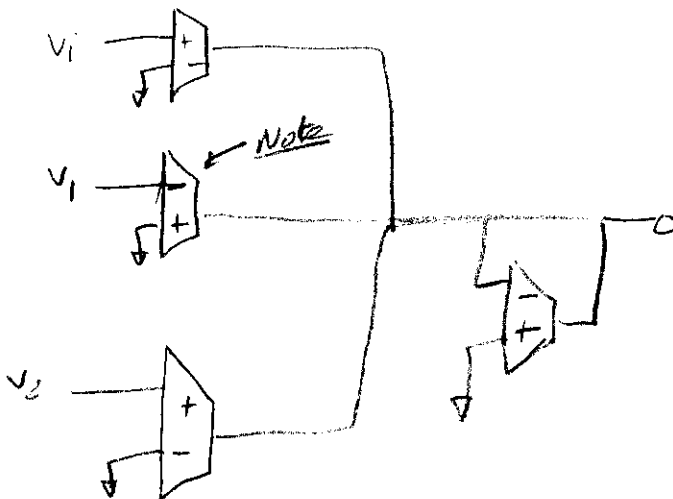

Problem 4

$L \approx$

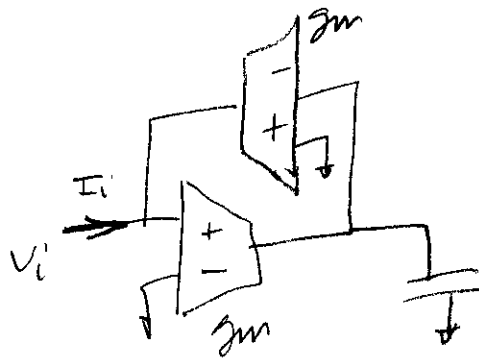


$$L = \frac{C}{g_m^2} = 100H$$

$$C = 100PF$$

$$\Rightarrow g_m = 1mS$$

(b)

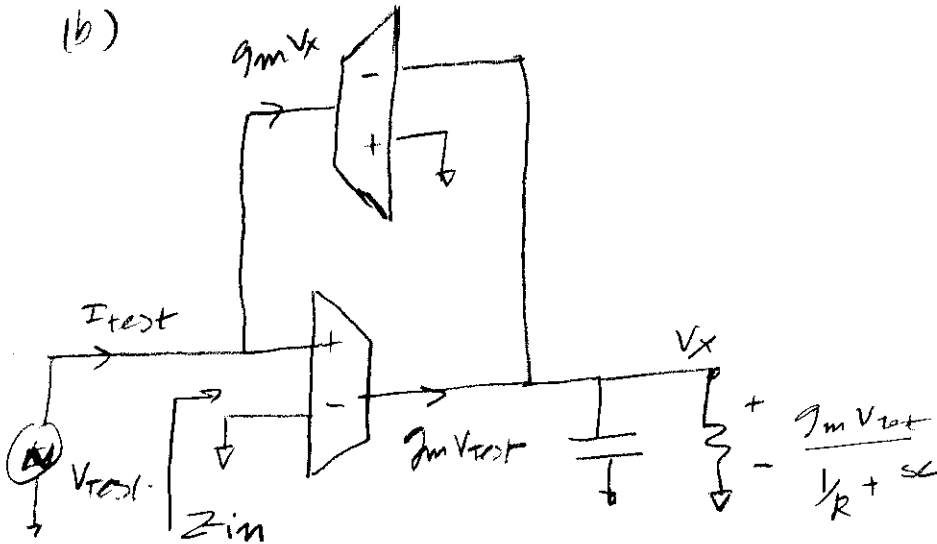


$$V_x = (g_m V_{TEST}) \left[ \frac{1}{\frac{1}{R} + sC} \right]$$

$$\therefore I_{TEST} = g_m^2 V_{TEST} \times \frac{1}{\frac{1}{R} + sC}$$

$$Z_{in} = \frac{V_{TEST}}{I_{TEST}} = \frac{\frac{1}{R} + sC}{g_m^2} = \underbrace{\frac{1}{g_m^2 R}}_{\text{Resistance}} + \underbrace{\frac{sC}{g_m^2}}_{\text{capacitance}}$$

$$Z_{in} \approx \frac{1}{g_m^2 R} \parallel \frac{s}{g_m^2}$$

Problem 5

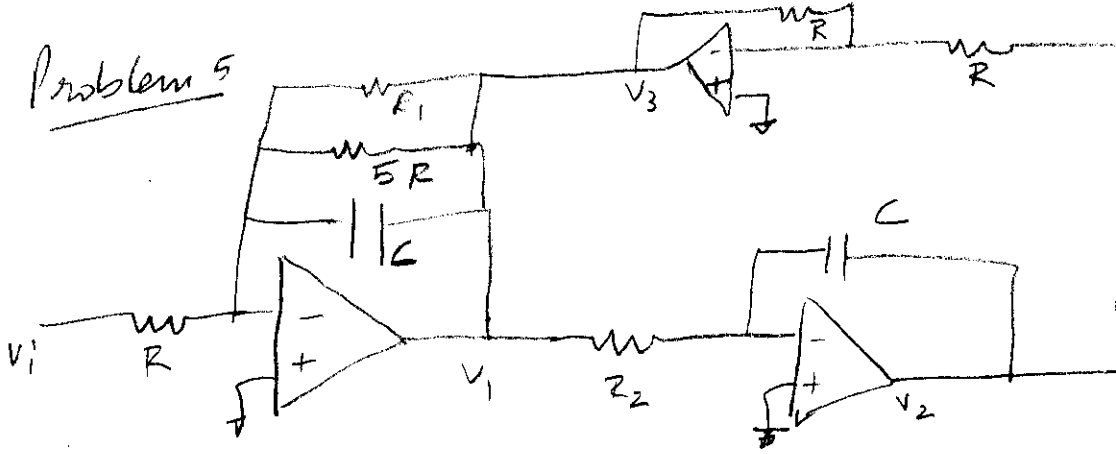

(a) Use KCL for all 3 opamps

$$\frac{V_i}{R} + V_1 sC + \frac{V_1}{5R} + \frac{V_3}{R_1} = 0 \quad (1)$$

$$V_3 = -V_2 \quad (2)$$

$$V_2 = -\frac{1}{sCR_2} V_1 \quad (3)$$

Eliminate  $V_2, V_3$

$$\frac{V_1}{V_i} = \frac{-R_1 R_2 C s}{R_1 R_2 C^2 s^2 + \frac{s R_1 R_2 C}{5R} + 1}$$

(i)  $R_1 = R_2 = R$

(ii)  $R_1 = 3R \quad R_2 = \frac{1}{3}R$

$$\frac{V_1}{V_i} = \frac{-sRL}{s^2(RC^2) + \frac{1}{5}RCs + 1}$$

$$\frac{V_1}{V_i} = \frac{-sRL}{s^2 R^2 C^2 + \frac{1}{5} sR + 1}$$

There's no difference

(b) Eliminate  $V_1, V_3$  from (1), (2) and (3) to get

(i)  $\frac{V_2}{V_i} = \frac{sR_1}{5R_1 R_2 R C^2 s^2 + R_1 R_2 C s + 5R}$

(ii)  $\frac{V_2}{V_i} = \frac{1}{R^2 C^2 s^2 + \frac{1}{3} RCs + 1}$

(iii)  $\frac{V_2}{V_i} = \frac{3}{R^2 C^2 s^2 + \frac{1}{5} RCs + 1}$

Different DC Gain but same BW,  $\omega_p$ , poles etc

$$\frac{V_3}{V_i} = - \left[ \frac{V_2}{V_i} \right]$$

$$(i) \quad \frac{V_3}{V_i} = \frac{-1}{R^2 C^2 S^2 + \frac{1}{5} RC S + 1}$$

$$\frac{V_3}{V_i} = -3 \times \frac{1}{R^2 C^2 S^2 + \frac{1}{5} RC S + 1}$$

$$\max \left| \frac{V_2}{V_i} \right| = \max \left| \frac{V_3}{V_i} \right|$$

$Q = 5 \gg \frac{1}{\sqrt{2}}$  - Peaking in frequency response

$$\max \left| \frac{V_2}{V_i} \right|$$

$$\frac{d}{d\omega} \left( \left| \frac{V_2}{V_i} \right| \right) = 0 \Rightarrow \omega_{peak} = \omega_p \sqrt{1 - \frac{1}{2Q^2}} = \omega_p \sqrt{1 - \frac{1}{50}} \approx \omega_p$$

$$(i) \quad R_1 = R, R_2 = R$$

$$\max \left( \left| \frac{V_2}{V_i} \right| \right) \approx Q$$

[Remember  $|Transfer\ Func|_{\omega=\omega_p} = Q$   
for low pass filters]

$$(ii) \quad R_1 = 3R, R_2 = \frac{R}{3}$$

$$\max \left( \left| \frac{V_2}{V_i} \right| \right) \approx 3 \times Q = 15$$

(c) To maintain opamps in linear region max output voltage for the opamps should be  $< 1V$ .

$$\text{for opamps 2,3 } |V_3| = |V_2| = \left| \frac{V_2}{V_i} \right| \times V_i < 1 \text{ Volt for all } \omega$$

$$(i) \quad \max \left| \frac{V_2}{V_i} \right| = 5 \text{ at } \omega = \omega_p$$

$$5 V_{ip} < 1$$

$$V_{ip} < \frac{1}{5} \text{ Volts}$$

$$(ii) \quad \text{Similarly } 15 V_{ip} < 1$$

$$V_{ip} < \frac{1}{15} \text{ Volts}$$