

1(a)

(a)

$$V_o = b_0 I_R + b_1 I_E$$

$$= b_0 \left( \frac{1}{1+sRC} \right) v_i + b_1 \left( \frac{sRC}{sRC+1} \right) v_i$$

$$= b_0 \left( \frac{1}{1+s/\omega_p} \right) v_i + b_1 \left( \frac{b_1 s/\omega_p}{1+s/\omega_p} \right) v_i$$

$$\frac{V_o}{v_i} = \frac{b_0 + b_1 s/\omega_p}{1 + s/\omega_p}$$

$$(b) \quad V_o = b_0 I_c + b_1 I_R + b_2 I_E$$

$$\frac{V_o}{v_i} = b_0 \left[ \frac{sC}{sC + Y_R + Y_{SL}} \right] v_i + b_1 \left[ \frac{Y_R}{sC + Y_R + Y_{SL}} \right] v_i + b_2 \left[ \frac{Y_{SL}}{sC + Y_R + Y_{SL}} \right] v_i$$

$$= b_0 \left[ \frac{(s/\omega_p)^2}{(s/\omega_p)^2 + s/\omega_p + 1} \right] v_i + b_1 \left[ \frac{s/\omega_p}{(s/\omega_p)^2 + (s/\omega_p) + 1} \right] v_i + \frac{1}{(s/\omega_p)^2 + (s/\omega_p) + 1} v_i$$

$$= \frac{b_0 + b_1 \left( \frac{s}{\omega_p} \right) + b_2 \left( \frac{s}{\omega_p} \right)^2}{1 + \frac{s}{\omega_p} + \left( \frac{s}{\omega_p} \right)^2}$$

## 2(a) Butterworth filter

8 order filter.

$$\rightarrow \omega_p = \sqrt{\omega_z^2 + \omega_i^2} \quad Q = \frac{\omega_p}{2\omega_z}$$

$\omega_r$ : real part of pole

$\omega_i$ : imaginary part of pole

$$\omega_{p1} = \sqrt{1.1031^2 + 0.2194^2} = 1.1247$$

$$\omega_{p2} = 1.1246$$

$$\omega_{p3} = 1.1247 \quad \omega_{p4} = 1.1246$$

$$Q_1 = 0.509 \quad Q_2 = 0.6013 \quad Q_3 = 0.9 \quad Q_4 = 2.563$$

## Chebyshev

5 order filter.

$$\omega_{p1} = 0.9941 \quad \omega_{p2} = 0.655 \quad \omega_{p3} = 0.2895$$

## Inverse Chebyshev

$$\omega_{p1} = 1.1366 \quad \omega_{p2} = 1.288 \quad \omega_{p3} = 1.42$$

$$Q_1 = 2.0217 \quad Q_2 = 0.6817$$

$$\omega_{z1} = 3.0671 \quad \omega_{z2} = 1.895$$

## Elliptic

4th order filter

$$\omega_{p1} = 0.6014$$

$$Q_1 = 0.8955$$

$$\omega_{z1} = 3.525$$

$$\omega_{p2} = 0.999$$

$$Q_2 = 4.145$$

$$\omega_{z2} = 1.6095$$

(b) Cascade order.

(i) bilinear before biquads (if exists)

(ii) smaller Q biquads before larger Q biquads

Bessel Filter

$\omega_{p1} = 1.165 \quad \omega_{p2} = 1.052 \quad \omega_{p3} = 0.9843 \quad \omega_{p4} = 0.943$

$\omega_{p5} = 0.9202$

$Q_1 = 1.506 \quad Q_2 = 0.858 \quad Q_3 = 0.652 \quad Q_4 = 0.557 \quad Q_5 = 0.513$

you should get  $A_5 = -40dB$  at approx  $\Omega_5 = 233mHz$

so  $\Omega_p \approx 233 \frac{m}{g} Hz$  with  $A_p \approx -8dB$

so it will not meet the specs.

(c) Max gain of each filter stage is 1. So max possible input voltage should be 1 volt.


(d)	Butterworth	Chebyshev	Inv-Chebyshev	Elliptic	Bessel
$f_{pmax}$	1.124 M	0.994 M	1.42 M	0.999 M	1.16 M
$Q_{max}$	9.56	5.55	9.02	4.74	1.5
Group delay (max variation)	550 ns	1.15 $\mu s$	300 ns	1 $\mu s$	500 ps



AC Response

Δ: dB20(VF("/Inv\_Chebyshev"))  
□: dB20(VF("/Elliptic"))

□: dB20(VF("/Chebyshev"))

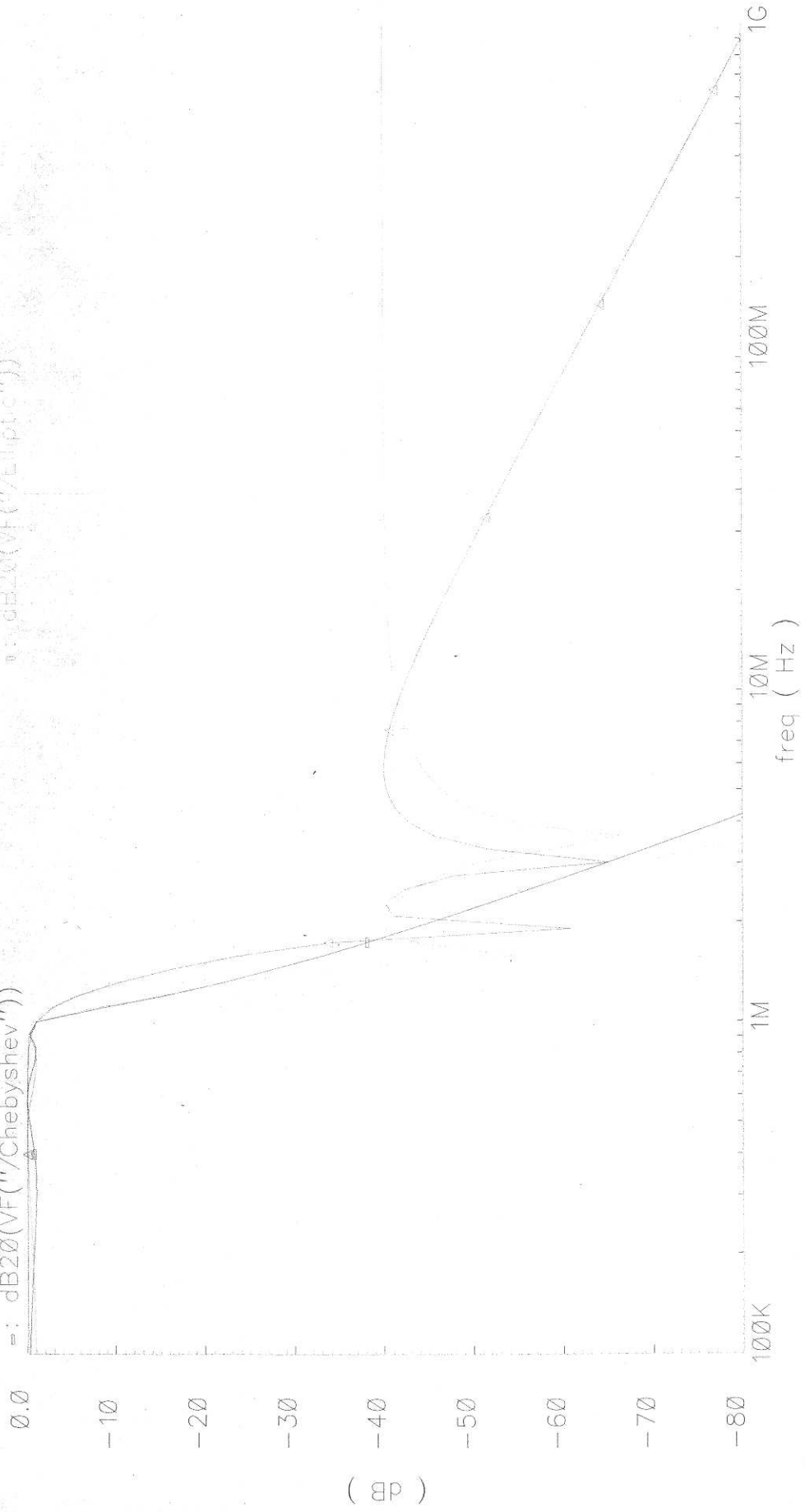



Mag Resp

AC Response

Δ: phase(VF("/Chebyshev"))  
□: phase(VF("/Butterworth"))


—: phase(VF("/Inv\_Chebyshev"))

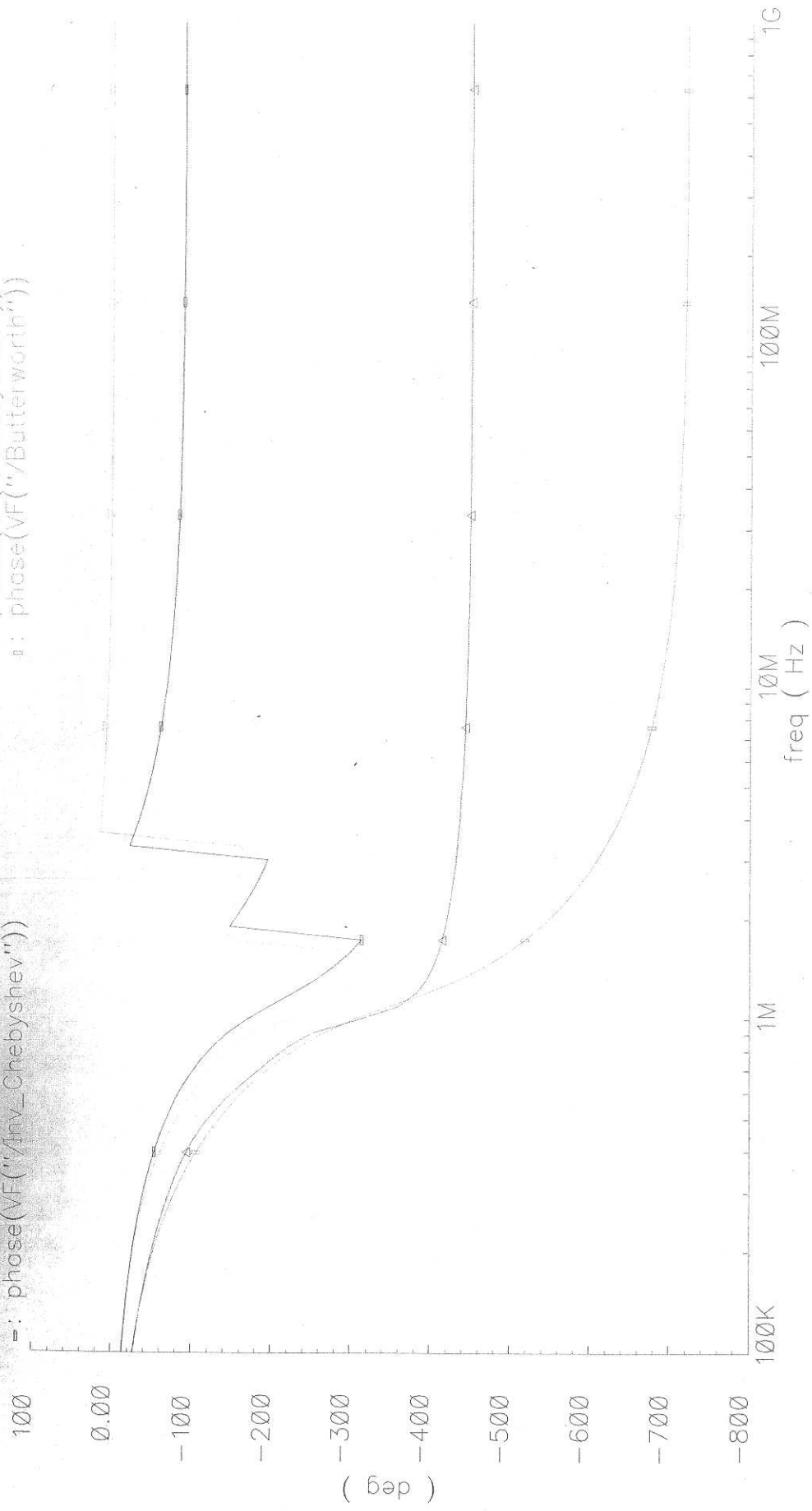

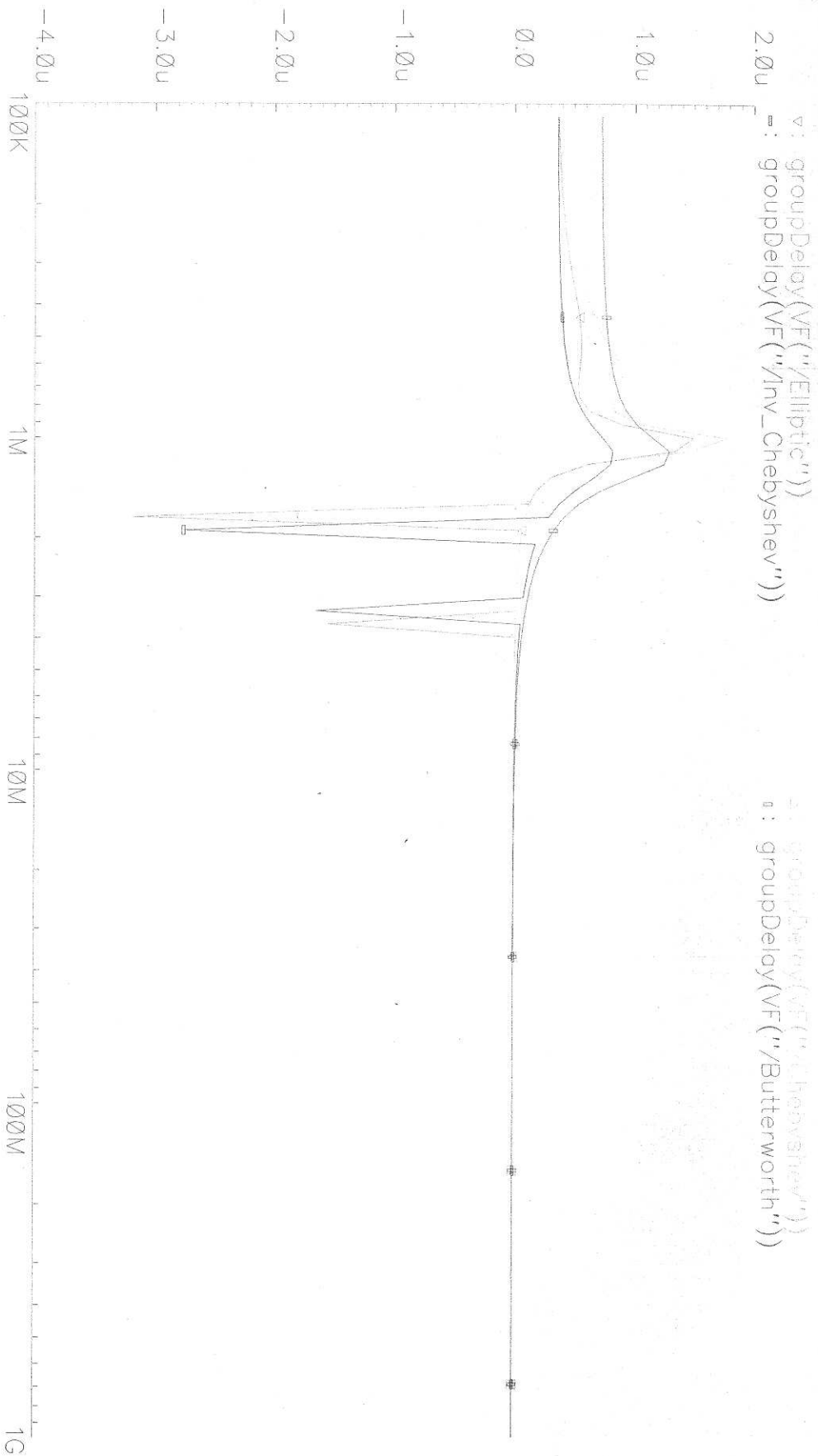


*Group Delay*

# Bessel Prototype

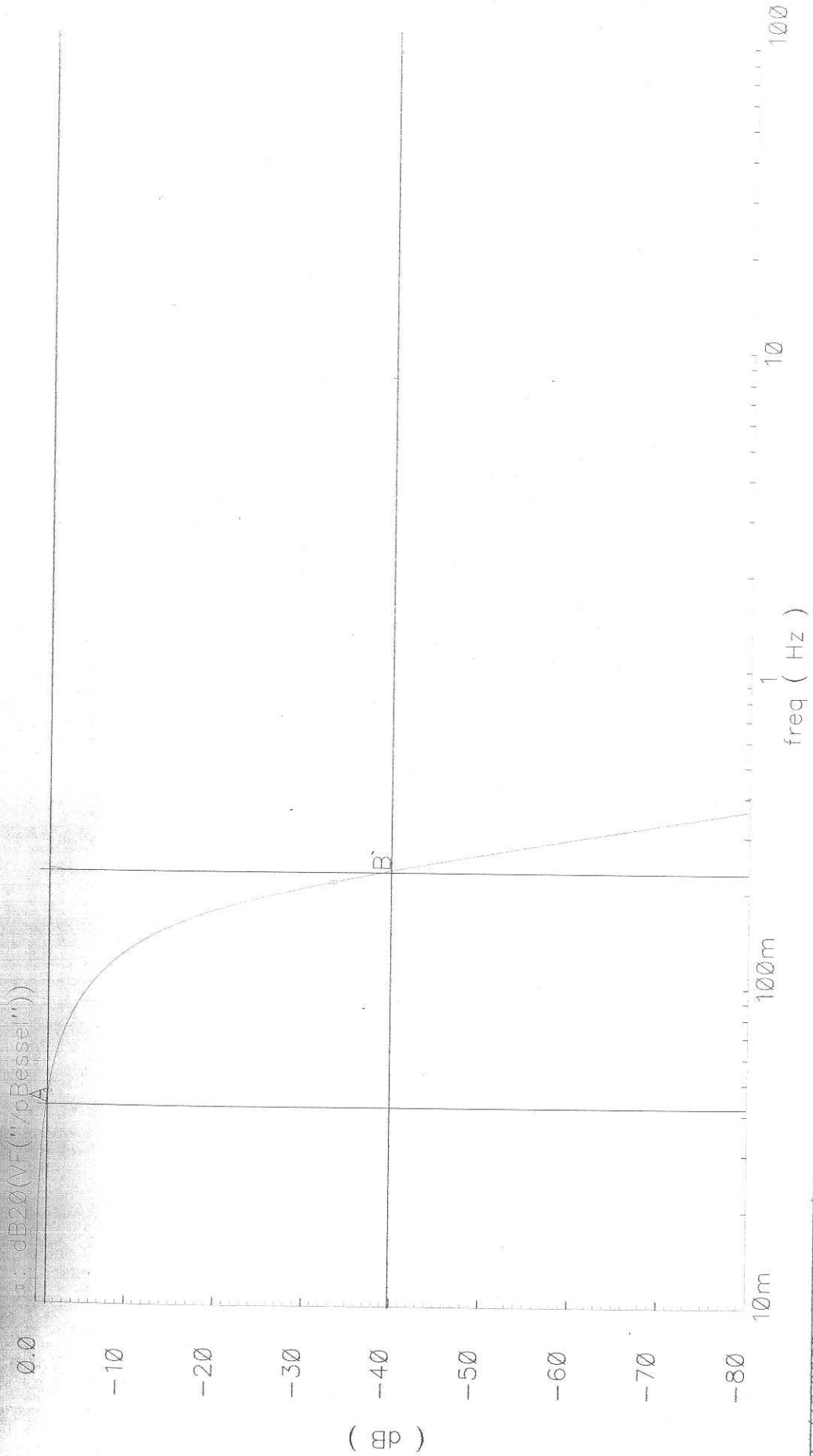

A: (42.2669m -1.02338)

B: (232.274m -39.7566)

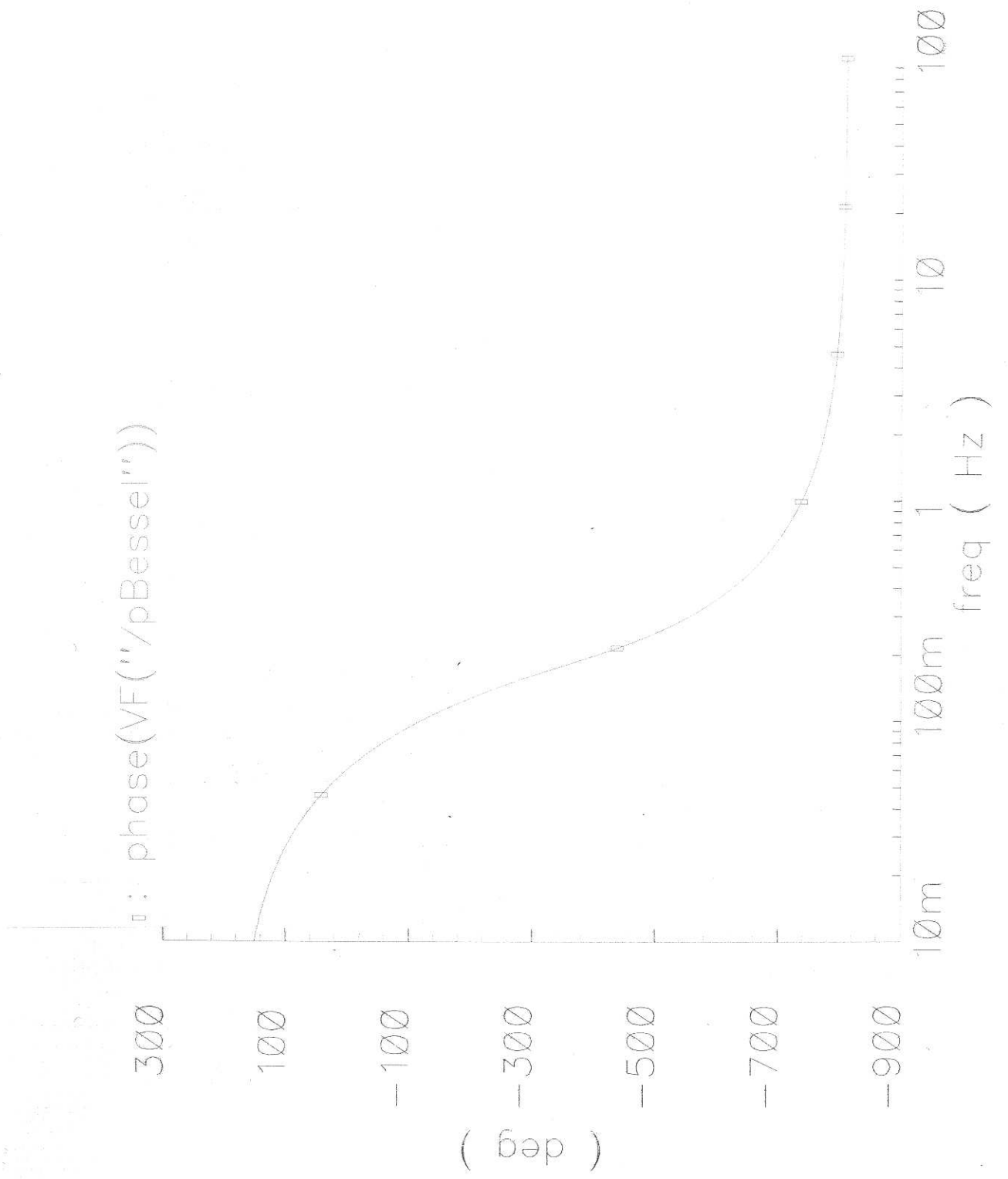

Bessel filter



