

Spring 2004; E4215: Analog Filter Synthesis and Design; HW0

Nagendra Krishnapura (nkrishna@vitesse.com)

due on 21 Jan. 2004

This assignment has ZERO credit and does not contribute to the final grade. Its purpose is to gauge your familiarity of prerequisite topics.

1. Check the terms that are unfamiliar to you:

- Laplace transform
- Impulse response
- Frequency response
- Transfer function
- Bode plot
- Operational amplifier
- Bipolar transistor
- MOS transistor
- Common drain amplifier
- Loop gain
- Gain margin
- Phase margin
- dB units

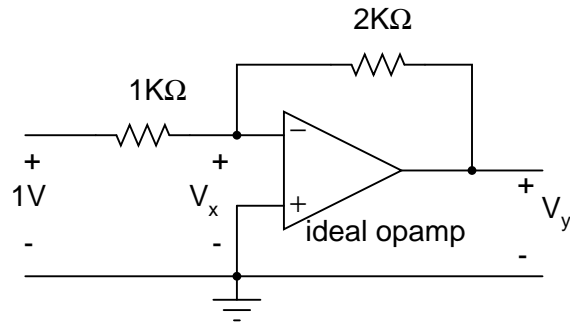


Figure 1:

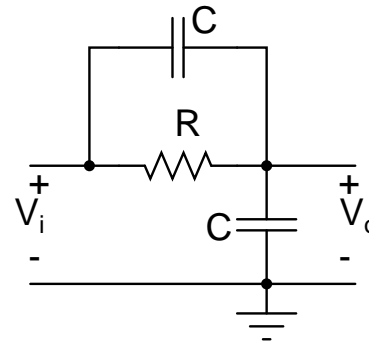


Figure 2:

2. The circuit in Fig. 1 is _____

$$V_x =$$

$$V_y =$$

3. Transfer function of the circuit in Fig. 2:

$$\frac{V_o(s)}{V_i(s)} =$$

$$\text{pole of the circuit} =$$

$$\text{zero of the circuit} =$$

4. In Fig. 3

$$V_o =$$

5. Transfer function of the circuit in Fig. 4:

$$\frac{V_o(s)}{V_i(s)} =$$

6. In Fig. 5:

$$\frac{v_o}{v_i} =$$

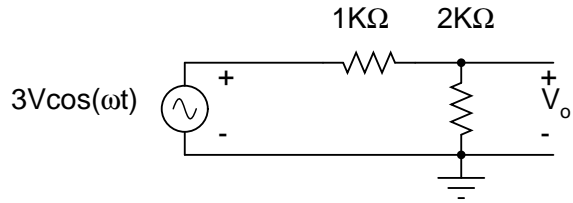


Figure 3:

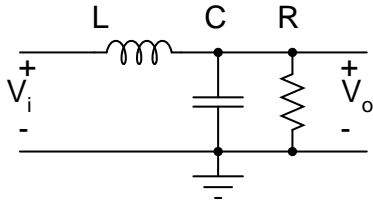


Figure 4:

7. In Fig. 5, if $R_L = r_{ds} = 1k\Omega$, and $g_m = 4\text{ mS}$, what is $\frac{v_o}{v_i}$ in dB?

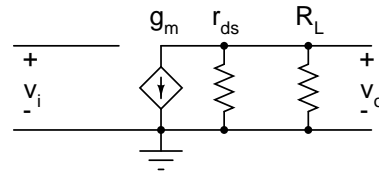


Figure 5: