

# E4215: Analog Filter Synthesis and Design

## Transfer functions realizable in a biquad

Nagendra Krishnapura (nkrishnapura@mltc.com)

11 Feb. 2004

### 1 opamp-RC filter

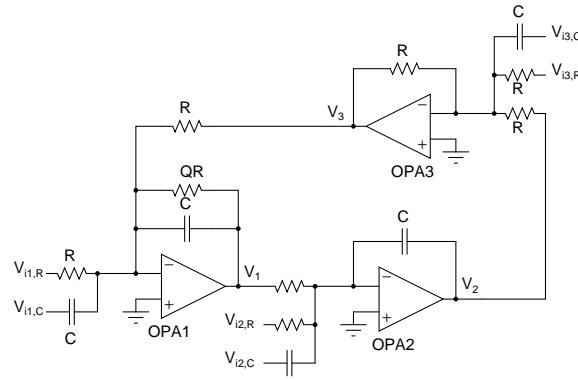


Figure 1: Tow-Thomas biquad with various possible inputs

Table 1: Transfer function between different inputs and outputs in Fig. 1.  $D(s) = 1 + \frac{sCR}{Q} + (sCR)^2$

	$V_1$	$V_2$	$V_3$
$V_{i1,R}$	$-\frac{sCR}{D(s)}$	$\frac{1}{D(s)}$	$-\frac{1}{D(s)}$
$V_{i2,R}$	$-\frac{1}{D(s)}$	$-\frac{1/Q + sCR}{D(s)}$	$\frac{1/Q + sCR}{D(s)}$
$V_{i3,R}$	$\frac{sCR}{D(s)}$	$-\frac{1}{D(s)}$	$-\frac{sCR/Q + (sCR)^2}{D(s)}$
$V_{i1,C}$	$-\frac{(sCR)^2}{D(s)}$	$\frac{sCR}{D(s)}$	$-\frac{sCR}{D(s)}$
$V_{i2,C}$	$-\frac{sCR}{D(s)}$	$-\frac{sCR/Q + (sCR)^2}{D(s)}$	$\frac{sCR/Q + (sCR)^2}{D(s)}$
$V_{i3,C}$	$\frac{(sCR)^2}{D(s)}$	$-\frac{sCR}{D(s)}$	$-\frac{(sCR)^2/Q + (sCR)^3}{D(s)}$

The last row in Table 1 using the capacitive input  $V_{i3,C}$  is not practical because it introduces an extra pole in the feedback around opamp OPA3, degrading stability (as in an opamp differentiator). **Do not use this!**

## 2 $g_m$ -C filter

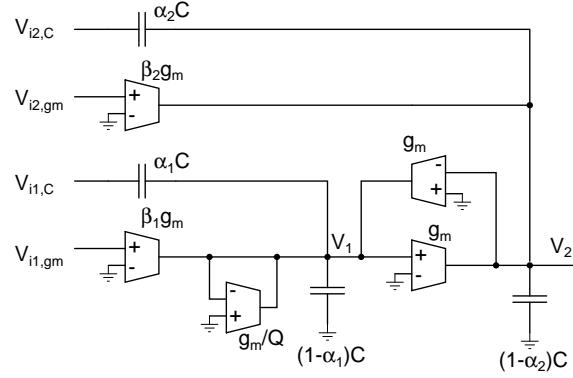


Figure 2:  $g_m$ -C filter with various possible inputs

Table 2: Transfer function between different inputs and outputs in Fig. 2.  $D(s) = 1 + \frac{sC}{g_m Q} + \left(\frac{sC}{g_m}\right)^2$

	$V_1$	$V_2$
$V_{i1,g_m}$	$\beta_1 \frac{sC/g_m}{D(s)}$	$\beta_1 \frac{1}{D(s)}$
$V_{i2,g_m}$	$\beta_2 \frac{1}{D(s)}$	$\beta_2 \frac{1/Q + sC/g_m}{D(s)}$
$V_{i1,C}$	$\alpha_1 \frac{(sC/g_m)^2}{D(s)}$	$\alpha_1 \frac{sC/g_m}{D(s)}$
$V_{i2,C}$	$\alpha_2 \frac{sC/g_m}{D(s)}$	$\alpha_2 \frac{sC/Q g_m + (sC/g_m)^2}{D(s)}$

## 3 Realization of arbitrary numerator polynomials

Arbitrary numerator polynomials can be realized by

- Voltage summing: The input voltage is applied to one of the possible input terminals in Fig. 1 or Fig. 2. A summing circuit is used to generate a linear combination of the input voltage and the available outputs ( $V_{in}, V_1, V_2, V_3$  in Fig. 1;  $V_{in}, V_1, V_2$  in Fig. 2). The result is a row-wise weighted summation in Table 1 or Table 2.
- Feedforward: The output is taken from one of the output terminals ( $V_1, V_2, V_3$  in Fig. 1;  $V_1, V_2$  in Fig. 2). The input is applied to more than one input ( $V_{ik,g_m}, V_{ik,C}$ ). The result is a column-wise weighted summation in Table 1 or Table 2.