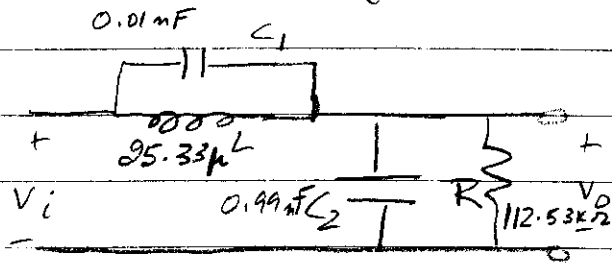


# Analog Filters Design/Synthesis

1



$$H(s) = \frac{(C_2 || R)}{(C_2 || R) + (C_1 || L)} = \frac{s^2 L C_1 + 1}{s^2 L (C_1 + C_2) + s C_1 R + 1}$$

$$|H(s)|_{\omega = 1 \times 10^6 \times 2\pi} = -0.0 \log \left| \frac{1 - \frac{(2\pi \times 10^6)^2}{2 \times 10^7}}{1 + j \frac{2\pi \times 10^6 \times 0.01}{4\pi^2 \times 10^3 \times 10^3} - \frac{(2\pi \times 10^6)^2}{2 \times 10^6}} \right|$$

$$= -20 \log \frac{|1 - \gamma_{100}|}{|\sqrt{2}j|}$$

$$\approx -20 \log \frac{1}{\sqrt{2}} \approx 3 \text{ dB}$$

$$\therefore A_p = 3 \text{ dB}$$

2

$$\omega_2 = 2\pi \times 10^7 \text{ rad/s} \quad \Omega_2 = 10 \text{ rad/s}$$

Use frequency scaling

$$\omega \rightarrow s/\beta \quad 2\pi \times 10^7 \leftrightarrow 10/\beta \Rightarrow \beta = \frac{1}{2\pi \times 10^6} \equiv \text{frequency axis contracts}$$

$$R \leftrightarrow R$$

$$R' = 112.5 \Omega$$

$$\omega L \rightarrow s(L/\beta) \quad \therefore L' = \frac{L}{2\pi \times 10^6} \equiv 159 \text{ H}$$

$$L' = 159 \text{ H}$$

$$\omega C \rightarrow s(C/\beta)$$

$$C_1' = 62.8 \mu\text{F} \quad C_2' = 62 \mu\text{F}$$

Now do impedance scaling

$$R \leftrightarrow \alpha R$$

$$1 \rightarrow \alpha (110 \cdot 5)$$

$$L \leftrightarrow \alpha L$$

$$L = \frac{159.84}{110.5} \approx 1.444 \text{ H}$$

$$C \leftrightarrow \frac{C}{\alpha}$$

$$C_1 = 7.072 \text{ mF}$$

$$C_2 = 698 \text{ } \mu\text{F}$$

$$H(s) = \frac{1 + \left(\frac{s}{\Omega_p}\right)^2}{1 + \frac{s}{Q\Omega_p} + s^2/\Omega_p^2} \quad \left[ \Omega_p \approx 1 \text{ rad/sec} \right]$$
$$= \frac{1 + \left(\frac{s}{10}\right)^2}{1 + \sqrt{0.5}s + s^2}$$

$$\Omega_s = ?$$

$$|H(s)| = -20 \text{ dB} \approx 0.1$$

$$\left| \frac{1 - \frac{\Omega^2}{100}}{1 + \sqrt{0.5}j\Omega - \Omega^2} \right| = 0.1$$

$$\Omega = 3 \text{ rad/sec}$$

3

Low pass to High Pass Transform

$$s \cdot S = \omega_p \cdot S_p \quad \left[ \text{invert the frequency axis} \right]$$

$$\omega_p = 10 \text{ M} \quad S_p = 1 \text{ rad/sec}$$

$$H(S) = \frac{1 + \left(\frac{S}{10}\right)^2}{1 + \sqrt{2}S + S^2} \quad \dots \quad H(s) = \frac{1 + \left(\frac{R_p \omega_p}{10s}\right)^2}{1 + \sqrt{2} \frac{R_p \omega_p}{s} + \left(\frac{R_p \omega_p}{s}\right)^2}$$

$$H(s) = K \frac{\left(1 + \frac{s}{\omega_2}\right)^2}{1 + \frac{s}{\omega_p} + \left(\frac{s}{\omega_p}\right)^2} = \frac{1 + \left(\frac{\omega_p}{10s}\right)^2}{1 + \sqrt{2} \frac{\omega_p}{s} + \left(\frac{\omega_p}{s}\right)^2}$$

$\omega_2 = \frac{\omega_p}{10} \approx 1 \text{ M rad/s} = \text{frequency of the notch}$

$K = \frac{1}{100}$

$$L = 1.414 \text{ H} \quad \equiv \quad C = \frac{1}{\omega_p \omega_p L} = 70.7 \text{ nF}$$

$$C_1 = 7.07 \text{ mF} \quad \equiv \quad L_1 = \frac{1}{C_1 \omega_p \omega_p} = 14.98 \text{ mH}$$

$C_1 \text{ depends}$

$$L_2 \approx 691.11 \text{ mF} \quad \equiv \quad L_2 \approx 0.14 \text{ mH}$$

$$R = 1 \Omega$$

Impedance Scaling


$$R \leftrightarrow \alpha R$$

$$1 \leftrightarrow \alpha (10^4) \quad \alpha = 10^{-4}$$

$$C' = 7.07 \text{ pF}$$

$$L_1' \approx 14.98 \text{ mH}$$

$$L_2' \approx 1.498 \text{ mH}$$

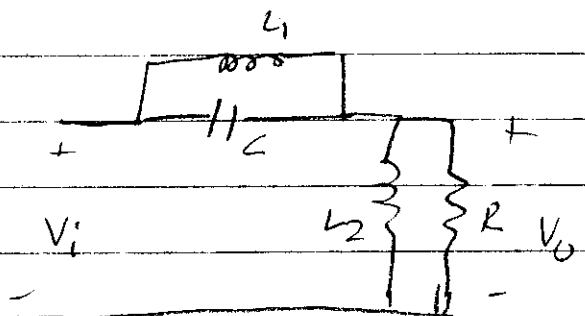


replace  $L_1', L_2'$  by gyrators

$$g_m = 10^{-4}$$

$$L_1 = \frac{C_1}{g_m^2} \Rightarrow C_1 = 1.41 \mu F$$
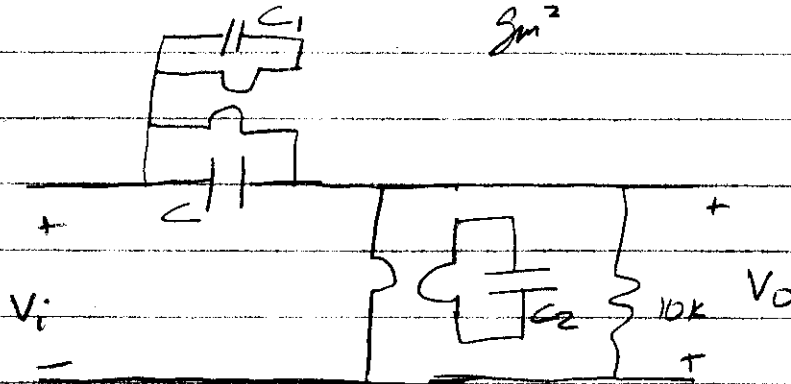
$$L_2 = 1.498 \text{ m} = \frac{C_2}{g_m^2} \Rightarrow C_2 = 14.28 \text{ pF}$$



4.

LP  $\leftrightarrow$  BP

$$\frac{S}{\Omega_2} = \frac{\Omega_p}{\Omega_2 \omega_0} \frac{S^2 + \omega_0^2}{S}$$

$$\omega_0 = \sqrt{\omega_{p1} \omega_{p2}} = 110 \text{ M rad/s}$$

$$\omega_0 = \omega_{p2} - \omega_{p1} = 91 \text{ M rad/s}$$

$$L \equiv (L' + C') \quad L' = \frac{L \Omega_p}{\omega_0} = 67.2 \mu \text{mH}$$

$$C' = \frac{\omega_0}{\omega_0^2 \Omega_p L} = 1.23 \text{ nF}$$

$$C_1 \equiv (L_1' \parallel C_1') \quad L_1' = \frac{\omega_b}{\omega_0^2 R_p C_1} = 0.1248 \mu\text{H}$$

$$C_1' = \frac{C_1 R_p}{\omega_b} = 0.33 \mu\text{F}$$

$$C_2 \equiv (L_2' \parallel C_2') \quad L_2' = 2.5 \text{ nH} \quad C_2' = 32.9 \text{ nF}$$

### Impedance Scaling

$$R \leftrightarrow \alpha R$$

$$1 \leftrightarrow \alpha (2 \times 10^3) \quad \alpha = \frac{1}{2 \times 10^3}$$

$$\therefore L' = 134.58 \mu\text{H}$$


$$C' = 0.615 \text{ pF}$$

$$L_1' = 0.496 \text{ mH}$$

$$L_2' = 5.02 \mu\text{H}$$

$$C_1' = 0.165 \text{ pF}$$

$$C_2' = 16.455 \text{ pF}$$

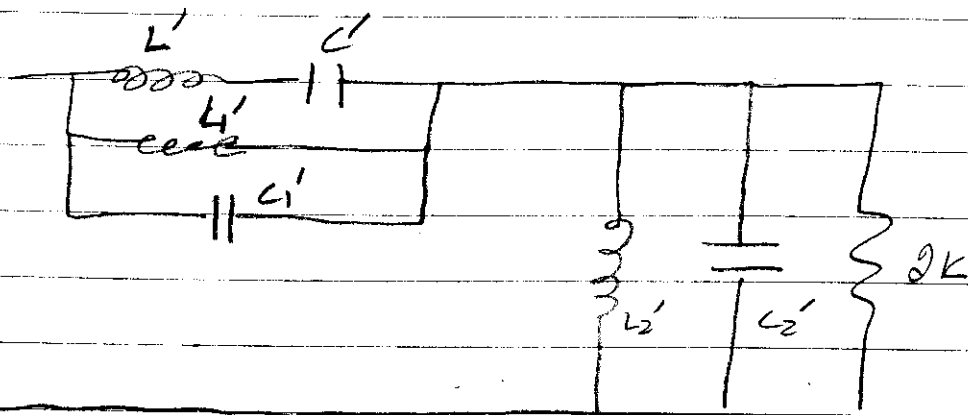

Stopband edges  $R_s = \frac{R_p}{\omega_b} \frac{\omega_0^2 - \omega_s^2}{\omega_s} \quad 3 = \frac{1}{0.1 \text{ M}} \frac{(\omega_s^2 - (110 \text{ M})^2)}{\omega_s}$

solve to get  $\omega_{s1} = 145.9 \text{ M} \quad \omega_{s2} = 82.9 \text{ M rad/s}$

Gain @  $110 \text{ M rad/s} \equiv 1 \equiv 0 \text{ dB} \quad (\omega_0 = 110 \text{ M rad/s})$

$$\omega_{z1}, \omega_{z2} = \omega_0^2 \quad \omega_{z2} = \frac{(110 \text{ M})^2}{47 \text{ M}} = 257.45 \text{ M rad/s}$$

5

## LP - BR transform

$$\frac{s}{\Omega_p} \leftrightarrow \frac{\omega_b \cdot s}{\omega_0^2 + s^2}$$

$$\omega_0 = \sqrt{\omega_{s1} \omega_{s2}} = \sqrt{8.1 \text{ M} \times 10 \text{ M}} = 9 \text{ M rad/s}$$

$$\frac{\Omega_s}{\Omega_p} = \frac{\omega_b \omega_s}{\omega_0^2 - \omega_s^2} = \frac{\omega_b \omega_{s1}}{(\omega_{s1} \omega_{s2} - \omega_{s1}^2)} = \frac{\omega_b}{\omega_{s2} - \omega_{s1}}$$

$$\therefore \omega_b = 3 \times 1.9 \text{ M rad/s} = 5.7 \text{ M rad/s}$$

$$L \equiv (L' || C') \quad L' = \frac{\omega_b \Omega_p L}{\omega_0^2} = 99.5 \text{ mH}$$

$$C' = \frac{1}{\Omega_p \omega_b L} = 194.9 \text{ nF}$$

$$C_1 \equiv (L'_1 + C'_1) \quad L'_1 = \frac{L}{\Omega_p \omega_b C_1} = 94.8 \text{ } \mu\text{H}$$

$$C'_1 = \frac{\Omega_p \omega_b C_1}{\omega_0^2} = 497.6 \text{ pF}$$

$$L_2 \equiv (L'_2 + L_2') \quad L'_2 = 953.8 \text{ mH}$$

$$L_2' = 48.7 \text{ mH}$$


## Impedance Scaling

$$R \leftrightarrow \alpha R \quad 1 \leftrightarrow \alpha (10^4) \quad \alpha = 10^{-4}$$

$$L' = (99.5 \text{ m} \times 10^4) = 994 \text{ } \mu\text{H}$$

$$C'_1 = 19.416 \text{ pF} \quad L_1' = 950.6 \text{ mH}$$
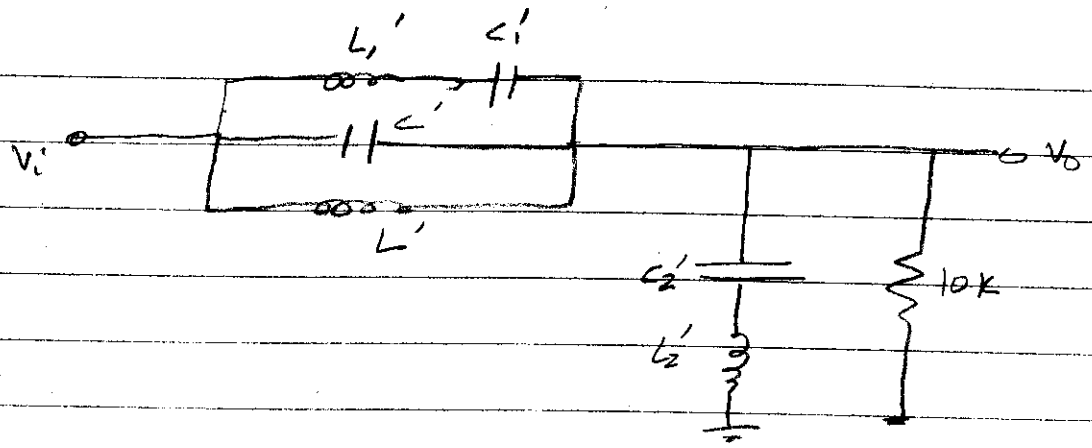
$$C_1' = 49.26 \text{ pF} \quad L_2' = 9.54 \text{ } \mu\text{H} \quad C_2' = 4.86 \text{ pF}$$



Passband edges

$$\omega_{p1} - \omega_{p2} = \omega_0 = 5.7 \text{ M}$$

$$\sqrt{\omega_{p1} \omega_{p2}} = \omega_0 = 9 \text{ M rad/s}$$

solve to get  $\omega_{p1} = 6.59 \text{ M rad/s}$      $\omega_{p2} = 10.89 \text{ M rad/s}$


@  $9 \text{ M rad/sec}$   $|H(j\omega_0)| = |H_{\text{prototype}}(j\omega)| = -40 \text{ dB}$

6

$$H(s) = \left(\frac{\omega_0}{\omega_p}\right)^2 \frac{1 + \left(\frac{s}{\omega_0}\right)^2}{1 + \frac{s}{\omega_p} + \left(\frac{s}{\omega_0}\right)^2}$$

Use  $V_{ig}, R \leftarrow \frac{\left(\frac{\omega_0}{\omega_p}\right)^2}{D(s)} + \frac{\left(\frac{s}{\omega_0}\right)^2}{D(s)} \rightarrow$  Use  $V_{ig}, Z$

Take output at output of first opamp

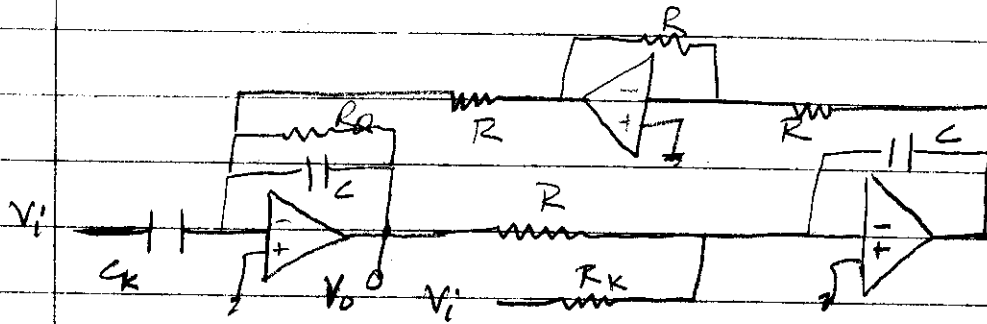

$$\omega_p = \frac{1}{RC} = 10 \text{ M rad/s}$$

$$C = 100 \text{ pF} \quad R = 1 \text{ k}\Omega \quad R_Q = \frac{1}{\sqrt{3}} \text{ k}\Omega$$

$$\frac{R_K}{R} = \left( \frac{\omega_p}{\omega_2} \right) \therefore R_K = 100 R = 1 \text{ M}\Omega$$

7

Frequency Scaling [from filter in (4)]

$$s \leftrightarrow s/\beta$$

$$100 \text{ M} \leftrightarrow 10 \text{ M} \times 2\pi/\beta \quad \beta = \frac{2\pi}{10} = \frac{\pi}{5}$$

$$L' = \frac{134 \mu\text{H}}{\beta} = 0.81 \text{ mH} \quad C' = \frac{.615}{\beta} \text{ pF} = 0.97 \text{ pF}$$

similarly  $L_1' = 0.79 \text{ mH} \quad C_1' = 0.96 \text{ pF}$

$$L_2' = 7.99 \mu\text{H} \quad C_2' = 26 \text{ pF}$$

