

# Pipelined A/D converters

---

Nagendra Krishnapura,



Fall 2004: Analog Systems in VLSI  
Columbia University  
New York, NY 10027.

## OUTLINE

---

- **Two step A/D converter**
- **Two step A/D converter with digital correction**
- **1.5 b/stage pipelined converter with digital correction**

# Two step flash converter

 
 


## Two step flash converter

---

- A/D 1 quantizes the input to  $M$  bits
- Ideally,  $0 \leq V_q \leq V_{LSB1}$  ( $V_{LSB1} = V_{ref}/2^M$ )
- A/D 2 quantizes the amplified residue ( $2^M V_q$ ) of A/D 1 to  $K$  bits
- A/D 1 needs to be accurate to  $N = M + K$  bits, A/D 2 to  $K$  bits. See HW4 solutions for detailed calculations.
- Overall resolution is  $N = M + K$  bits. A/D 1 provides  $M$  bits (MSB), A/D 2 provides  $K$  bits (LSB)
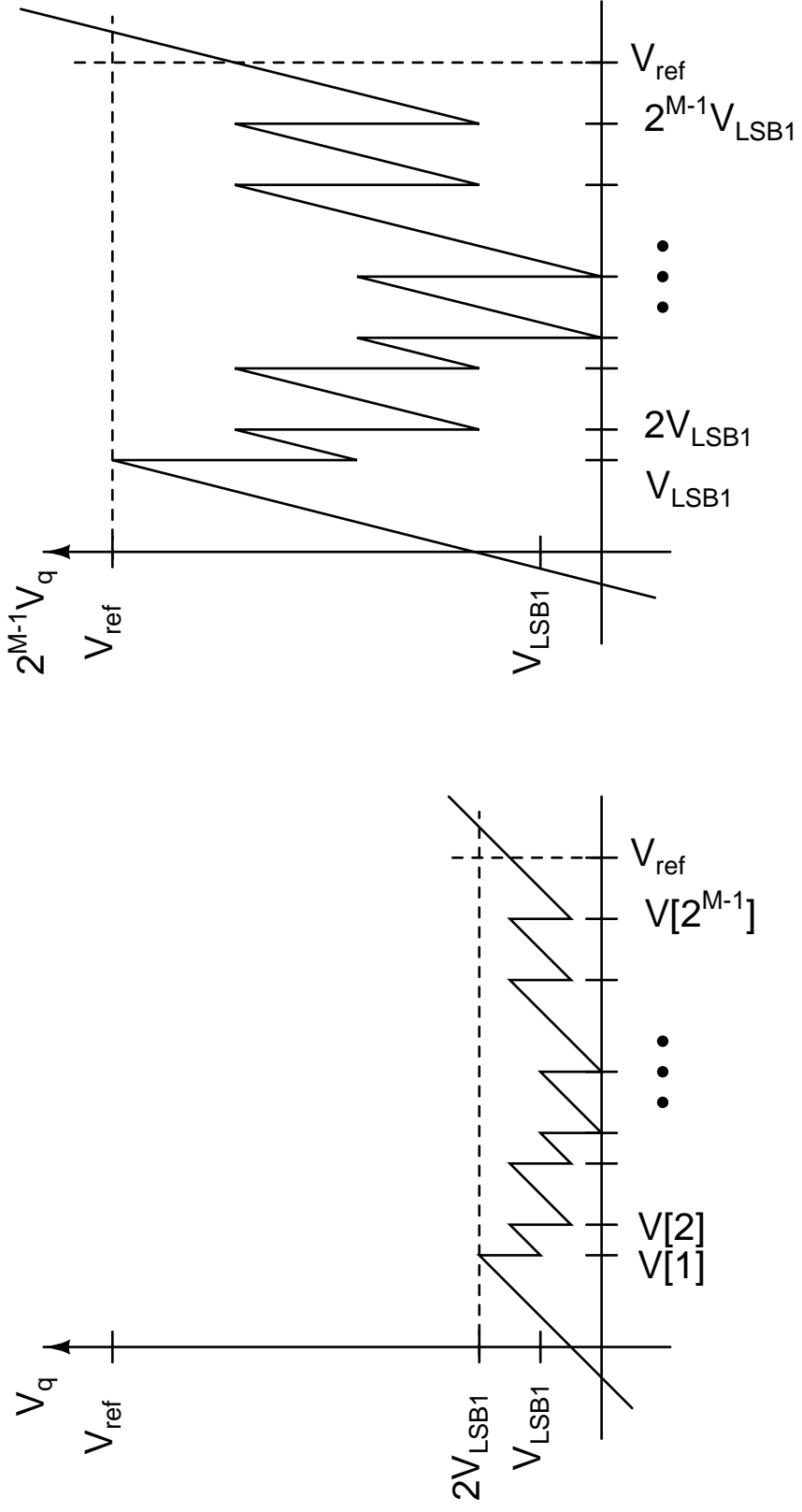 
# Two step flash converter with digital correction



## Two step flash converter with digital correction

---

- A/D 1 quantizes the input to  $M$  bits
- With  $\text{INL}=0.5\text{LSB}$ ,  $0 \leq V_q \leq 2V_{LSB1}$  ( $V_{LSB1} = V_{ref}/2^M$ )
- Amplify by  $2^{M-1}$  instead of  $2^M$  so that the amplified residue is contained in  $(0, V_{ref})$ , the range of A/D 2
- A/D 2 quantizes the amplified residue ( $2^{M-1}V_q$ ) of A/D 1 to  $K$  bits

## Two step flash converter with digital correction

---

- A/D 2 output can be used to determine if the output of A/D 1 needs correction
  - $0 \leq 2^{M-1}V_q < V_{ref}/4$  : reduce A/D 1 output by 1
  - $V_{ref}/4 \leq 2^{M-1}V_q < 3V_{ref}/4$  : Use A/D 1 output as is
  - $3V_{ref}/4 \leq 2^{M-1}V_q < V_{ref}$  : increase A/D 1 output by 1
- A/D 1 needs to be accurate to  $M$  bits, A/D 2 to  $K + 1$  bits.
- Overall resolution is  $N = M + K$  bits. 1 bit redundancy in A/D 2 helps relax A/D,1 requirements from  $N$  bits to  $M$  bits. A significant practical advantage. A/D 1 provides  $M-1$  bits (MSB) and A/D 2 provides  $K+1$  bits (LSB).

## Multi step (pipelined) A/D converter with 1 effective bit/stage





---

- Having a multi step converter with 1 corrected bit per stage as described above implies 2 bit raw resolution in each stage. This means a 2 bit A/D converter, 2 bit D/A converter and an amplifier of gain 2. It turns out that this is not necessary and a 1.5 bit resolution in each stage provides *exactly* the same effective resolution as a 2 bit resolution in each stage. This leads to significant savings in hardware.









# 1.5 bits/stage vs. 2 bits/stage: Structure

---

    
 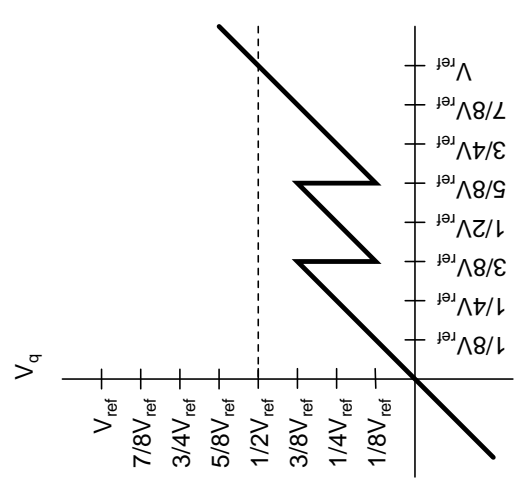    
# 1.5 bits/stage vs. 2 bits/stage: Residue




## 1.5 bits/stage vs. 2 bits/stage

---

- In the ideal case, having 2 bits per stage has a smaller range of residue than having 1.5 bits/stage
- In the nonideal case ( $\text{INL} < 0.5 \text{ LSB}$  at the 2 bit level), having 2 bits per stage and 1.5 bits/stage result in exactly the same range of residues
- Therefore, there is no need to resolve 2 bits. 1.5 bits are enough

# Digital correction

obtaining 3 bit output  $D_3$

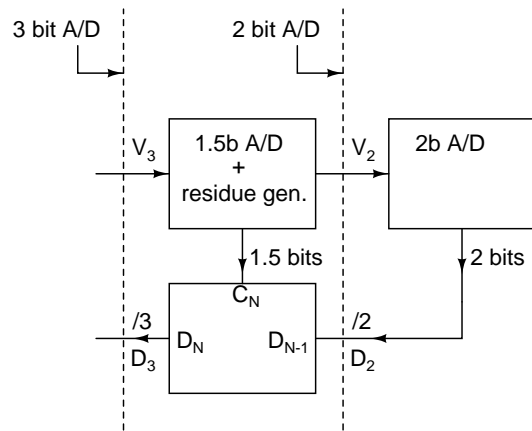

ideal 1.5b stage

1.5 bit stage o/p

	0	1	2
0	0	x	x
1	1	3	5
2	2	4	6
3	x	x	7

2 bit stage o/p

nonideal 1.5b stage


1.5 bit stage o/p

	0	1	2
0	0	2	4
1	1	3	5
2	2	4	6
3	3	6	7



2 bit stage o/p

x: redundant combinations; they don't occur in the ideal case. they provide correction in the nonideal case

 Analog path  
Quantizer and  
residue generator





Digital path  
Digital correction

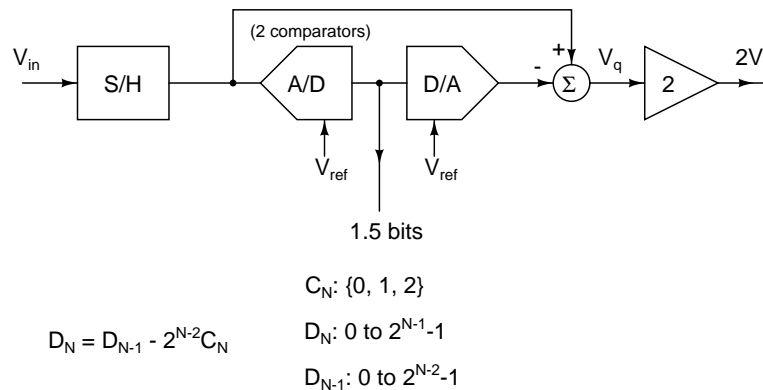 

- 1.5 b stage is followed by an ideal 2 bit stage. This can be used to obtain 1 effective bit from the first stage.
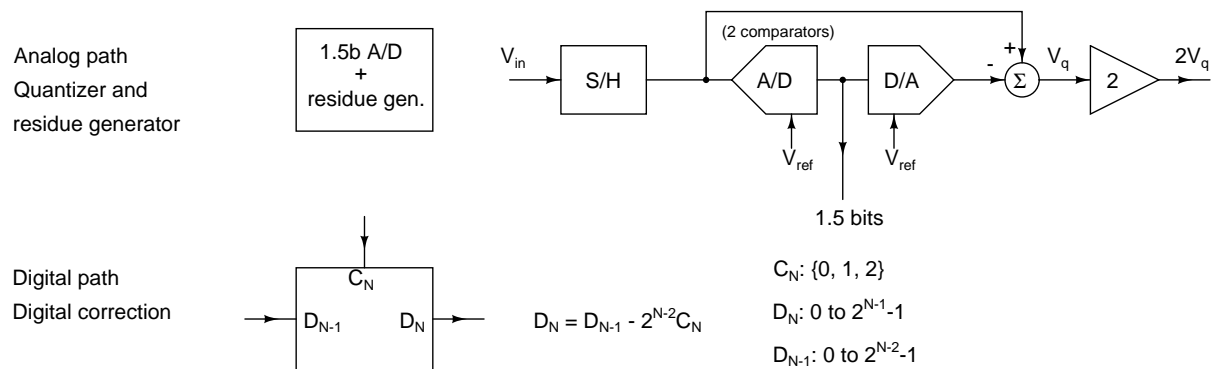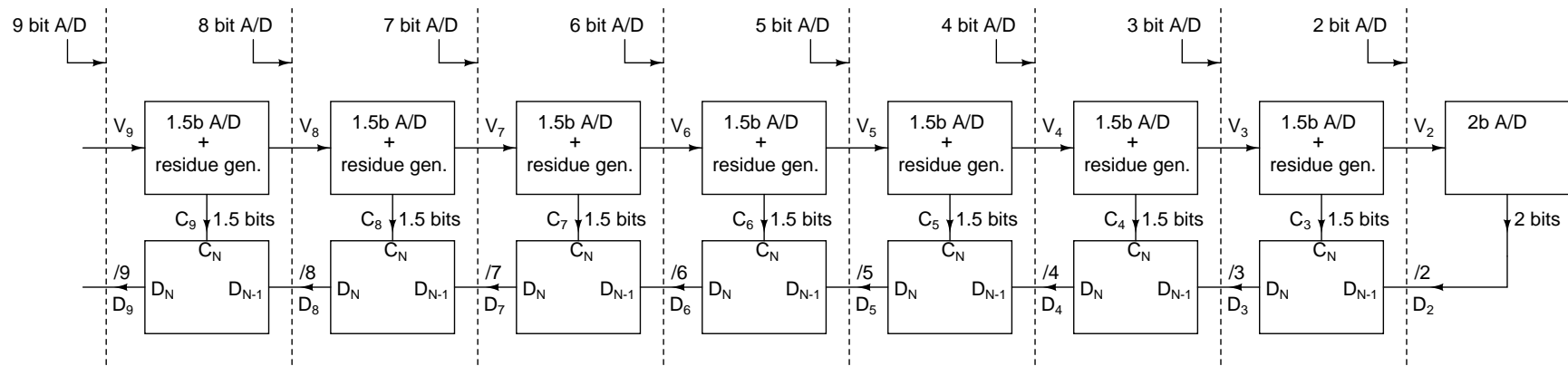
# 1.5 b/stage pipelined A/D converter with digital correction



## 1.5 b/stage pipelined A/D converter with digital correction

---

- The last stage is not digitally corrected. It has an output  $D_2$  with a 2 bit resolution.
- The last stage provides digital correction to the previous stage.  $D_2$  and  $C_3$  are used to obtain a 3 bit output  $D_3$  corresponding to the analog voltage  $V_3$ .
- $D_3$  and  $C_4$  are used to obtain  $D_4$ , the digital representation of  $V_4$  and so on...

## 1.5 b/stage pipelined A/D converter with digital correction

---

- The analog residue propagates from the left to the right in the figure. The digitally corrected output propagates from the right to the left.
- Digital delays are needed to combine the stage outputs ( $C_N, D_{N-1}$ ) appropriately. These are not shown in the figure.
- If the residue needs one clock cycle to propagate through each stage and the digital correction needs 1 cycle in each stage, the net latency is  $\approx 2NT_{clk}$  where  $N$  is the resolution of the A/D converter.