

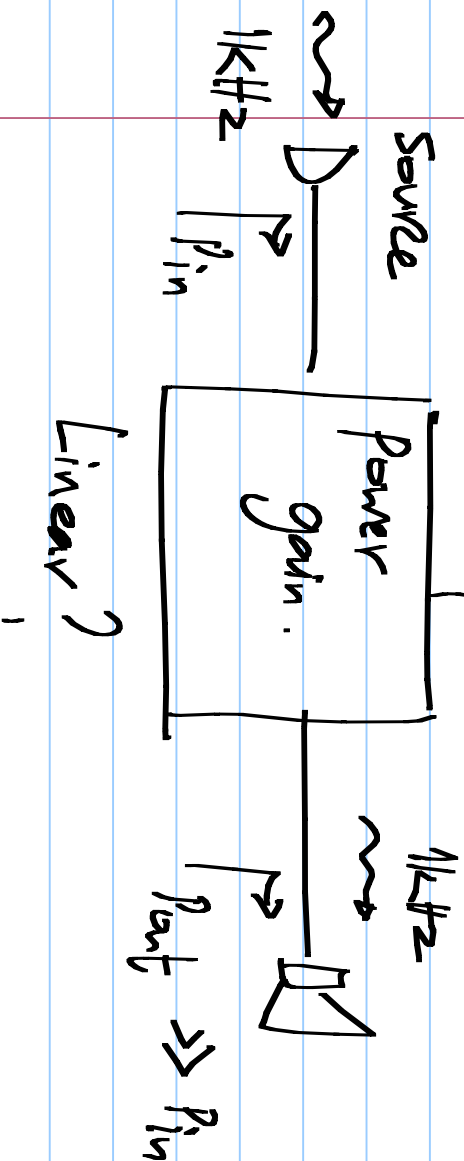
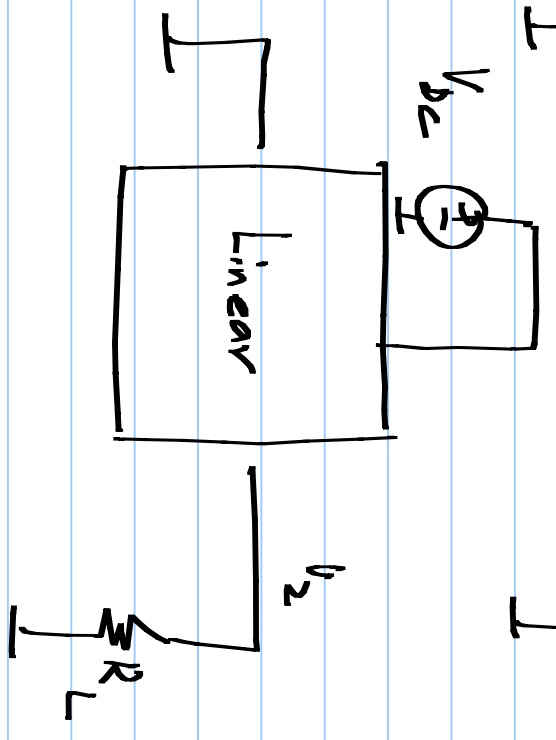


# Lecture 1. Obtaining power gain?

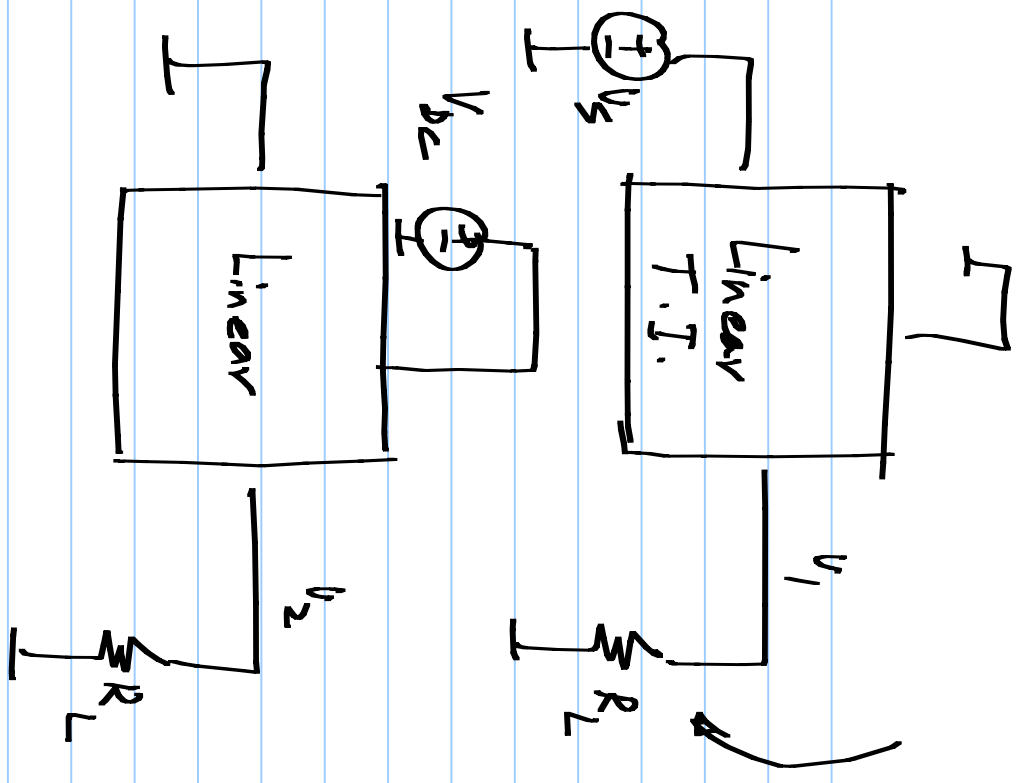

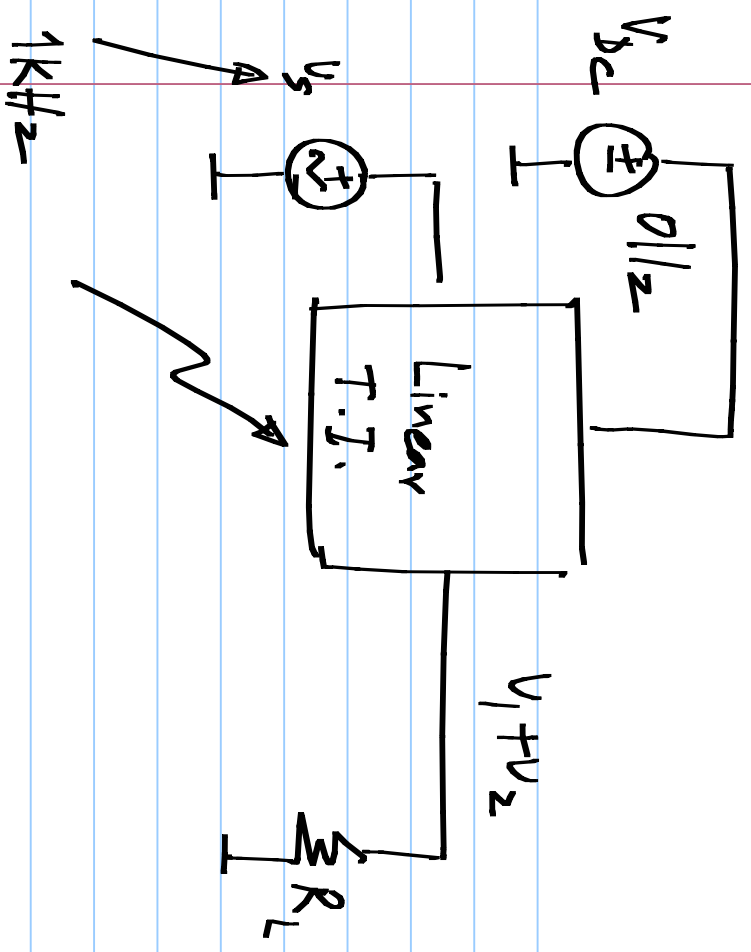\* Everything is passive  
(except batteries / power source)



Nonlinearity is essential for power amplification


[ Increased signal power at some  
desired frequency ]

Cannot be done at all with linear, time-invariant systems.

## Nonlinear two-port

$$I_1 = f_1(V_1, V_2)$$


$$I_2 = f_2(V_1, V_2)$$

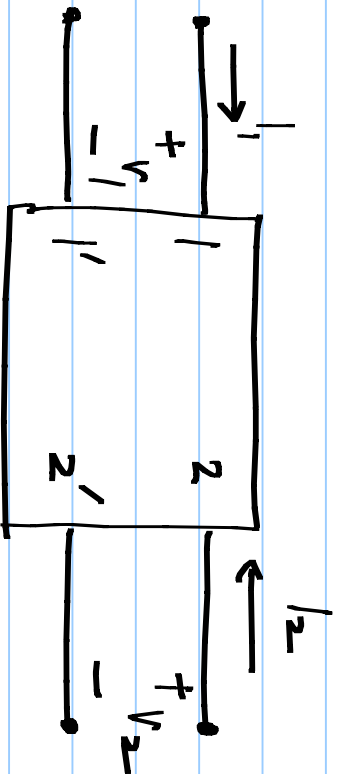

$$I_{10} = f_1(V_{10}, V_{20})$$

$$I_{20} = f_2(V_{10}, V_{20})$$

operating point:  $V_{10}, V_{20}$

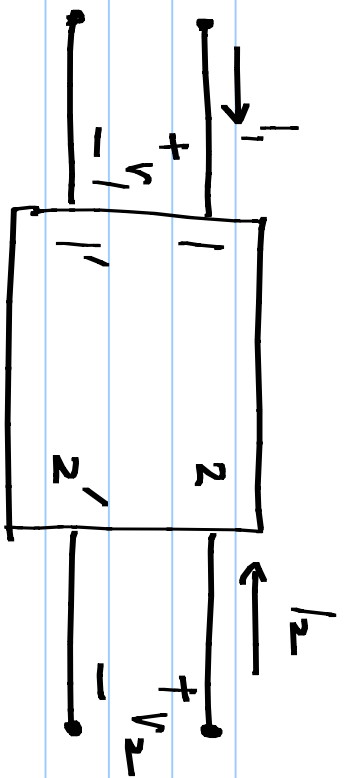

$$I_1 = f_1 (V_{10} + v_1, V_{20} + v_2)$$

$$I_2 = f_2 (V_{10} + v_1, V_{20} + v_2)$$

$$I_{10} = f_1 (V_{10}, V_{20})$$

$$I_{20} = f_2 (V_{10}, V_{20})$$

Operating point:


Signals

$v_1, v_2$

(incremental)

$$i_1 = I_1 - I_{10} \approx \left. \frac{\partial f_1}{\partial v_1} \right|_{dp} \cdot v_1 + \left. \frac{\partial f_1}{\partial v_2} \right|_{dp} \cdot v_2$$

$$i_2 = I_2 - I_{20} \approx \left. \frac{\partial f_2}{\partial v_1} \right|_{dp} \cdot v_1 + \left. \frac{\partial f_2}{\partial v_2} \right|_{dp} \cdot v_2$$

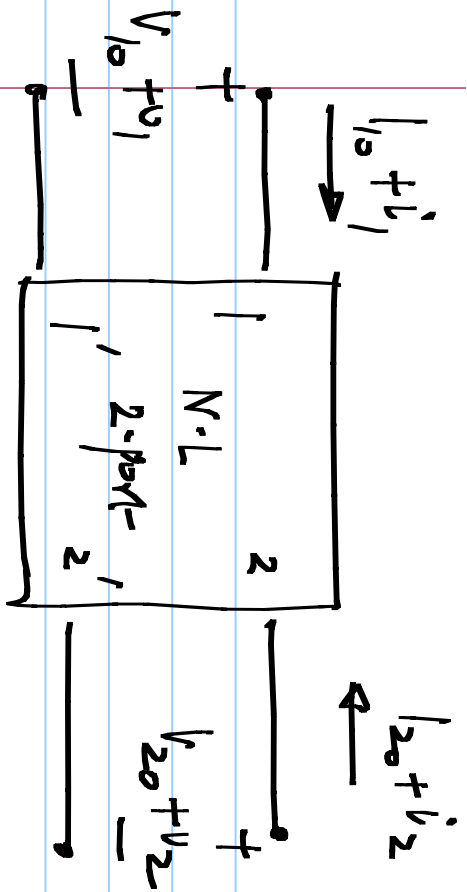


$$i_1 = \begin{bmatrix} y_{11} & y_{12} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$i_2 = \begin{bmatrix} y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

Incremental y-parameters


@ op. point

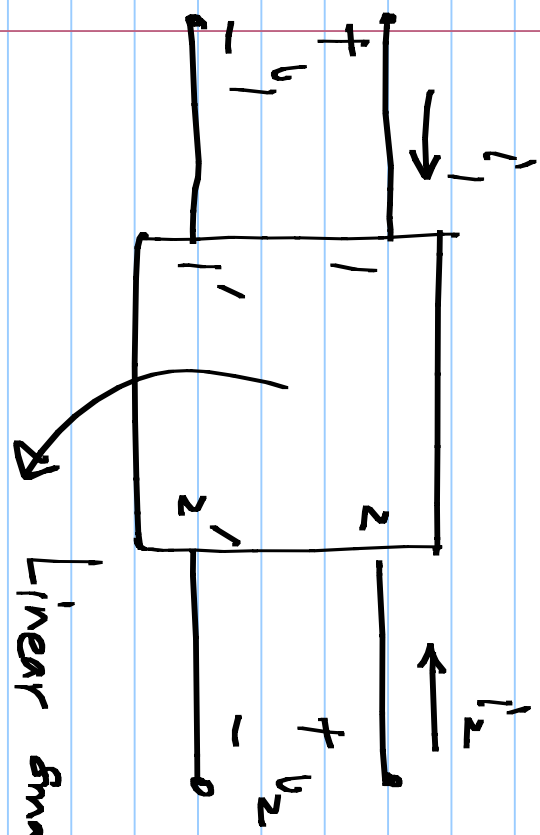

eg. circuit

op  $\{v_{10}, v_{20}\}$

$$\frac{\partial f_1}{\partial v_1} \Big|_{op}$$

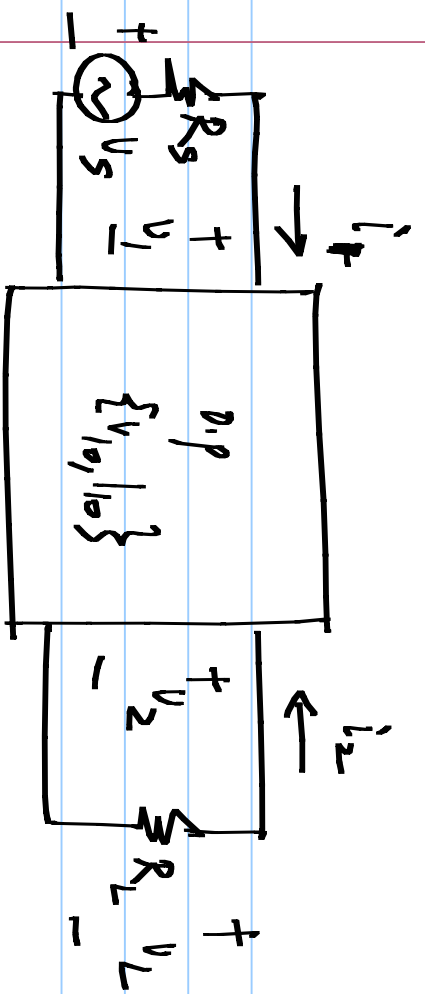

$$\frac{V_L}{V_s} = ?$$

$$i_1 = y_{11} V_1 + y_{12} V_2$$

$$V_L = V_2$$

$$i_2 = y_{21} V_1 + y_{22} V_2$$

$$y_{21} V_1 = - \left( y_{22} + \frac{1}{R_L} \right) V_2$$

$$V_1 = V_s - i_1 R_s$$

$$\left( y_{11} + \frac{1}{R_s} \right) \left( - \left( y_{22} + \frac{1}{R_L} \right) V_2 \right) = \frac{V_s}{R_s}$$

$$V_2 = - \frac{V_s}{y_{21} \left( y_{22} + \frac{1}{R_L} \right)}$$

$$\frac{V_2}{V_S} = \frac{y_{21} \cdot \frac{1}{R_S}}{y_{12} y_{21} - \left( y_{11} + \frac{1}{R_S} \right) \left( y_{22} + \frac{1}{R_L} \right)}$$

$$= \frac{-y_{21} \cdot \frac{1}{R_S}}{}$$

$$= \frac{-y_{21} \cdot \frac{1}{R_S}}{\left( y_{11} + \frac{1}{R_S} \right) \left( y_{22} + \frac{1}{R_L} \right) - y_{12} y_{21}}$$

$$= \frac{-y_{21} \cdot R_S}{\left( y_{11} + G_S \right) \left( y_{22} + G_L \right) - y_{12} y_{21}}$$