

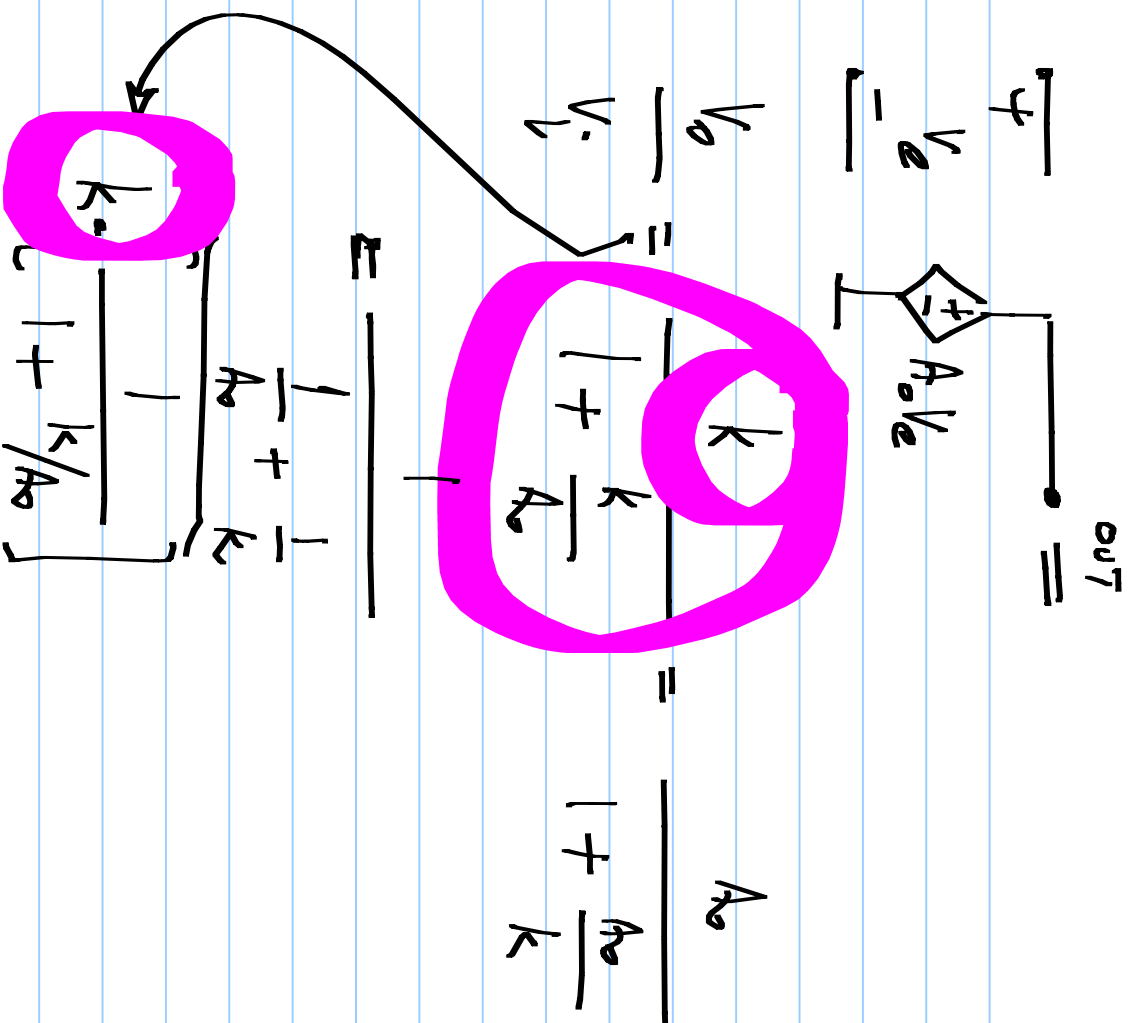


Lecture 7

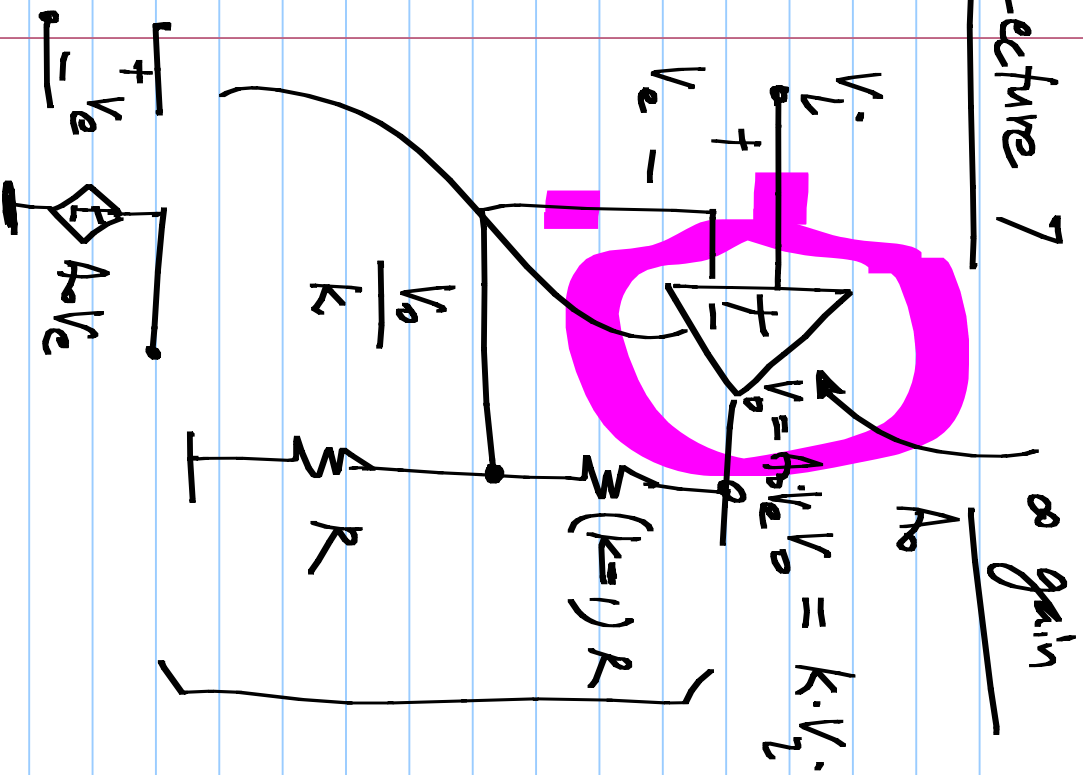

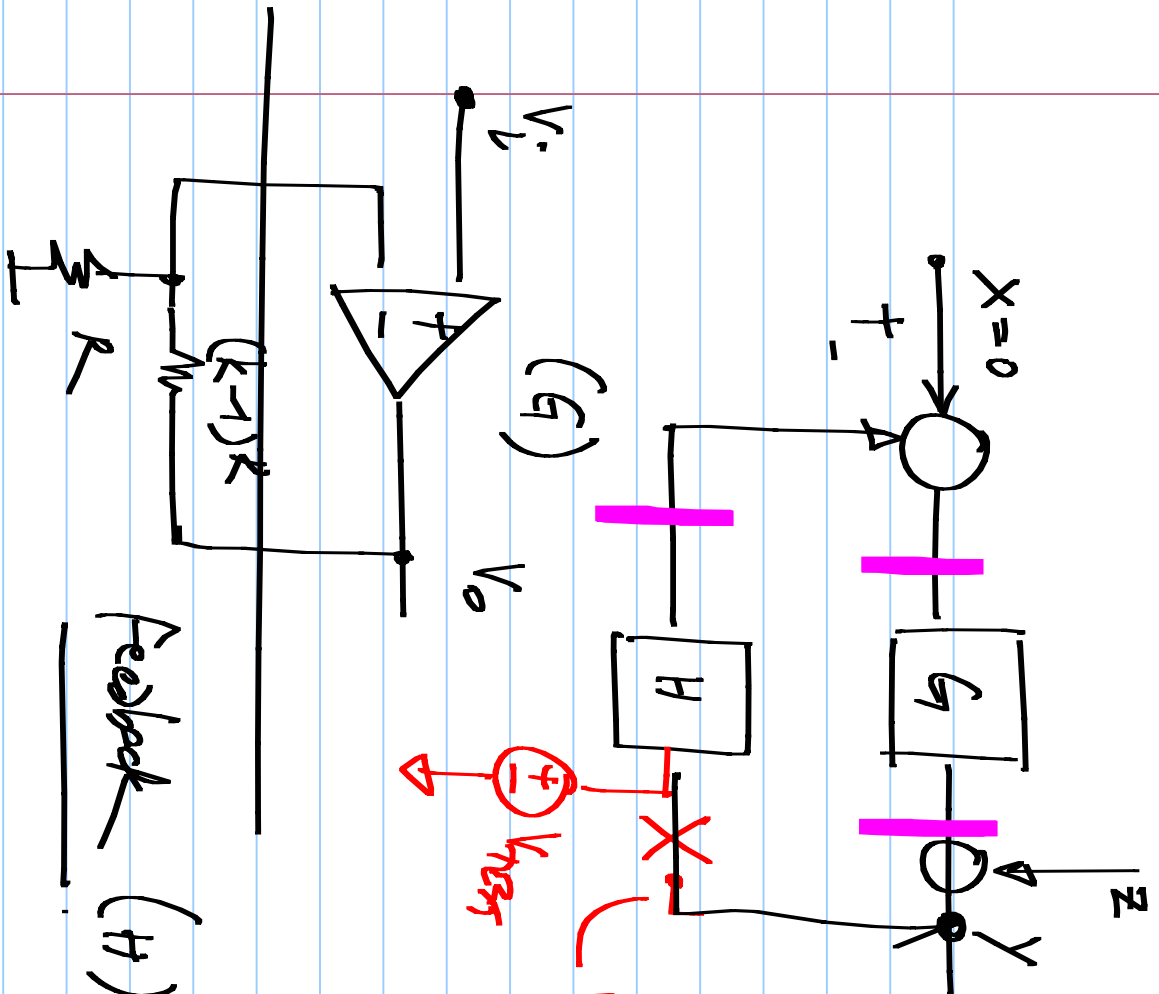


$$\frac{Y}{X} = \frac{G}{1 + GH}$$



$$= \frac{1}{\frac{1}{H} \cdot \left(1 + \frac{1}{GH}\right)}$$

$$= -GH \cdot V_{REST}$$

loop gain

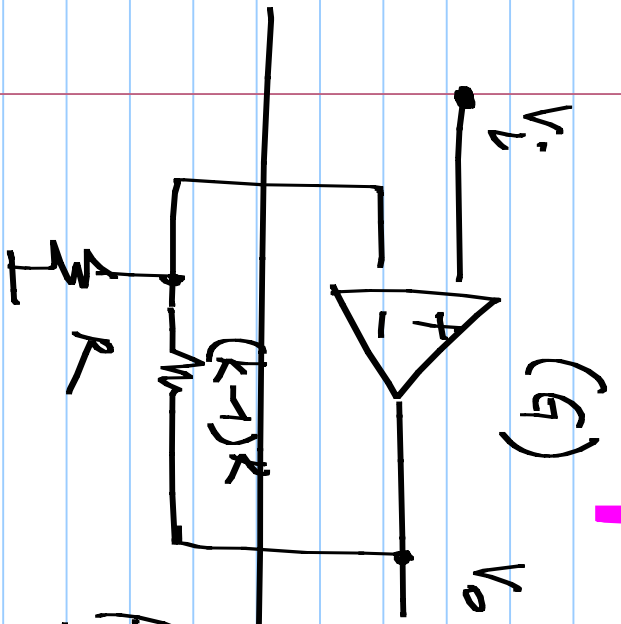
$$\text{Feedback } (H) \quad \frac{V_o}{V_i} = k \cdot \frac{1}{1 + (k/A_o)}$$




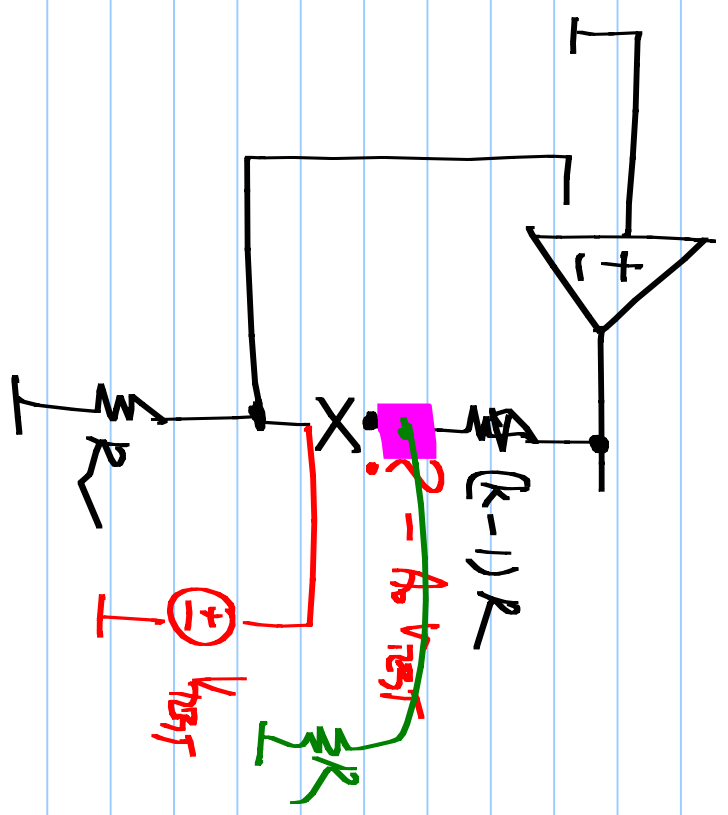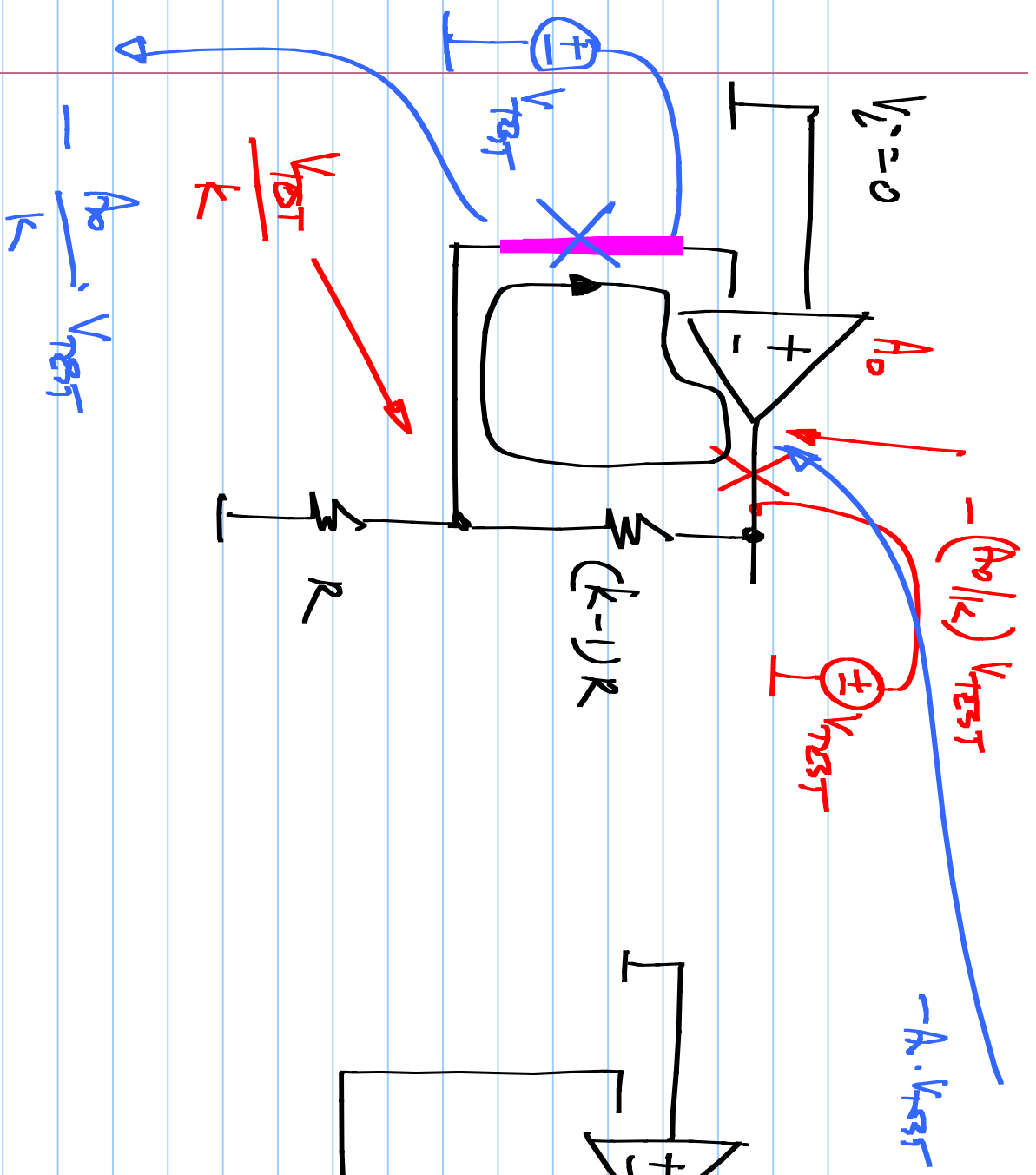

$$-\frac{A_0}{k} V_{test}$$



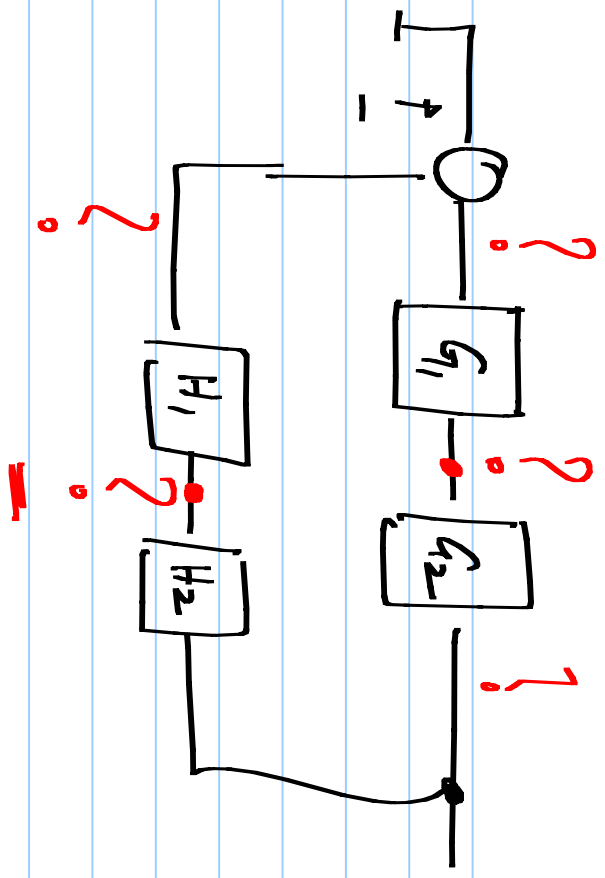

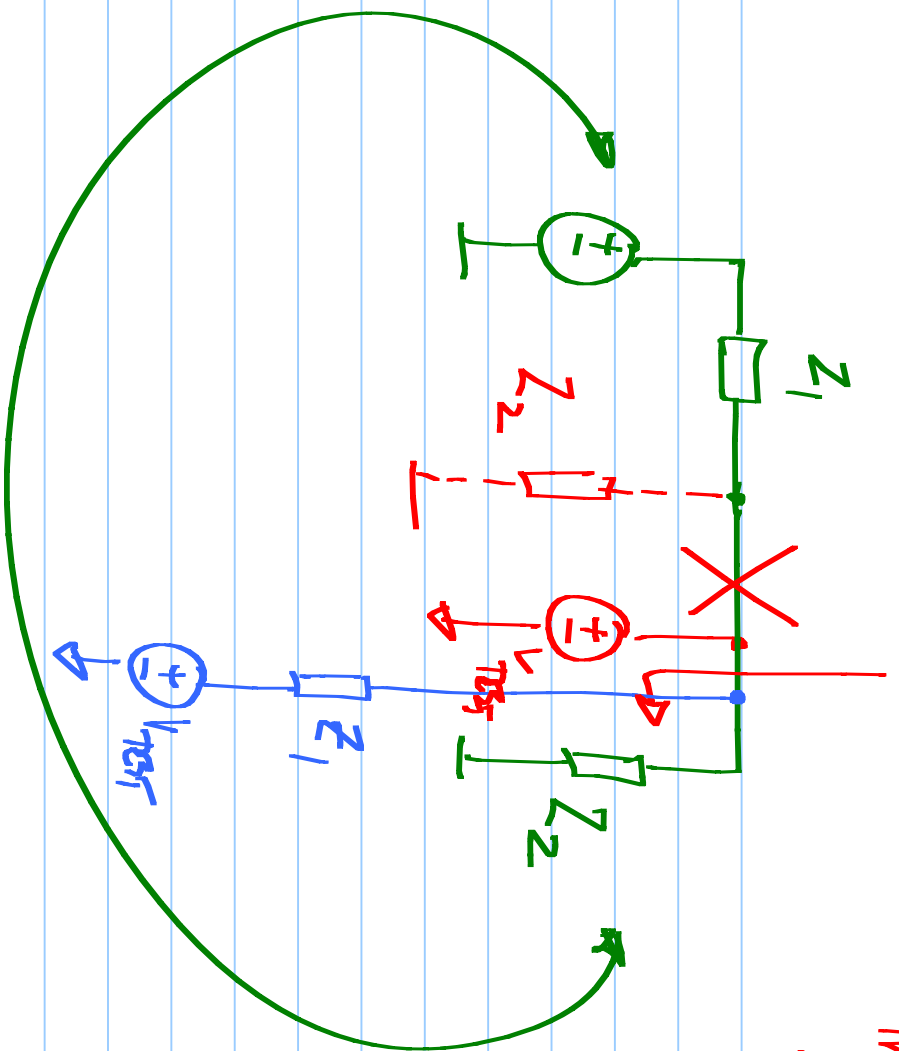


Impedance seen after
the break must be
added before the
break

$$\frac{k}{\left(1 + \frac{k}{A_0}\right)} \approx k \left(1 - \frac{k}{A_0}\right)$$



$$K = 10 \quad \frac{9.99}{10.01}$$

$$\frac{A_0 \gg 1}{k} \quad \left(\frac{0.1\%}{\quad}\right)$$

$$A_0 > 10,000$$

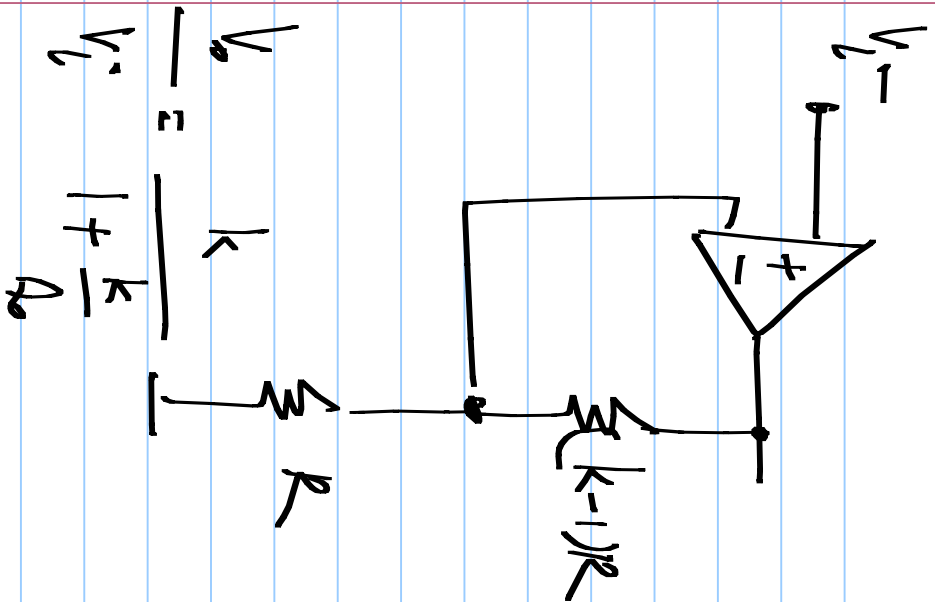
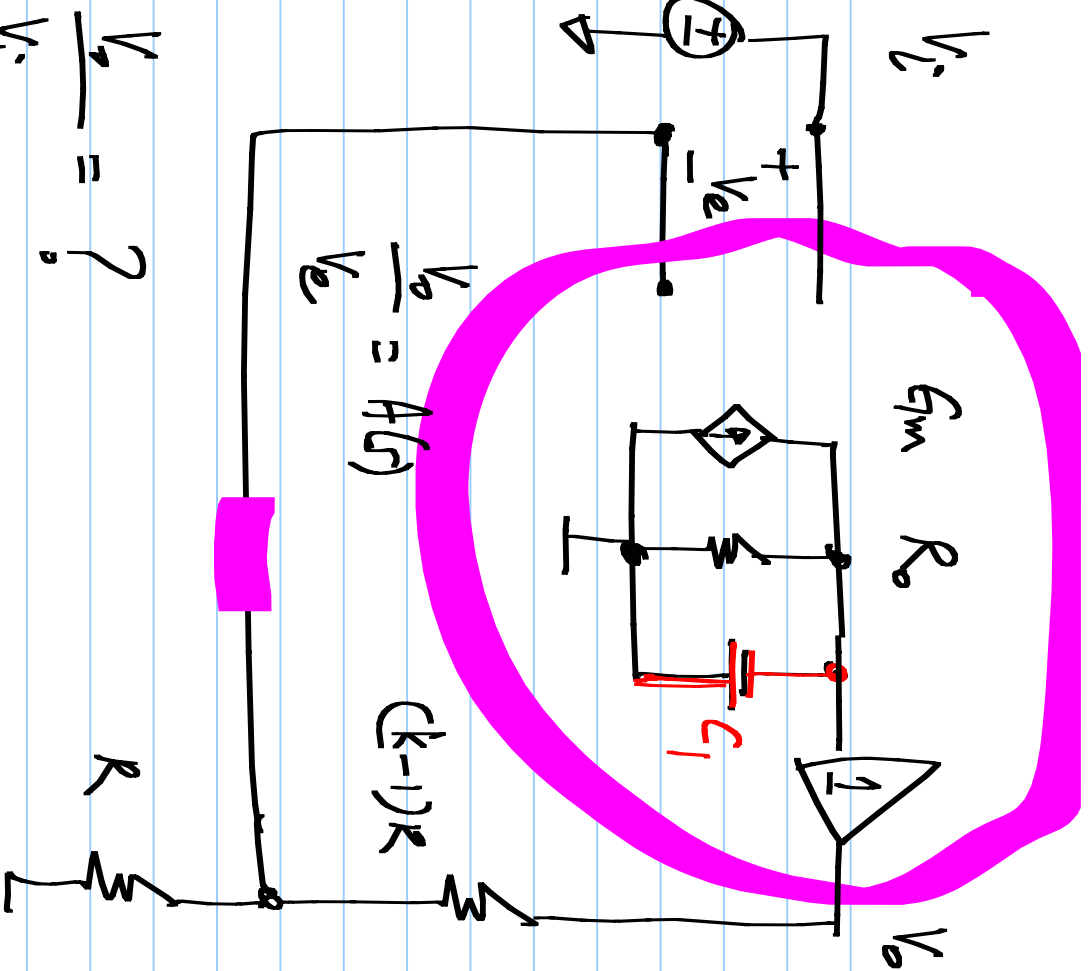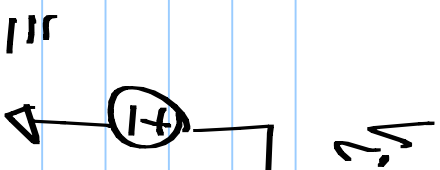
$$\frac{V_o}{V_i} = \frac{k}{1 + \frac{k}{A_o}}$$



$$\frac{V_o}{V_e} = A(G)$$

$$(k-1)R$$

$$\frac{V_o}{V_i} = ?$$

$$A(s) = \frac{G_m}{G_o + sC_1} = \frac{G_m R_o}{1 + sC_1 R_o} = \frac{A_o}{1 + s/p_1}$$

$$\frac{V_o}{V_i} = \frac{k}{1 + k/A(s)} = \frac{k}{1 + \frac{k}{A_o} (1 + s/p_1)}$$

$$= \frac{k}{1 + \frac{k}{A_o} + \frac{s}{p_1 \cdot A_o/k}}$$