

Lecture 11

* Loop gain: Predominantly 1st order behavior.

* Phase margin = $\angle L | + 180^\circ$


$\sim 60^\circ$

$\zeta = 1: 76^\circ$

$\zeta = 1/2: 45^\circ$

Dominant pole

freq. compensation slight ringing

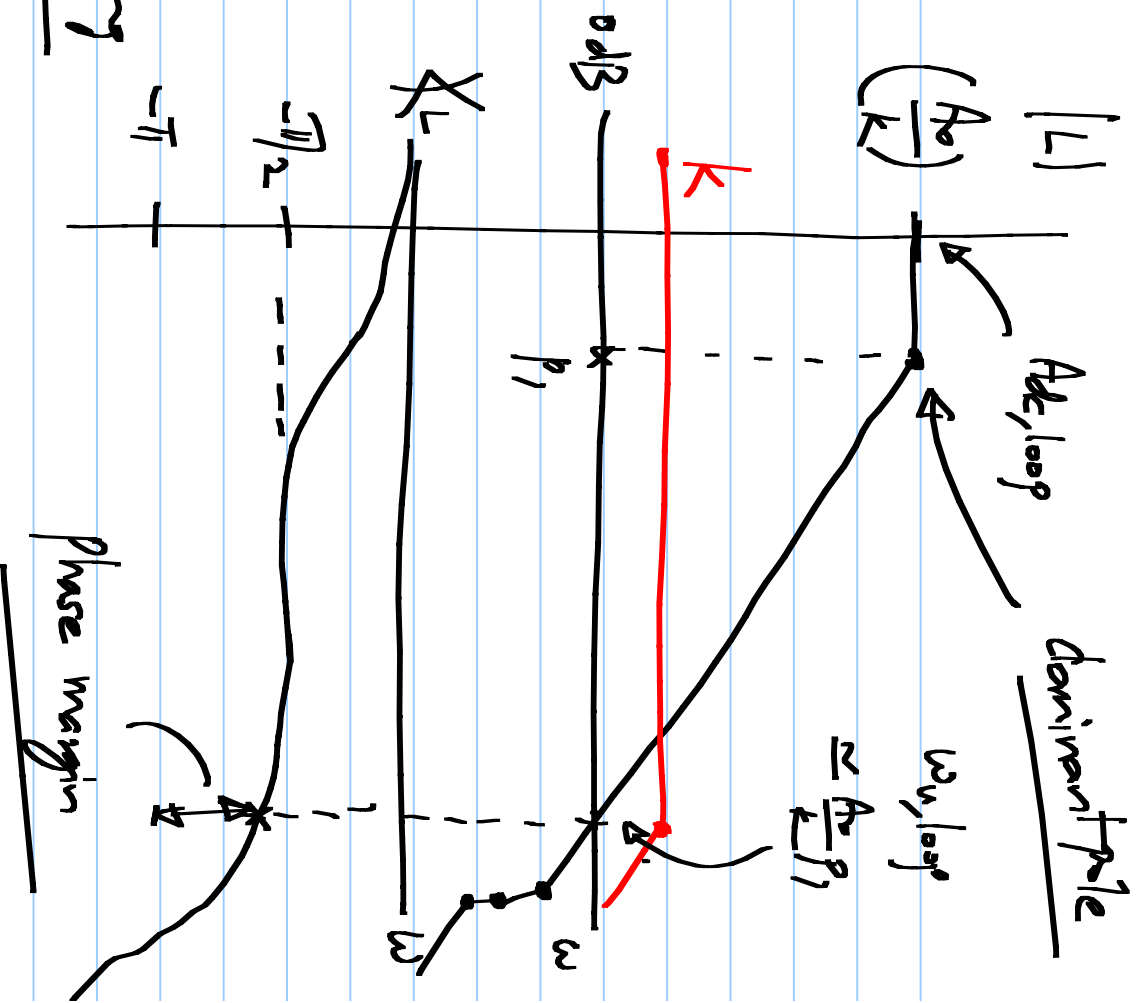



$$\tau \gg |L|$$

$$\tau \sim L$$

$$\tau \ll |L|$$

$$\frac{1}{1 + \frac{\tau}{L}}$$

$$\sim \frac{1}{\tau}$$

$$(k_0/k) \leftarrow A_{dc/loop} \left(1 + \frac{s}{z_1}\right)$$


$$z_1 > \omega_{y,loop}$$

$$\left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right) \left(1 + \frac{s}{p_3}\right)$$

$$* \omega_{y,loop} \approx \frac{k_0}{k} p_1 \quad \text{should not be more than } 30^\circ \text{ lag}$$

$$\underbrace{-\tan^{-1}\left(\frac{\omega_{y,loop}}{p_1}\right) - \tan^{-1}\left(\frac{\omega_{y,loop}}{p_2}\right) - \tan^{-1}\left(\frac{\omega_{y,loop}}{p_3}\right) + 180^\circ}_{-90^\circ} = 60^\circ$$
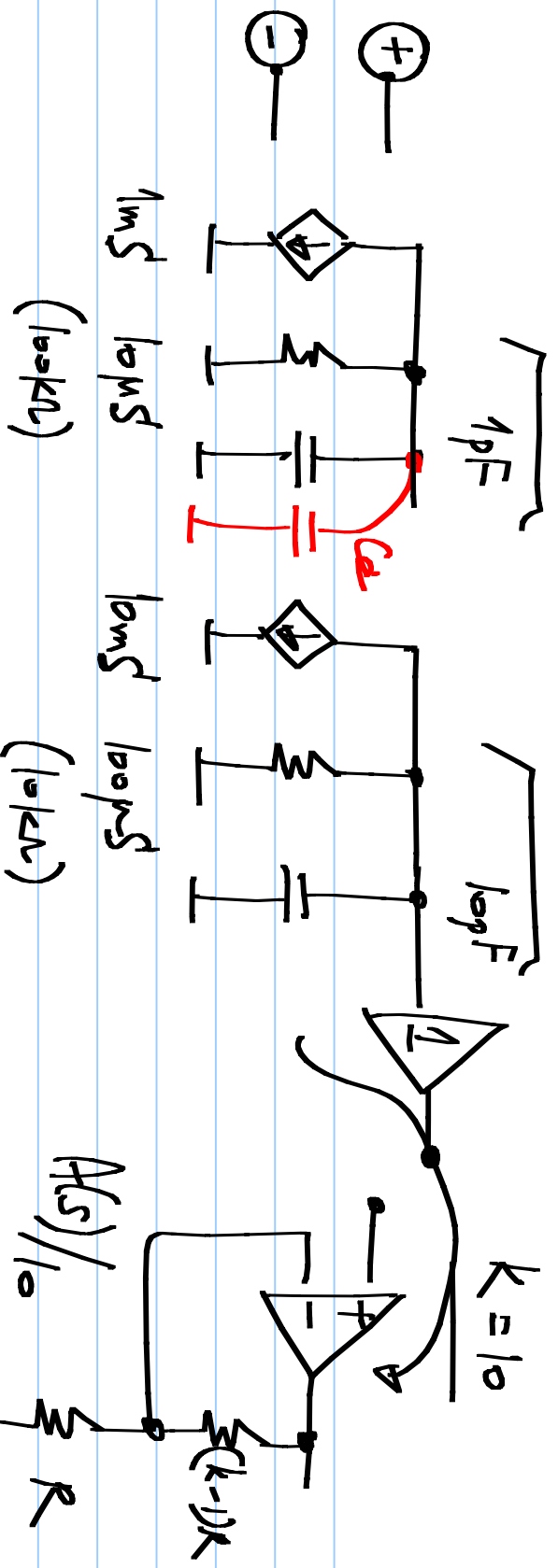
$$+ \tan^{-1}\left(\frac{\omega_{y,loop}}{z_1}\right)$$



$$A_0 = 10^4 \quad ; \quad f_{dc/loop} = 10^3$$


$$p_1 = 10^7 \text{ rad/s} \approx \frac{10^7}{2\pi} \text{ Hz}$$

$$p_2 = 10^7 \text{ rad/s}$$



$$\zeta = \frac{1}{2} \sqrt{\frac{k}{A_0}} \left(\sqrt{\frac{p_1}{p_2}} + \sqrt{\frac{p_2}{p_1}} \right)$$

$$\zeta = \frac{1}{\sqrt{10^3}} \quad ; \quad Q = \frac{\sqrt{10^3}}{2}$$


$$\zeta = 1$$

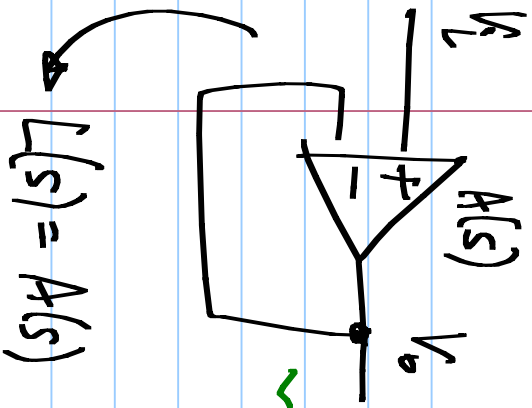


$L(s) = A(s)$

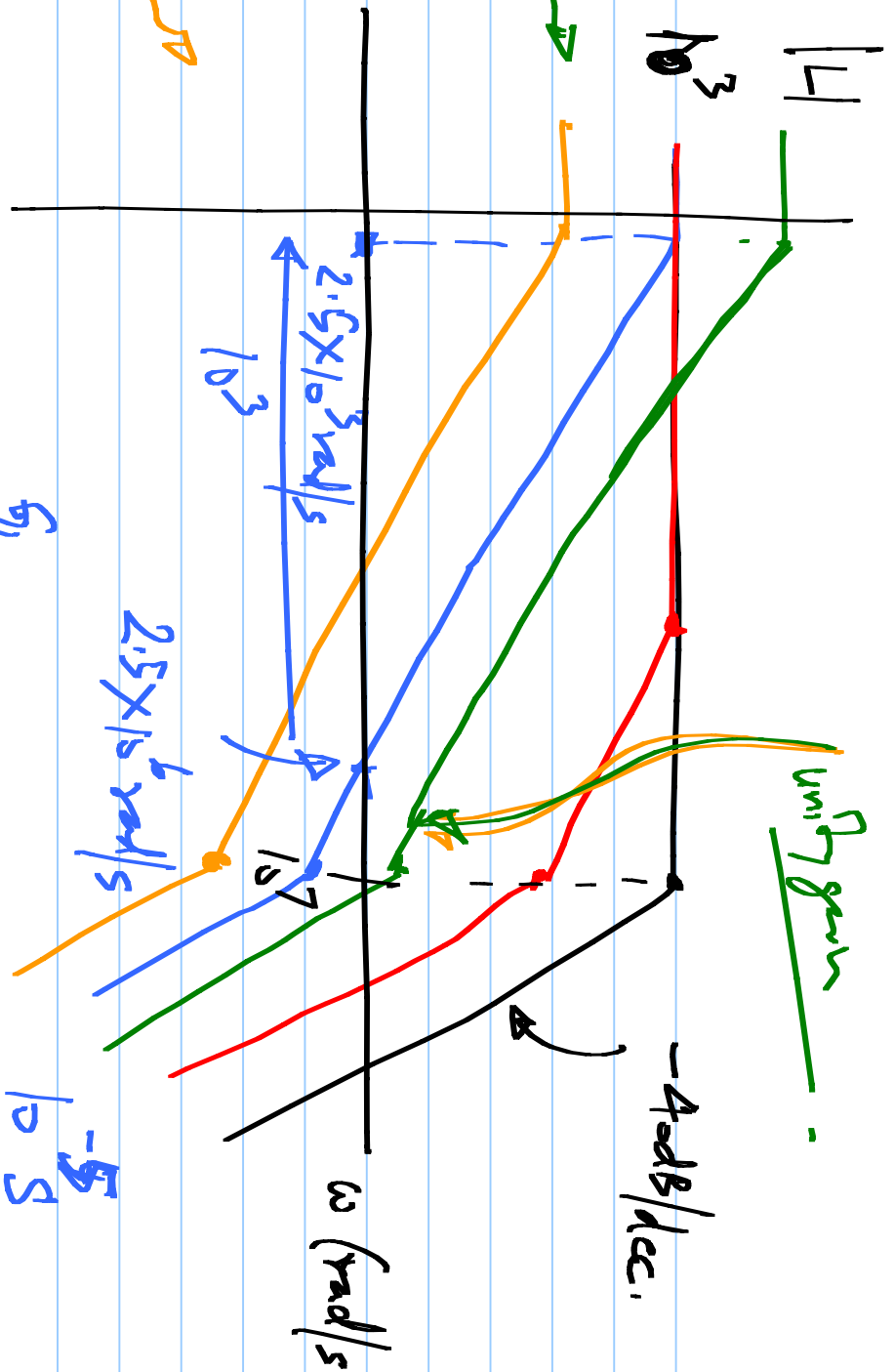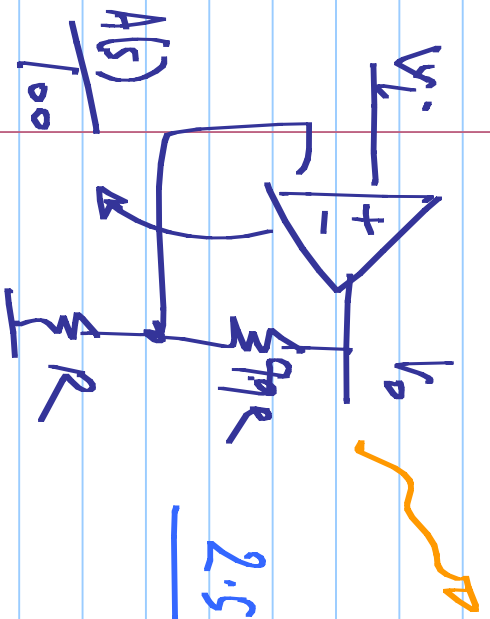


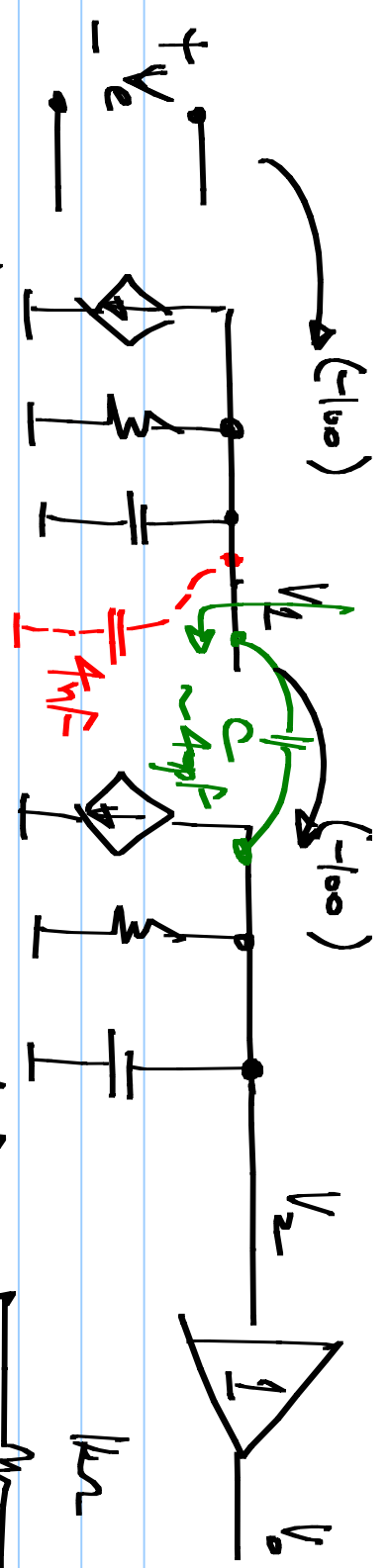
$$2.5 \times 10^3 \text{ rad/s} = \frac{\omega_{c1}}{C_{in} R} = \frac{1}{4 \times 10^{-9} \text{ F}} = 4 \times 10^8 \text{ rad/s}$$



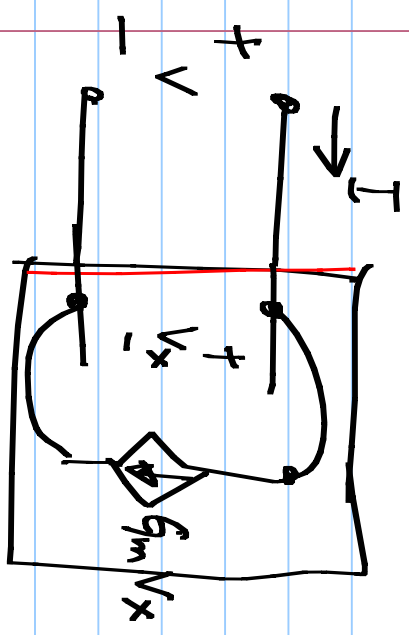$10mS$ $10pF$ $10pF$ $10mS$ $10pF$ $10mS$ $10pF$ $10mS$ $10pF$ $10mS$ $10pF$ $10mS$ $10pF$




$$V = R \cdot I$$

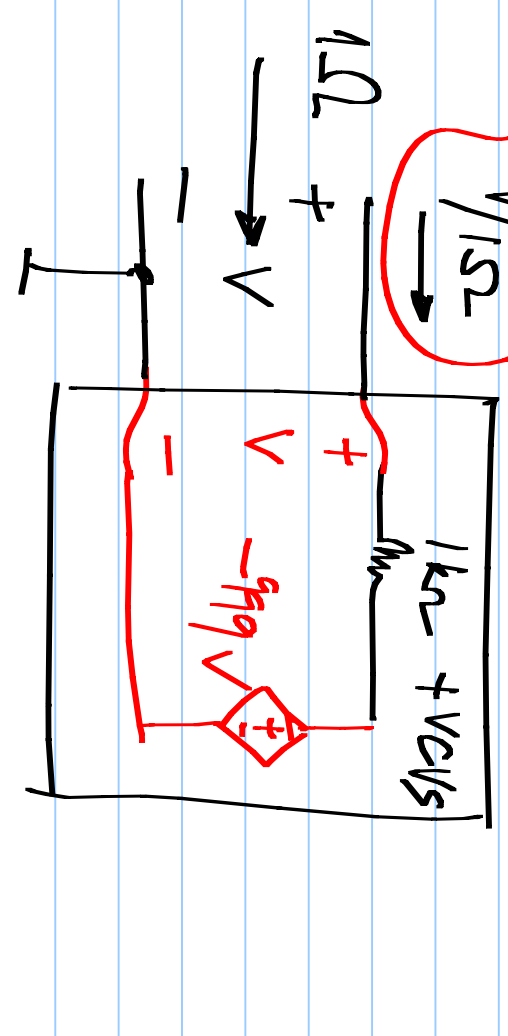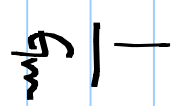

$$V/15\Omega$$

$V/15\Omega$ $+ 1000V$

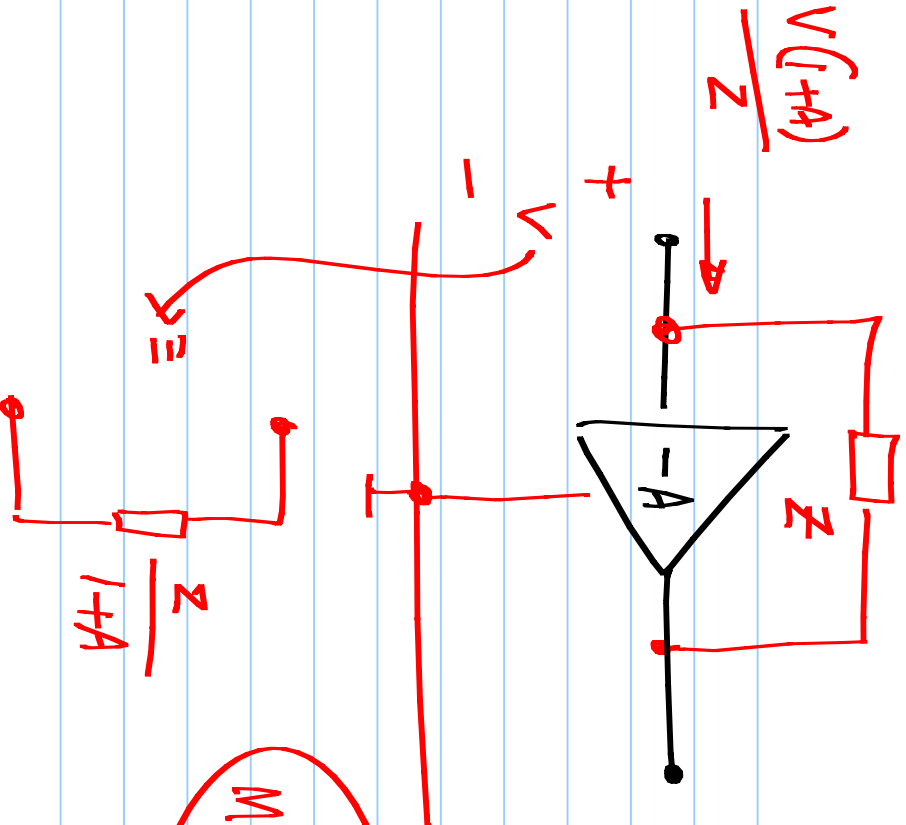

Miller effect