

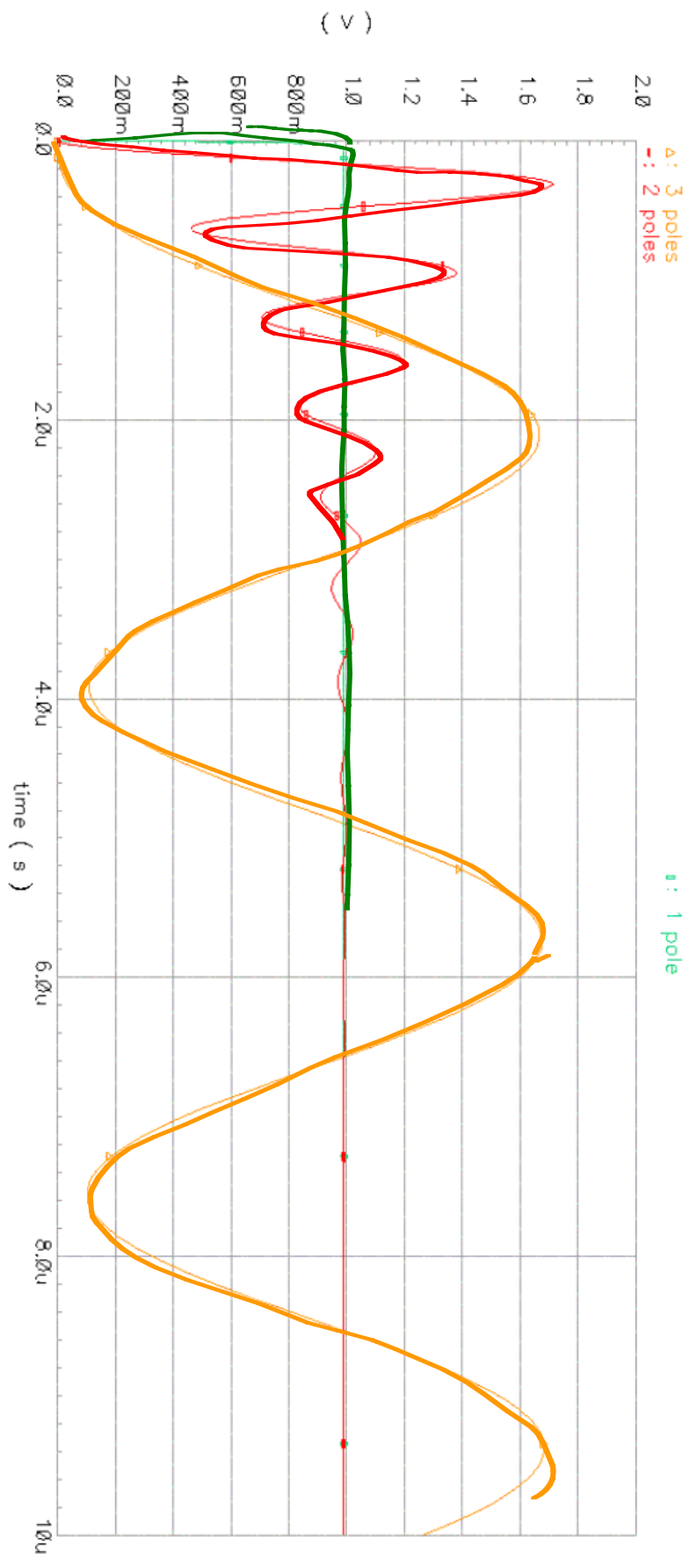


Lecture 12

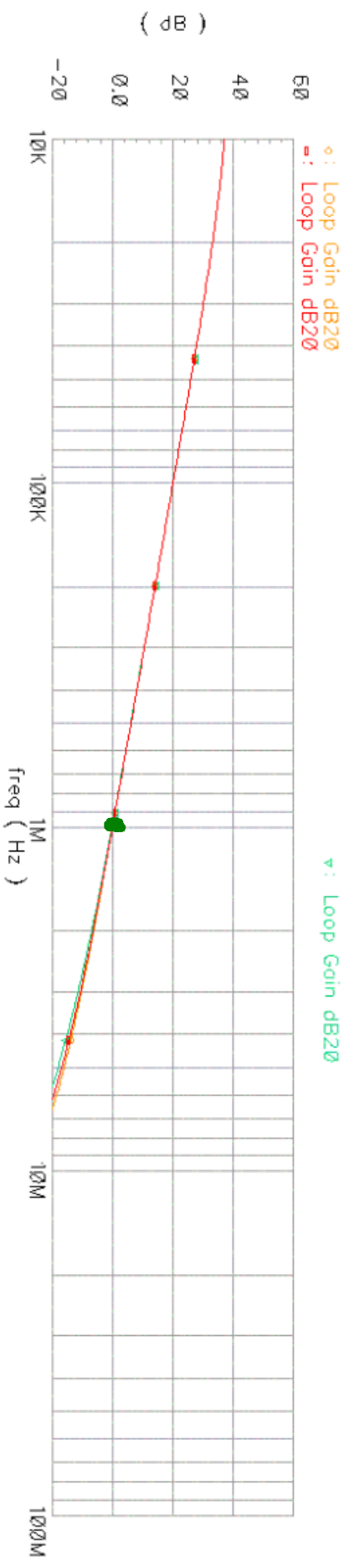
DC loop gain of 100; 1, 2, or 3 poles at 1Mrad/s
Transient Response



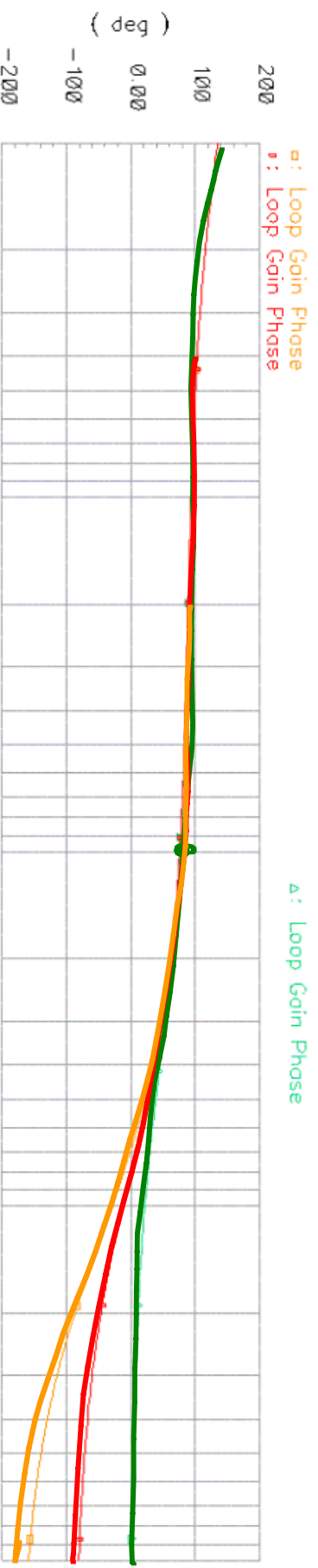
1, 2, and 3 nondominant poles: dc loop gain=100; phase margin=76.5deg.; Unity loop gain frequency=1MHz



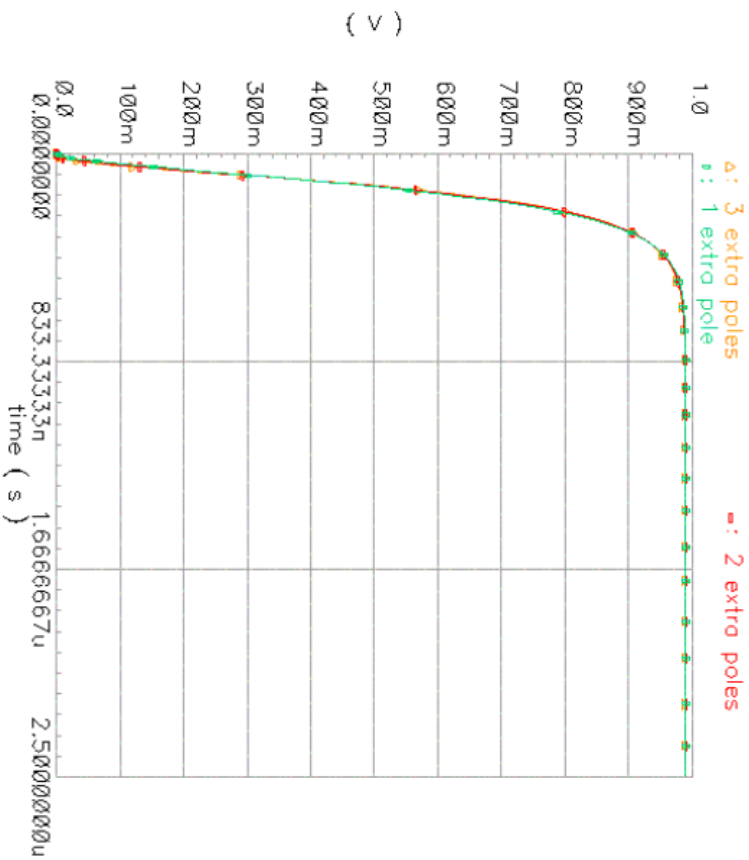1, 2, and 3 nondominant poles: dc loop gain=100, phase margin=76.5deg.: Unity loop gain frequency=1MHz
 Transient Response






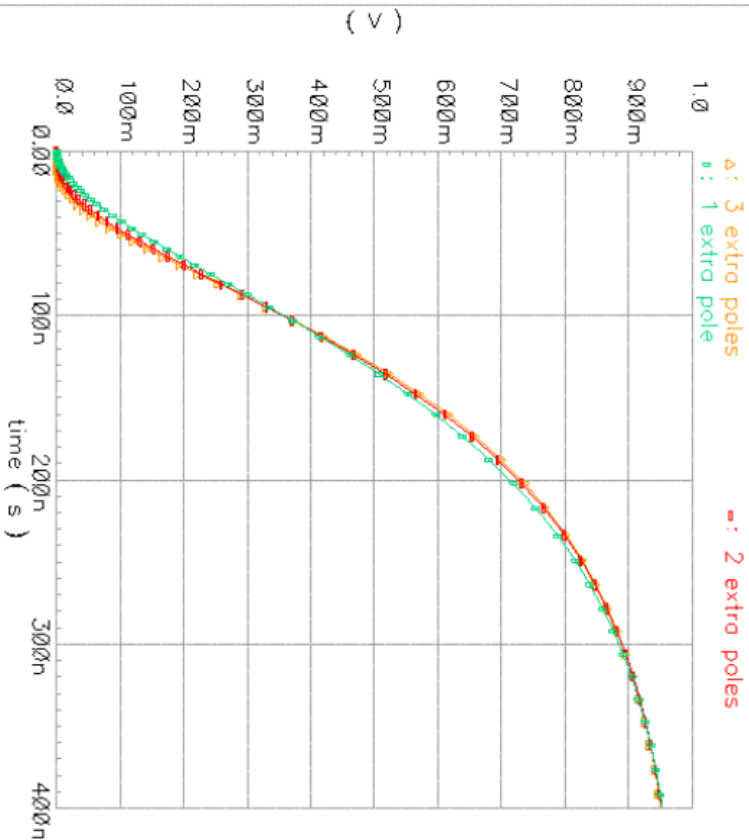
Unity loop gain frequency=1MHz
 Transient Response



1, 2, and 3 nondominant poles: dc loop gain=100; phase margin=44deg; Unity loop gain frequency=1MHz
 Stability Response


0

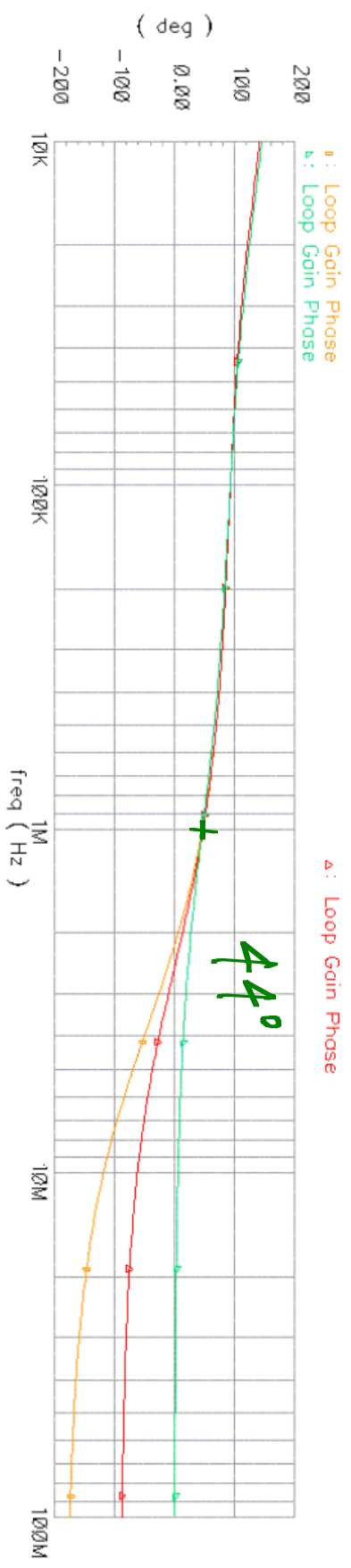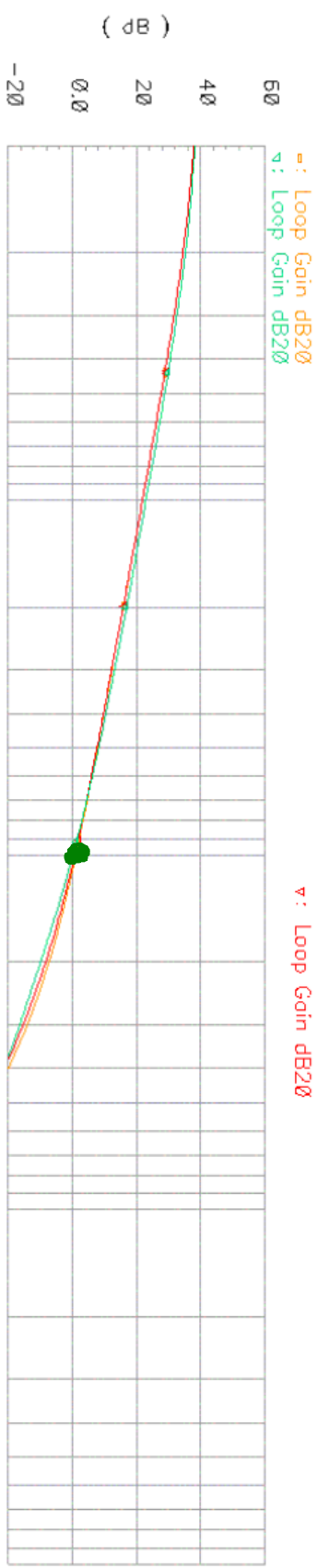

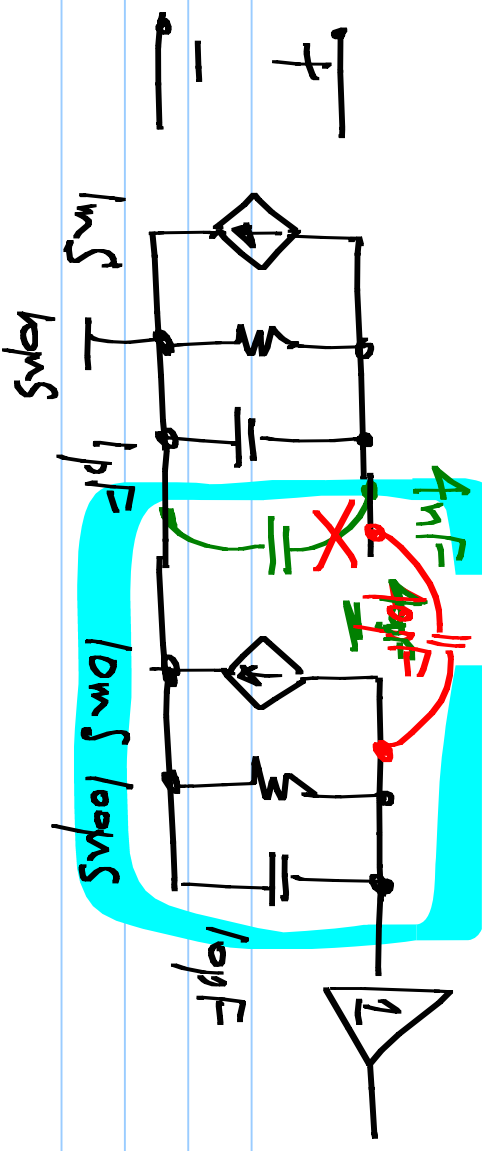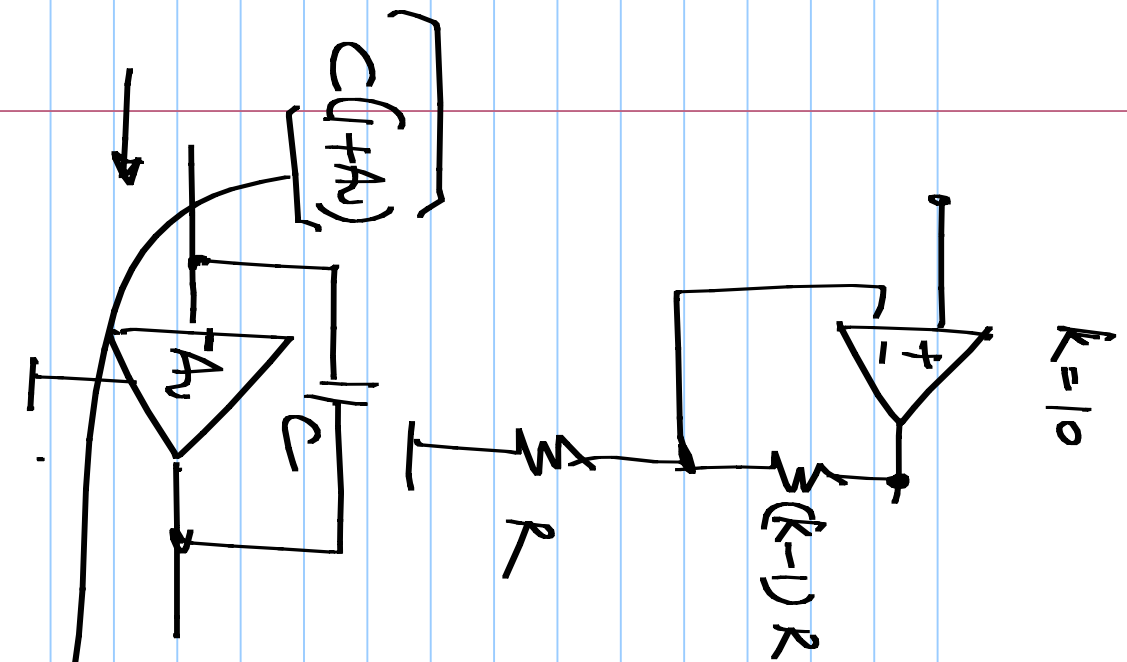

$4nF$ across stage 1:

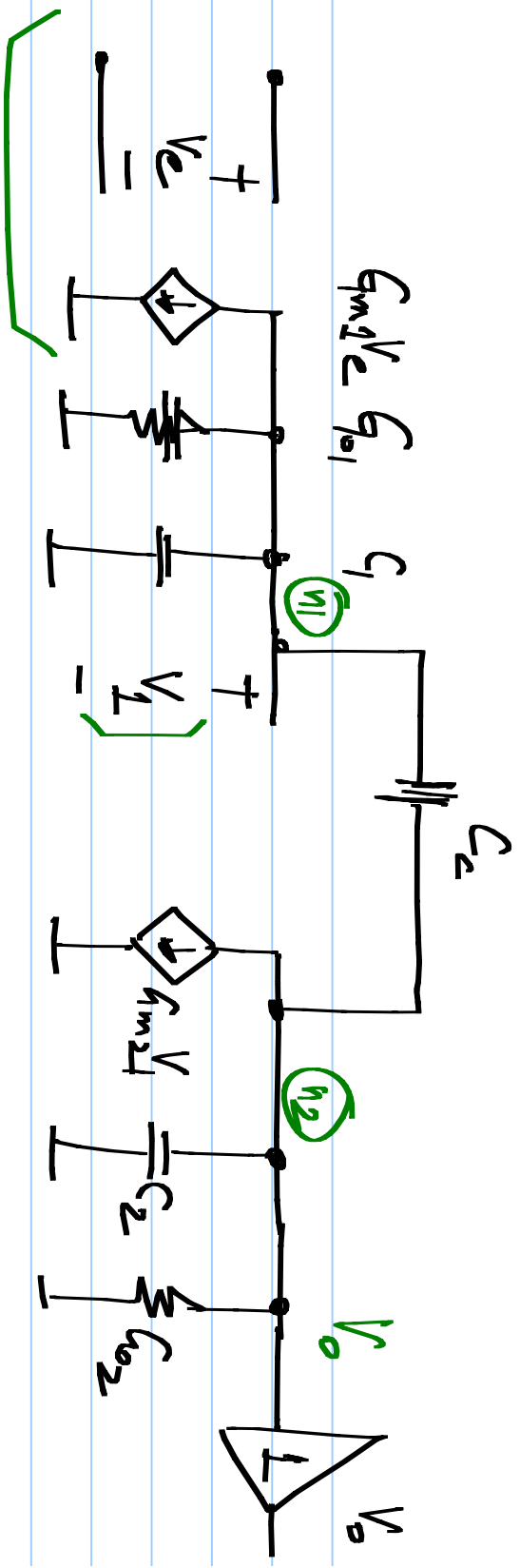$\omega_{c,loop} \rightarrow 2.5 Mrad/s$
 $p_2 : 10 Mrad/s$
 $\zeta = 1 \left(Q = \frac{1}{2} \right)$




$$\begin{bmatrix} G_{o1} + s(C_1 + C_c) & -sC_c \\ G_{m2} - sC_c & G_{o2} + s(C_2 + C_c) \end{bmatrix} \begin{bmatrix} V_1 \\ V_o \end{bmatrix} = \begin{bmatrix} -g_{m1}V_e \\ 0 \end{bmatrix}$$

$$\frac{V_o}{V_e} = \frac{\begin{vmatrix} g_{o1} + s(C_1 + C_d) & -g_{m1} V_e \\ g_{m2} - sC_c & 0 \end{vmatrix}}{\begin{vmatrix} g_{o1} + s(C_1 + C_c) & -sC_c \\ g_{m2} - sC_c & g_{o2} + s(C_2 + C_c) \end{vmatrix}}$$

$g_{m1} = 1 \text{ mS}$
 $C_1 = 1 \text{ pF}$
 $C_2 = 10 \text{ pF}$
 $C_c = 40 \text{ pF}$

$g_{m2} = 10 \text{ mS}$
 $g_{o1} = 1 \text{ pS}$
 $g_{o2} = 100 \text{ pS}$
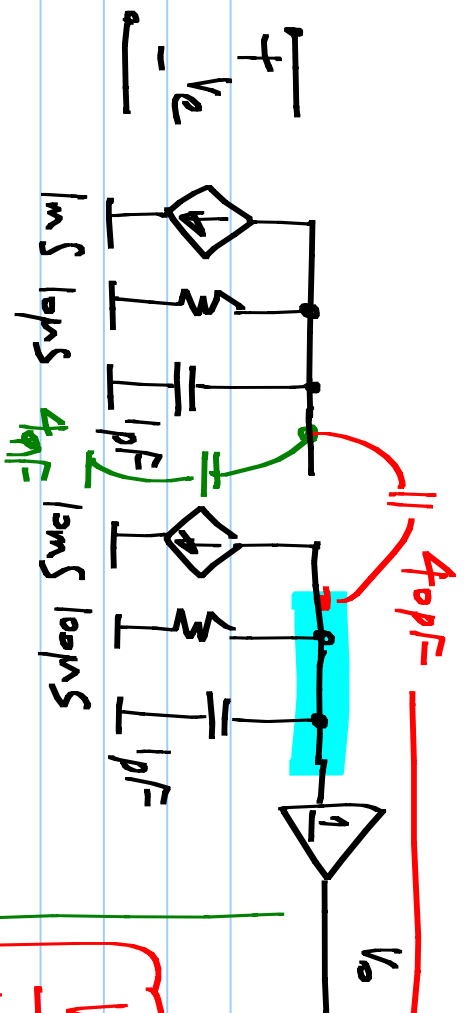
$$= \frac{g_{m1} (g_{m2} - sC_c)}{s^2 (C_1 C_2 + C_2 C_c + C_c C_1) + s (g_{m2} C_c + g_{o1} (C_2 + C_c) + g_{o2} (C_1 + C_c)) + g_{o1} g_{o2}}$$



Avf @ first stage o/p.

$$\frac{V_o}{V_e} = \frac{10^4}{\left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right)}$$

$2.5 \times 10^3 \text{ rad/s}$ 10 Mrad/s

Miller compensation

$4pF$ across the 2nd stage.

$$\frac{V_o}{V_e} = \frac{K=10}{\left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right)}$$

$2.5 \times 10^3 \text{ rad/s}$ 890 Mrad/s

2.5 Mrad/s 250 Mrad/s (RHp)

(pole splitting)

$$as^2 + bs + c = 0$$

s_1, s_2

~~$$as_1^2 + bs_1 + c = 0$$~~

$$|s_1| \ll |s_2|$$

~~$$as_2^2 + bs_2 + c = 0$$~~

$$\left[\begin{array}{l} s_1 \approx -\frac{c}{b} \\ s_2 \approx -\frac{b}{a} \end{array} \right]$$