

Lecture 14


$K=10$

Differential amplifier

Common Source

Amp.

Buffer

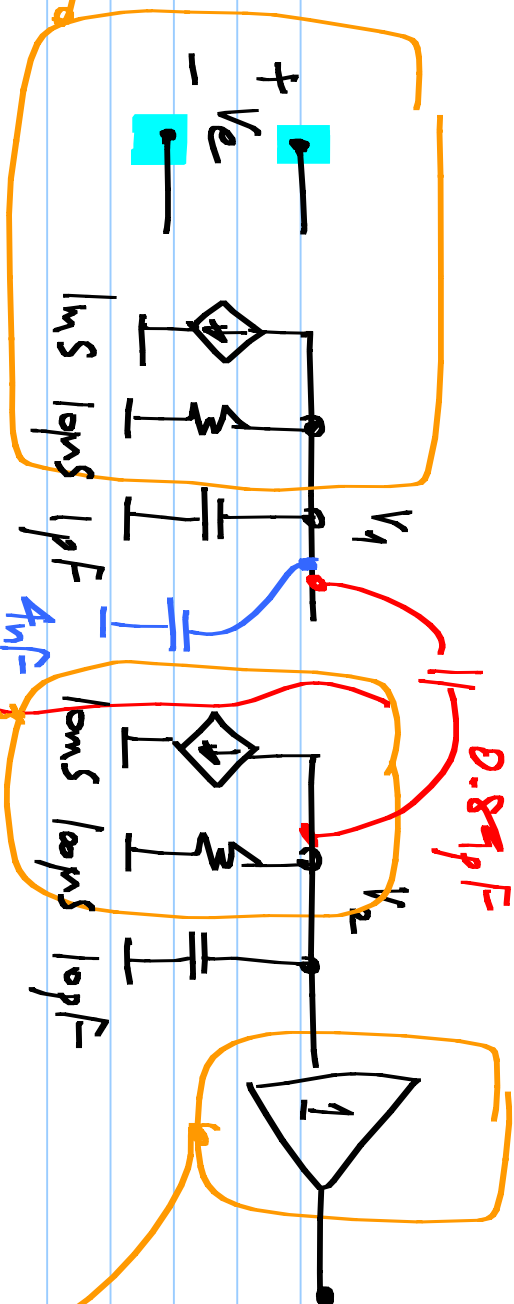


$$\left(\frac{G_{m1}}{C} \right) \cdot \frac{1}{K}$$

$$\frac{1 \text{ms}}{0.9 \text{pF}} \cdot \frac{1}{10} = \frac{10^{-3}}{10^{-12}} \cdot \frac{1}{10}$$

$$\omega_{u/loop} = 2.5 \text{Mrad/s}$$

$$110 \text{Mrad/s} \checkmark$$

Common source amplifier:

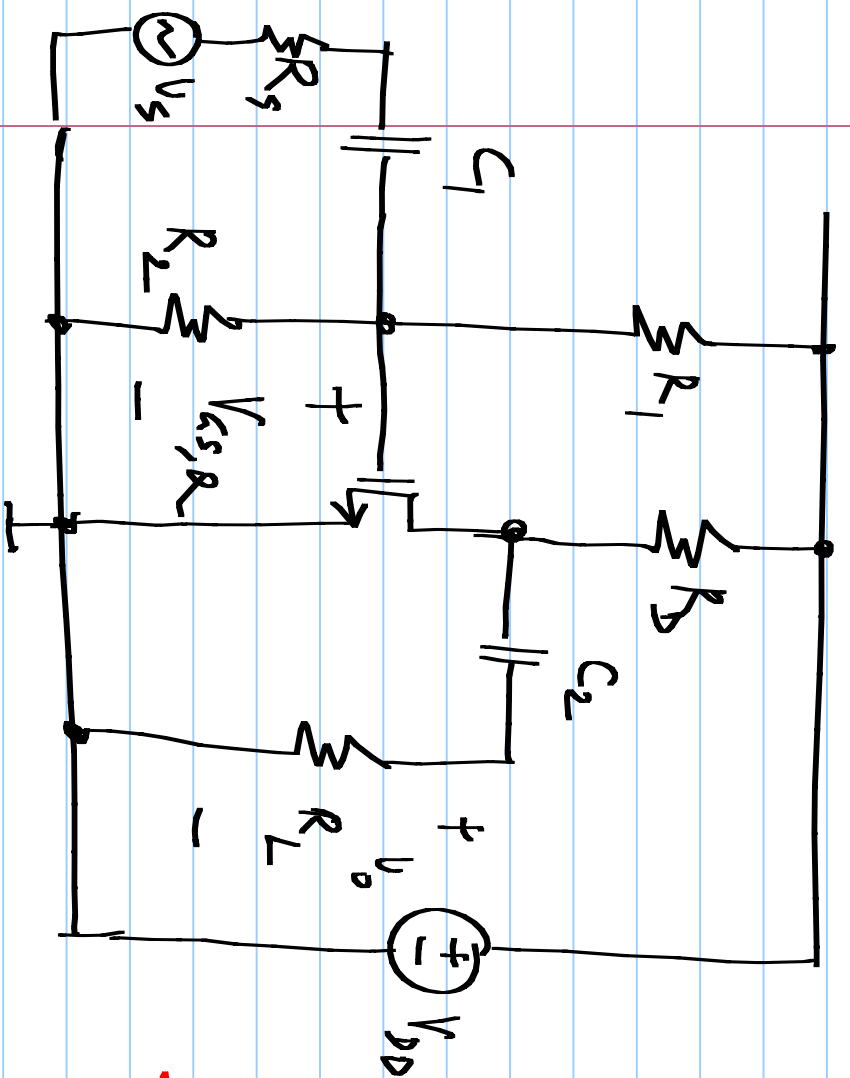

Gain:

C1,2 : large

$$\frac{v_o}{v_s} = -g_m (R_D \parallel R_L) \left[\frac{R_1 \parallel R_2}{R_s + R_1 \parallel R_2} \right]$$

$$g_m = \mu_n C_{ox} \frac{W}{L} \cdot (V_{gs,R} - V_T) \cdot K_n$$

$V_{gs,R} = 1.5V$

Vary with process

temp.


$$g_m = \underbrace{\mu}_{\Delta K_n, \Delta V_T} \cdot \underbrace{\left(V_{GS} - V_T \right)}_{\text{Biasing @ constant } V_{GS}}$$

$$= \sqrt{2 \cdot K_n \cdot I_D}$$

Less sensitive to ΔK_n


insensitive to ΔV_T

Biasing @ constant I_D


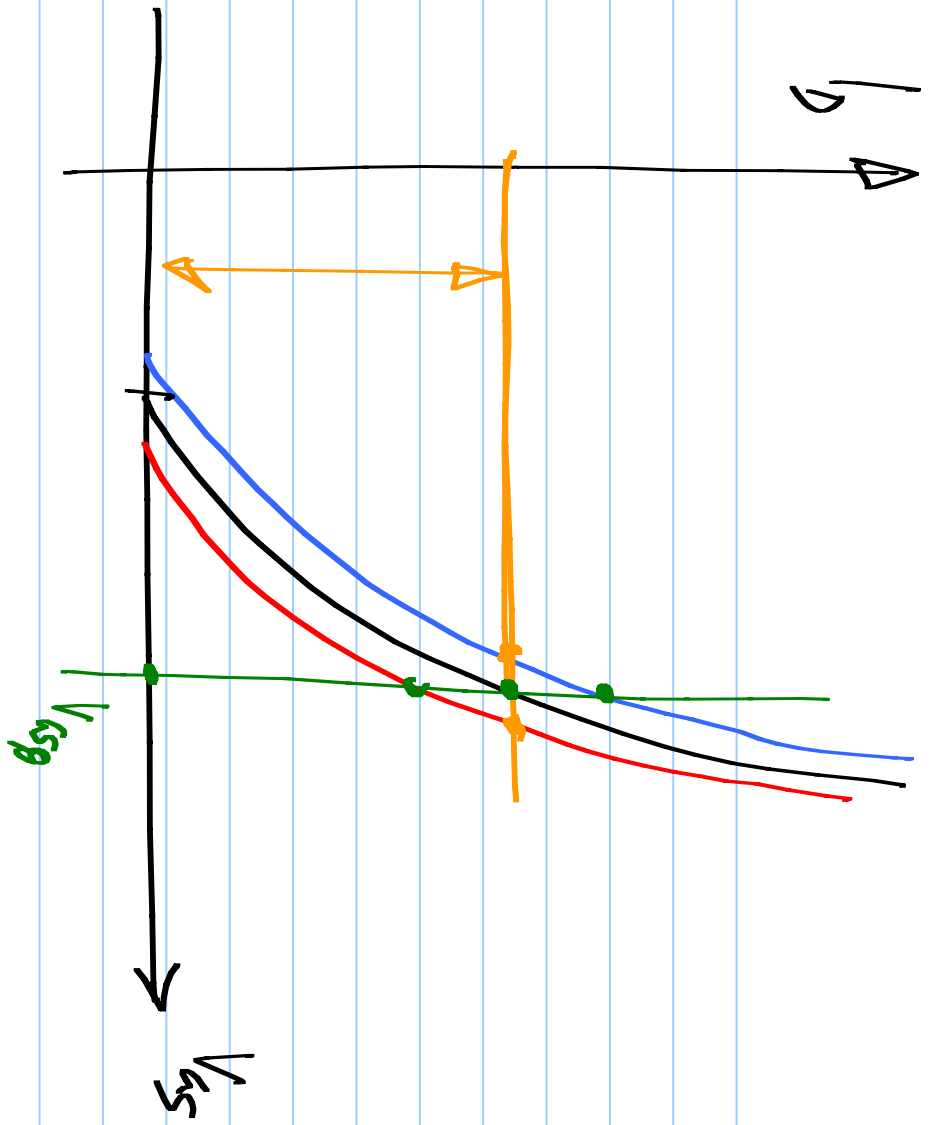


Biasing a transistor @ constant I_D
 (as r opposed f_i constant V_{GS})

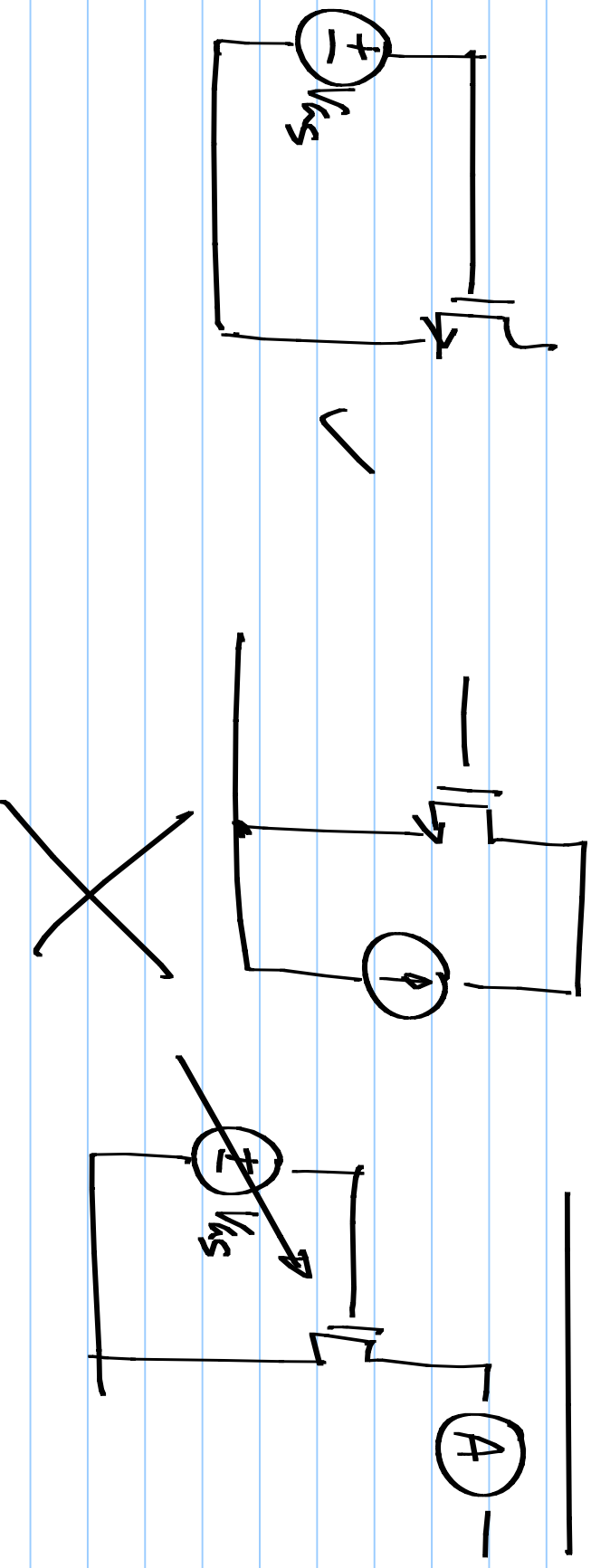Insensitive to V_T changes
 Less sensitive to k_n changes



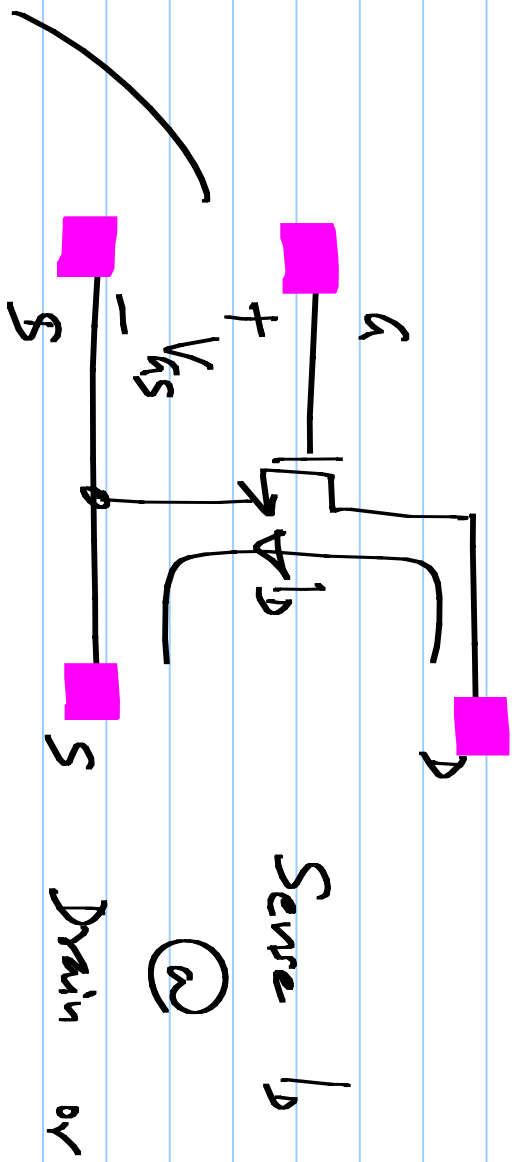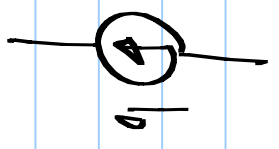
Biasing @ constant $I_D \equiv I_{D0}$ Adjust V_{GS} until the desired I_D flows



Vary V_G or V_S

4 topologies

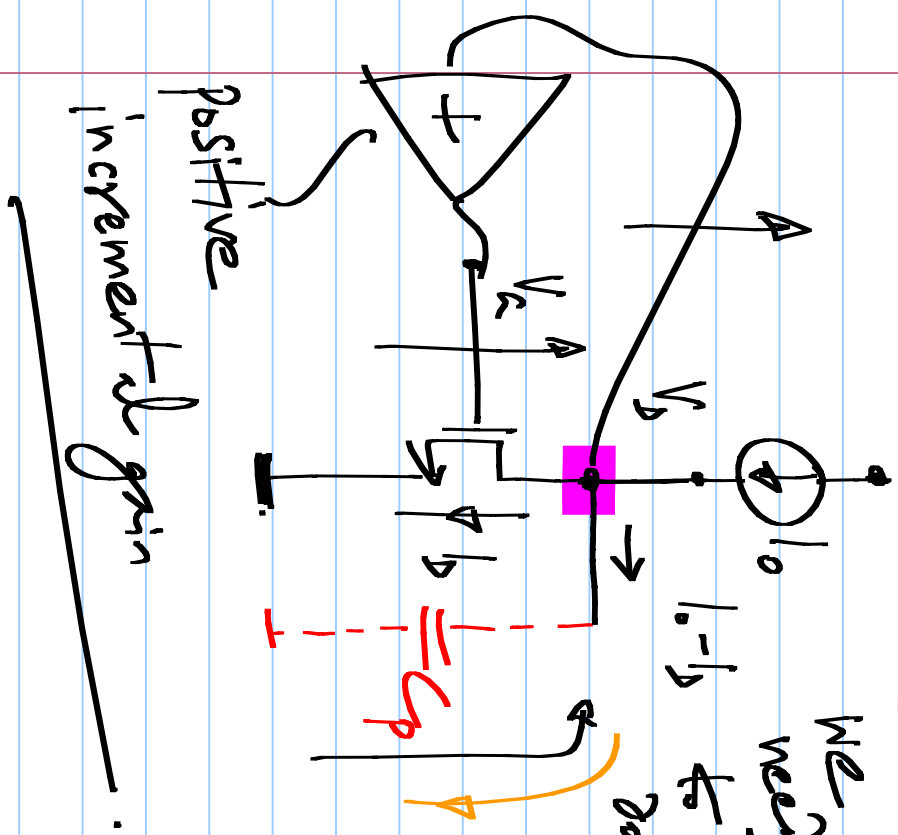
Sensing I_D @ drain; control the gate voltage.



We need $I_D > I_o$: must reduce V_G
 $I_D < I_o$: must increase V_G

$I_D > I_o$: V_D decreases
 $I_D < I_o$: V_D increases

positive increment of gain

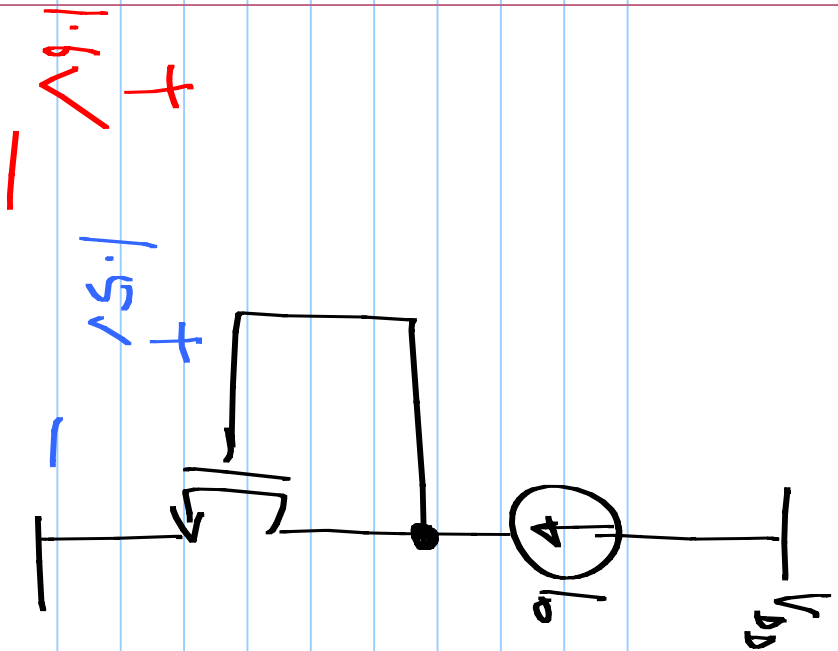

Simplest realization

$$V_{DS} \geq V_{GS} - V_T$$

$$\underline{\underline{(V_T > 0)}}$$

$V_T > 0 \Rightarrow$ transistor is in
saturation