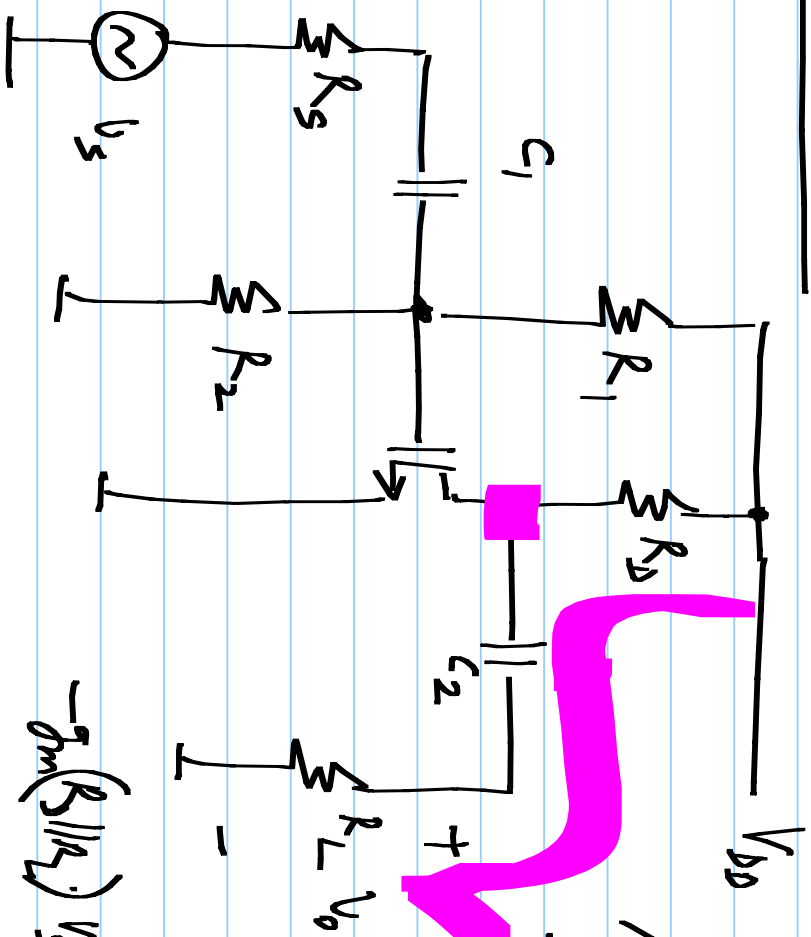


Lecture 17




Input swing limits: $V_{s,max}$

$$V_{s,min} < V_s < \frac{V_{DD} \cdot \frac{R_1}{R_1 + R_2} - (R_D + V_T)}{1 + g_m(R_D || R_L)}$$

Output swing limits:

$$-g_m(R_S || R_L) V_{s,max} < V_o < -g_m(R_D || R_L) V_{s,min}$$

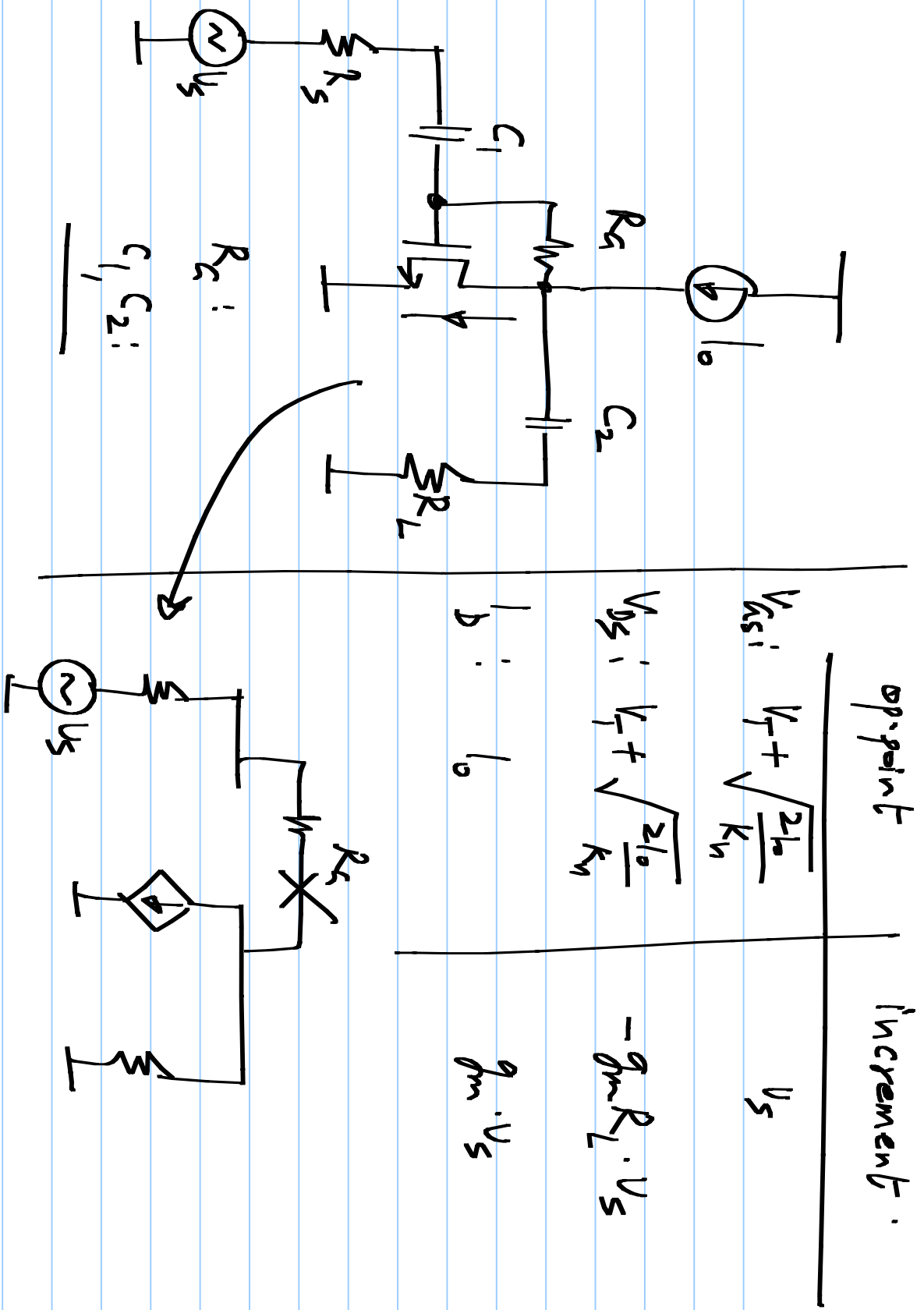


$$V_{DS, \text{sat}} \geq V_{GS, \text{sat}} - V_T$$

$$V_T + \sqrt{\frac{2I_D}{k_n}} - g_m R_L V_S \geq V_T + \sqrt{\frac{2I_D}{k_n}} + V_S - V_T$$

$$V_S \leq \frac{V_T}{1 + g_m R_L}$$

$$\left| \frac{V_{DD} \cdot \frac{R_1}{R_1 + R_2} - I_{D0} R_D}{1 + g_m (R_1 \parallel R_2)} - V_T \right|$$
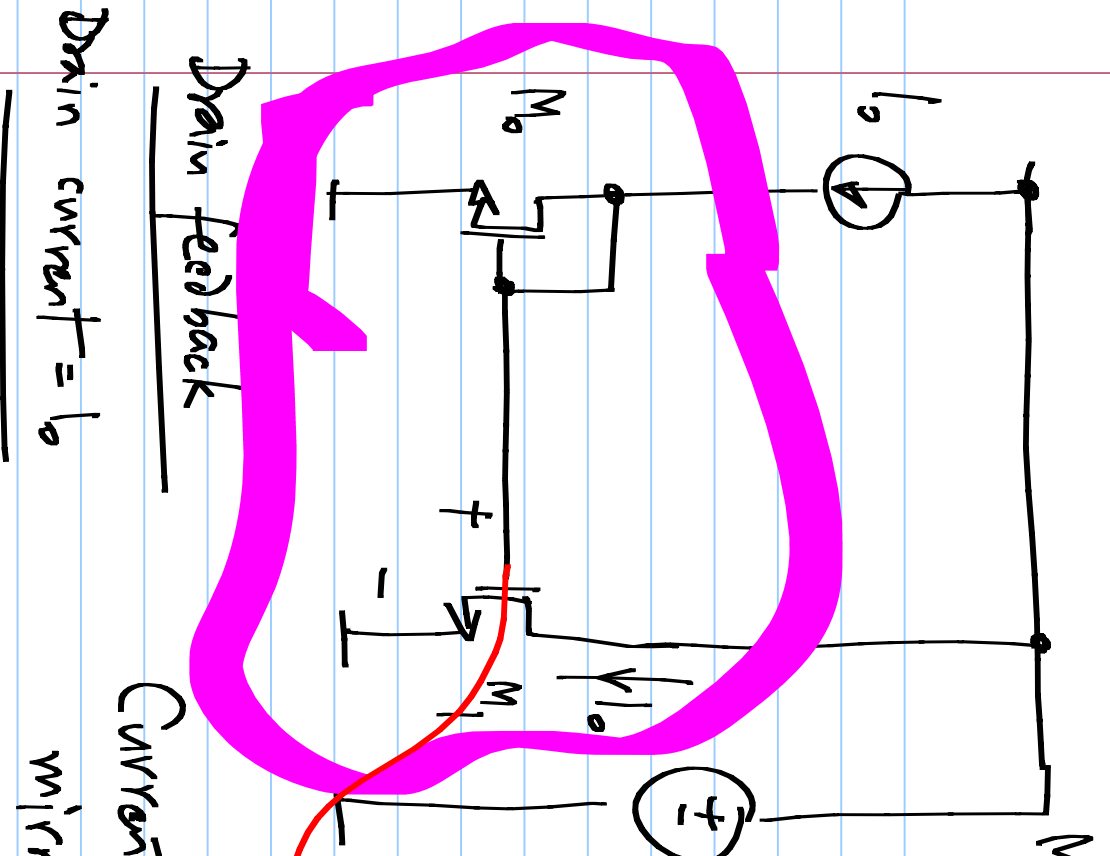
$$I_D + g_m V_S \geq 0 \quad V_S \geq -\frac{I_D}{g_m}$$



Drain feedback

Drain current = I_0


Current mirror

Matched transistors on an IC:

Identical parameters (K_n, V_T)

Same V_{GS} & in saturation

\Rightarrow same I_D .

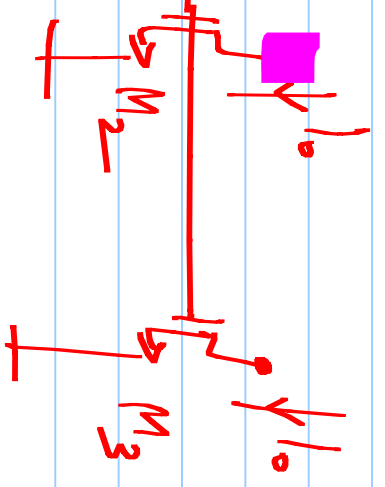

Calculate:

* Incremental voltage @ gate of M_1

(without neglecting R_n or M_o)

Assume C_1 is open-

* Calculate constraints of C_1 & C_2

for a given ω
