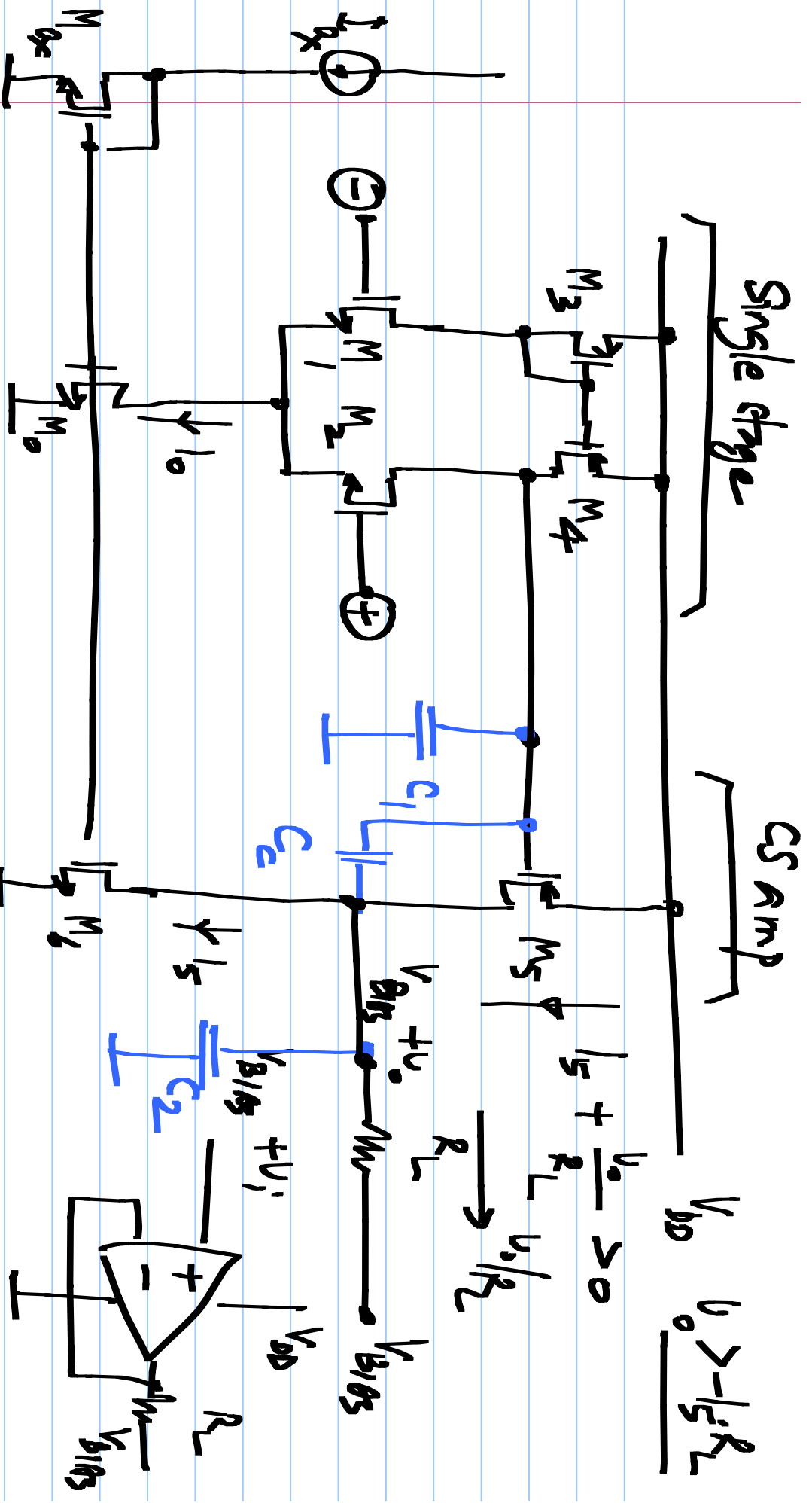



Two-stage opamp:

+ higher gain

+ higher swing, o/p isolated from the input




Miller compensated two-stage opamp

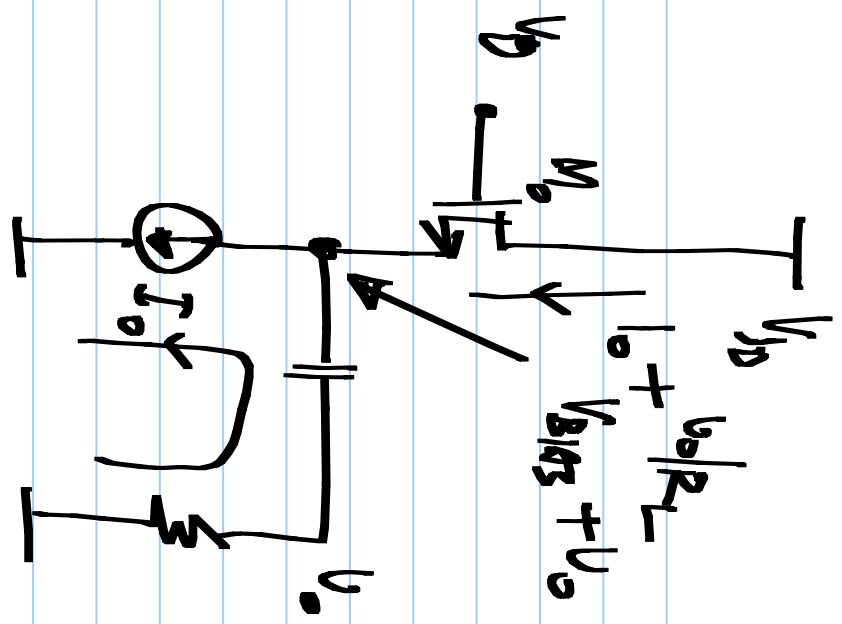

$$I_0 + \frac{V_0}{R_L} > 0$$

$$V_0 > -I_0 R_L$$

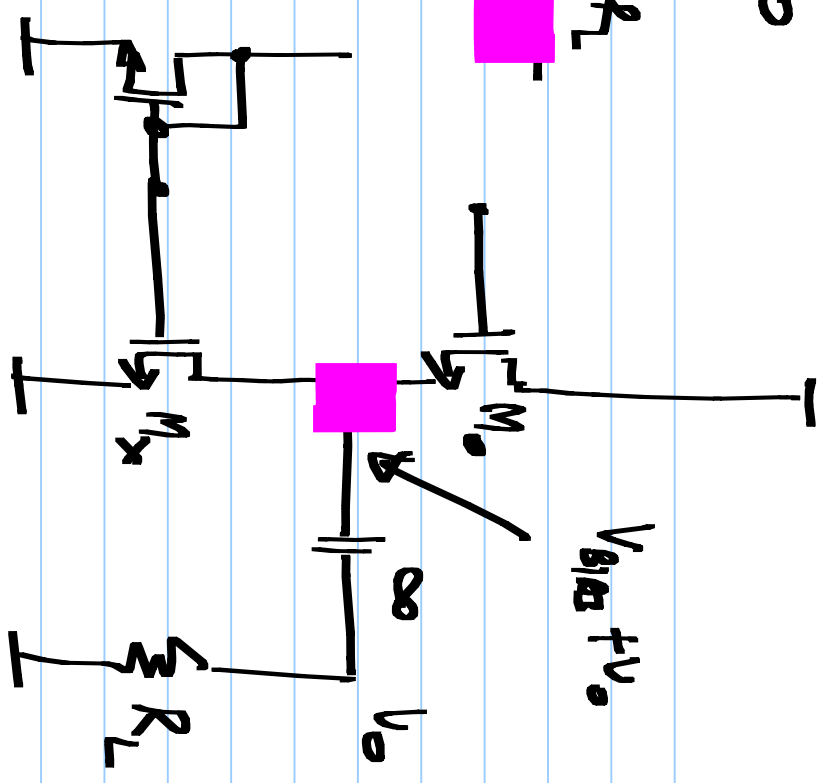


$$V_{BIA3} + V_0 > V_{DSATX}$$

$$A_0 = \frac{g_{m1}}{g_{d1} + g_{d5}} \cdot \frac{g_{m5}}{g_{d5} + g_{d6}}$$

W_{opt} ≈ $\frac{g_{m1}}{C_c}$

$$f_1 \approx \frac{g_{d1} + g_{d3}}{C_1 + \left(1 + \frac{g_{m5}}{g_{d5} + g_{d6}}\right) \cdot C_c} + \dots \quad \left| \quad Z_1 = \frac{g_{m5}}{C_c} \right.$$

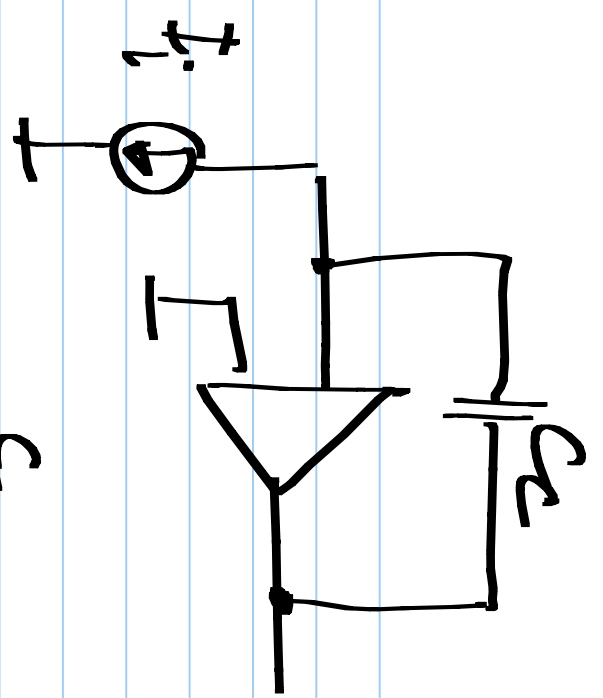
$$f_2 \approx \frac{g_{m5} \cdot \frac{C_c}{C_c + C_1} + g_{d5} + g_{d6} + g_L}{C_2 + \frac{C_c \cdot C_1}{C_c + C_1}}$$




$$V_o = \frac{I_i(s)}{sC_c}$$


$$\left| \frac{g_{m1}}{sC_c} \right| = 1$$

$$|g_{mid}| = \frac{g_m}{C_c}$$

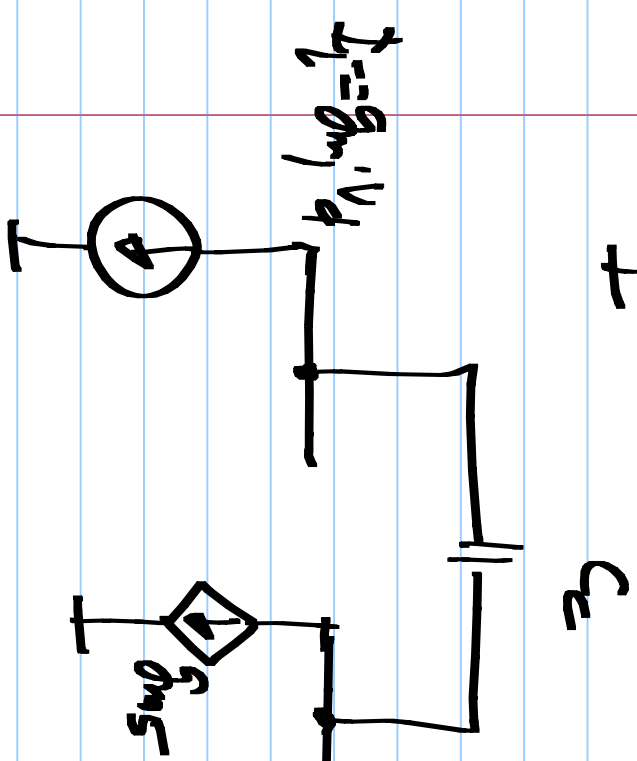

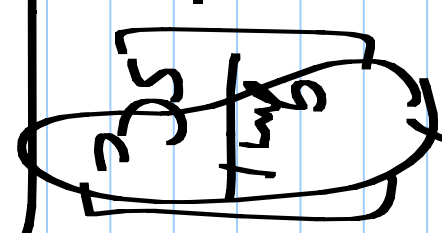
$$V_o(s) = \frac{g_{m1} \cdot V_d(s)}{sC_c} = V_d(s) \cdot \left[\frac{g_{m1}}{sC_c} \right]$$



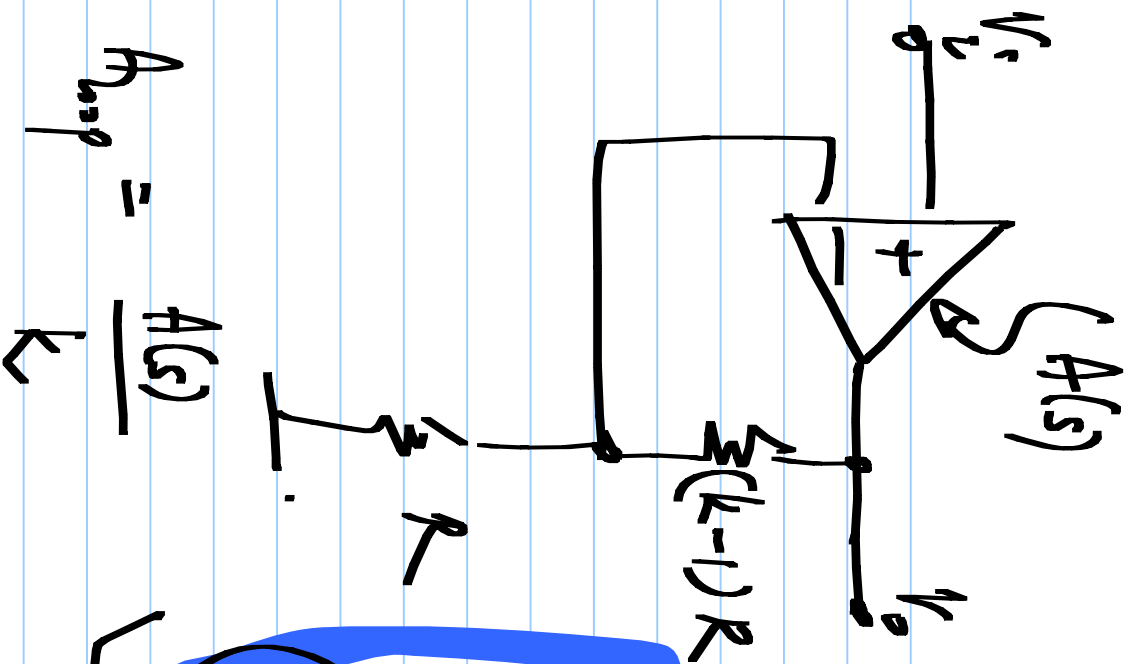

$$\frac{-180^\circ + \phi_m > -120^\circ}{\omega_{y,loop} = \frac{\omega_{y,opp}}{k}} \quad \phi_m > \omega_i$$

Total phase shift @ $\omega_{y,loop}$

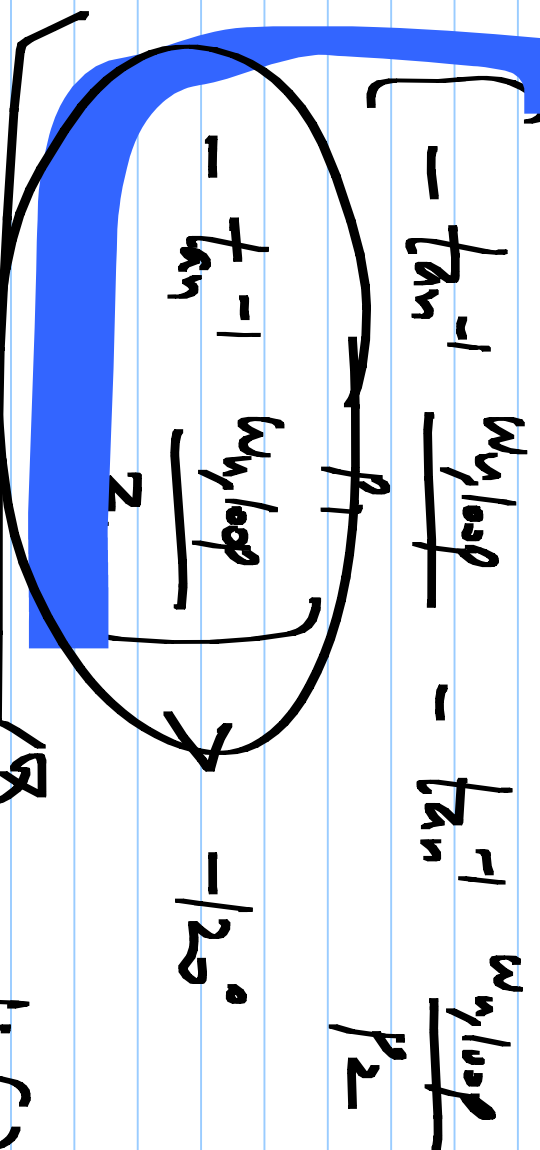

Adjust C so that ϕ is satisfied

$$A_{loop} = \frac{A(s)}{k}$$

$$\tan^{-1} \frac{\omega R / \omega_0}{Z} = \tan^{-1} \left[\frac{\omega R / k}{\omega_0} \right]$$

