

EE2015

$$Q_c = C \cdot V_c$$



$$I_c = C \cdot \frac{dV_c}{dt}$$


7/8/2017

Inductor:



$$V_L = L \cdot I_L$$

$$L \frac{dI_L}{dt} = V_L$$

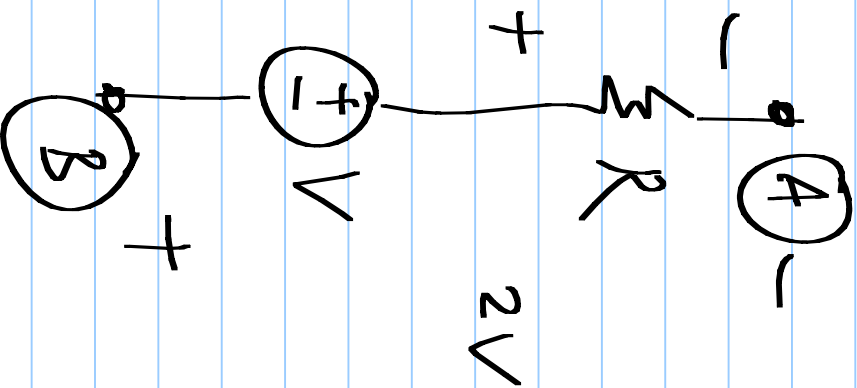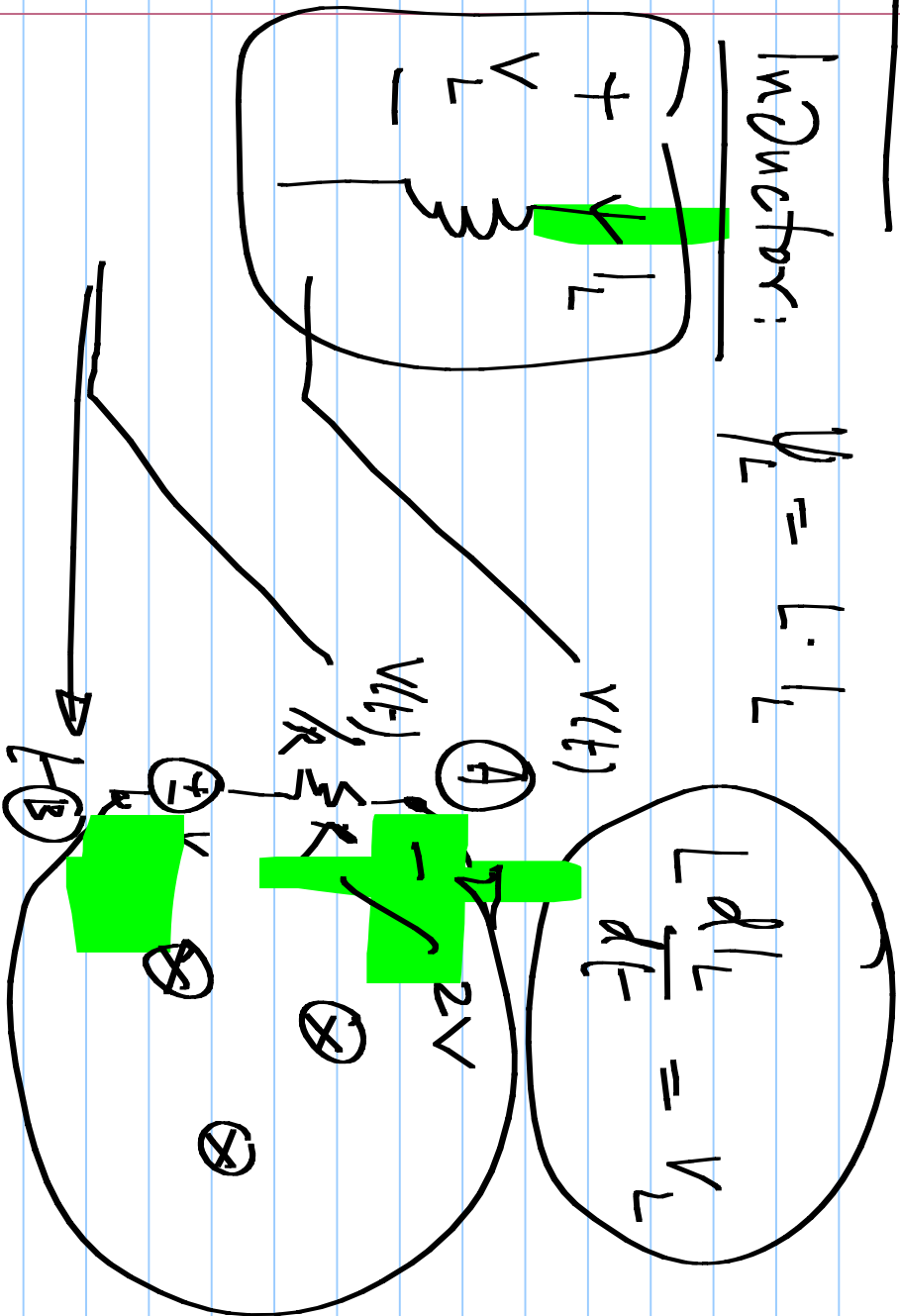

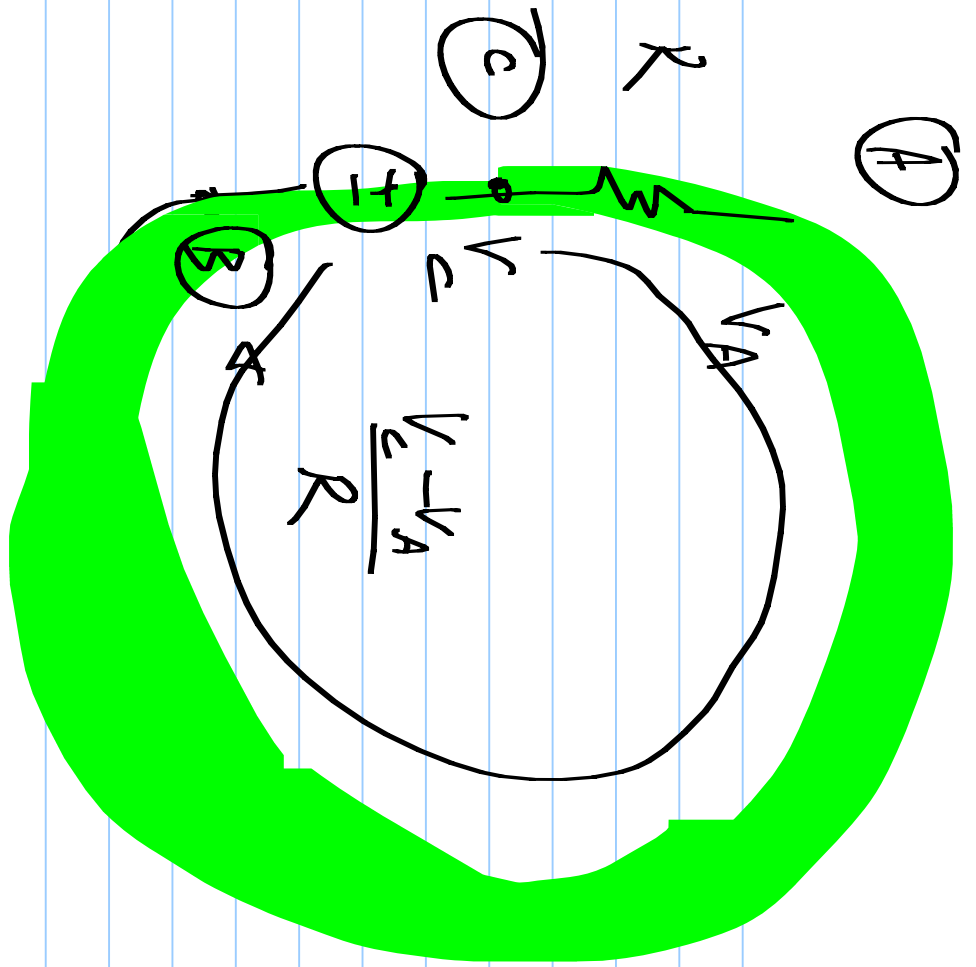


Ideal Voltage source:

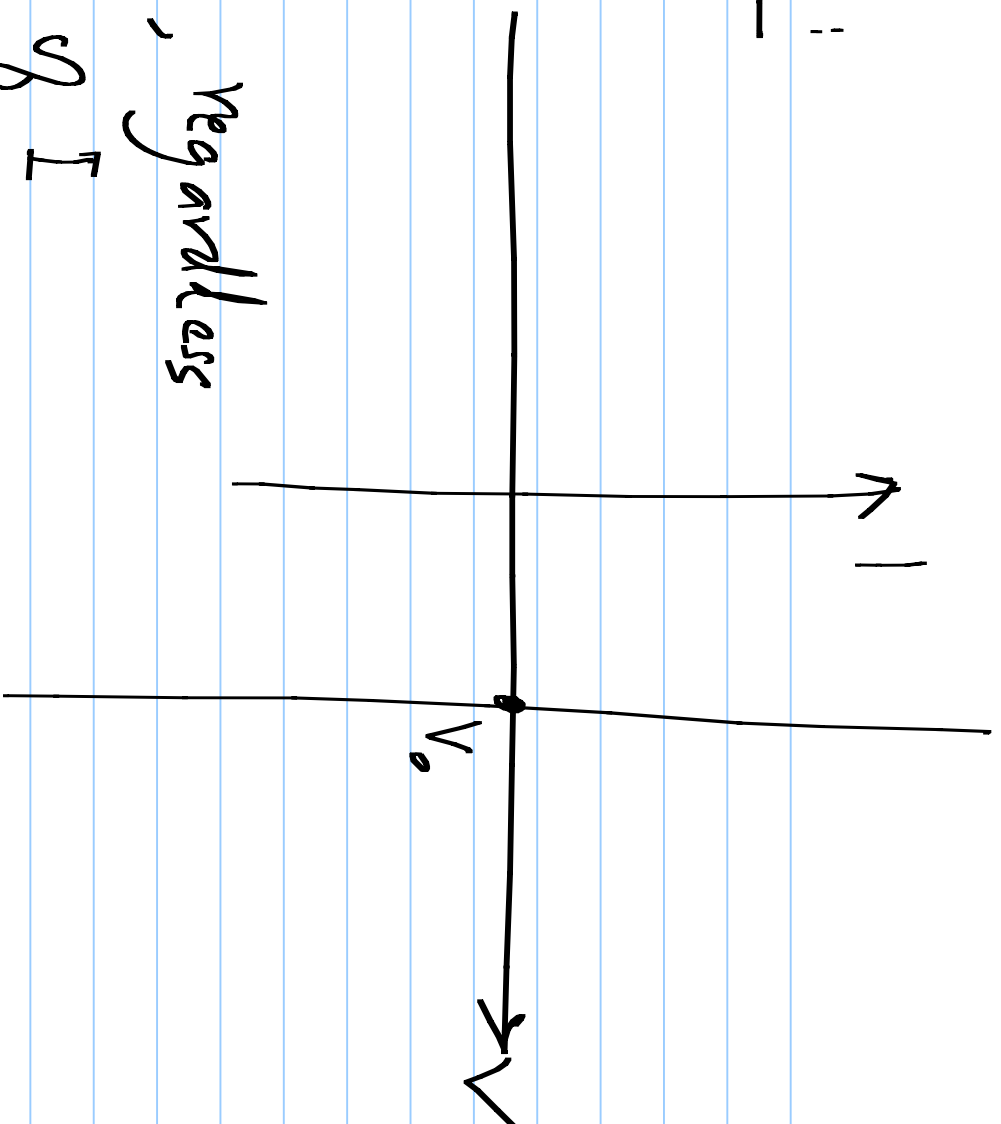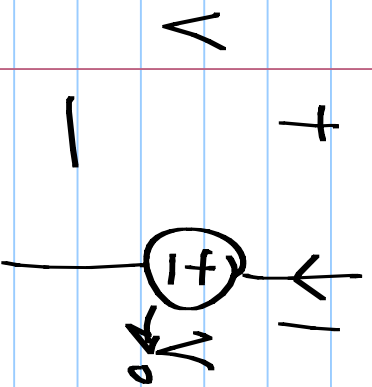

Maintains $V = V_0$, regardless


of I


Current source

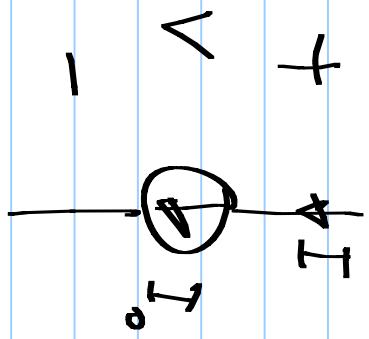


Maintains $I = I_0$ regardless

of V

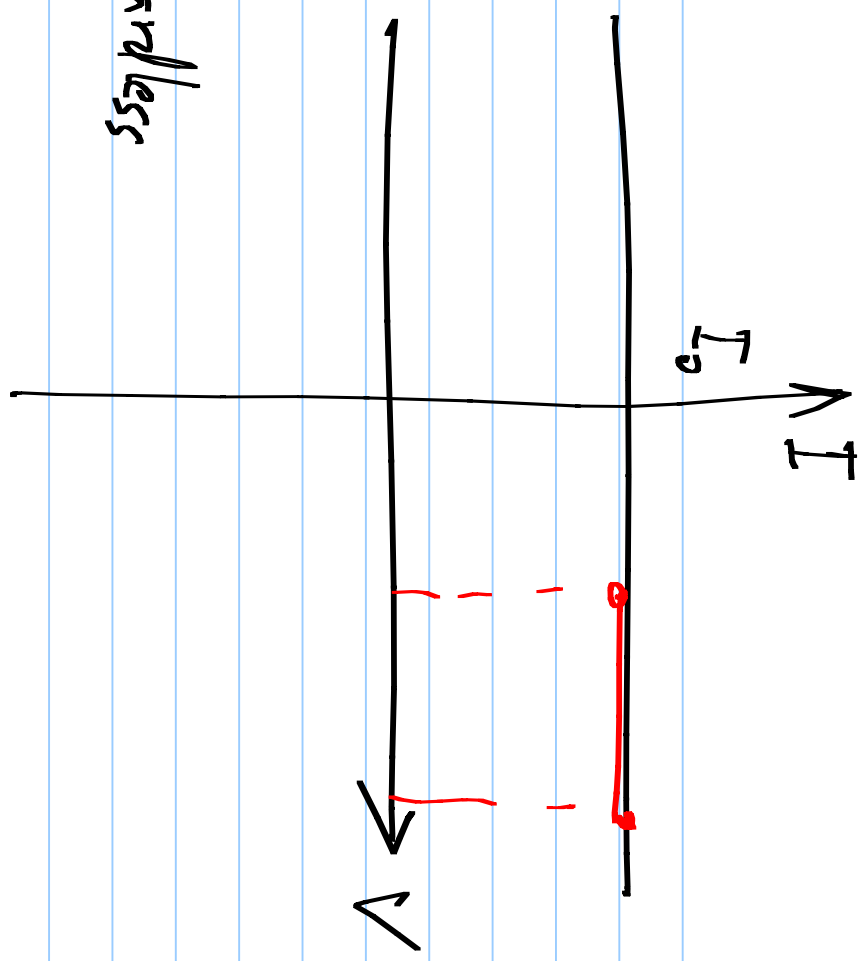

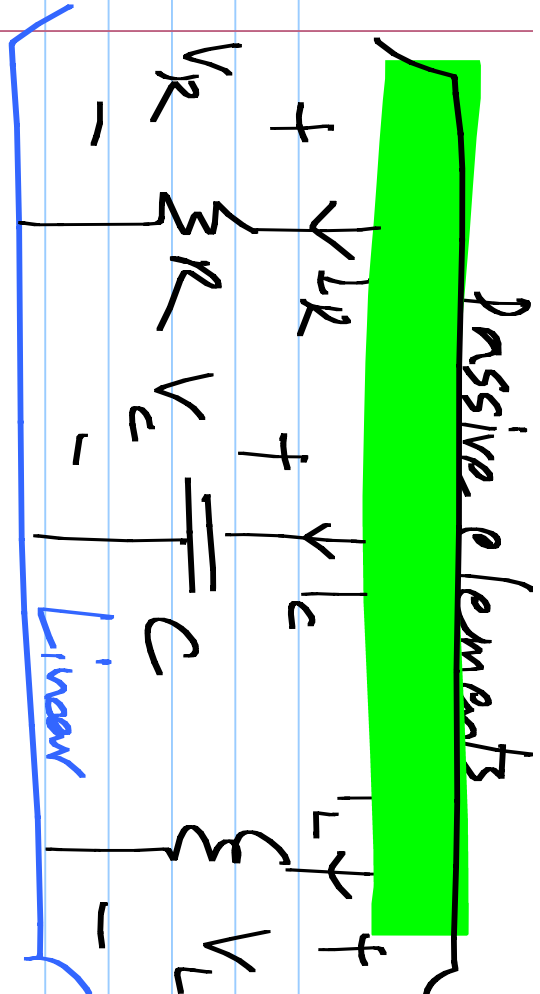

$$V_R = R \cdot I_R \quad | \quad V_C = C \frac{dV_C}{dt} \quad | \quad V_L = L \cdot \frac{dI_L}{dt}$$

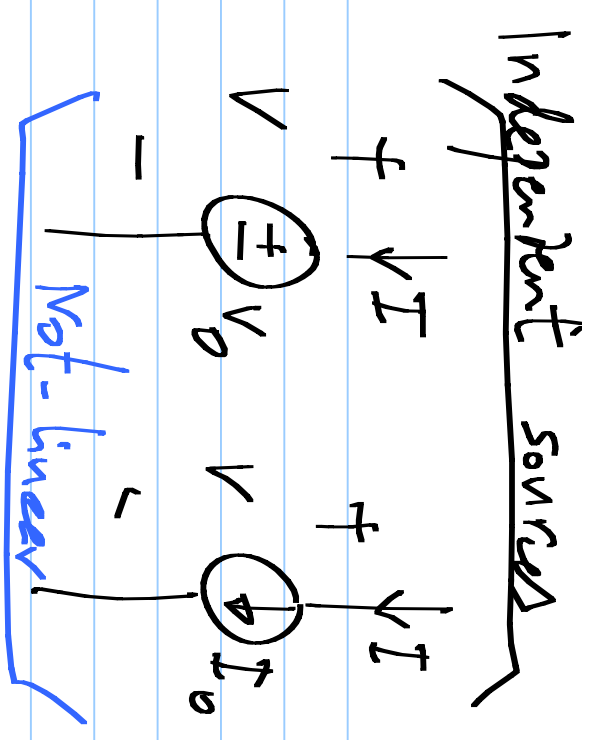



$$V = V_0 \quad | \quad I = I_0$$

Are the I-V relationships linear?

Linearity & superposition:

homogeneity


$$x=0 : y=0$$

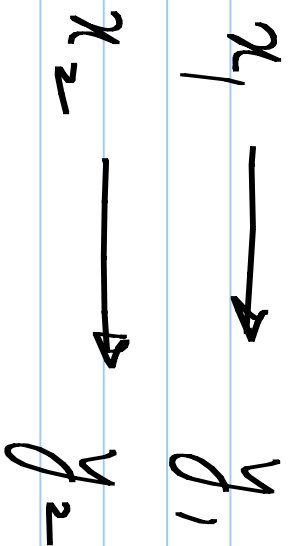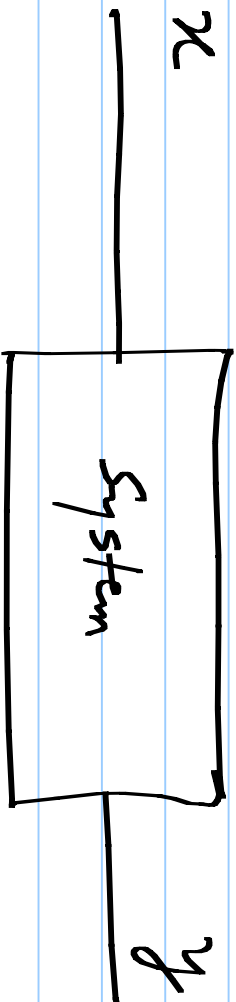

$$ax_1 + bx_2 \rightarrow ay_1 + by_2$$




Mutual inductor.

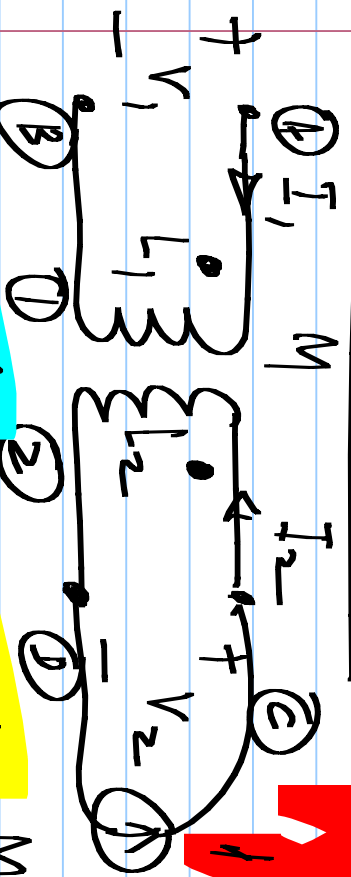

Coupling $k = \frac{M}{\sqrt{L_1 L_2}}$ $|k| \leq 1$

self inductance

Mutually-

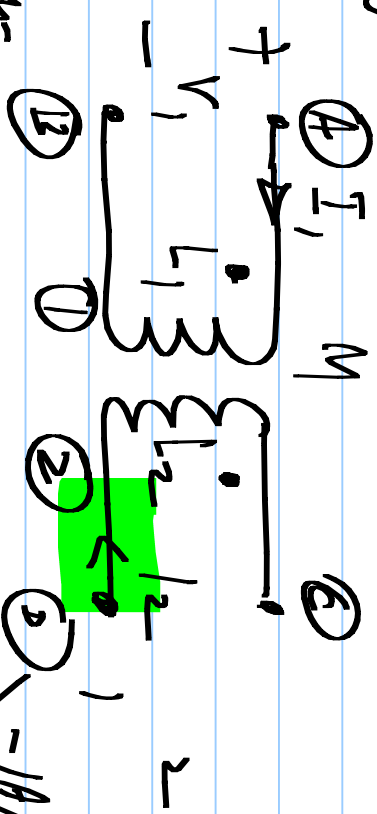

$$V_1 = L_1 \frac{dI_1}{dt} + M \frac{dI_2}{dt}$$



induced voltage $V = L_1 \frac{dI_1}{dt} - M \frac{dI_2}{dt}$

$-1/s$

$$V_2 = M \frac{dI_1}{dt} + L_2 \frac{dI_2}{dt}$$

L_1, L_2 : Self inductance

M : Mutual inductance

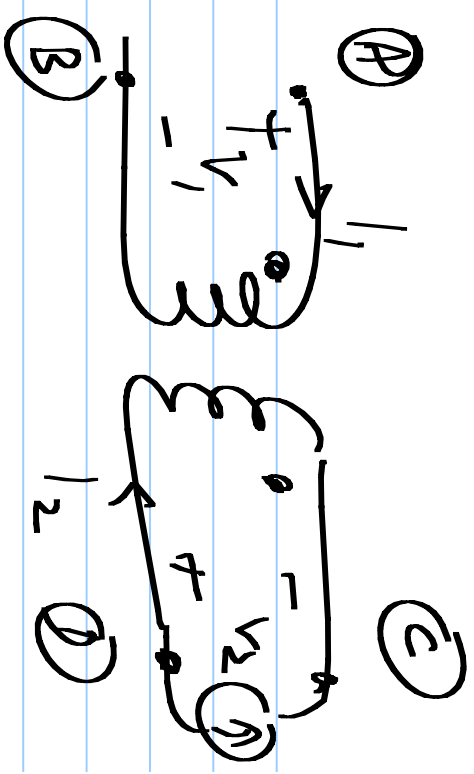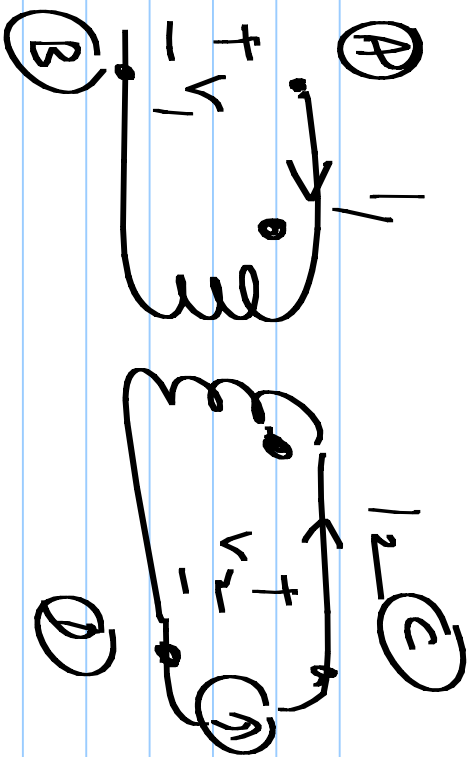

dot-convention: avoids ambiguity in the sign of the mutually-induced voltage