

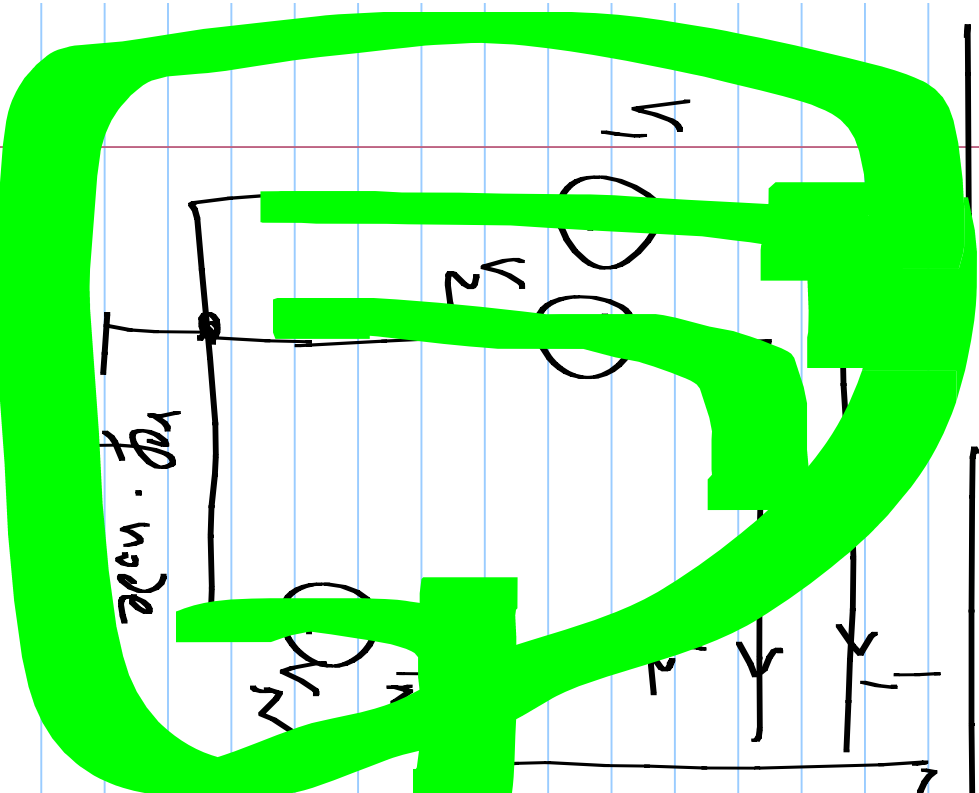


EE2015

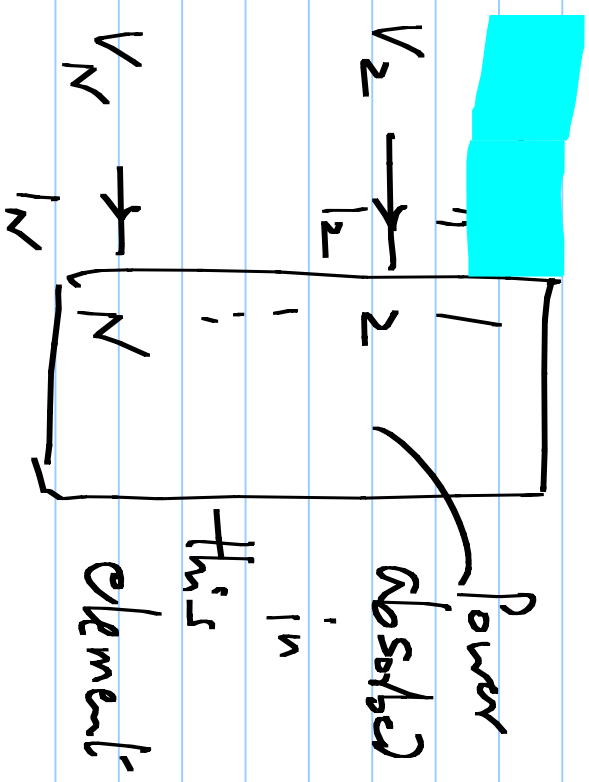Power in a multi-terminal element 9/8/2017



$$\sum_{k=1}^N V_k$$

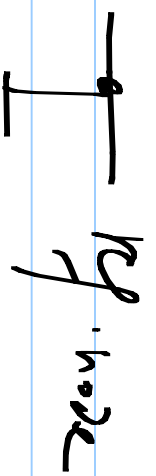

$$I_N = -(I_1 + I_2 + \dots + I_{N-1})$$


$$-I_1 + V_2 I_2 + \dots + V_{N-1} I_{N-1} - V_N I_N = 0$$

$$(V_1 - V_N) I_1 + (V_2 - V_N) I_2 + \dots + (V_{N-1} - V_N) I_{N-1}$$

Power in an n-terminal element = $\sum_{k=1}^{N-1} (V_k - V_N) \cdot I_k$

Mutual inductor:

$$P = V_1 I_1 + V_2 I_2$$

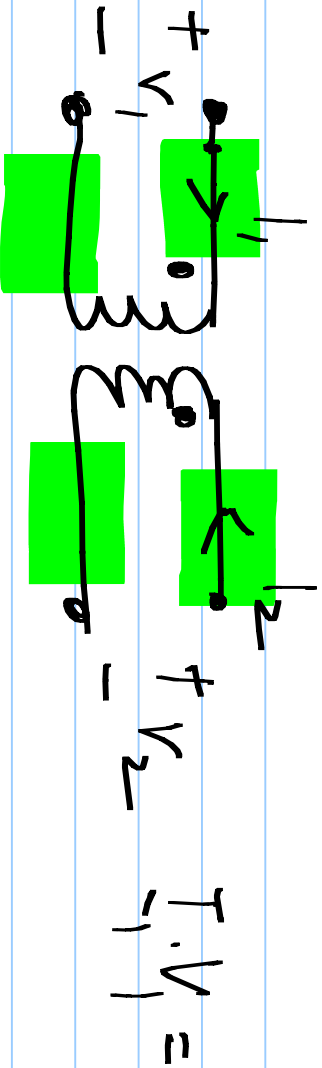

$$I_1 \cdot V_1 =$$

Calculate the energy stored in the mutual inductor

in the mutual inductor

$$I_1 = 0, I_2 = 0$$



$$\int_0^t P \cdot dt =$$

$$\frac{1}{2} L_1 I_1^2 + M \cdot I_1 I_2$$

$$\frac{1}{2} \|l_1\|_2^2 + \frac{1}{2} \|l_2\|_2^2 + M \|l_1\|_2 > 0$$




$\frac{1}{2}$


$$\left(\sqrt{\frac{1}{2}} \|l_1\|_2 + \sqrt{\frac{1}{2}} \|l_2\|_2 \right)^2 + (M - \sqrt{L_1 L_2}) \|l_1\|_2 > 0$$

$$|M| \leq \sqrt{L_1 L_2} \quad M = k \cdot \sqrt{L_1 L_2}$$

$$k \leq 1$$

$$\sum_{L} \sum_{L} \quad M < L$$

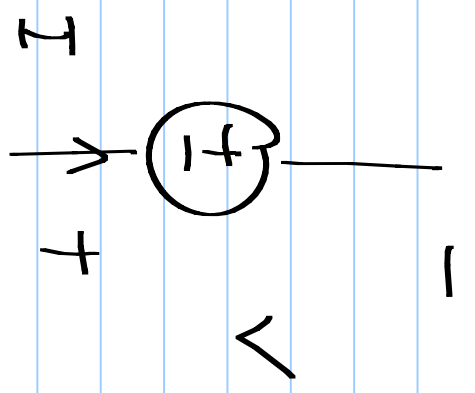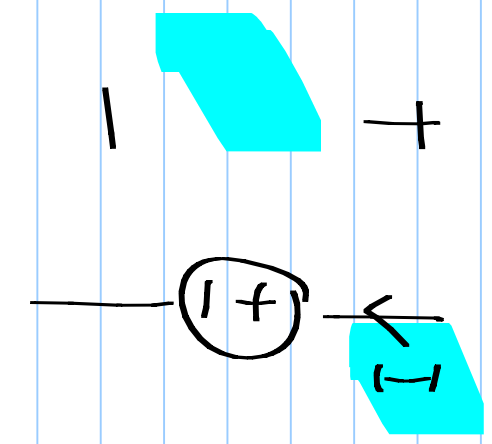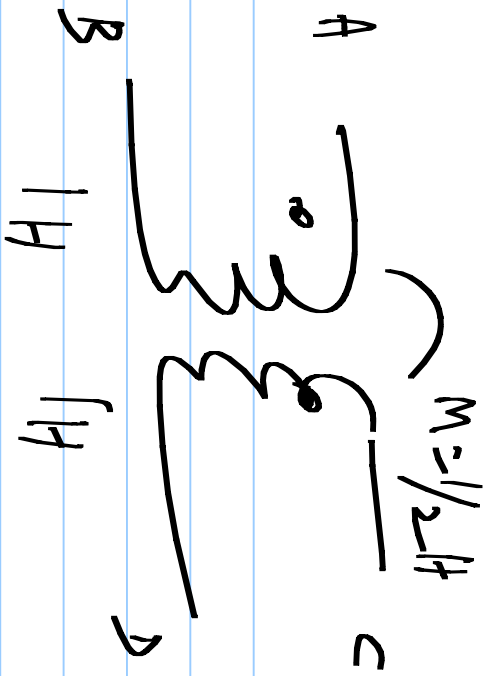


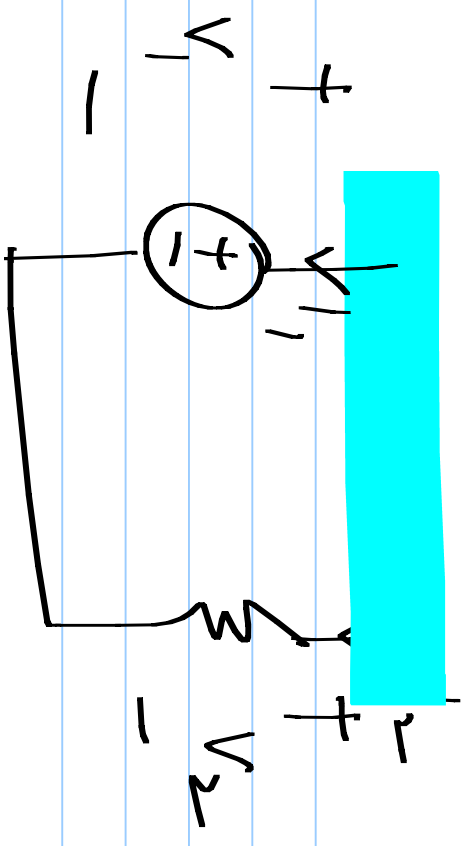


$$I_1 + I_2 = 0$$


$$V_1 - V_2 = 0$$

Open circuit:

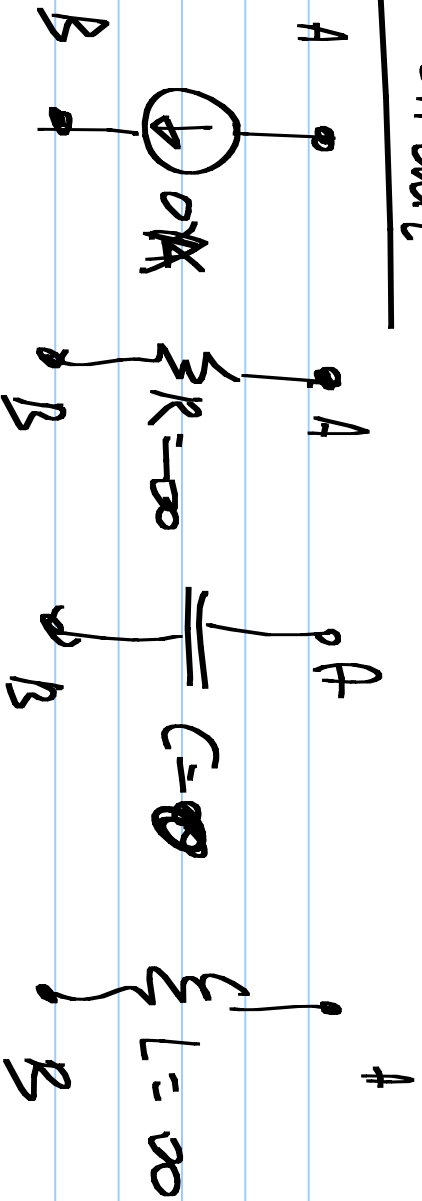

Short circuit:

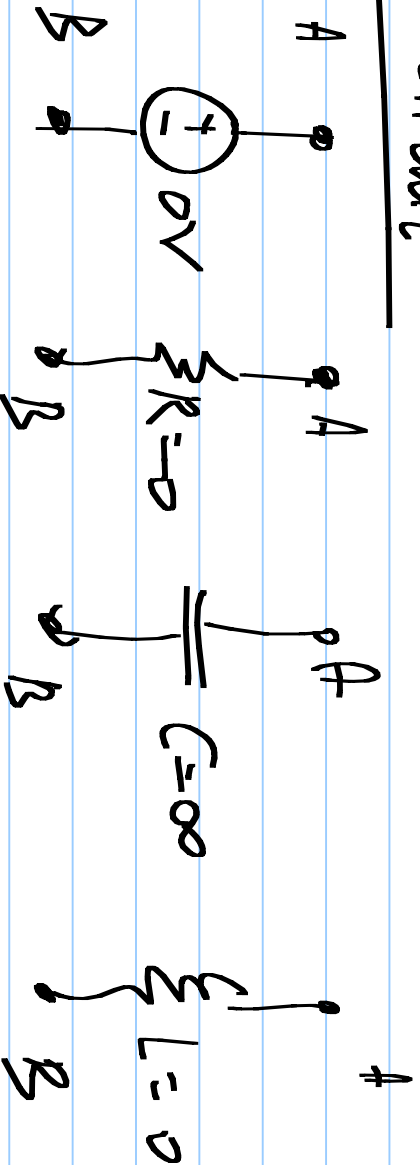

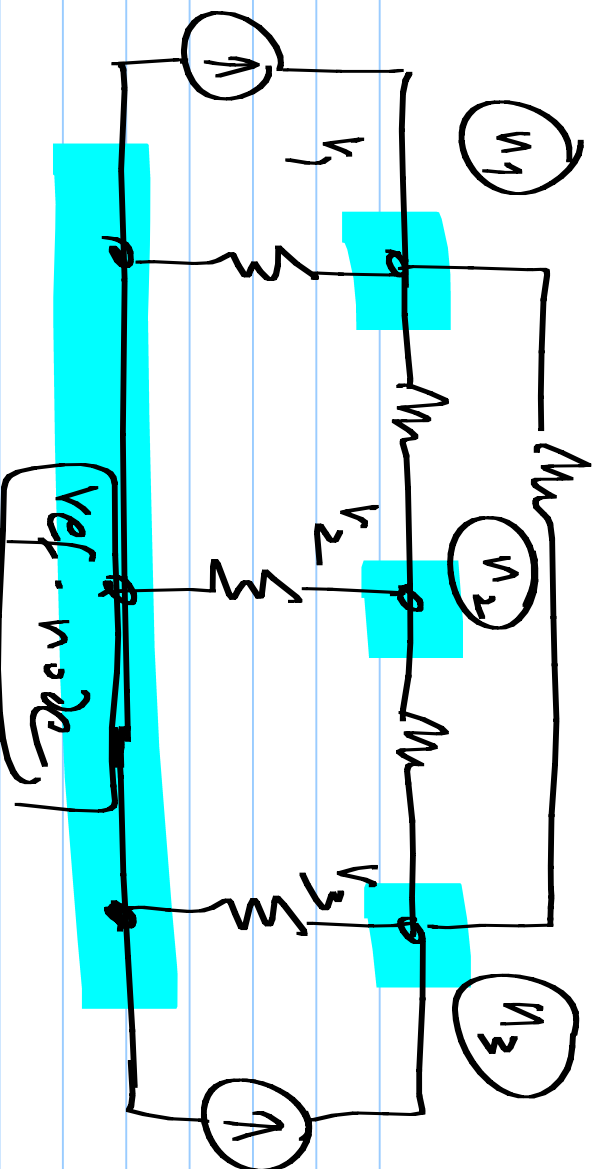

$$N = 4$$

$$B = 8$$

$$\frac{3}{3} \text{ KCL}$$

$$\frac{5}{5} \text{ KVL}$$


Nodal analysis: Start with KCL eq. @ $N-1$ nodes

Circuits w/ linear elements & ind. sources

resistors

Resistors & ind. current sources

KCL @ n_1, n_2, n_3

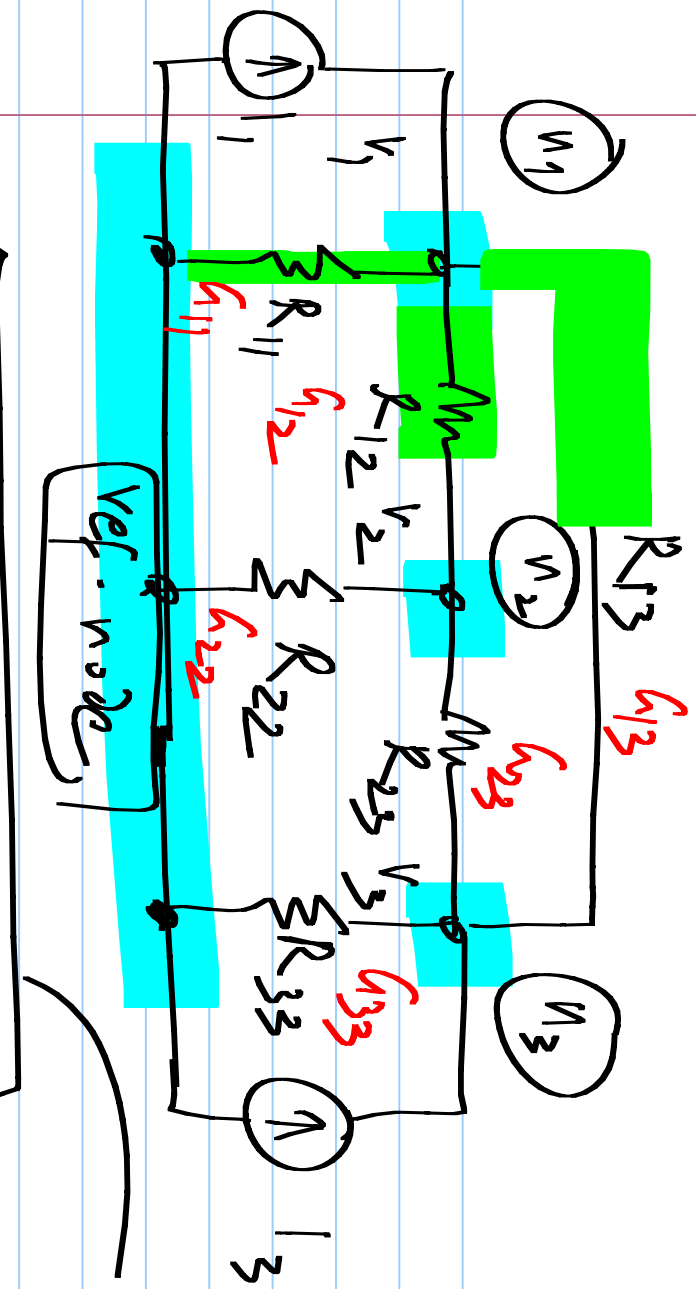

currents flowing out

of n_1


(n_1) :
$$\frac{V_1}{R_{11}} + \frac{V_1 - V_2}{R_{12}} + \frac{V_1 - V_3}{R_{13}} = 1$$

current flowing into n_1 by an

$$V_1 \cdot g_{11} + (V_1 - V_2) g_{12} + (V_1 - V_3) g_{13} = 1$$

in). current source
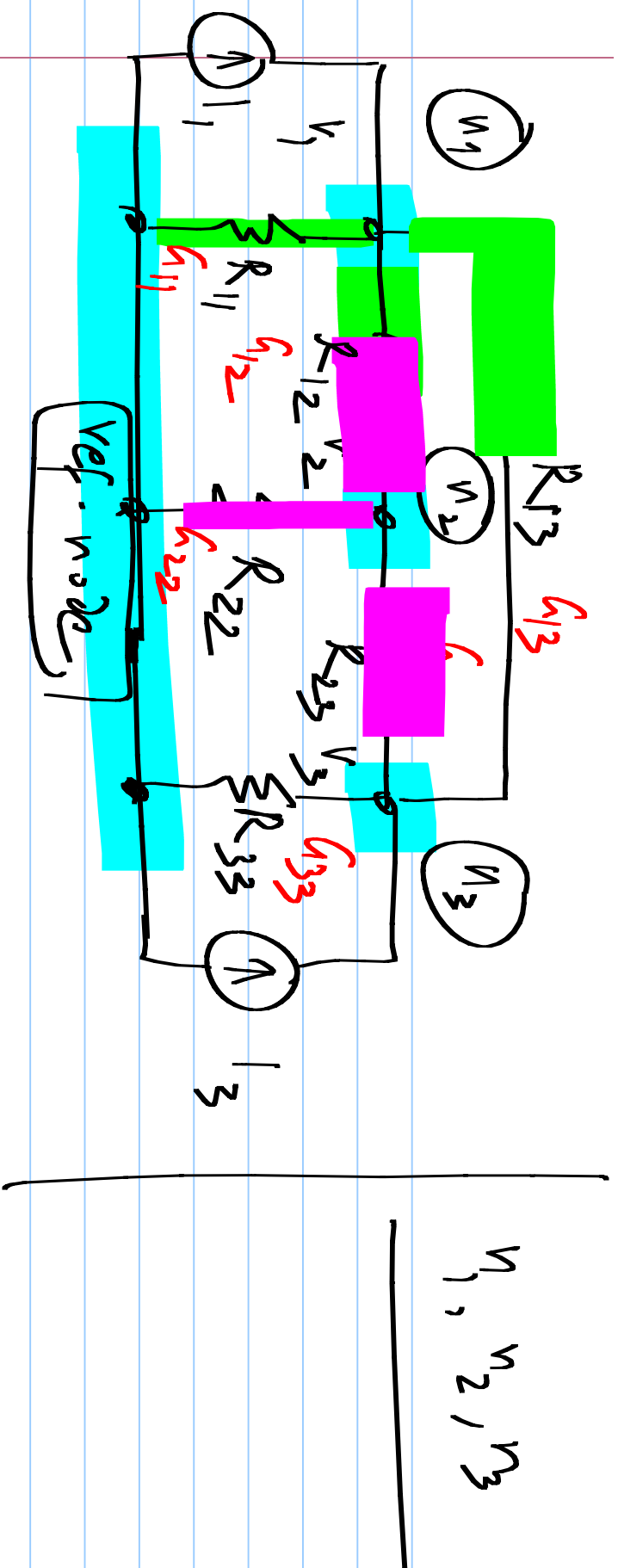
$$V_1 (g_{11} + g_{12} + g_{13}) - V_2 g_{12} - V_3 g_{13} = 1$$



$$n_2: (V_2 - V_1) \cdot g_{12} + V_2 \cdot g_{22} + (V_2 - V_3) g_{23} = 0$$

$$-V_1 \cdot g_{12} + V_2 (g_{12} + g_{22} + g_{23}) - V_3 g_{23} = 0$$