
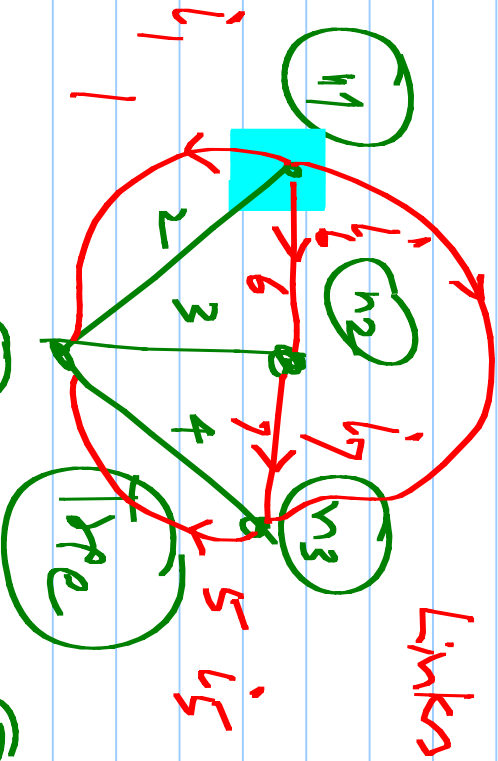





EE 2015


i_8

16/8/2017

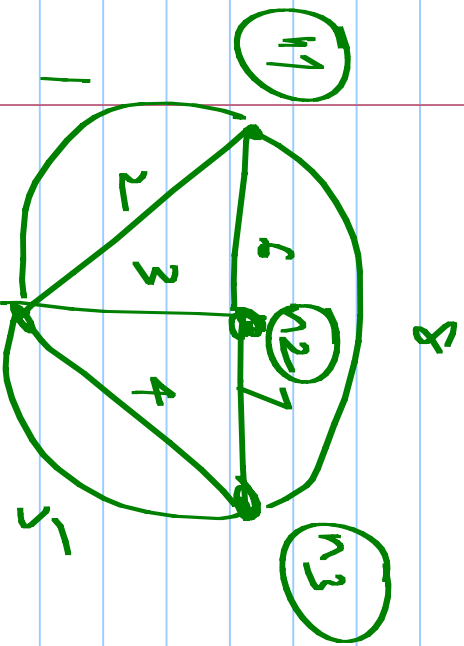


Links

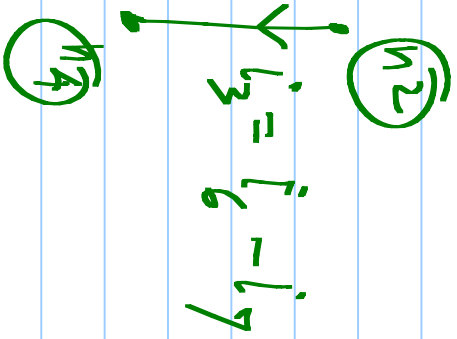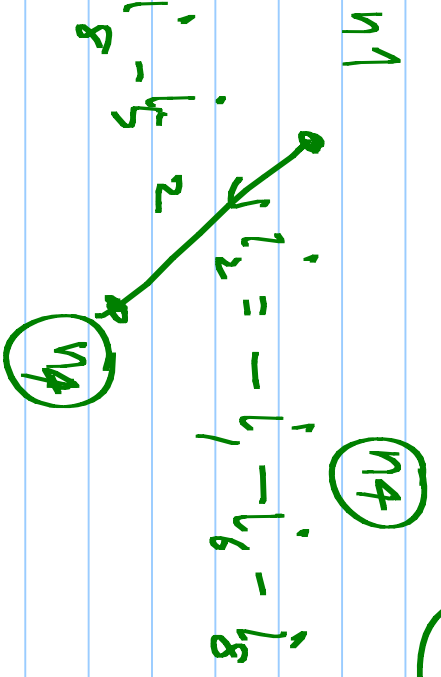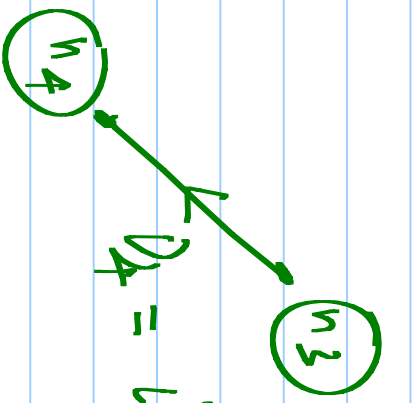


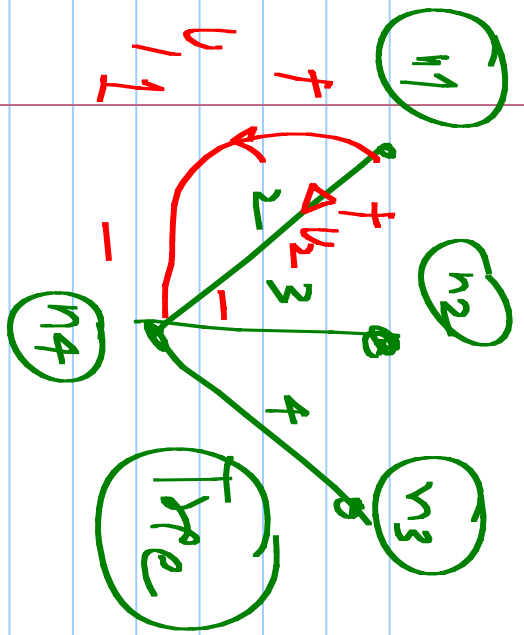


$$v_1 - v_2 = 0$$

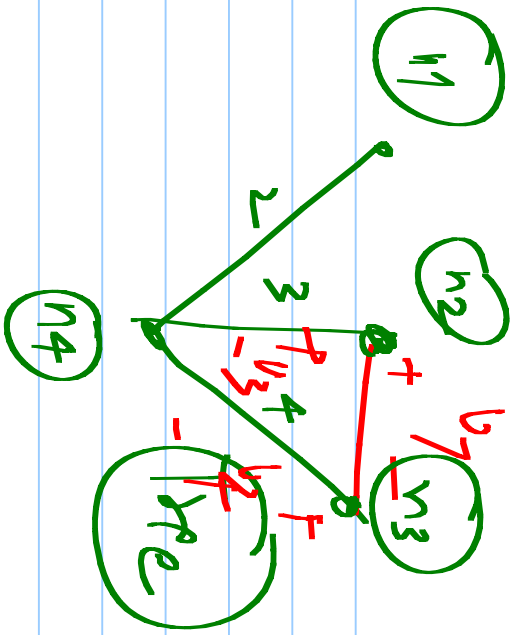


$$v_7 + v_4 - v_3 = 0$$

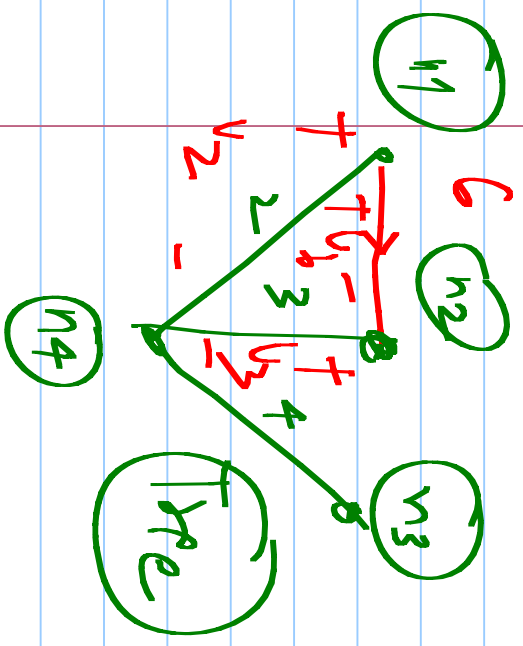


$$v_6 + v_3 - v_2 = 0$$

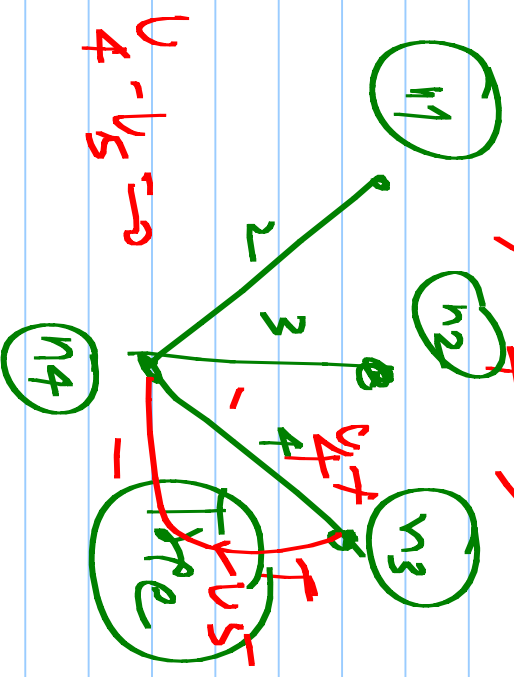

$$v_4 - v_5 = 0$$

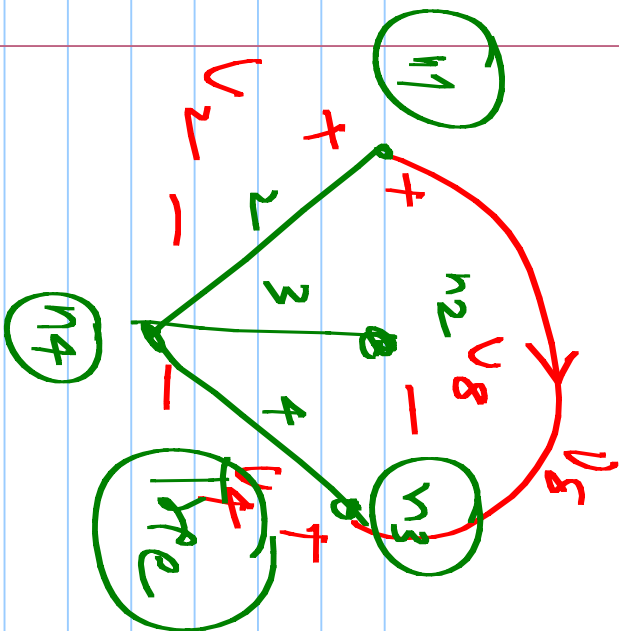

$$v_8 + v_4 - v_2 = 0$$

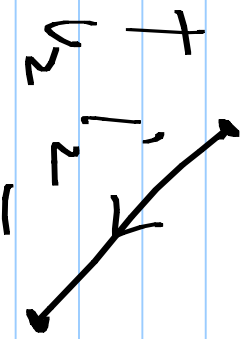

$$v_1 + \blacksquare = 0$$

$$v_6 + v_3 - \blacksquare = 0$$



$$v_7 + v_4 - v_3 = 0$$

$$v_4 - v_5 = 0$$

$$v_8 + v_4 - \blacksquare = 0$$


$$[R] \underline{i} = \underline{V_s}$$

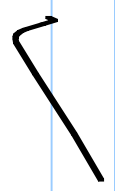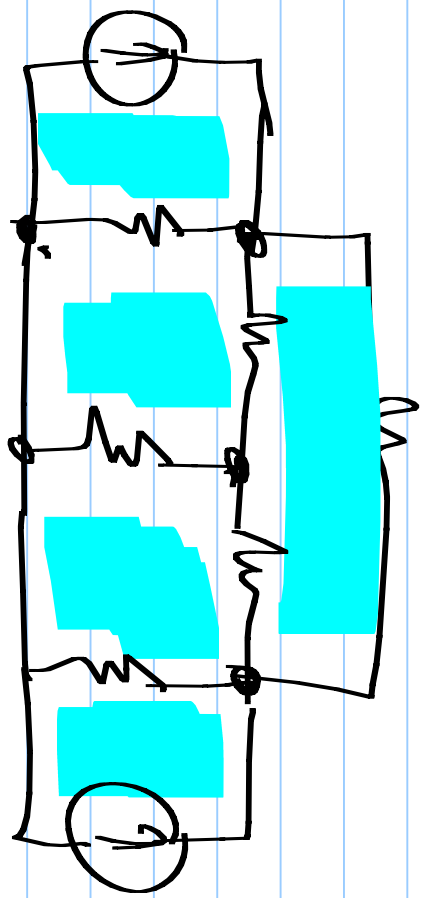
Mesh analysis: Loop-based analysis for planar circuits



Circuits which can be drawn on a plane without

two branches crossing over each other

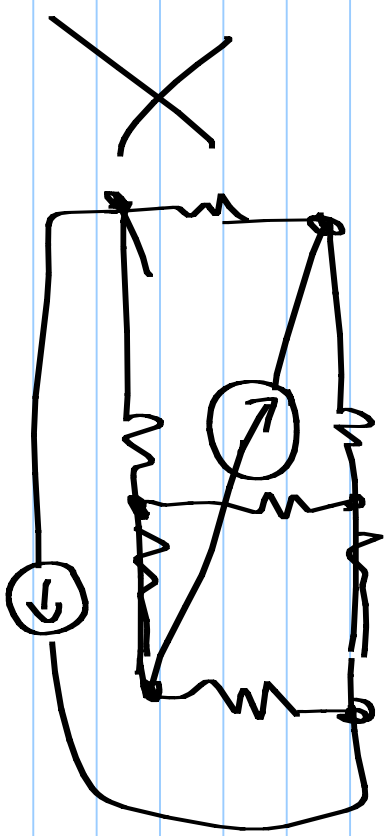

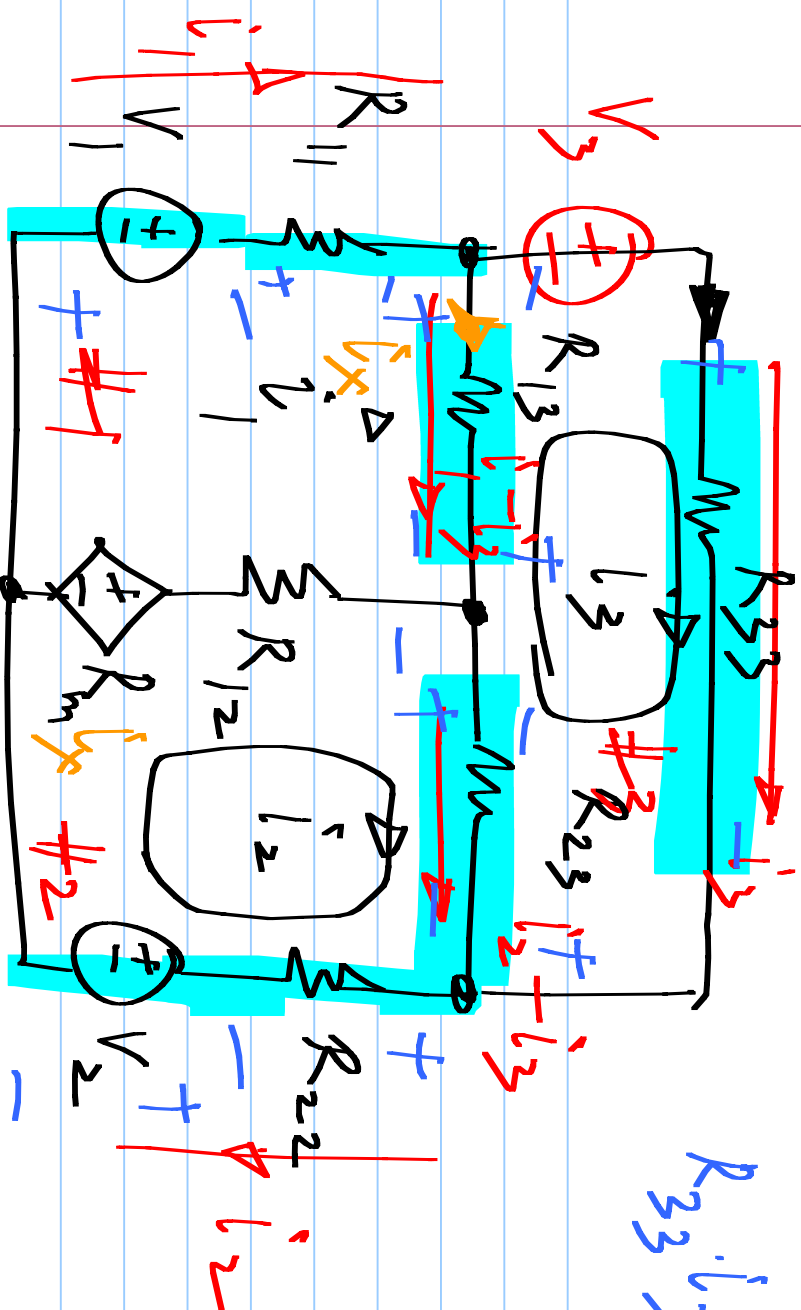

$$R_{33}i_3 + R_{23}(i_3 + i_2) = 0$$

$$-R_m(i_1 - i_2)$$

$$R_{13}(i_1 - i_3) + R_{12}(i_1 - i_2) + R_{11}i_1 = V_1 - R_m i_3$$

$$R_{12}(i_2 - i_1) + R_{23}(i_2 - i_3) + R_{22}i_2 = -V_2 + R_m i_3$$

$$\text{Mesh \#1} \quad (R_{11} + R_{12} + R_{13}) i_1 - R_{12} i_2 - R_{13} i_3 = V_1$$


$$\text{Mesh \#2} \quad -R_{12} i_1 + (R_{12} + R_{22} + R_{23}) i_2 - R_{23} i_3 = -V_2$$

$$\text{Mesh \#3} \quad -R_{13} i_1 - R_{23} i_2 + (R_{13} + R_{23} + R_{33}) i_3 = 0$$

$$\begin{bmatrix} R_{11} + R_{12} + R_{13} & -R_{12} & -R_{13} \\ -R_{12} & R_{12} + R_{22} + R_{23} & -R_{23} \\ -R_{13} & -R_{23} & R_{13} + R_{23} + R_{33} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ -V_2 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix}
 R_{11} + R_{12} + R_{13} + R_m & -R_{12} & -R_{13} & -R_m \\
 -R_{12} - R_m & R_{12} + R_{22} + R_{23} & -R_{23} + R_m \\
 -R_{13} & -R_{23} & R_{13} + R_{23} + R_{33}
 \end{bmatrix}
 \begin{bmatrix}
 i_1 \\
 i_2 \\
 i_3
 \end{bmatrix}
 =
 \begin{bmatrix}
 -V_1 \\
 -V_2 \\
 0
 \end{bmatrix}$$

$$i_1 - i_2 = I_s$$

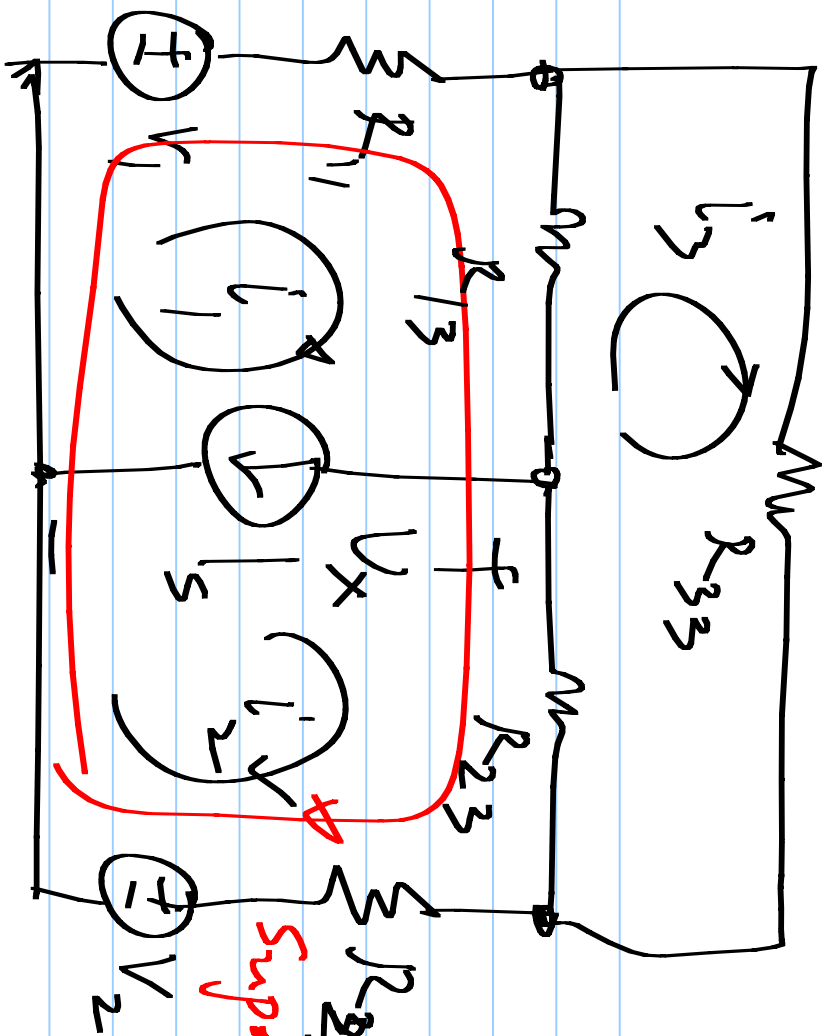

From a Supermesh

Supermesh

$$(R_{11} + R_{13}) i_1 - R_{13} i_2 - V_x = V_1$$

$$V_x + (R_{22} + R_{23}) i_2 - R_{23} i_3 = V_2$$