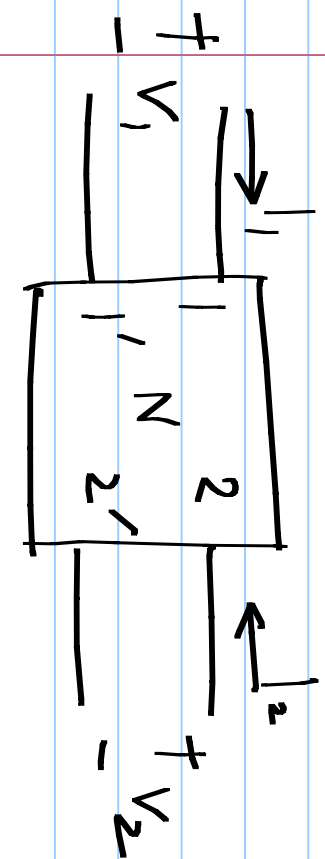


EE 2015

Two-port networks


30/8/2017



$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

y -parameters

admittance parameters



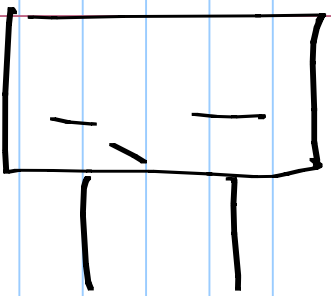


R or G

$$\underline{I} = [Y] \underline{V}$$

conductance

$$I = G \cdot V$$

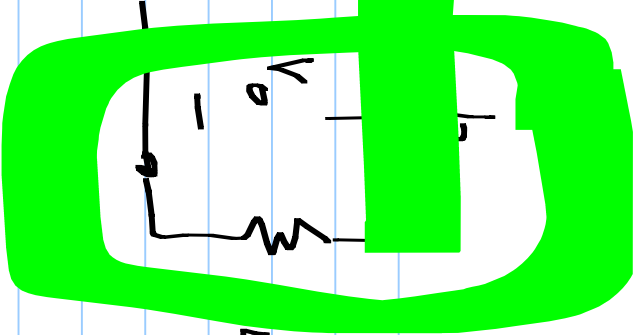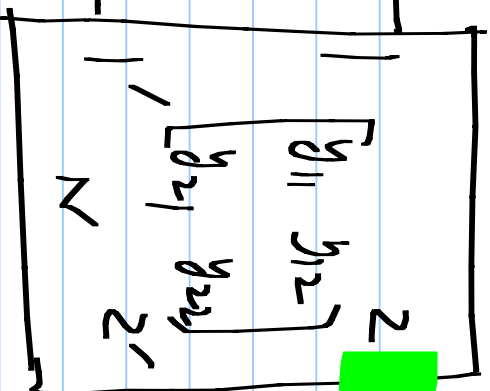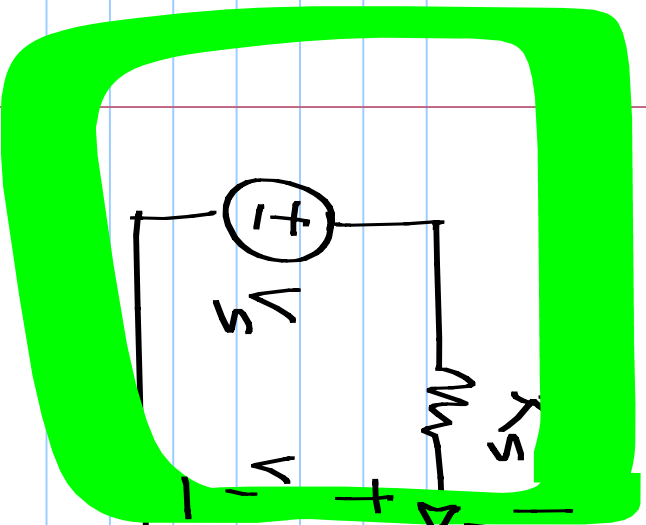

$$I_1 = y_{11} V_1 + y_{12} V_2$$

$$I_2 = y_{21} V_1 + y_{22} V_2$$

$$-I_2 = \frac{V_o}{R_L}$$

$$I_2 = -\frac{V_o}{R_L}$$

Eliminate V_1 , I_1 , I_2

$$(V_s, V_2)$$

$$\frac{V_s}{R_s} = \left(\frac{1}{R_s} + y_{11} \right) V_1 + y_{12} V_2$$

$$-\frac{V_2}{R_L} = y_{21} V_1 + y_{22} V_2$$

$$\frac{V_s}{R_s} = \left(\frac{1}{R_s} + y_{11} \right) V_1 + y_{12} V_2$$


$$-\frac{V_2}{R_L} = y_{21} V_1 + y_{22} V_2$$

$$V_1 = -V_2 \frac{\left(y_{22} + \frac{1}{R_L} \right)}{y_{21}}$$

$$\frac{V_s}{R_s} = \left[\frac{\left(\frac{1}{R_s} + y_{11} \right) \left(\frac{1}{R_L} + y_{22} \right)}{y_{21}} + y_{12} \right] \cdot V_2$$





$$\frac{V_s}{R_s} = \left[- \frac{\left(\frac{1}{R_s} + y_{11} \right) \left(\frac{1}{R_L} + y_{22} \right)}{\quad} + \quad \right] \cdot V_2$$
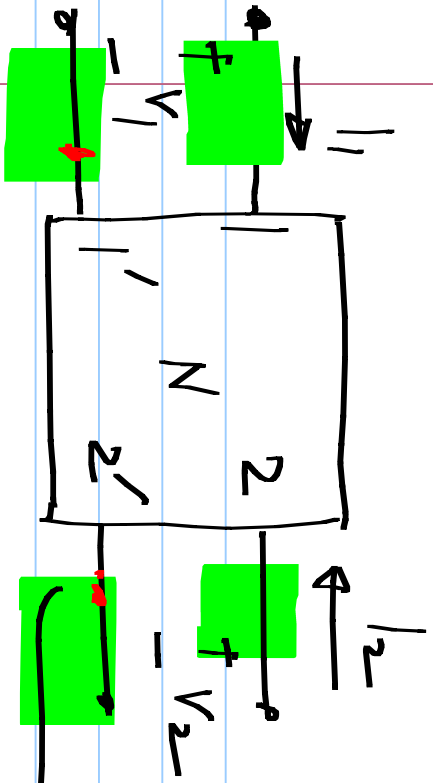
$$V_2 = \frac{- y_{21} / R_s}{\left(\frac{1}{R_s} + y_{11} \right) \left(\frac{1}{R_L} + y_{22} \right) - y_{12} y_{21}}$$




$$i_1 = \text{[redacted]} + \text{[redacted]}$$
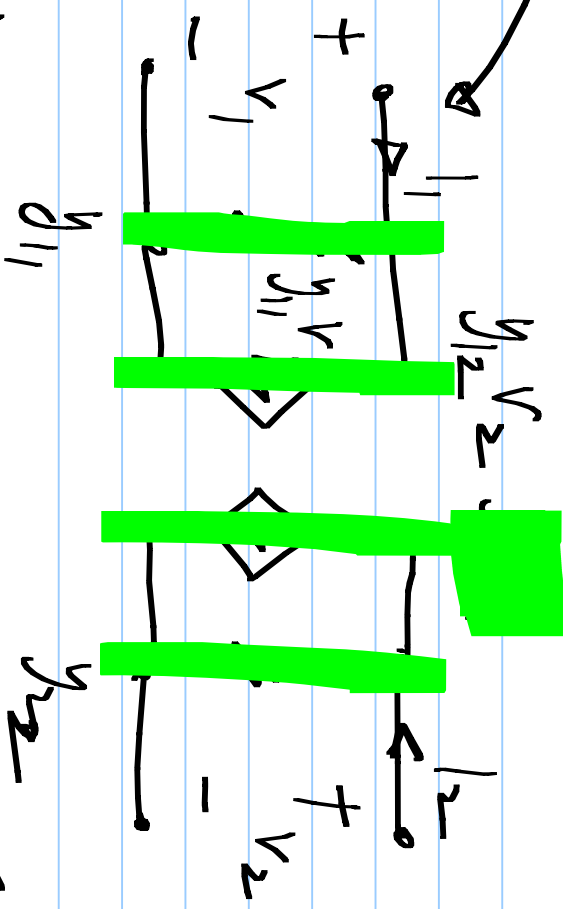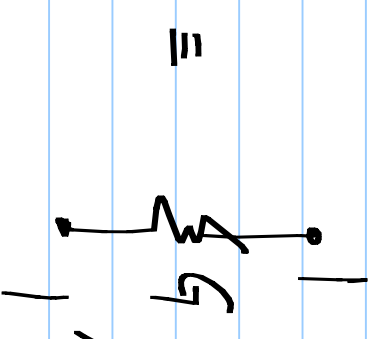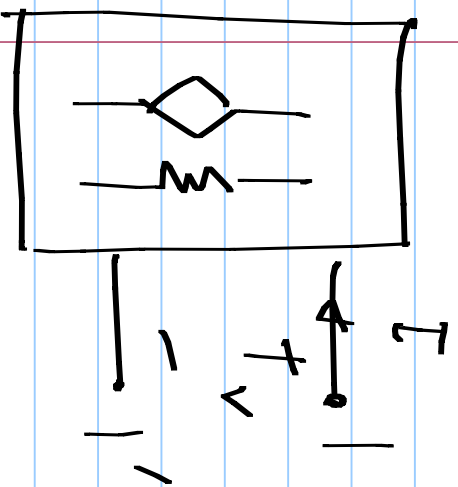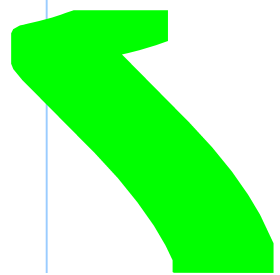
$$i_2 = \text{[redacted]} + \text{[redacted]}$$




Circuit representation of a two-port

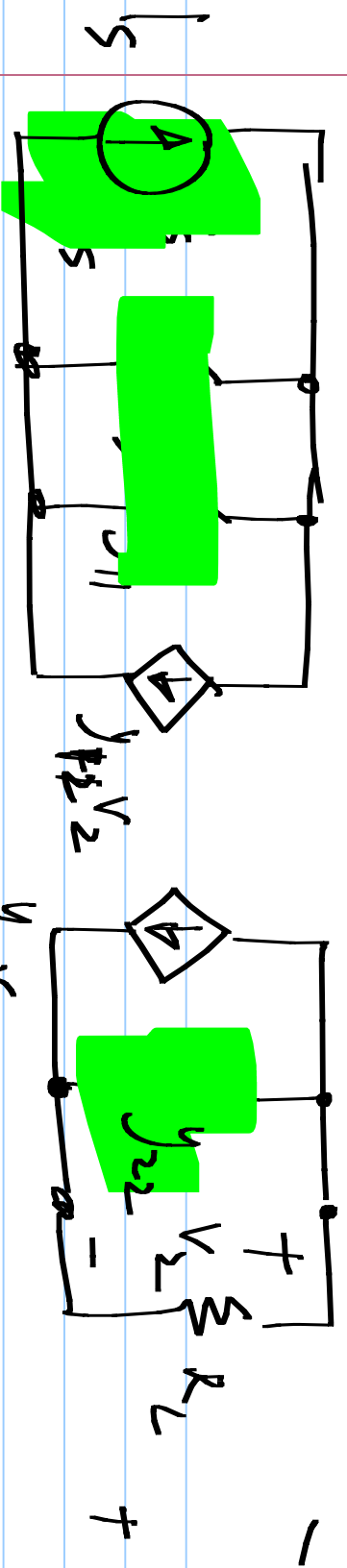

$$V_2 = -y_{21} \left(\frac{V_s}{R_s} \right) - y_{22} V_2$$
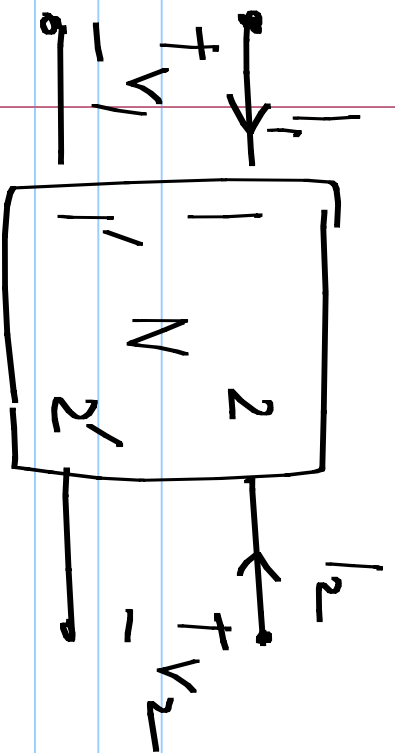
$$V_2 (1 + y_{22}) = -y_{21} \left(\frac{V_s}{R_s} \right)$$



y-parameters

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}^{-1} \frac{\begin{bmatrix} V_1 \\ V_2 \end{bmatrix}}{\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}}$$

$$\begin{bmatrix} y_{22} & -y_{12} \\ -y_{21} & y_{11} \end{bmatrix} \quad \text{Z-parameters}$$

$$\frac{1}{y_{11}y_{22} - y_{12}y_{21}} \quad \text{Impedance parameters}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

h -parameters

(Hybrid)

$$h_{21} : \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

dimensionless

current gain

$$h_{22} : \left. \frac{I_2}{V_2} \right|_{I_1=0}$$

conductance

$$h_{11} : \left. \frac{V_1}{I_1} \right|_{V_2=0}$$

resistance

$$h_{12} : \left. \frac{V_1}{V_2} \right|_{I_1=0}$$

dimensionless

$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

g -parameters

* Draw the circuit representation for Z -, h -, g -parameters

* Express h - & g -parameters in terms of g -parameters