
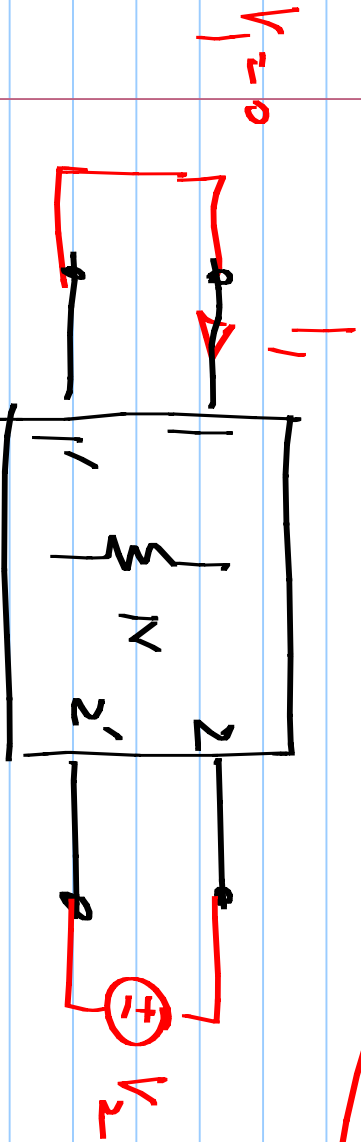


EE 2015

Reciprocity & two-ports


5/9/2017

$y_{12} = y_{21}$

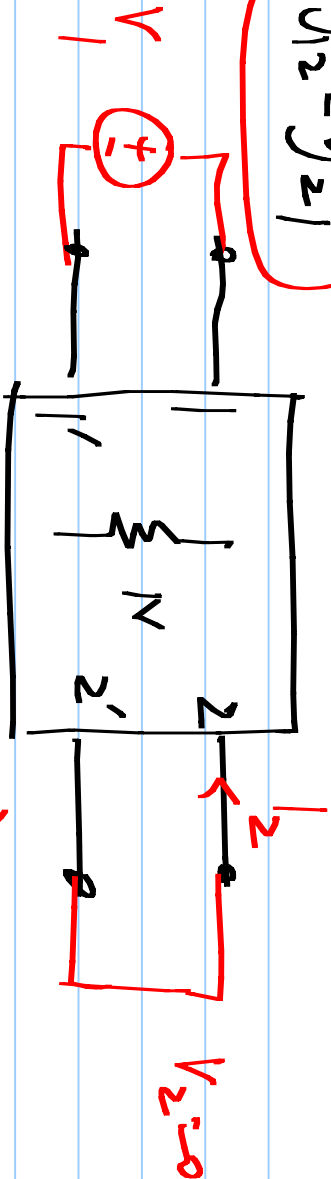


$$\left. \begin{matrix} I_1 \\ V_2=0 \end{matrix} \right| = \left. \begin{matrix} I_2 \\ V_1 \end{matrix} \right|_{V_2=0}$$


$$y_{12} = y_{21}$$

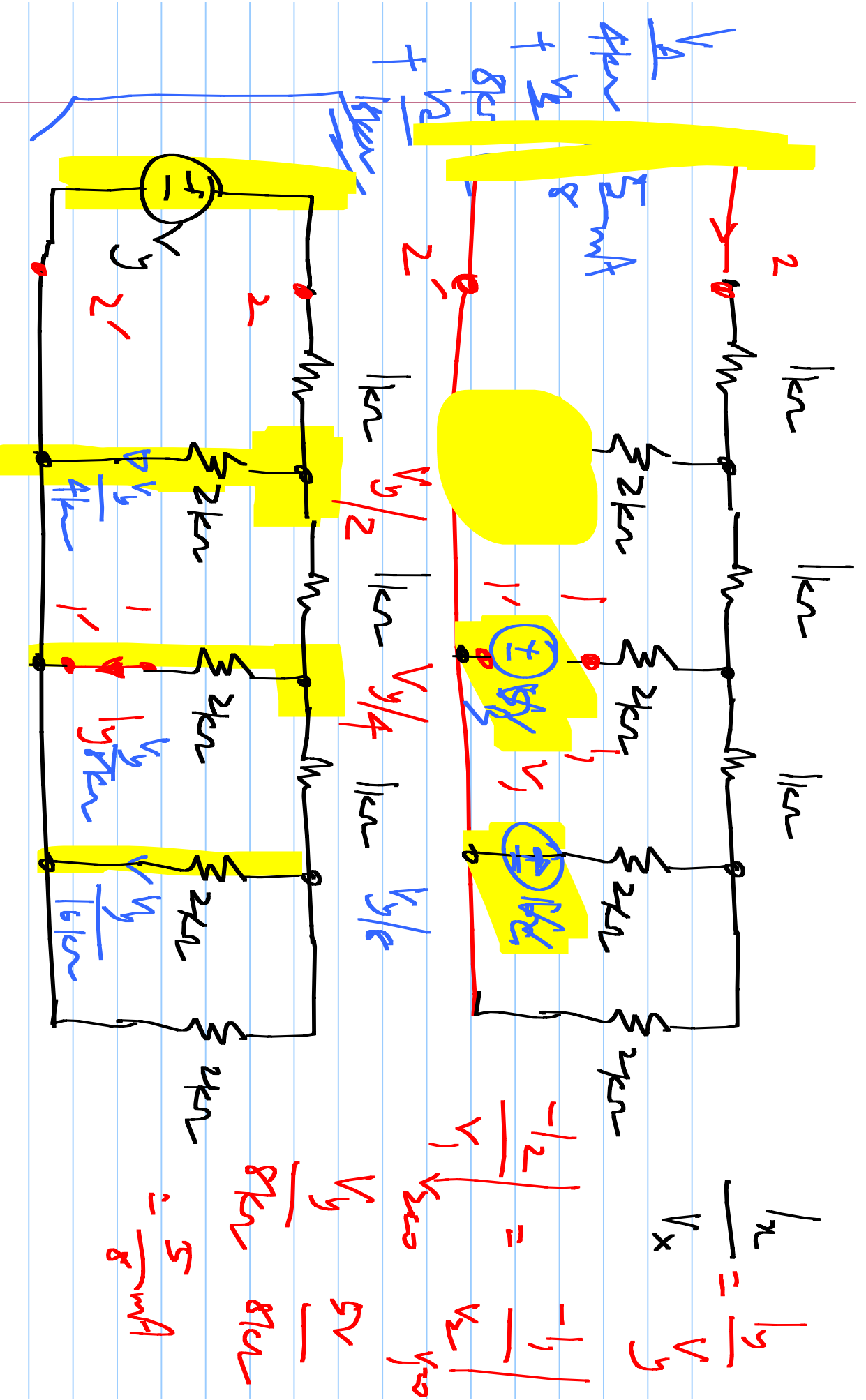

$$Z_{12} = Z_{21}$$

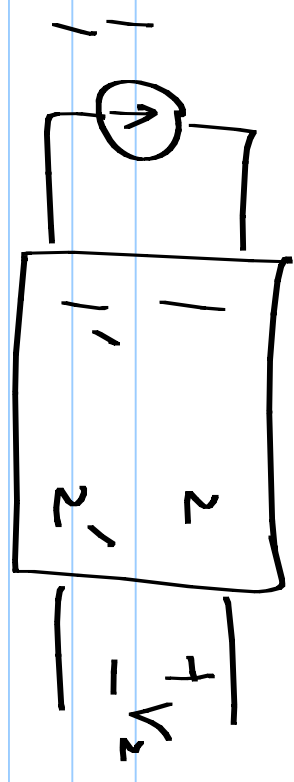


$$Z_{12} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

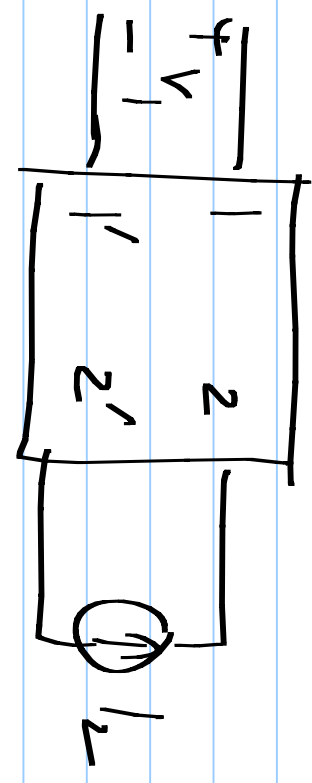


$$Z_{21} = \frac{V_1}{I_2} \Big|_{I_1=0}$$

$$h_{12} = -h_{21}$$

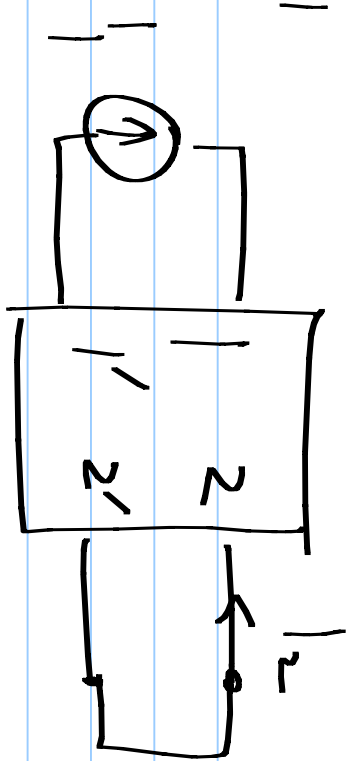

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$


short ckt current gain from 1 → 2

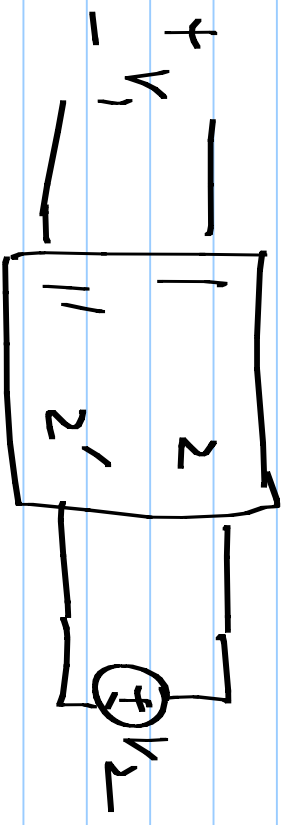

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

open circuit- voltage gain from 2 → 1


$$g_{12} = -g_{21}$$

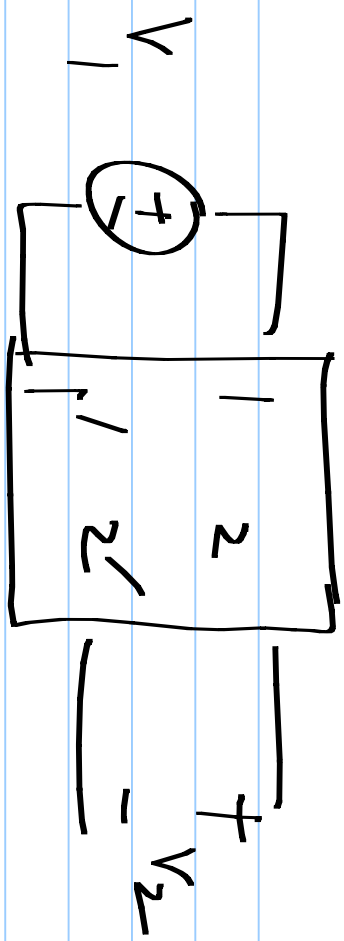

$$\frac{V_2}{V_1}$$

open circuit

voltage gain from 1 → 2

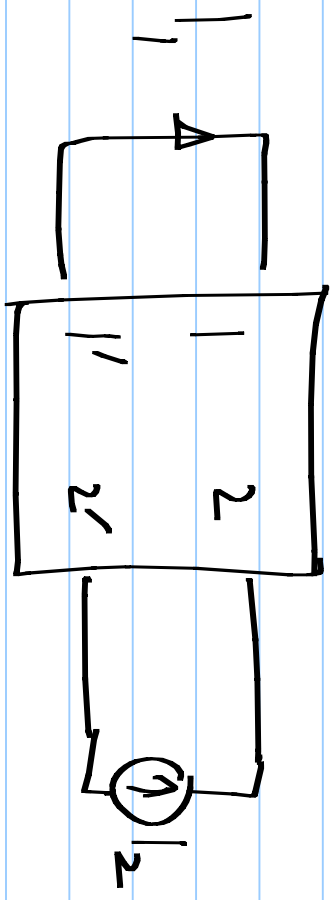


$$\frac{I_2}{I_1} \quad V_1 = 0$$

S.C. current


gain from 2 → 1

Resistive 2-ports are reciprocal
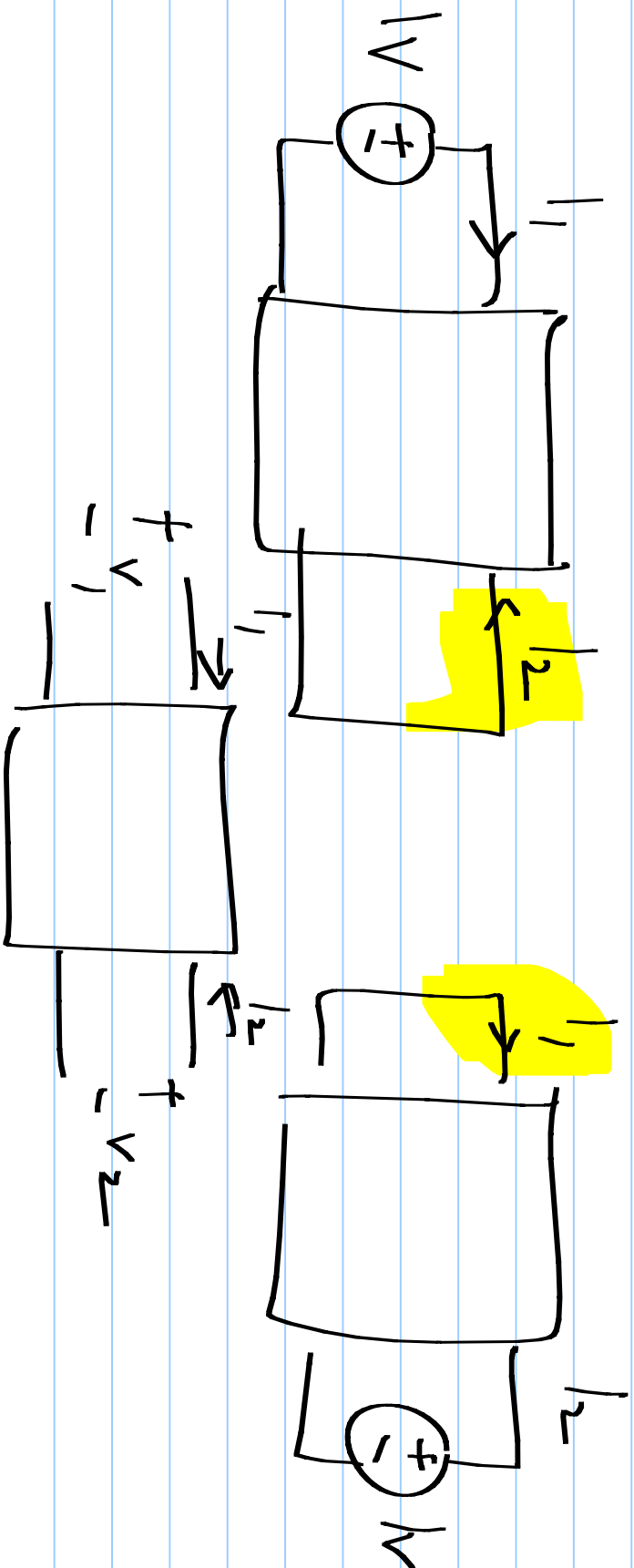
$$y_{12} = y_{21} ; z_{12} = z_{21} ; h_{12} = -h_{21} ; g_{12} = -g_{21}$$



Controlled Sources


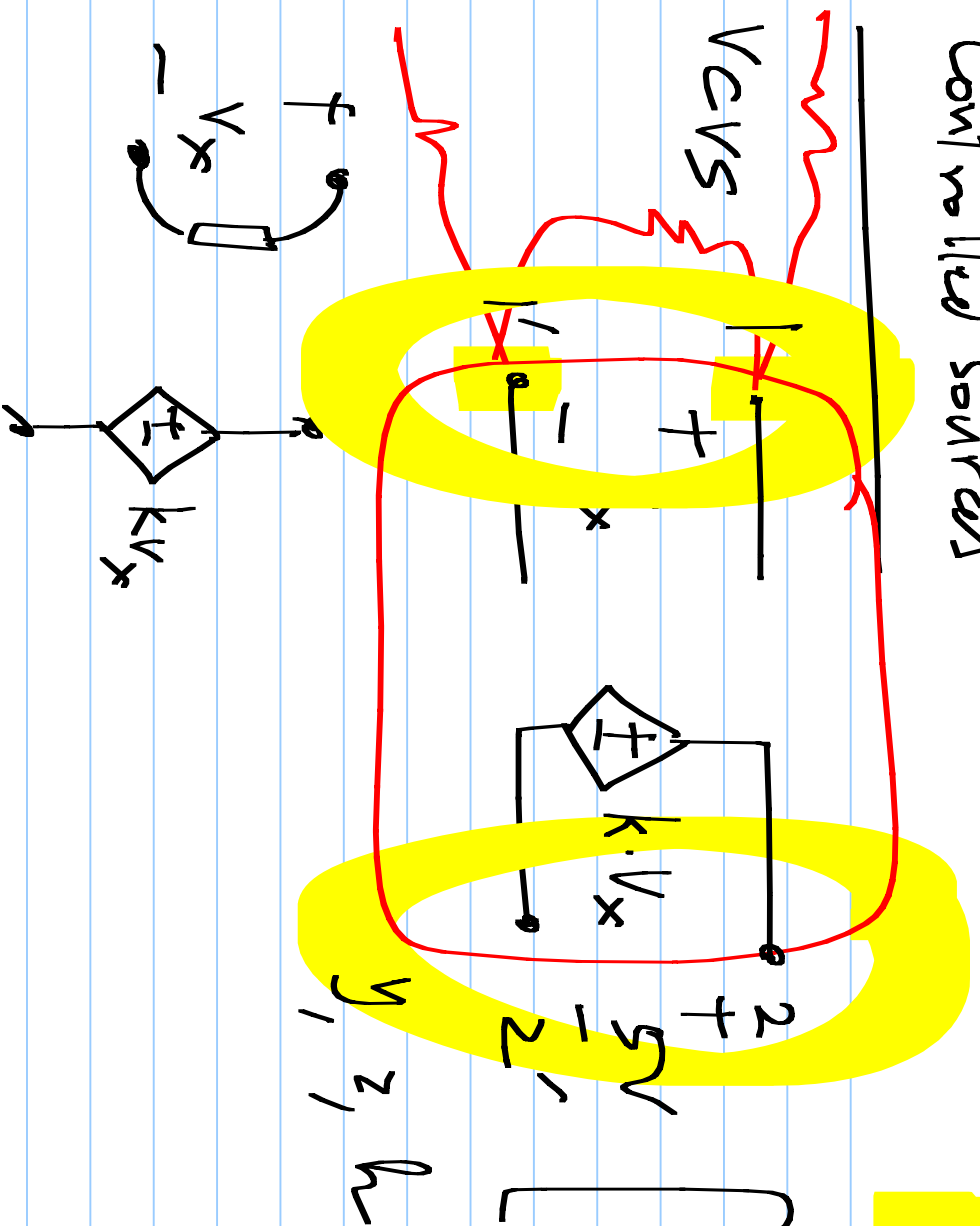


$$V_2 = k \cdot V_1$$

$$\begin{bmatrix} 1 \\ 1 \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ k & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

y_1, z_1, h

VCCS:

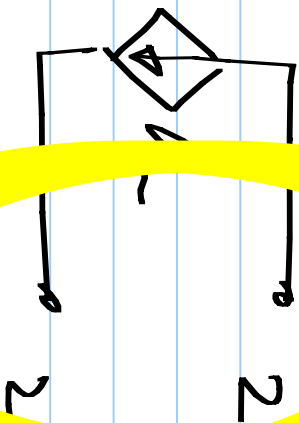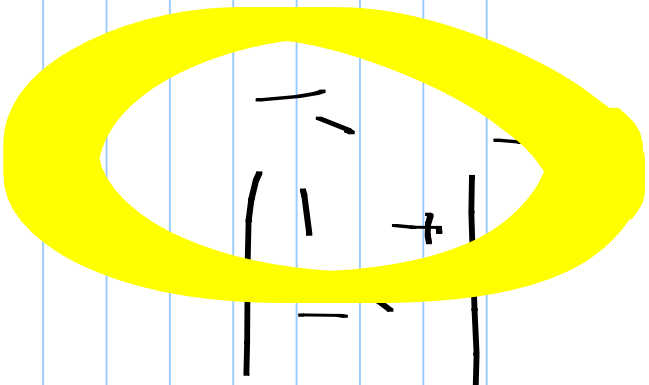

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ G_m & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$