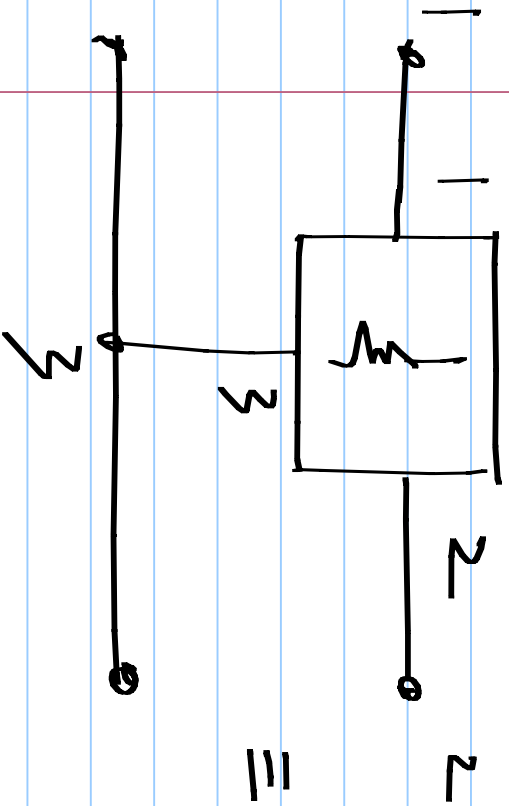


EE 2015




Π-network

11/9/2017

$-y_{12}$


Δ-network

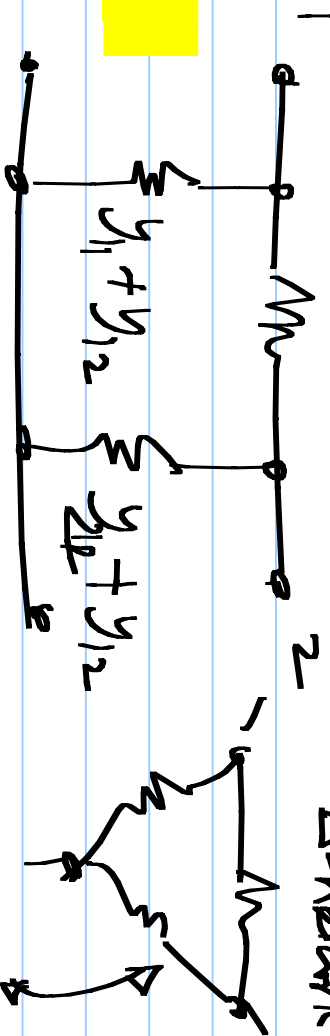


T-network

star-network


≡

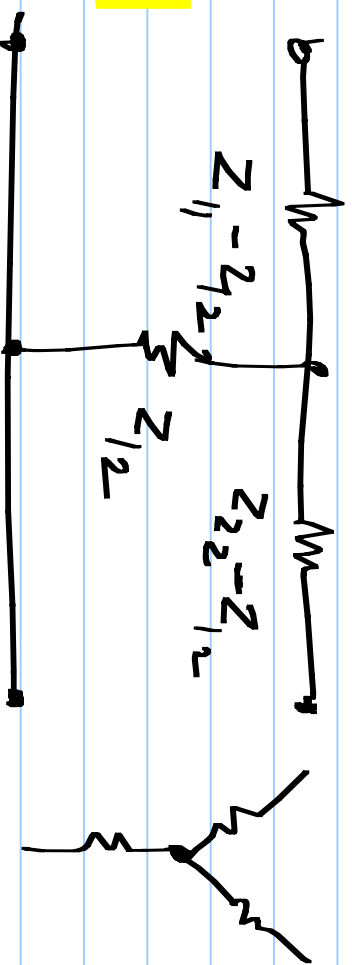


Makes $[y]$ or $[z]$ asymmetric

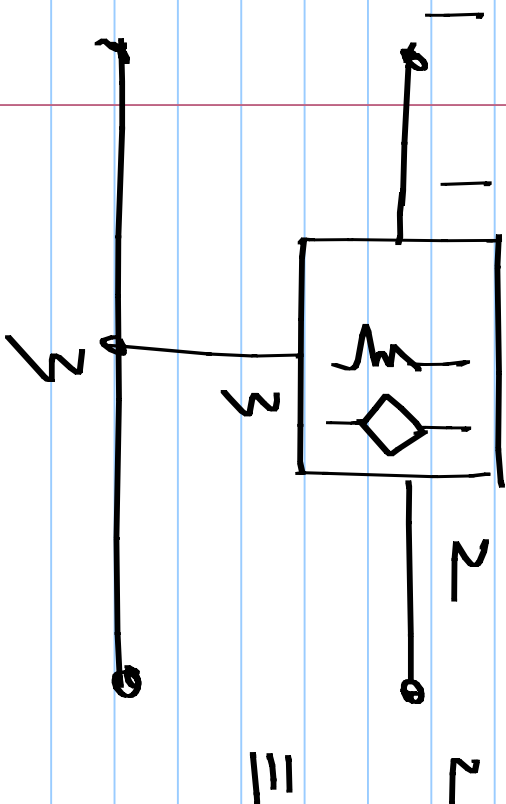
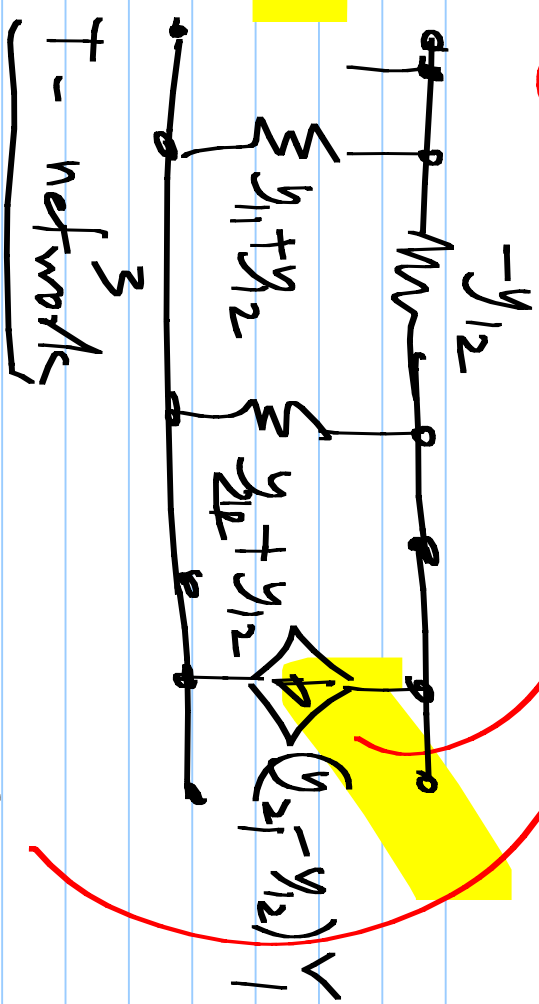
$$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \equiv$$



T-network

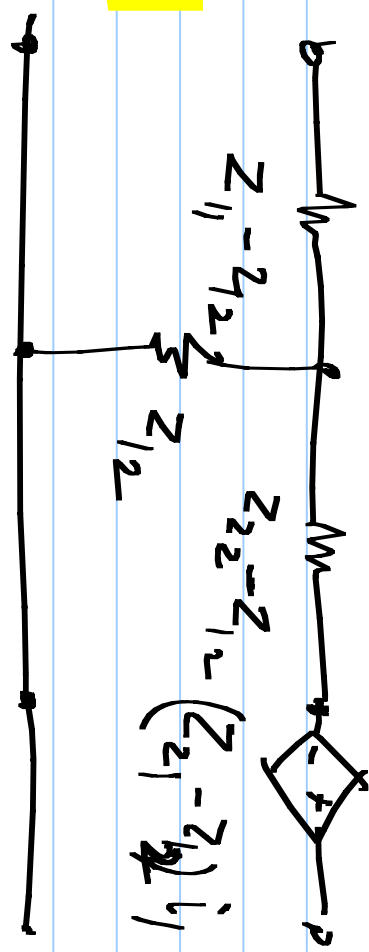

Star \longleftrightarrow Delta


$R_{12}, R_{23}, R_{31} \longleftrightarrow R_1, R_2, R_3$

$$R_{12} = \frac{1}{\frac{1}{Z_{11}Z_{22}} - \frac{1}{Z_{12}}} = \frac{Z_{12}}{-Y_{12}}$$

$$R_{23} = \frac{R_1}{(R_1 + R_3)(R_2 + R_3) - R_3}$$

$$= \frac{R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

$$\frac{R_3}{R_2 R_1 + R_3 R_1}$$

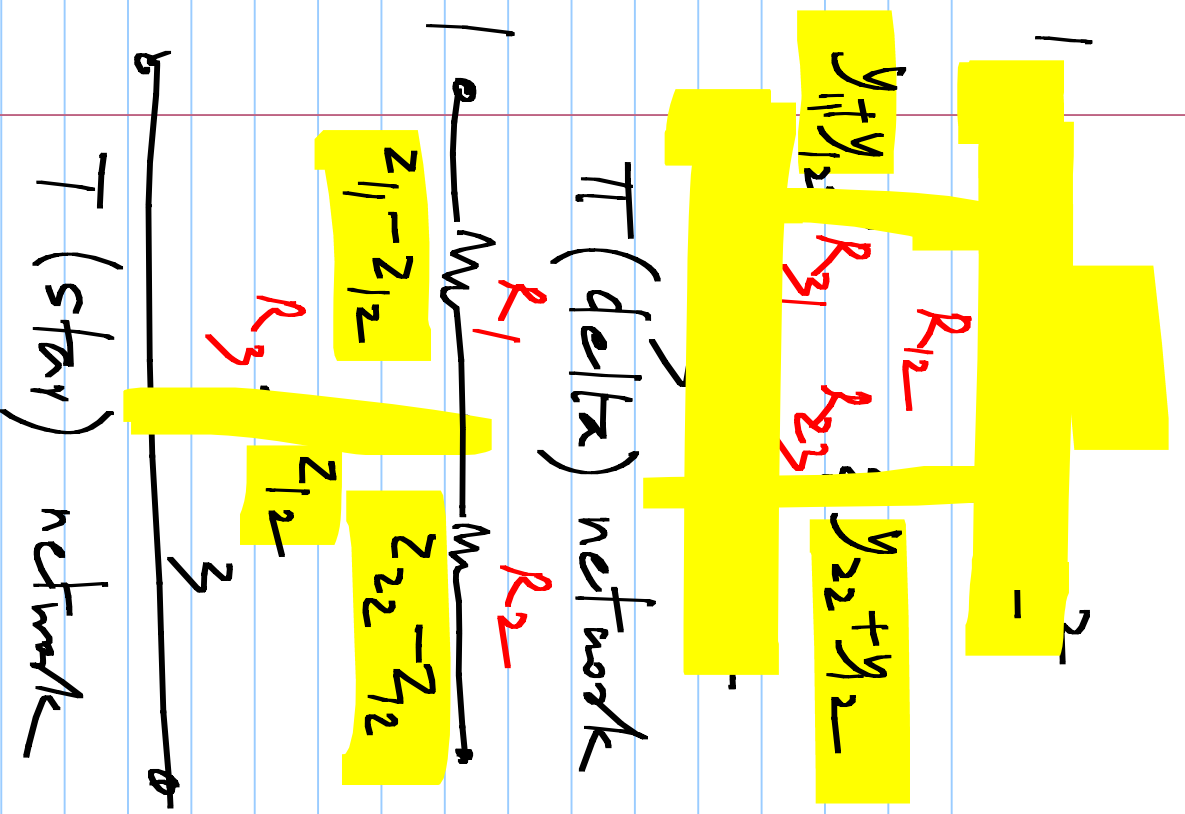

Star \rightarrow Delta

$$R_{12} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_{23} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$


$$R_3 = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_3 = Z_{12} = \frac{-y_{12}}{y_{11} y_{22} - y_{12}^2}$$

$$= \frac{(1/R_{12})}{\left(\frac{1}{R_{12}} + \frac{1}{R_{13}}\right) \left(\frac{1}{R_{12}} + \frac{1}{R_{23}}\right) - \left(\frac{1}{R_{12}}\right)^2}$$

$$= \frac{1/R_{12}}{\frac{1}{R_{13}} \cdot \frac{1}{R_{12}} + \frac{1}{R_{12}} \cdot \frac{1}{R_{23}} + \frac{1}{R_{12}} \cdot \frac{1}{R_{12}}}$$

Original circuit - solution: available

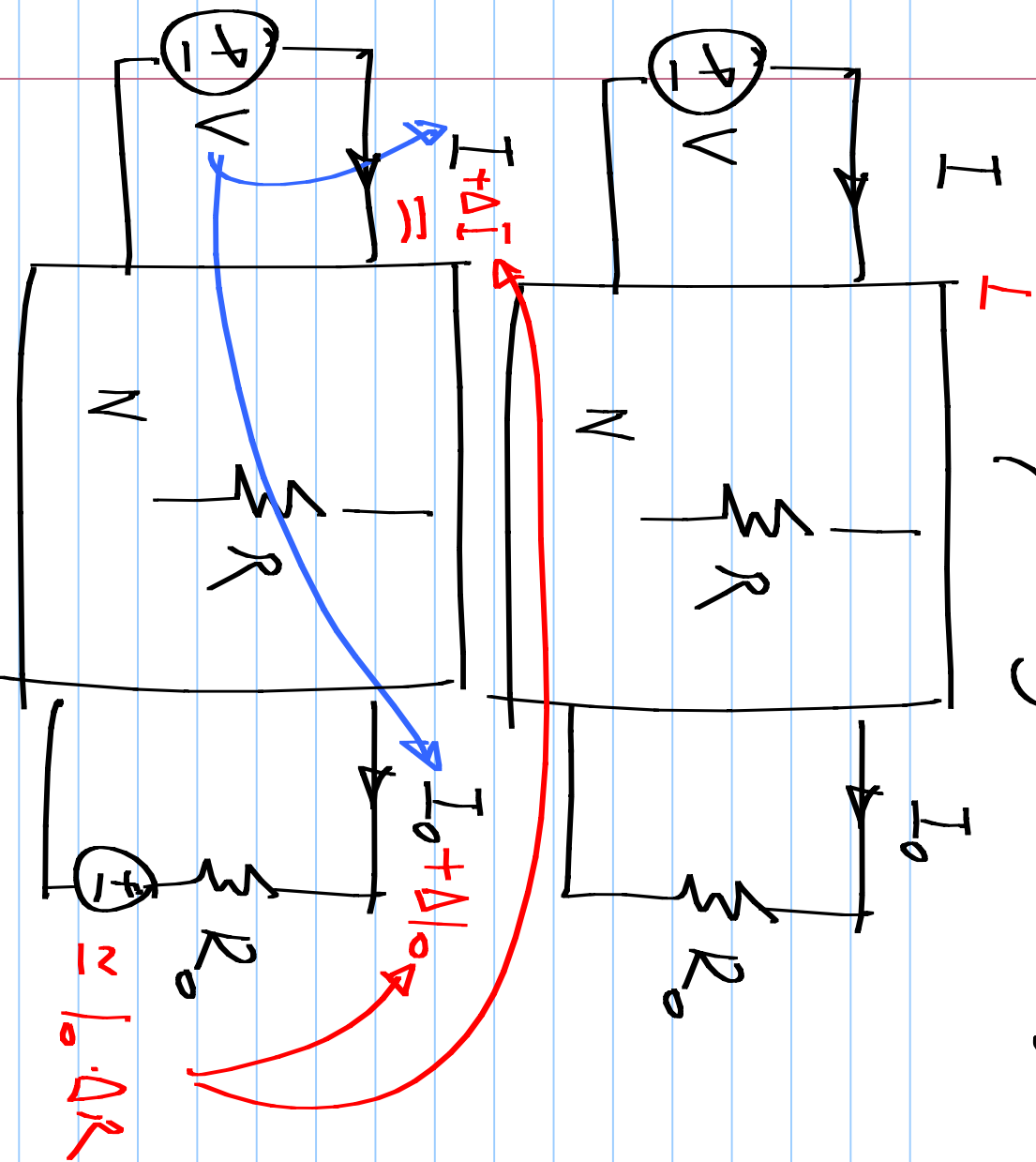


substitution

theorem

Approximation

Reciprocity


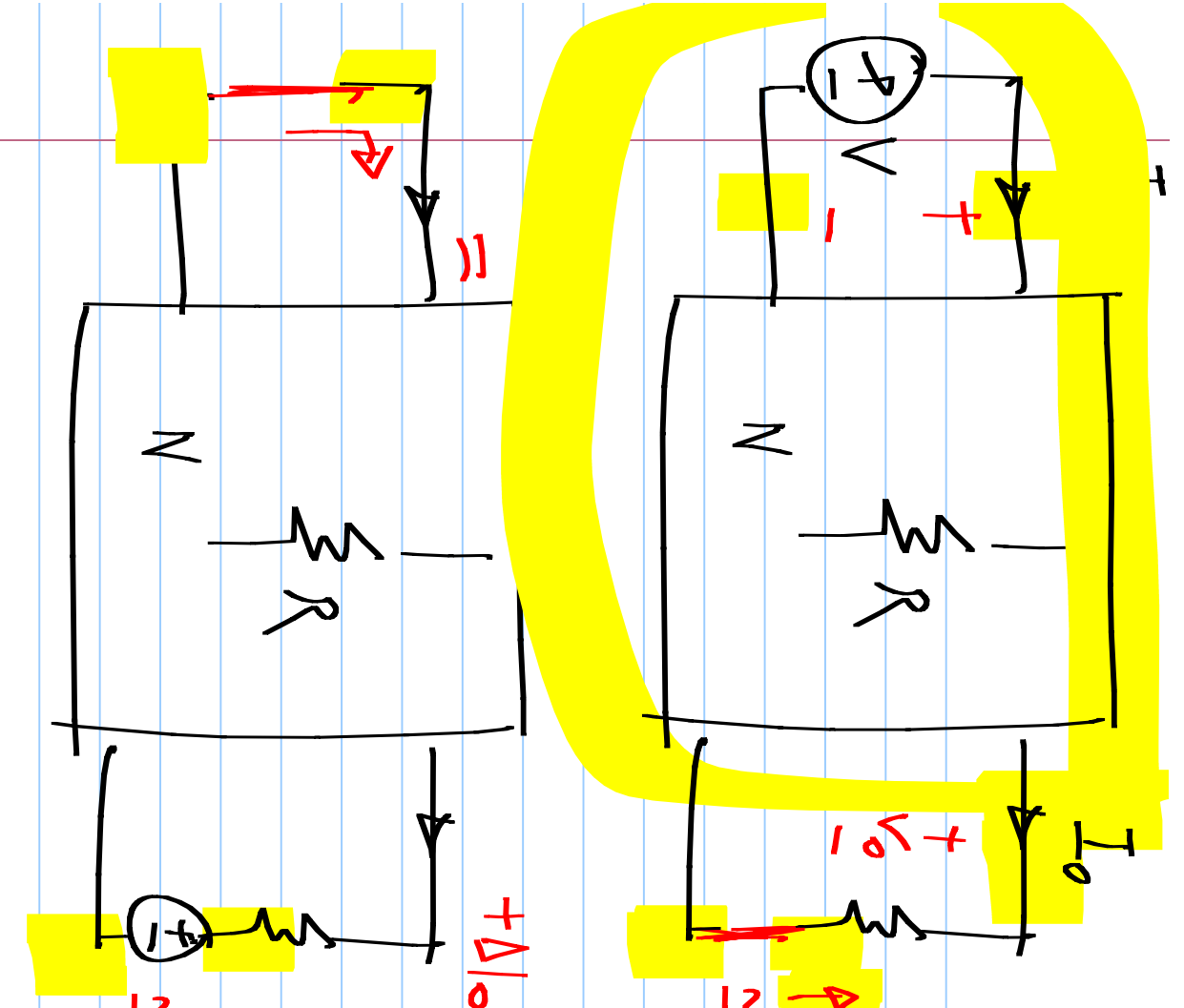


$$2 \cdot \frac{1}{10} \cdot \Delta R$$

$$+\Delta I_0$$

$$2 \cdot \frac{1}{10} \cdot \Delta R$$

$$-\frac{1}{10} V$$

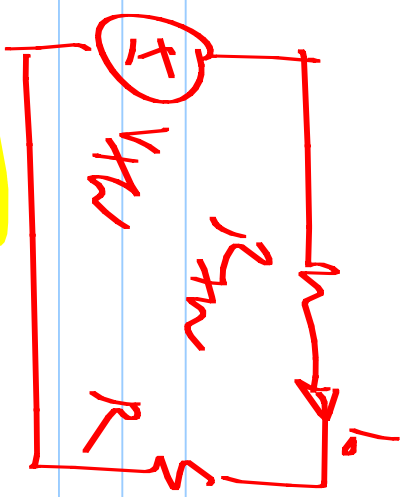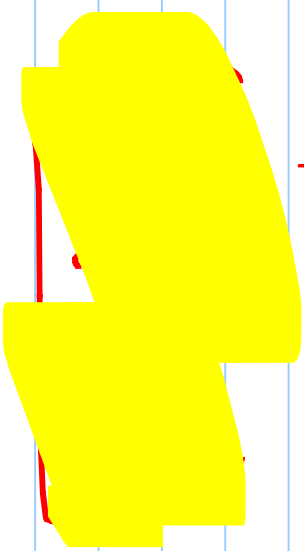

$$\Delta I = -\frac{1}{10} V$$

$$\Delta I = -\frac{1}{10} \cdot \Delta R$$