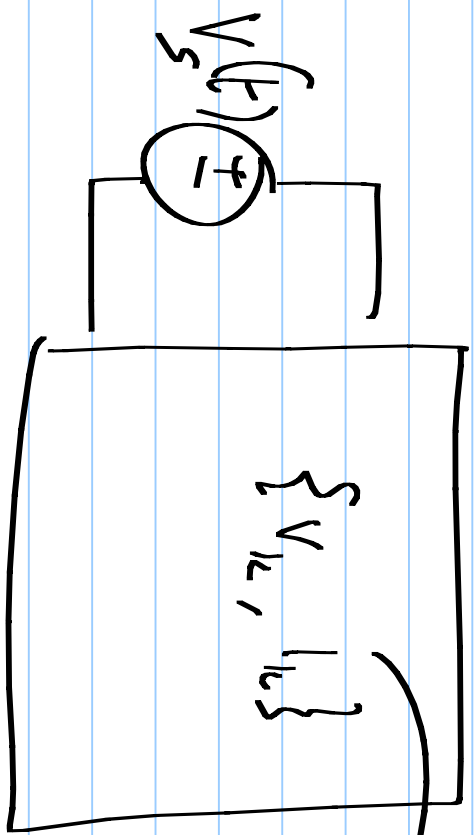


EE 2015

Memoryless circuit


$(V, I, R, \text{const. sources})$

15/9/2017



$$\frac{(\quad) \cdot V_s(t)}{}$$


Circuits with memory elements L, C

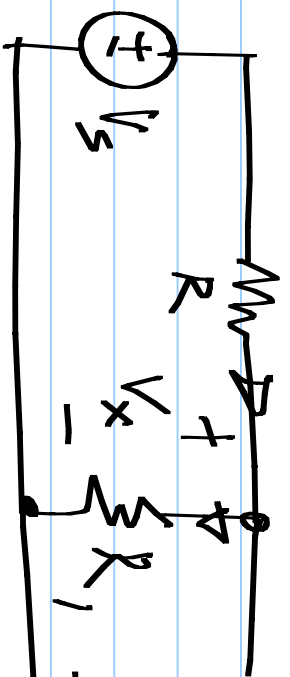

$$\frac{V_x}{R} = \frac{V_s - V_x}{R_1}$$

algebraic eq.


$$\frac{R_1}{R+R_1} V_s$$

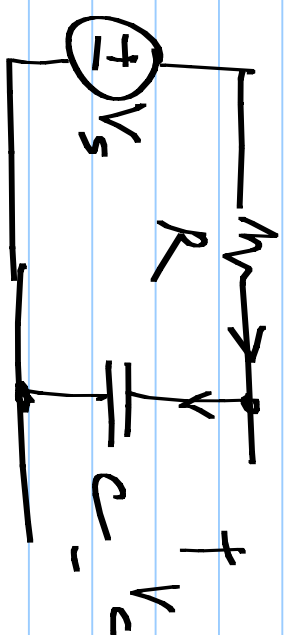

$$C \frac{dV_c}{dt} + \frac{V_c}{R} = \frac{V_s}{R}$$

differential eq.

$$RC \frac{dV_c}{dt} + V_c = V_s$$

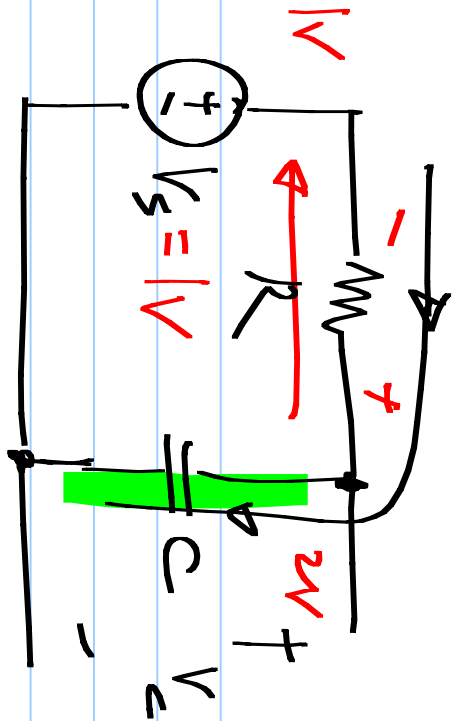



Find $V_C(t)$, $t \geq 0$

Need to specify the

V_S : constant $i_C = \frac{V_S}{R} = C \frac{dV_C}{dt}$ initial state of the memory element

$V_C(0^-) = 0V$

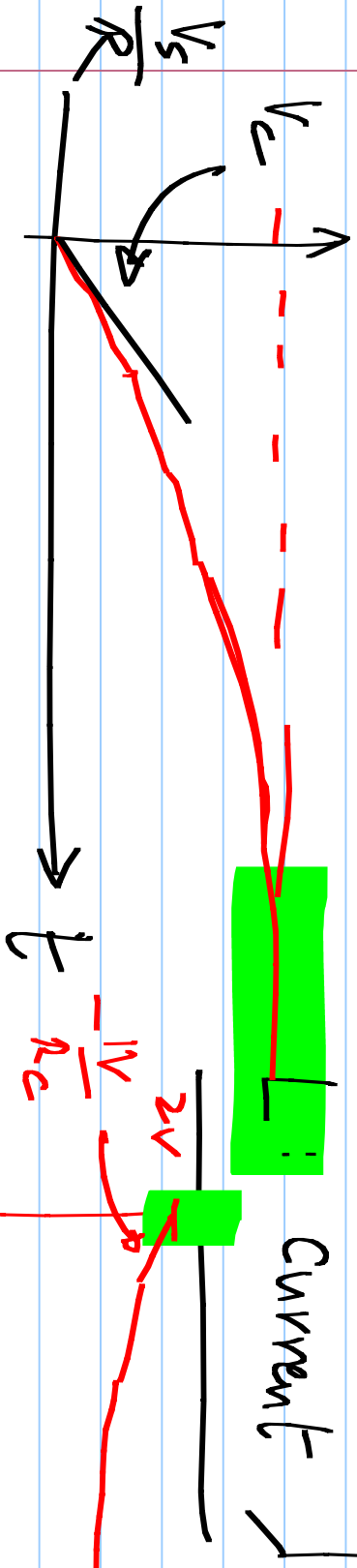

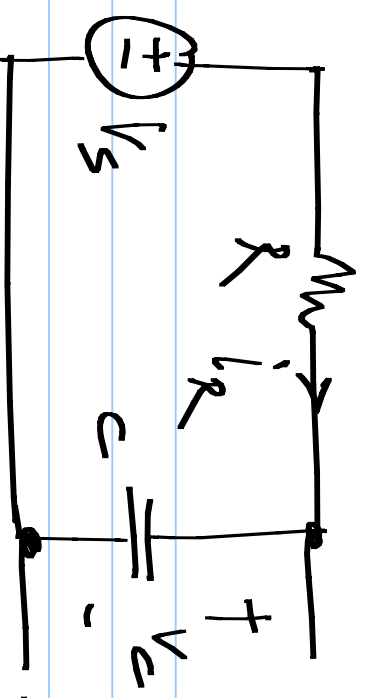

$$V_c(0^-) = 0V$$

$$V_s = 1V$$

