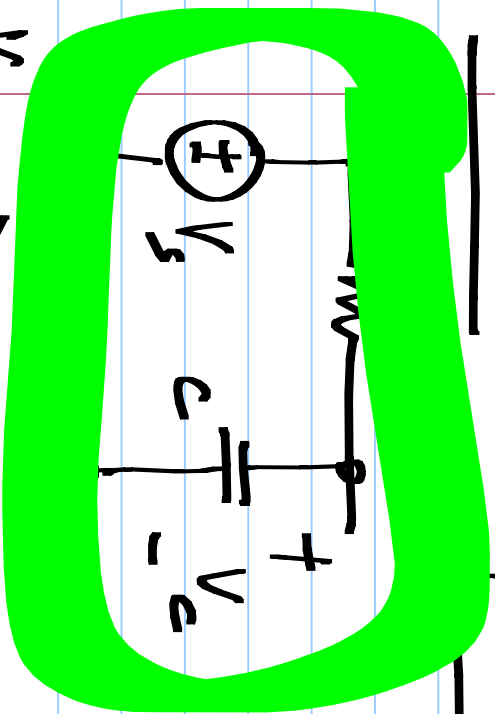


EE 2015

Circuits with $L, C(R)$

27/9/2017



→ Differential equations

$$RC \cdot \frac{dV_c}{dt} + V_c = V_s$$

$$V_s = 0 \Rightarrow$$

homogeneous eq.

$$a_N \frac{d^N V_c}{dt^N} + a_{N-1} \frac{d^{N-1} V_c}{dt^{N-1}} + \dots + a_1 \frac{dV_c}{dt} + a_0 V_c$$

(Natural response)

$$= V_s$$

Forced / steady-state response

Natural response

V_s : constant

$$V_s + (V_c(0) - V_s) \exp(-t/\tau_c)$$

$$1 + V_0 \cdot \exp(st)$$

Zero-state

Depends on initial conditions & input - Zero-input response

$$V_s (1 - \exp(-t/\tau_c)) + V_c(0) \exp(-t/\tau_c)$$

Input: $V_s = V_p$

$$V_c = H \cdot \exp(st)$$

Forced response to $V_p \exp(st)$ is $H V_p \exp(st)$

$$RC \cdot H \cdot s \exp(st) + H V_p \exp(st) = V_p \cdot \exp(st)$$


$$H = \frac{1}{1 + sCR} \left(a_N \cdot \frac{d^N V_c}{dt^N} + a_{N-1} \frac{d^{N-1} V_c}{dt^{N-1}} + \dots + a_1 \frac{dV_c}{dt} + a_0 V_c \right)$$
$$+ (a_1 s + a_0) H = 1 = V_s$$

Response to $\cos(\omega t + \phi)$ Real part of [response

$$\left[H(j\omega) \cdot \cos(\omega t + \phi + \angle H(j\omega)) \right]$$

Steady-state response to $\exp(st)$: $H(s) \cdot \exp(st)$

$$\begin{aligned} \text{"} \\ \exp(j(\omega t + \phi)) &: \underbrace{H(j\omega)} \exp(j(\omega t + \phi)) \\ \exp(j\phi) \cdot \exp(j\omega t) &: \underbrace{|H(j\omega)| \exp(j(\omega t + \angle H(j\omega)))} \end{aligned}$$

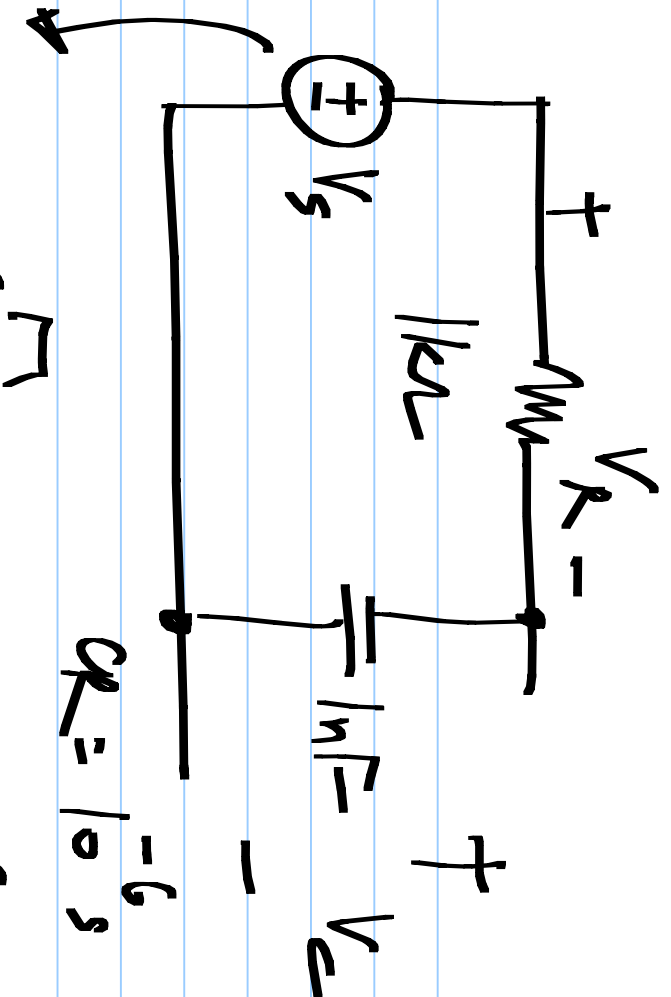

Find V_C & V_R

$$H_C(j\omega) = \frac{1}{1 + j\omega CR}$$

$$2V \cos(\omega_b t) = 2V \cos(2\pi f_b t)$$

$$\omega_b : 2 \cdot 10^6 \text{ rad/s}$$

$$f_0 = \omega / 2\pi$$

$$1 + j 2 \cdot 10^6 \cdot 10^{-6}$$

$$= \frac{1}{1 + j2} = \frac{1}{\sqrt{5}} \angle -63^\circ$$

$$2V \cos(2 \cdot 10^6 t) \rightarrow 0.89V \cdot \cos(2 \cdot 10^6 t)$$

$$V_R = V_S - V_C \quad R_C \cdot \frac{dV_C}{dt} \quad -63^\circ$$

[1.1 rad]

$$R_C \frac{dV_C}{dt} + V_C = V_S \quad V_R = V_S - V_C$$

$$R_C \frac{dV_S}{dt} - R_C \frac{dV_R}{dt} + V_S - V_R = V_S \quad V_C = V_S - V_R$$


$$R_C \cdot \frac{dV_R}{dt} + V_R = V_R \cdot R_C \frac{dV_S}{dt}$$

$$RC \cdot \frac{dV_R}{dt} + V_R = V_R C \frac{dV_S}{dt}$$


$$V_S : \exp(j\omega t) ; V_R : H_R \exp(j\omega t)$$

$$RC \cdot j\omega \cdot H_R \cdot \cancel{\exp(j\omega t)} + H_R \exp(j\omega t) = RC \cdot j\omega \cdot \cancel{\exp(j\omega t)}$$


$$H_R = \frac{j\omega RC}{1 + j\omega RC} = \frac{j^2}{1 + j^2} = \frac{2}{\sqrt{5}} \cdot \angle 27^\circ \quad | \cdot 8V \cos(\omega t + 27^\circ)$$

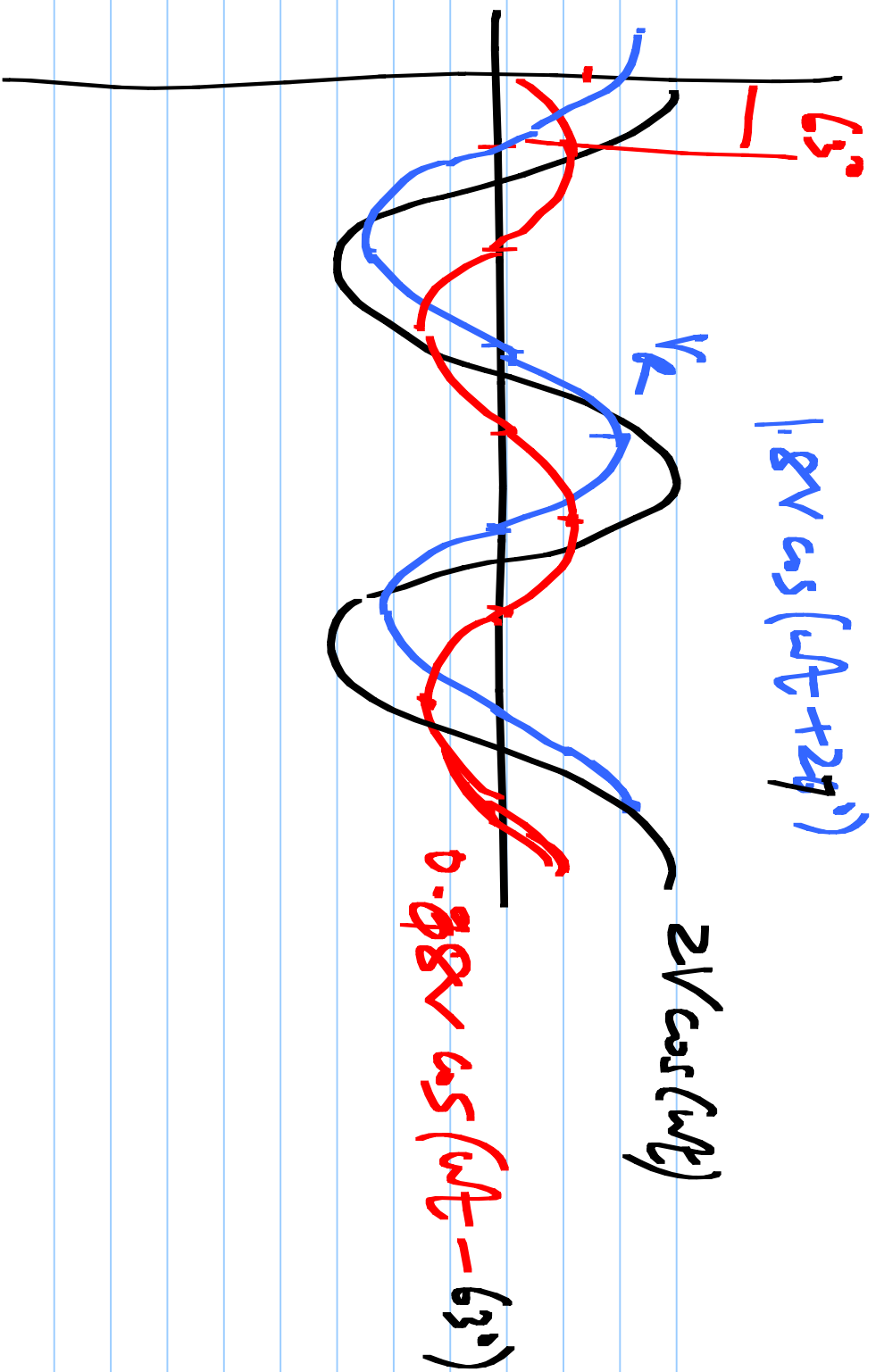


$$V_p \cdot \exp(j\omega t)$$

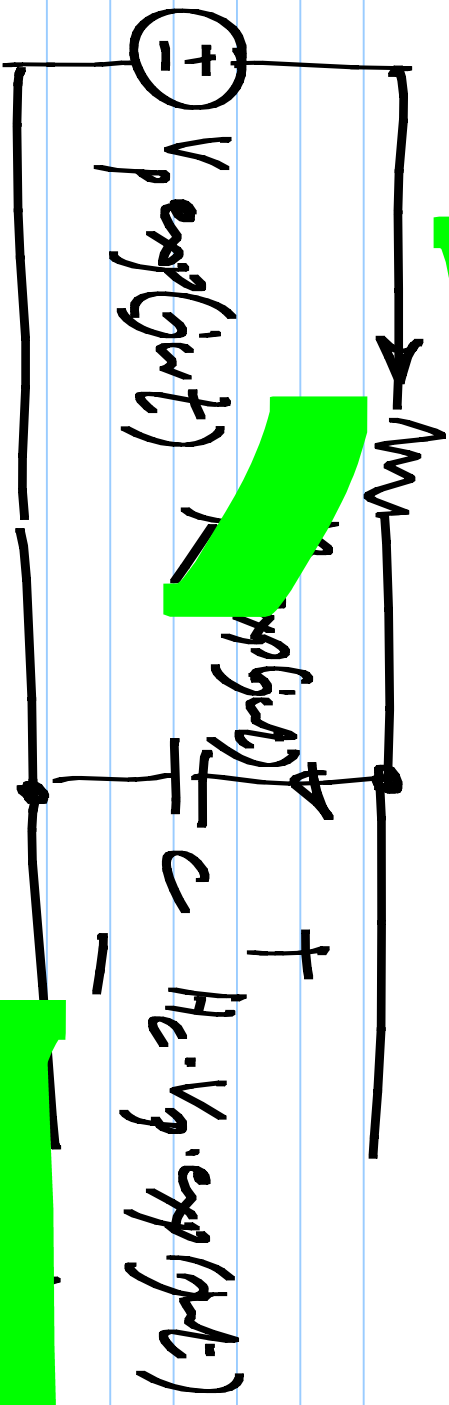

$$V_s = V_p \exp(j\omega t)$$

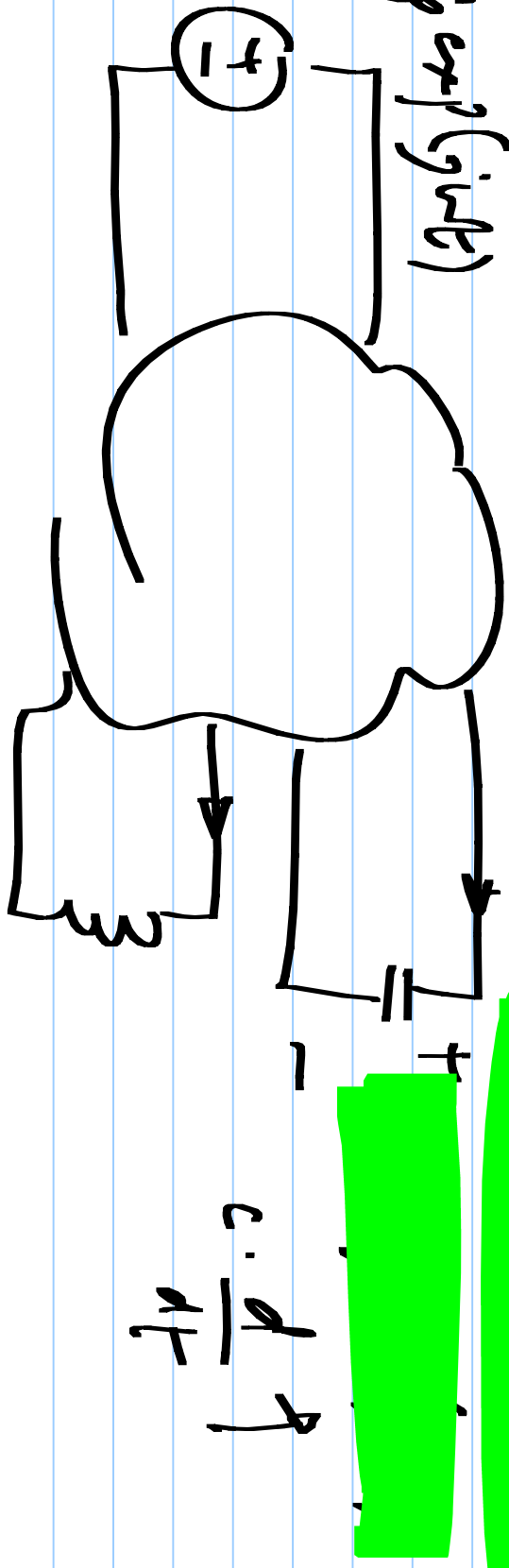

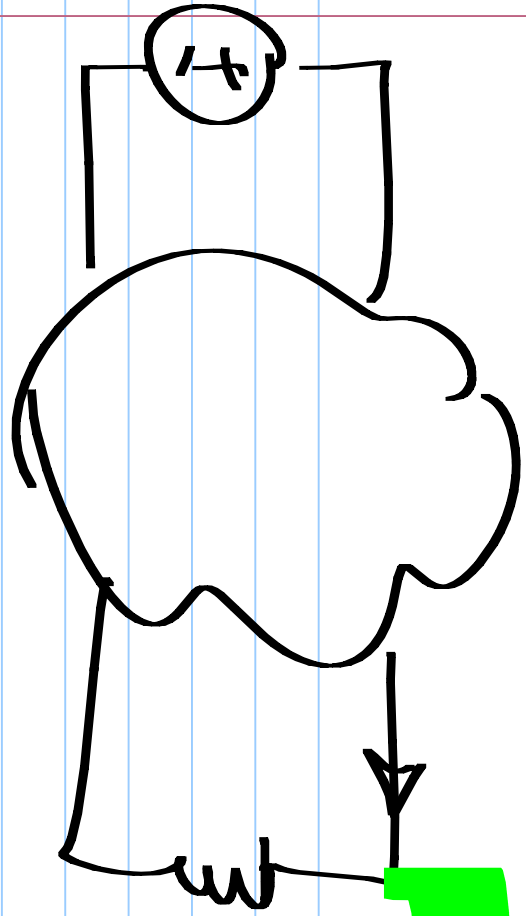

[Redacted]

$L \cdot \frac{d}{dt}$

[Redacted]

[Redacted]