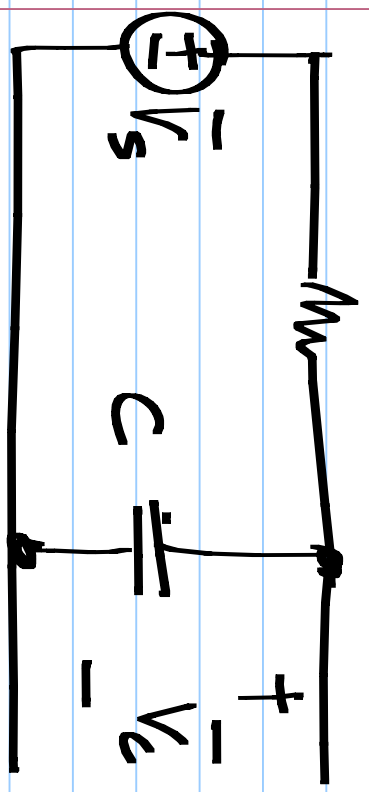


EE 2015 +  $V_R$

$$\left| \frac{V_R}{V_S} \right|$$

4/10/2017




$$H(j\omega) = \frac{V_C}{V_S} = \frac{1}{1 + j\omega RC}$$

$C = 1 \mu F, R = 1 k\Omega$



$$|H(j\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

$\omega RC \ll 1 \quad \approx 1$   
 $\omega RC \gg 1 \quad \approx 1/\omega RC$
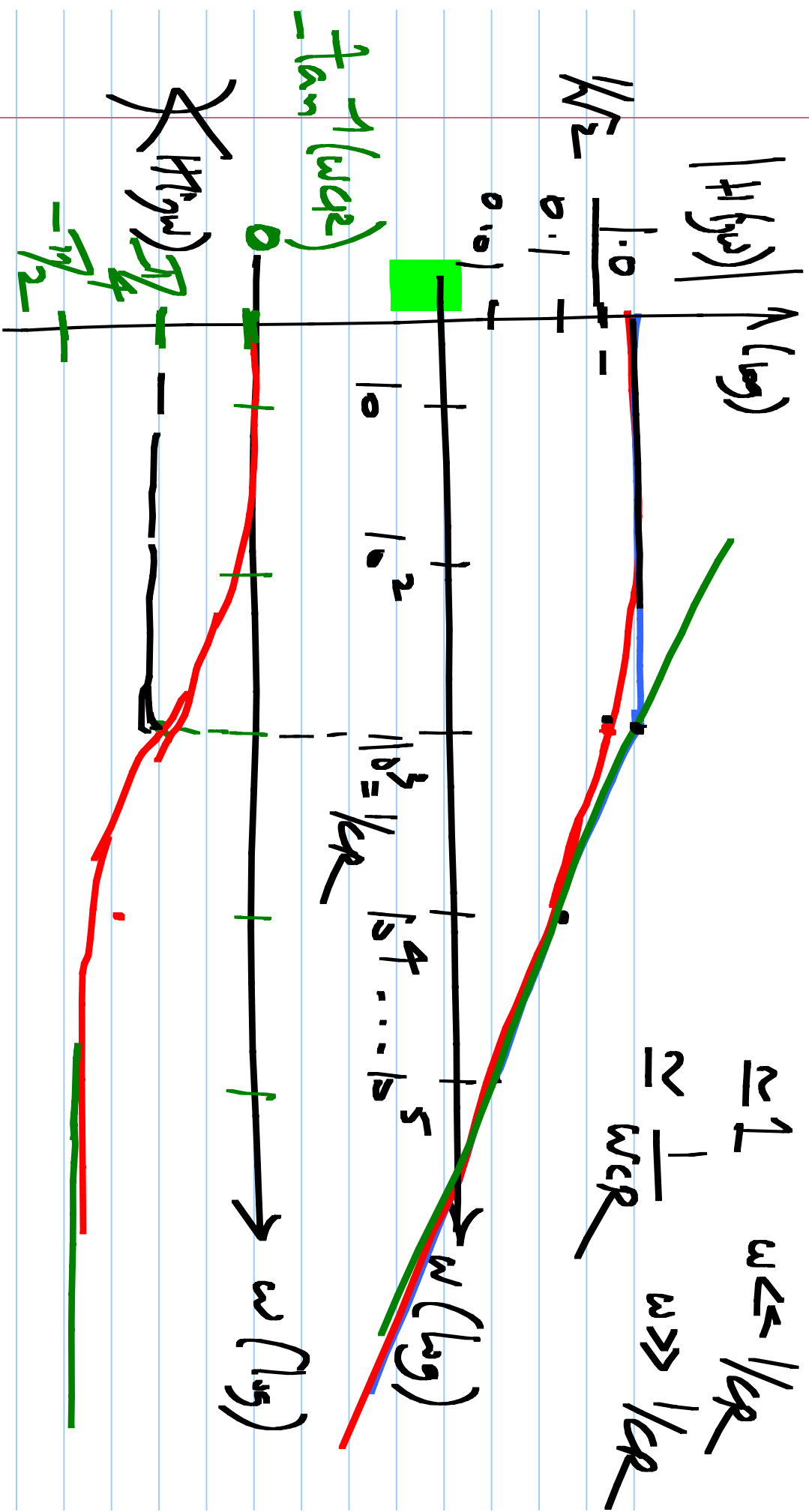
$$\angle H(j\omega) = -\tan^{-1}(\omega RC)$$


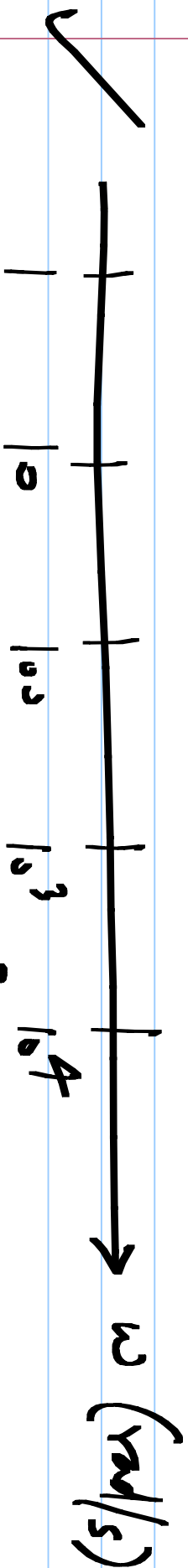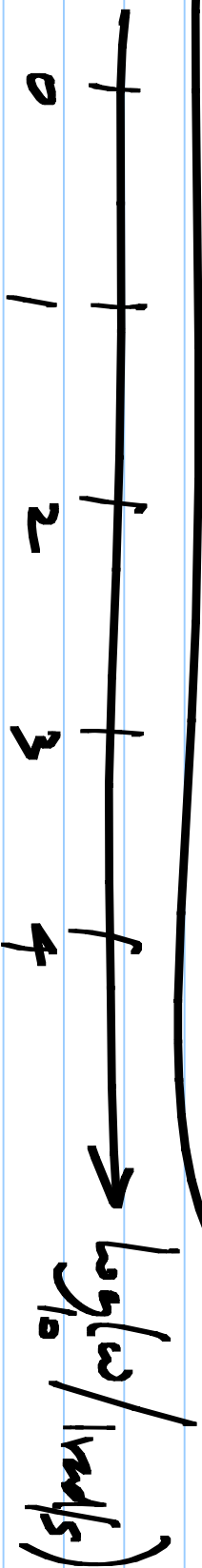
$$-10n^{-1}(x) + 12n^{-1}\left(\frac{1}{x}\right) = \pi/2$$





$$w = 10/cR$$

$$w = 10^3 \cdot 0.1/cR$$

$$12n^{-1}(10) + 12n^{-1}\left(\frac{1}{10}\right) = \pi/2$$
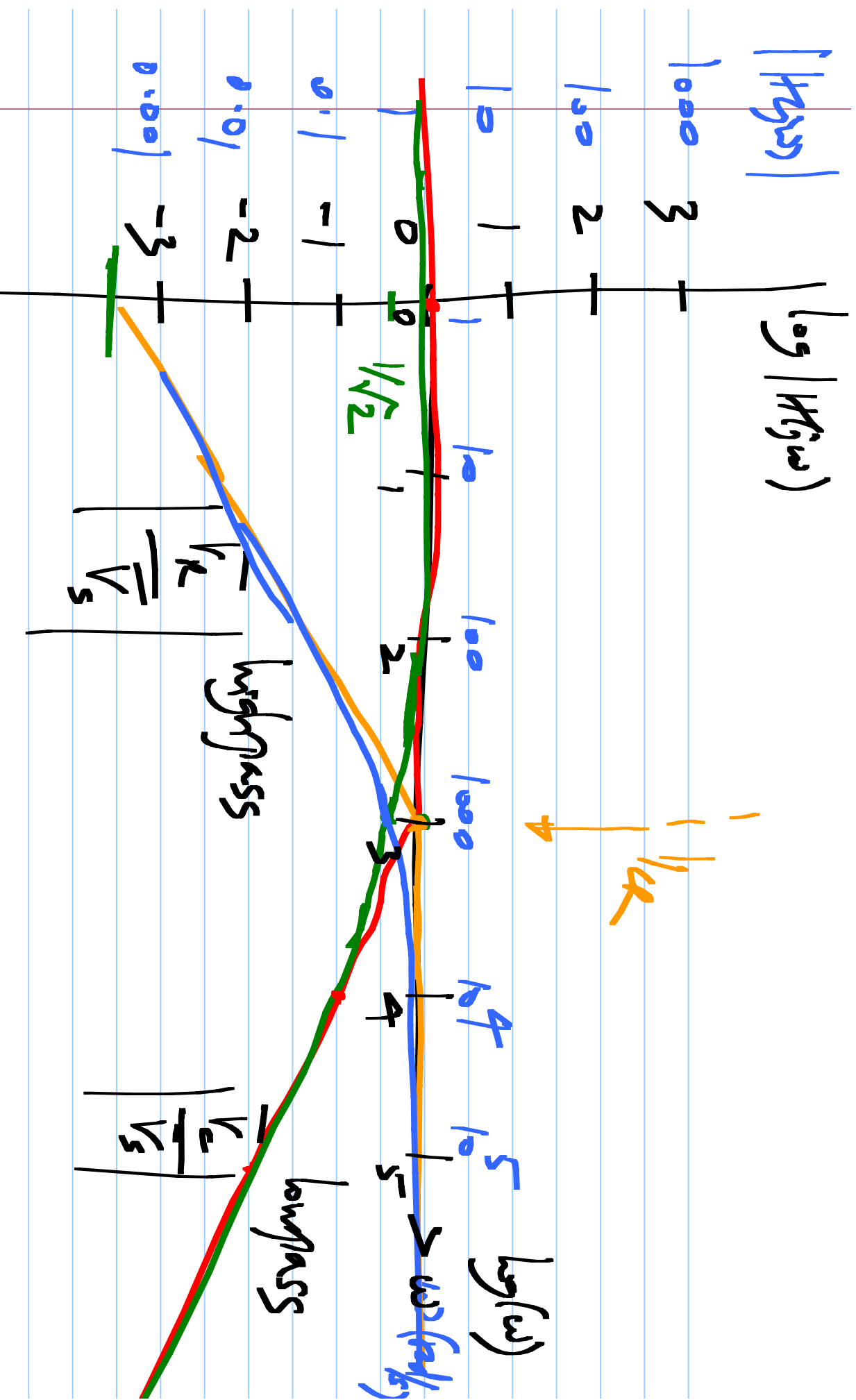
$$12n^{-1}(3) + 12n^{-1}\left(\frac{1}{3}\right) = \pi/2$$



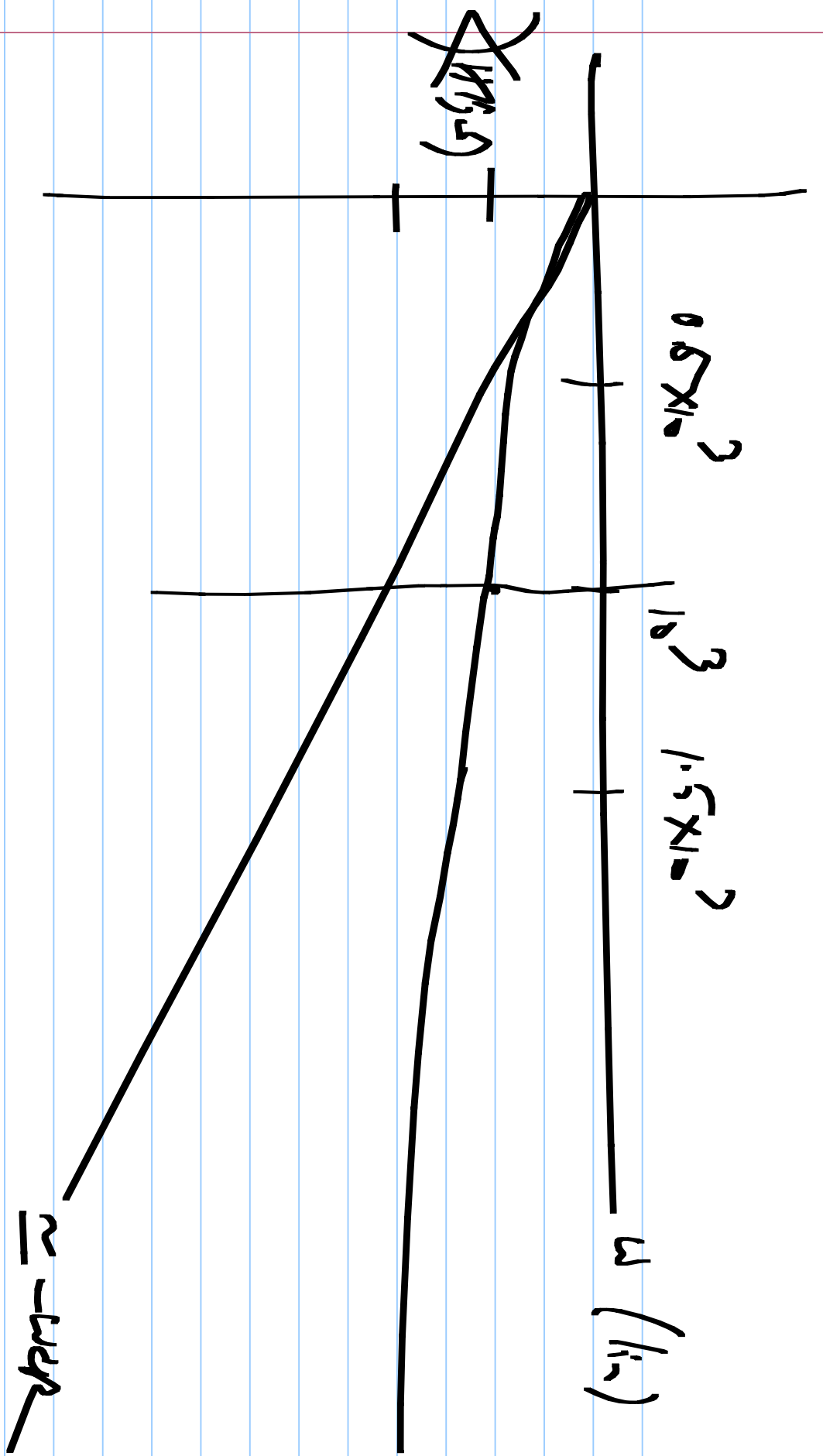


$$\frac{\dot{V}_R}{\dot{V}_S} = \frac{j\omega R}{1 + j\omega R}$$

$$\left| \frac{\dot{V}_R}{\dot{V}_S} \right|$$

$$= \frac{\omega R}{\sqrt{1 + (\omega R)^2}}$$

$\omega \ll 1/R$

$\omega \gg 1/R$

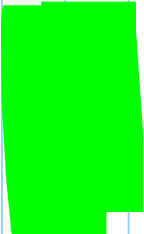


$$3V \sin(10^4 t)$$

$$1V \sin(10 t)$$

$$\rightarrow v_R(t) = 0.01V \sin(10t + \pi/5)$$

$$2V \sin(1000 t)$$

$$v_C(t) = 1V \sin(10t)$$

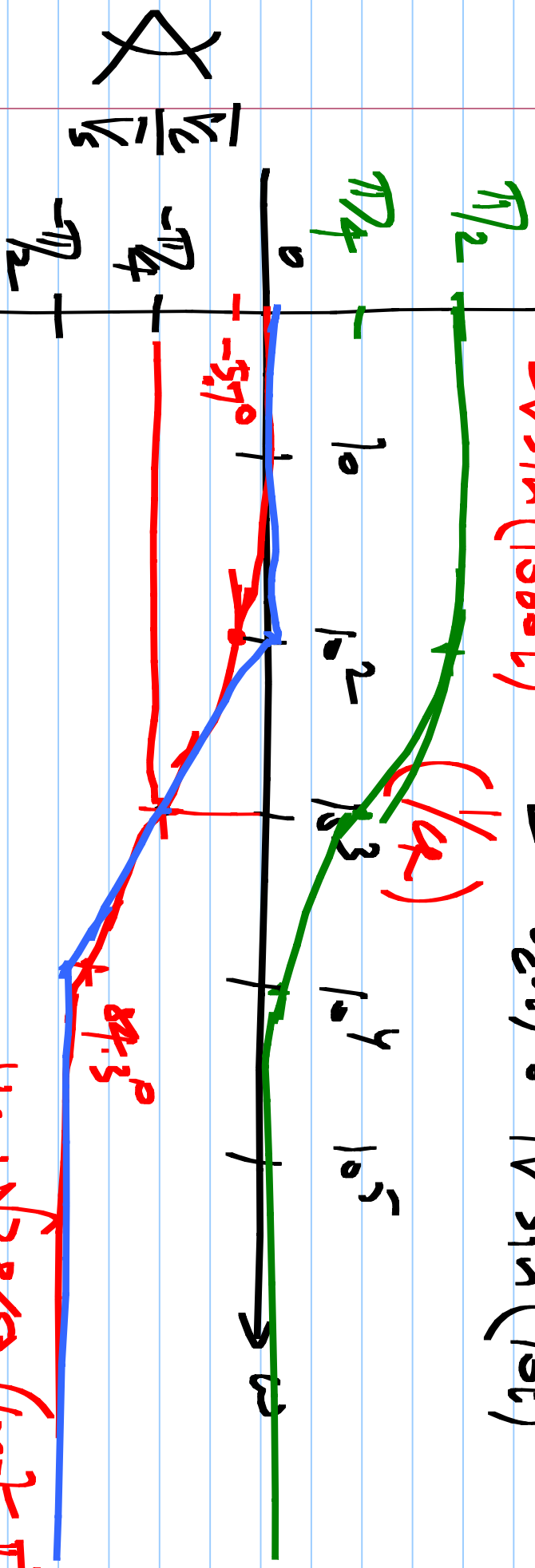

$$\sqrt{\frac{V_C}{V_S}} = \frac{1}{\sqrt{2}} \tan^{-1}(\omega RC)$$

$$v_R = \sqrt{2} V \sin(1000t + \frac{\pi}{4})$$

$$v_C = \sqrt{2} V \sin(1000t - \frac{\pi}{4})$$