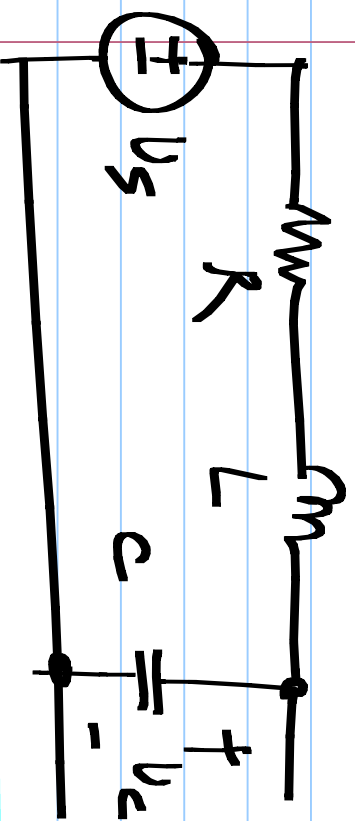



ECE 2015

Second order circuits

10/10/2017


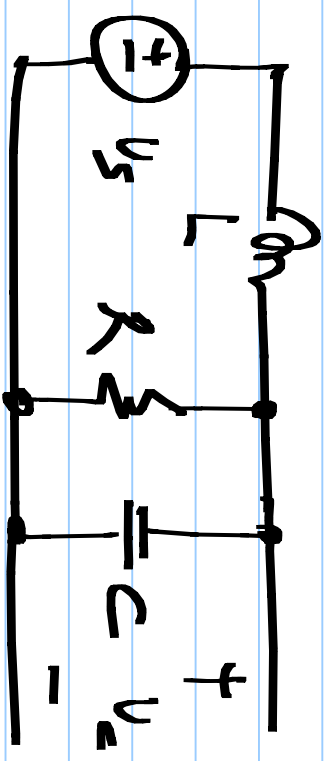
$$LC \frac{d^2 v_c}{dt^2} + RC \frac{dv_c}{dt} + v_c = v_s$$



$$LC \frac{d^2 v_c}{dt^2} + \frac{L}{R} \frac{dv_c}{dt} + v_c = v_s$$

Natural response:

$$LC \cdot \frac{d^2 v_c}{dt^2} + RC \frac{dv_c}{dt} + v_c = 0$$

$$v_c = \underbrace{A \cdot \exp(p t)}$$

$$(LC \cdot p^2 + RC \cdot p + 1) = 0$$

$$p_{1,2} = \frac{-RC \pm \sqrt{RC^2 - 4LC}}{2 \cdot LC}$$

$$LC \cdot \frac{d^2 v_c}{dt^2} + \frac{L}{R} \cdot \frac{dv_c}{dt} + v_c = 0$$

$$LC \cdot p^2 + \frac{L}{R} \cdot p + 1 = 0$$

$$p_{1,2} = \frac{-\frac{L}{R} \pm \sqrt{\frac{L^2}{R^2} - 4LC}}{2 \cdot LC}$$

$$p_{1,2} = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$p_{1,2} = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

Distinct real roots if:

$\underbrace{\exp(p_1 t), \exp(p_2 t)}_{\text{Natural modes}}$

$$p_1, p_2 < 0$$

$$\frac{1}{R^2} \cdot \frac{L}{C} < \frac{1}{4}$$

$\zeta > 1, R < 1/2$
overdamped case

$$R^2 \cdot \frac{C}{L} < \frac{1}{4}$$

$\underbrace{\exp(p_1 t), \exp(p_2 t)}_{\text{Natural modes}}$

Stable
Identical real roots if:

$$\frac{1}{R^2} \cdot \frac{L}{C} = \frac{1}{4}$$

$\zeta = 1, R = 1/2$
critically damped

$$R^2 \cdot \frac{C}{L} = \frac{1}{4}$$

$$p_{1,2} = -\frac{R}{2L}$$

$$p_{1,2} = -\frac{1}{2RC}$$

Complex conjugate

$$\frac{1}{L} \cdot \frac{L}{C} > \frac{1}{4} \quad \text{Series RLC}$$

$$p_1, p_2 = -\sigma \pm j \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$

$$p_1, p_2 = \sigma + j\omega$$

$$A \cdot \exp(\sigma + j\omega \cdot t) + A^* \exp(\sigma - j\omega \cdot t)$$

$$2 \operatorname{Re} (A \exp(\sigma + j\omega \cdot t))$$

$$2 \cdot |A| \cdot \cos(\omega t + \phi_A)$$

parallel RLC


$$R^2 \cdot \frac{C}{L} > \frac{1}{4}$$

$$p_1, p_2 = -\frac{1}{2RC} \pm j \sqrt{\frac{1}{LC} - \left(\frac{1}{2RC}\right)^2}$$

$$\} < 1, \quad R > 1/2$$

underdamped


$\phi = 0$ for $R = 0$

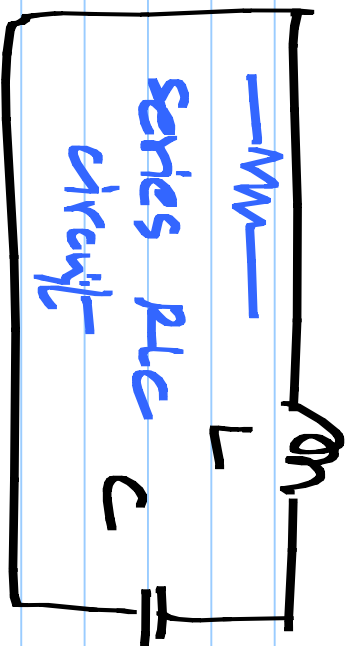

Lossless LC circuit:-
(Resonator)

Natural mode: $\sim \cos\left(\frac{t}{\sqrt{LC}} + \phi\right)$

$\phi = 0$ for $R = \infty$

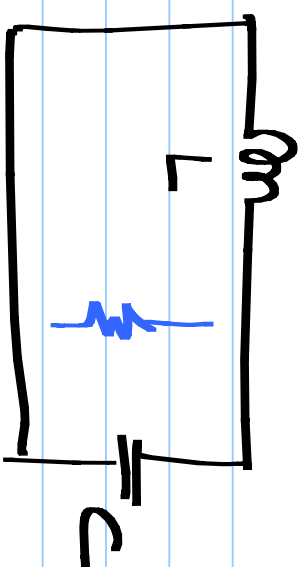

Parallel RLC
circuit:-

$\cos\left(\frac{t}{\sqrt{LC}} + \phi\right)$

Series RLC

ω_n, ζ, α

Char. equation:

$$LC \cdot p^2 + RC \cdot p + 1 = 0$$

$$\frac{p^2}{\omega_n^2} + \dots \cdot p + 1 = 0$$

$$\frac{p^2}{\omega_n^2} + \dots \cdot p + 1$$

$$p^2 + \frac{R}{L} \cdot p + \frac{1}{LC} = 0$$

$$p^2 + 2\zeta\omega_n \cdot p + \omega_n^2 = 0$$

$$p^2 + \frac{\omega_n}{\alpha} \cdot p + \omega_n^2 = 0$$

Parallel RLC

$$LC \cdot p^2 + \frac{L}{R} \cdot p + 1 = 0$$

$$p^2 + \frac{1}{RC} \cdot p + \frac{1}{LC} = 0$$

Series RLC

Natural frequency

$$\omega_n = \frac{1}{\sqrt{LC}}$$

$$\text{Quality factor } Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$\text{Damping factor } \zeta = \frac{R}{2} \sqrt{\frac{C}{L}}$$

Complex conj. roots:

$$R > \frac{L}{2} ; \zeta < 1$$

Parallel RLC

$$\omega_n = \frac{1}{\sqrt{LC}}$$

$$Q = \frac{1}{2\zeta}$$

$$\zeta = \frac{1}{2Q}$$


$$Q = R \sqrt{\frac{C}{L}}$$

$$\zeta = \frac{1}{2R} \sqrt{\frac{L}{C}}$$

Complex conj. roots:

$$R > \frac{1}{2} ; \zeta < 1$$

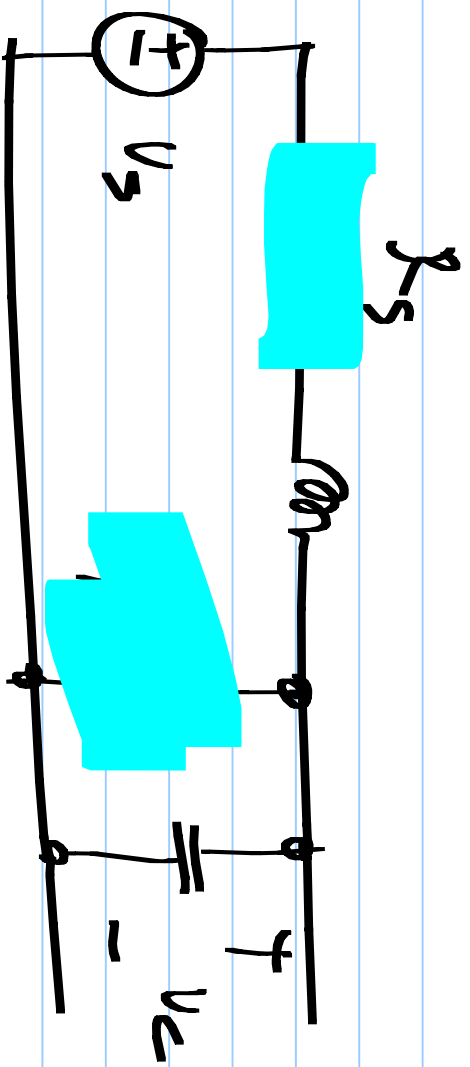$Q = \infty, \zeta = 0$: underdamped system
ideal resonator



$$Q < 1/2, \zeta > 1$$

overdamped

$$Q = 1/2, \zeta = 1$$

crit. damped

$$Q > 1/2, \zeta < 1$$

underdamped

$$Q = \infty, \zeta = 0$$

un damped

