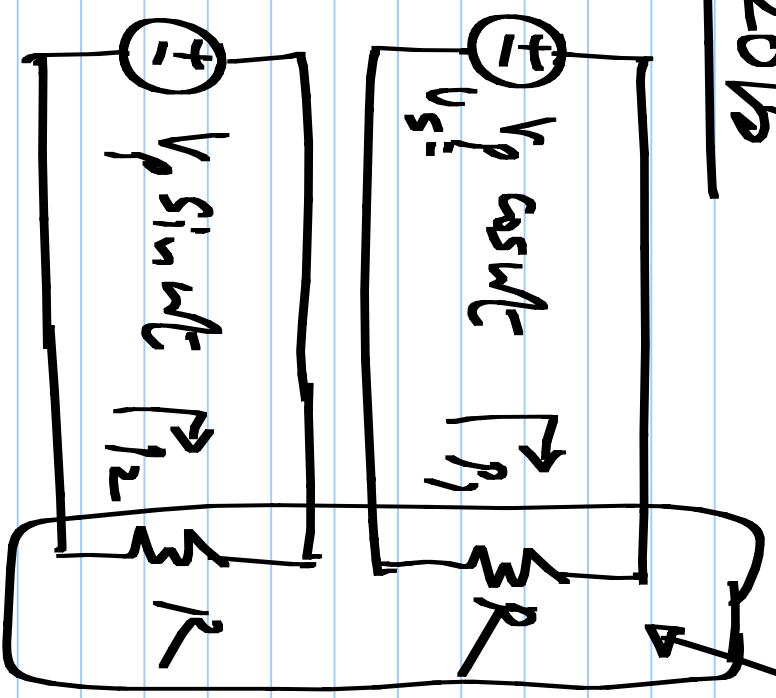


EFE 2015

25/10/2017


$$\underline{V_s} = V_p \angle 0$$




$$p_{tot} = p_1 + p_2$$

$$p(t) = \frac{V_p^2}{2R} (1 + \cos 2\omega t)$$
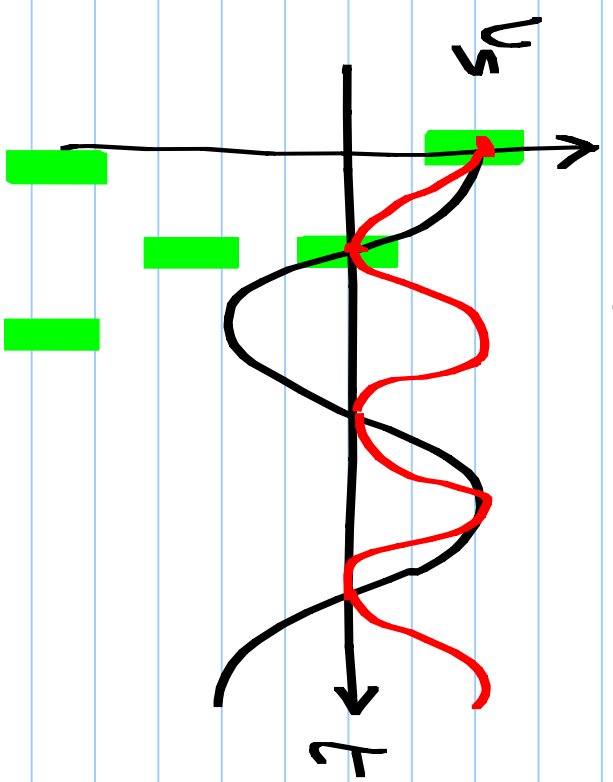
$$p_2(t) = \frac{V_p^2}{2R} (1 - \cos 2\omega t)$$




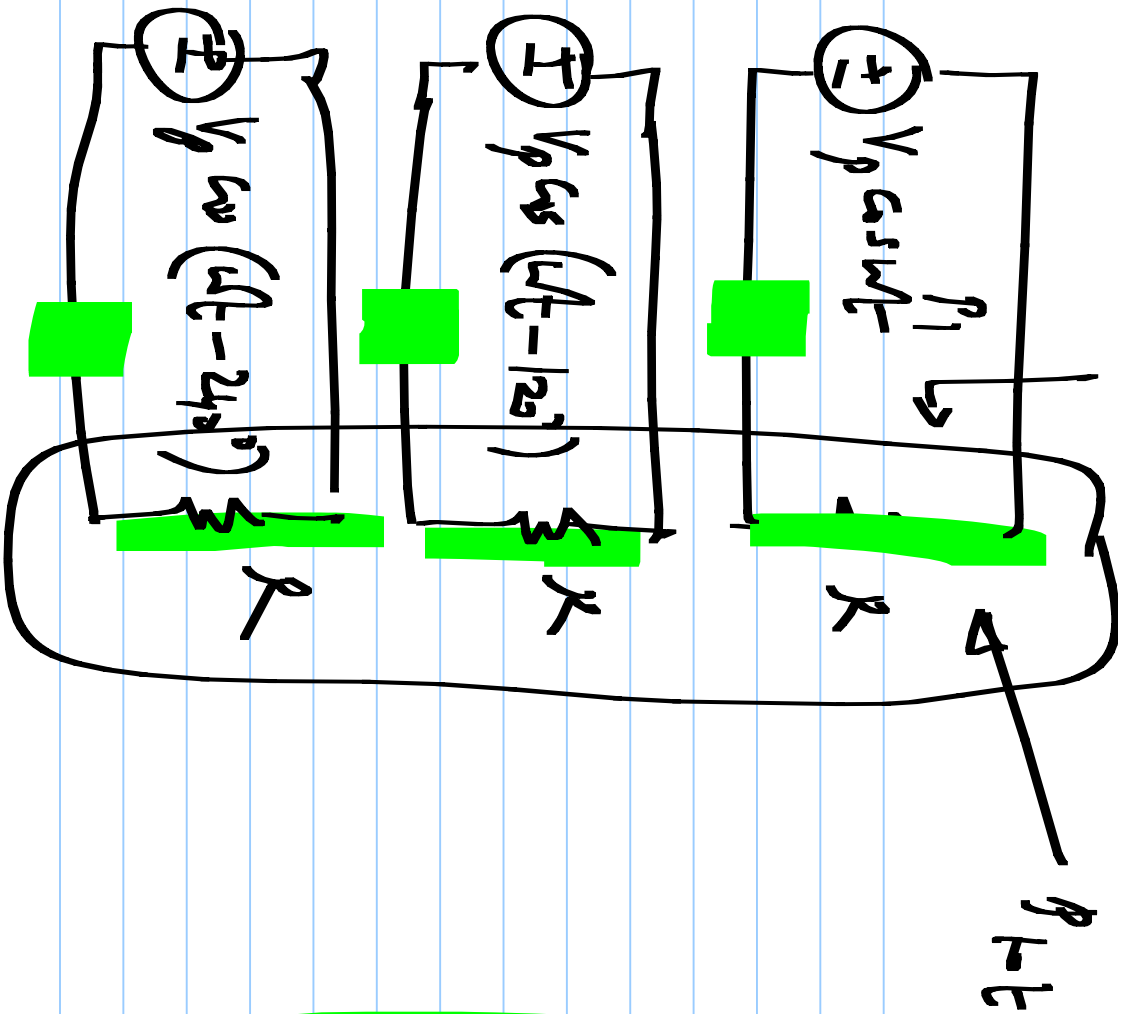



$$P_1 = \frac{V_p^2}{2R} (1 + \cos 240^\circ)$$

$$P_2 = \frac{V_p^2}{2R} (1 + \cos(120^\circ - 240^\circ))$$

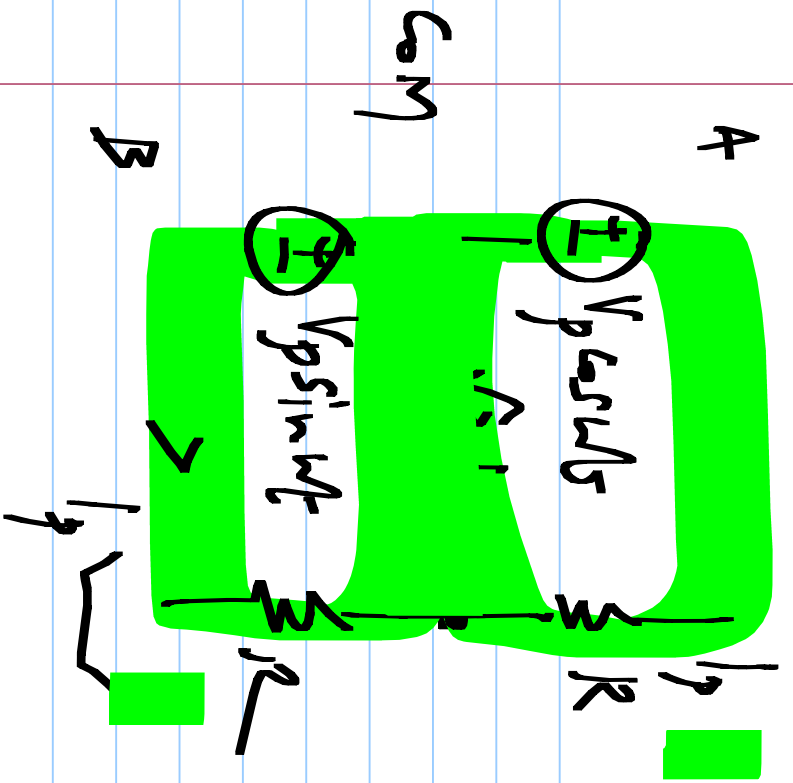
$$P_3 = \frac{V_p^2}{2R} (1 + \cos(240^\circ - 120^\circ))$$



$$P_{avg} = \frac{V_p}{R}$$

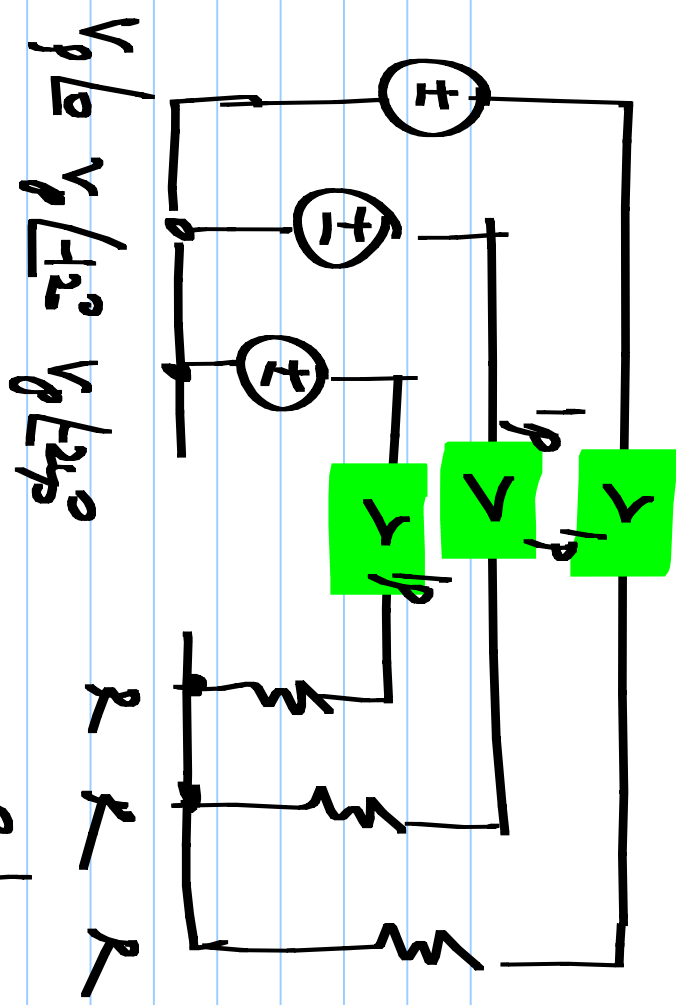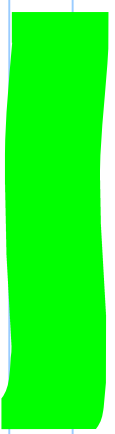


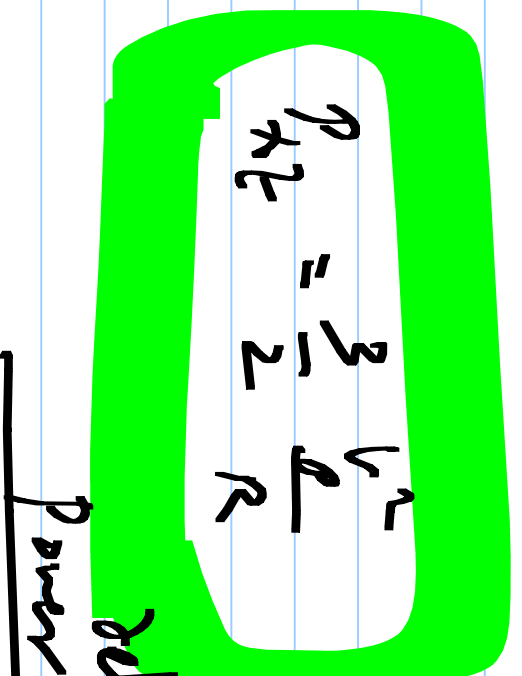
$$P_{avg} = \frac{3}{2} \frac{V_p^2}{R}$$



3 phase system is optimum for delivering power

3. phase system :

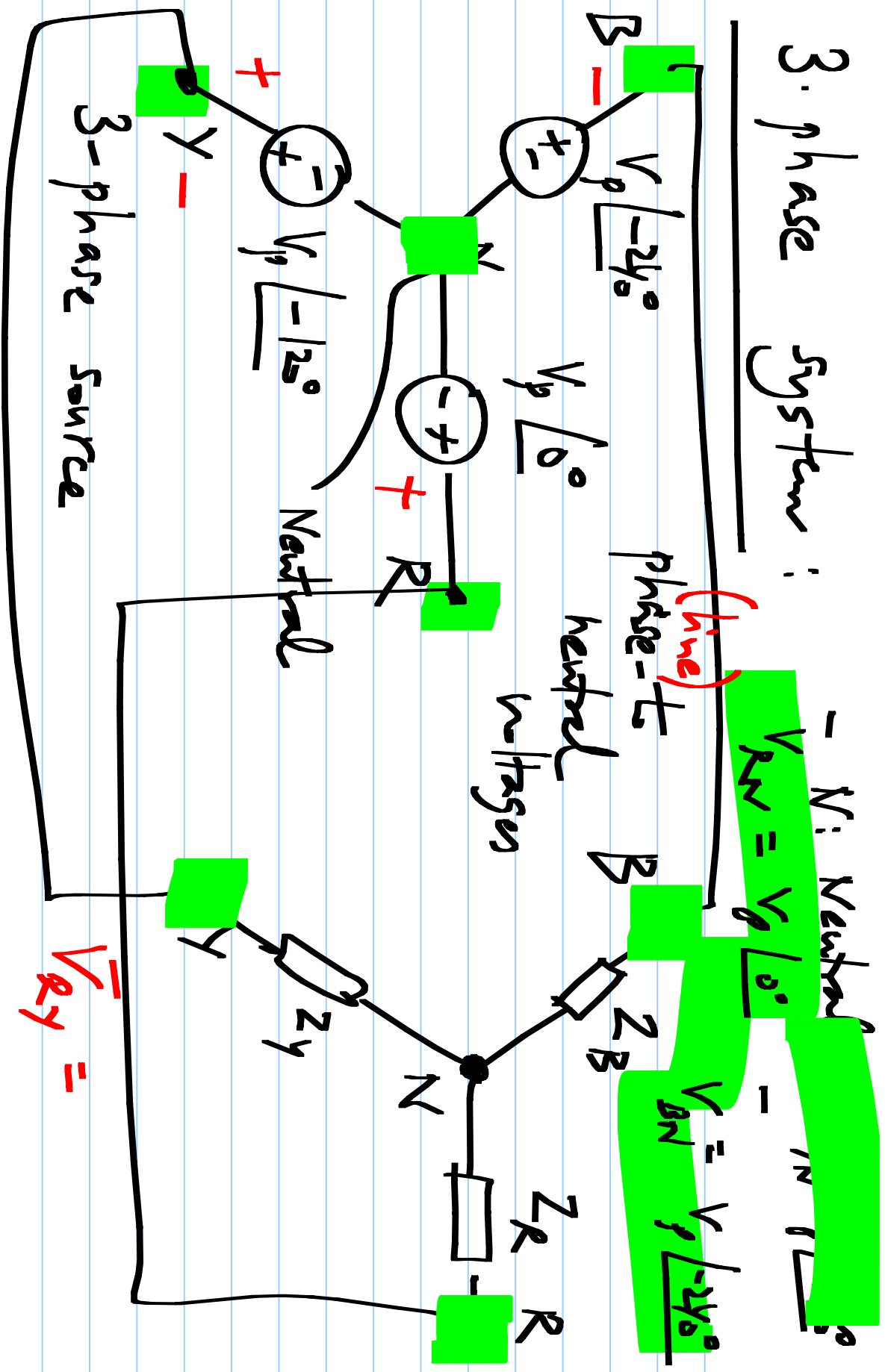

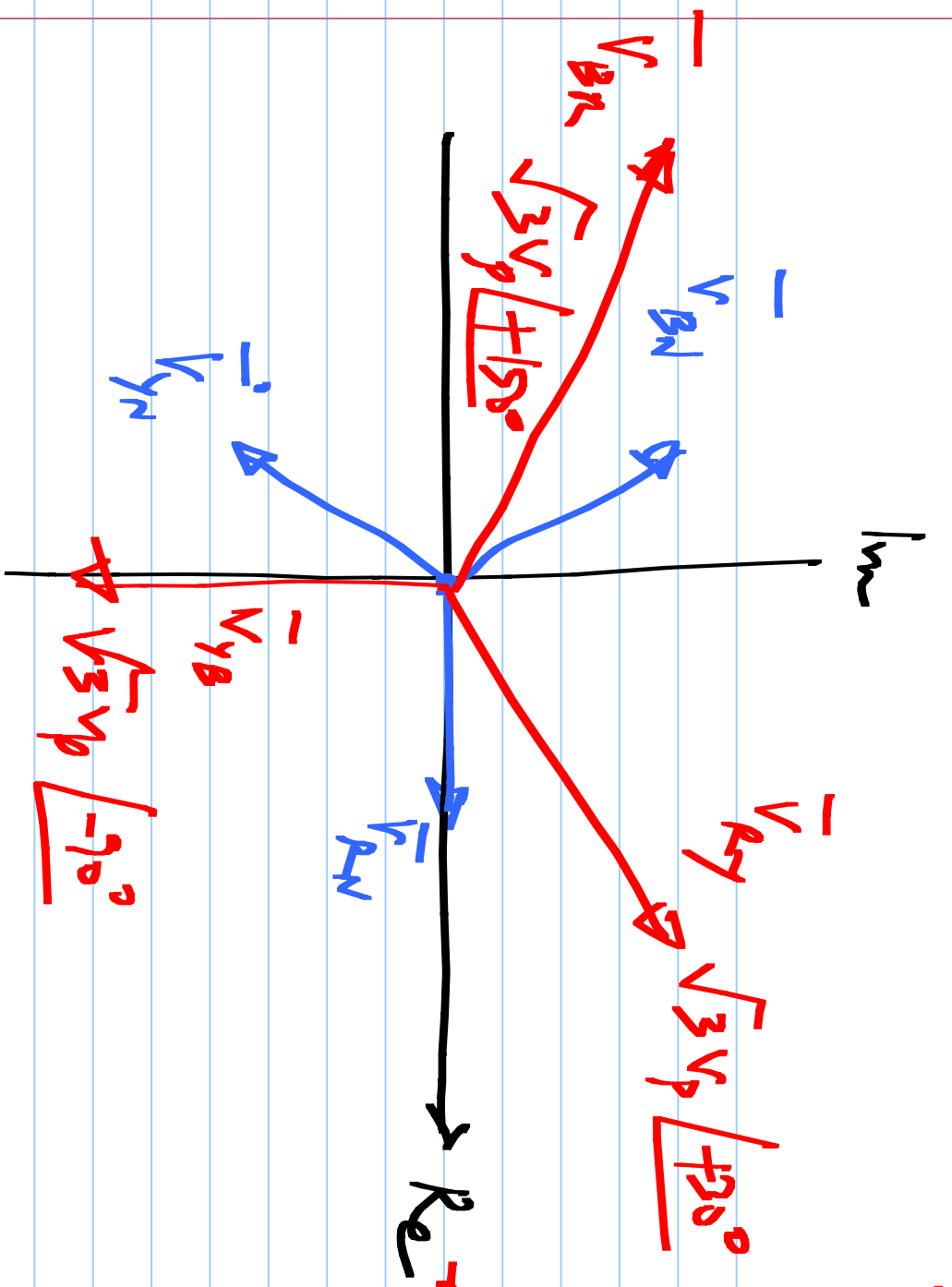

V_{RY}, V_{YB}, V_{BR}

: line-line

voltages


$398V_{rms}$

line-neutral


voltage:

$230V_{rms}$

$230\sqrt{2}V_{peak}$

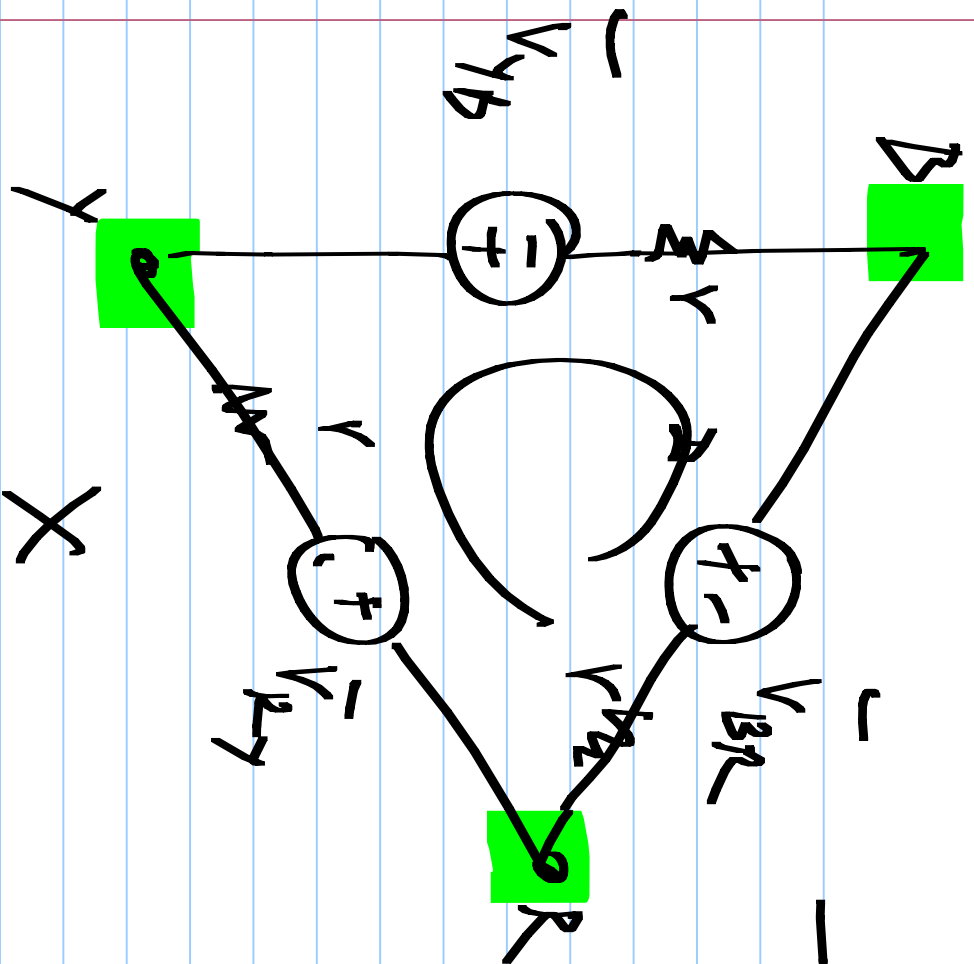

Source:
Balanced source

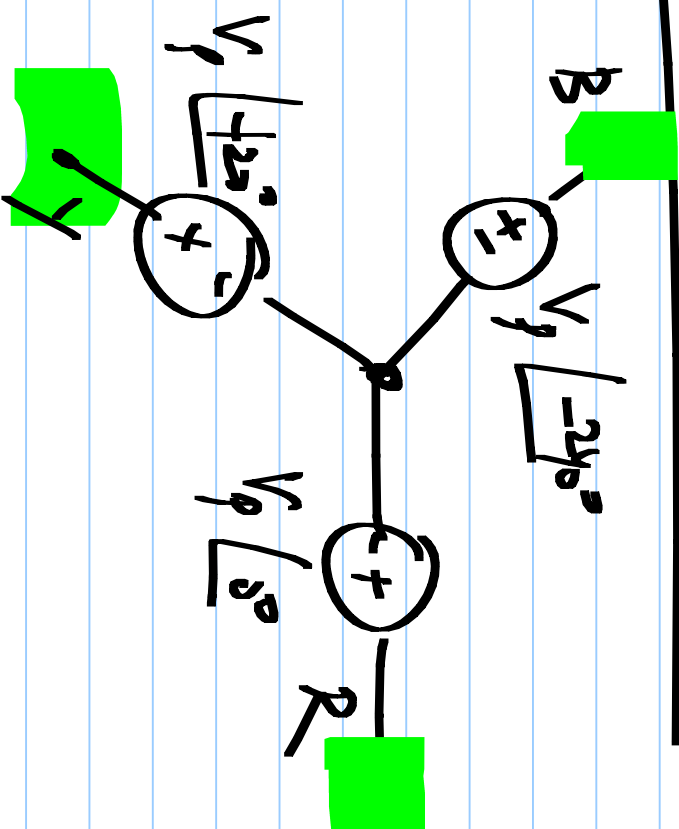


Star connected

(Y)

Load:


Star-connected

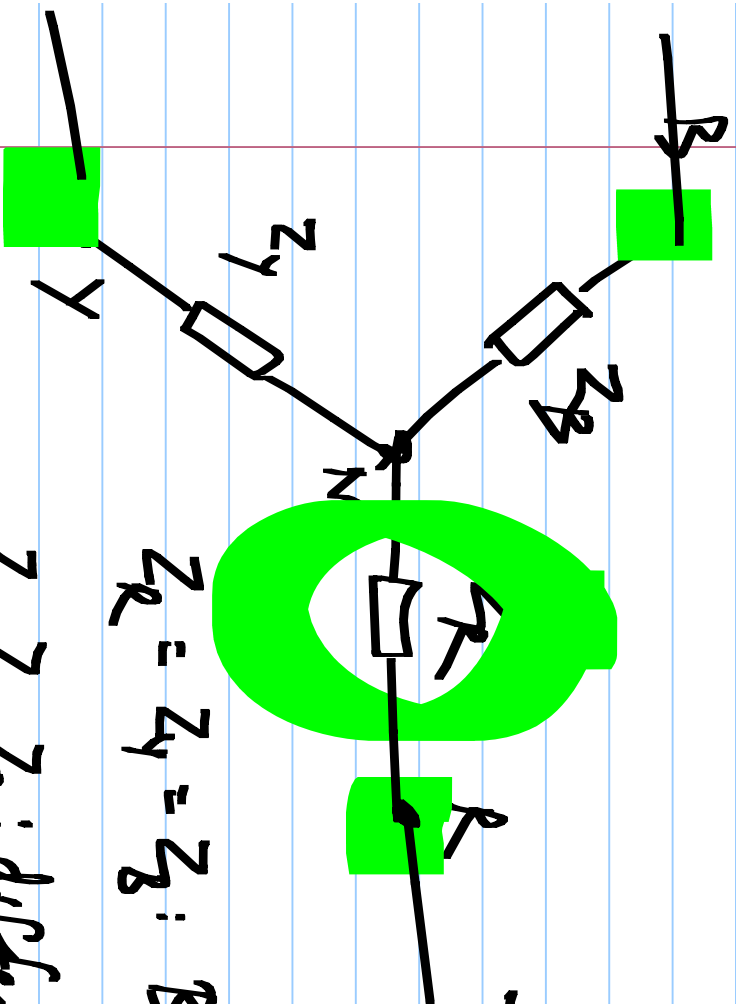

$Z_R = Z_Y = Z_B$: Balanced load

Z_R, Z_Y, Z_B : different: Unbalanced load

Delta connected

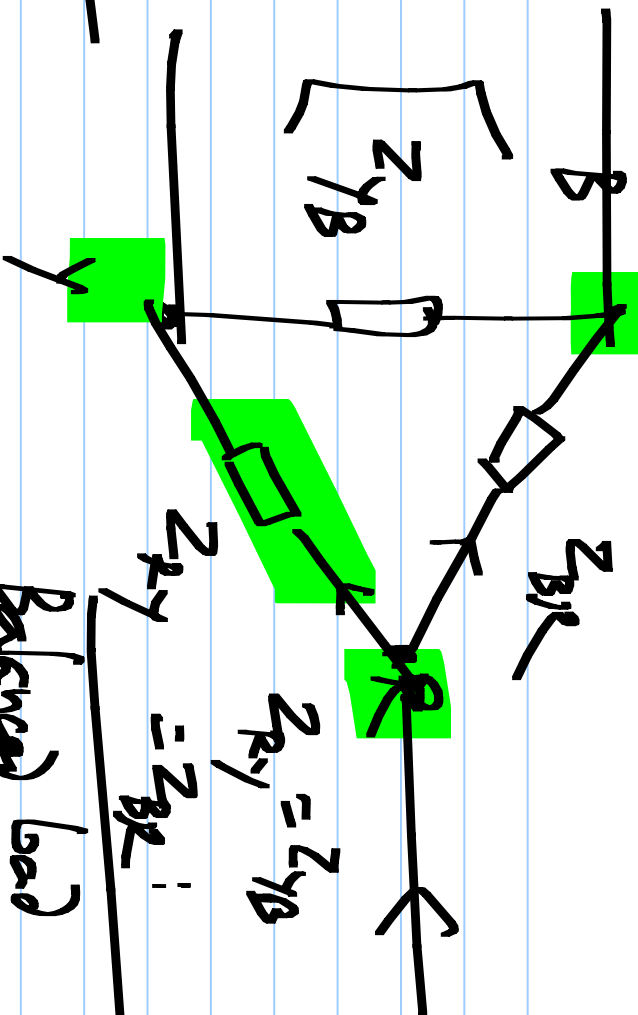

$Z_{RY} = Z_{YB}$


$Z_{RY} = Z_{BR}$!

Balanced load

Unbalanced load

$$Z_R = \frac{Z_{Ry} Z_{BR}}{Z_{Ry} + Z_{BR} + Z_B}$$


$$Z_Y =$$

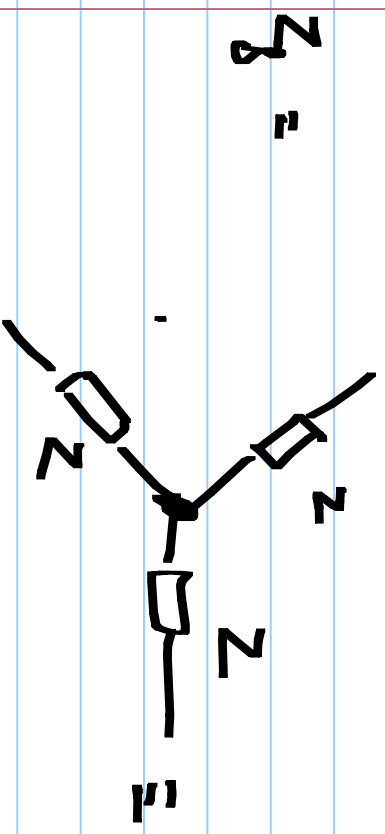



$$Z_{Ry} = \frac{Z_R Z_Y + Z_Y Z_B + Z_B Z_R}{Z_B}$$


$$Z_{YB} =$$

$$Z_{BR} =$$

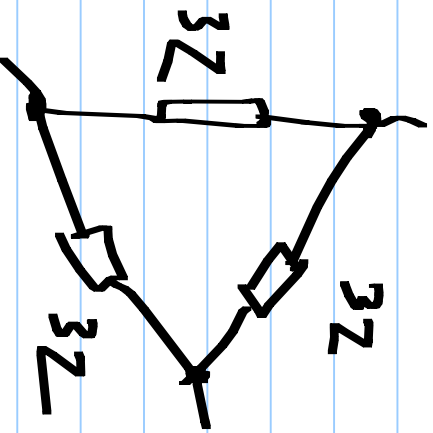

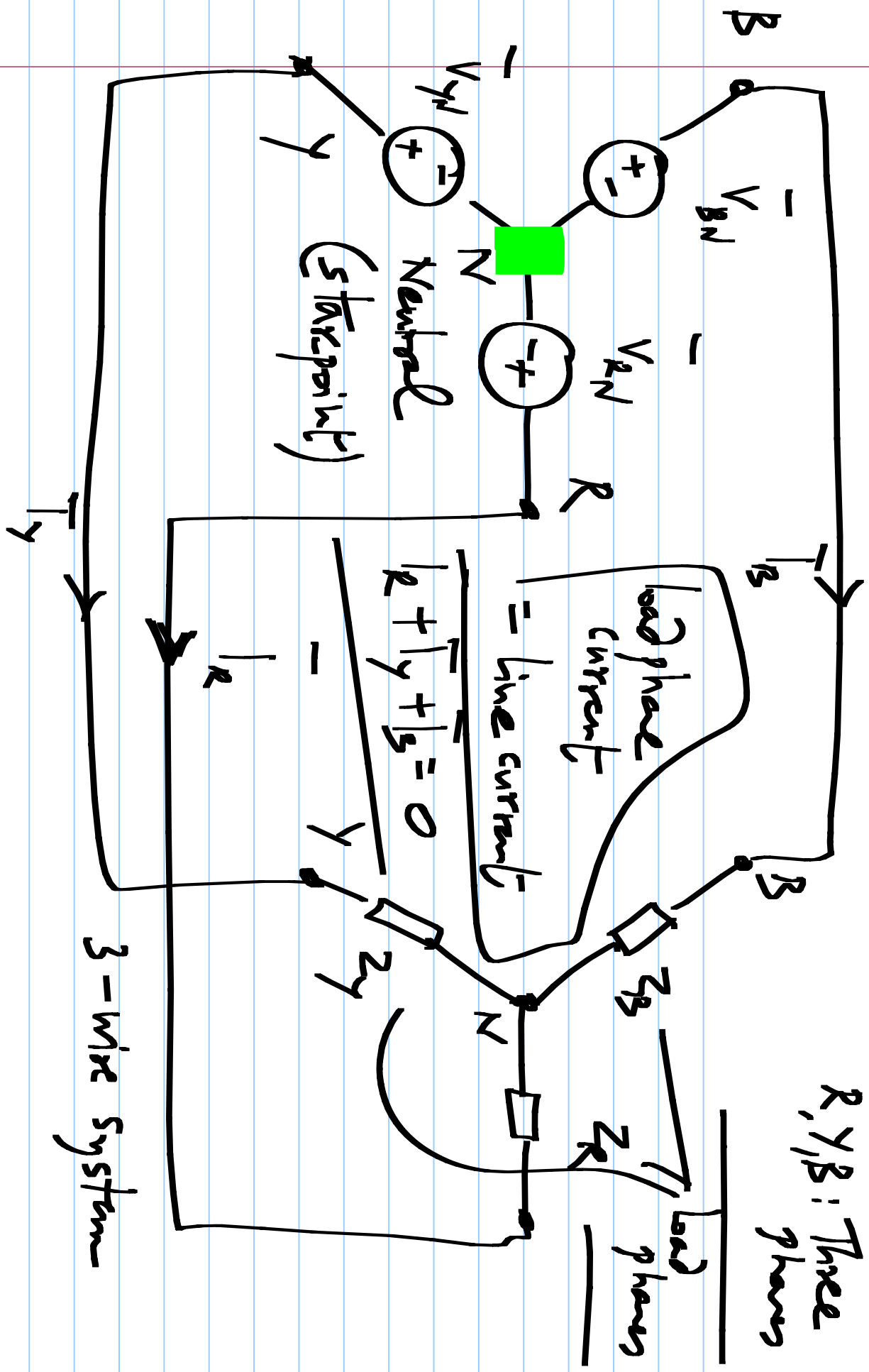

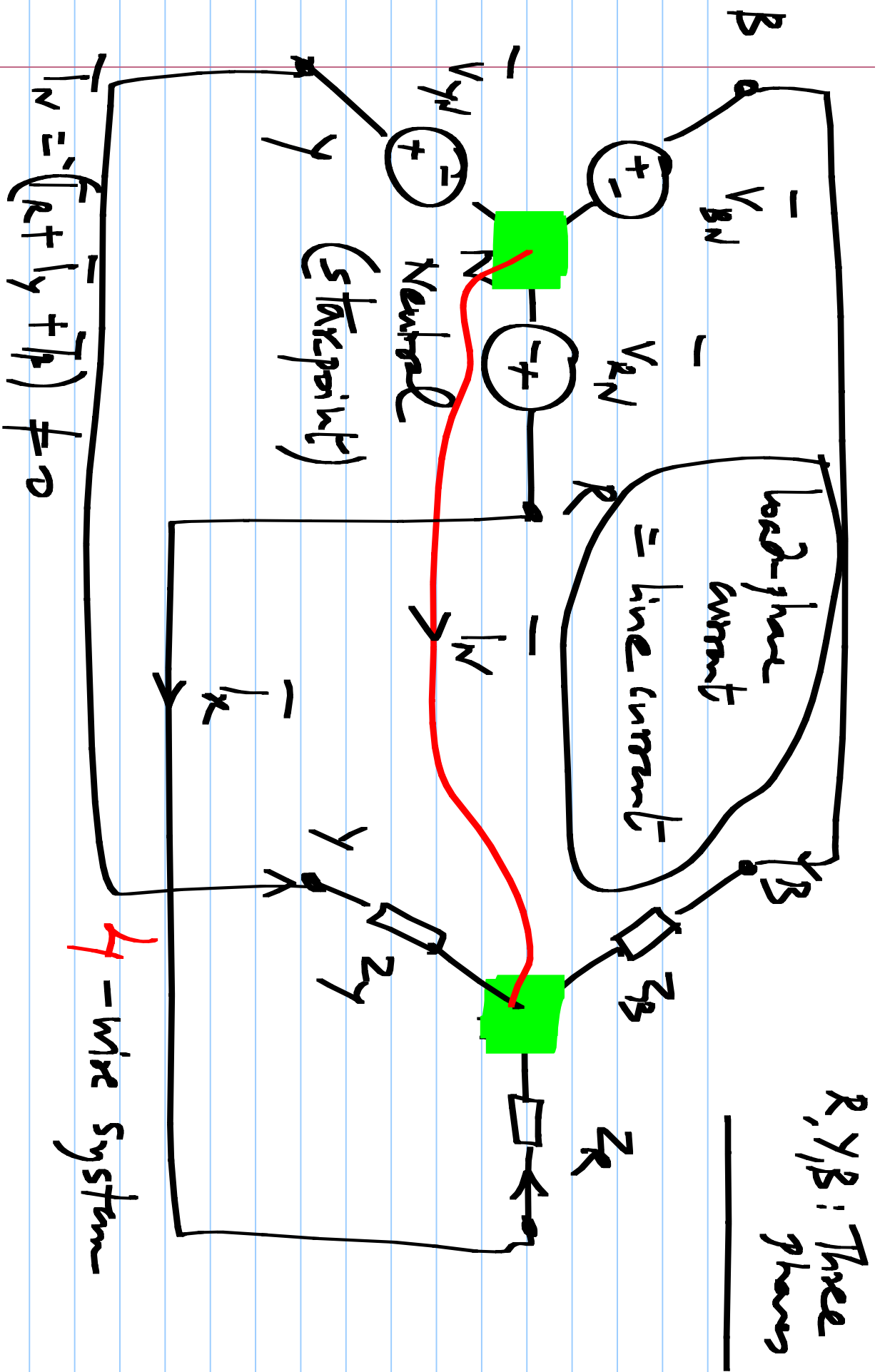


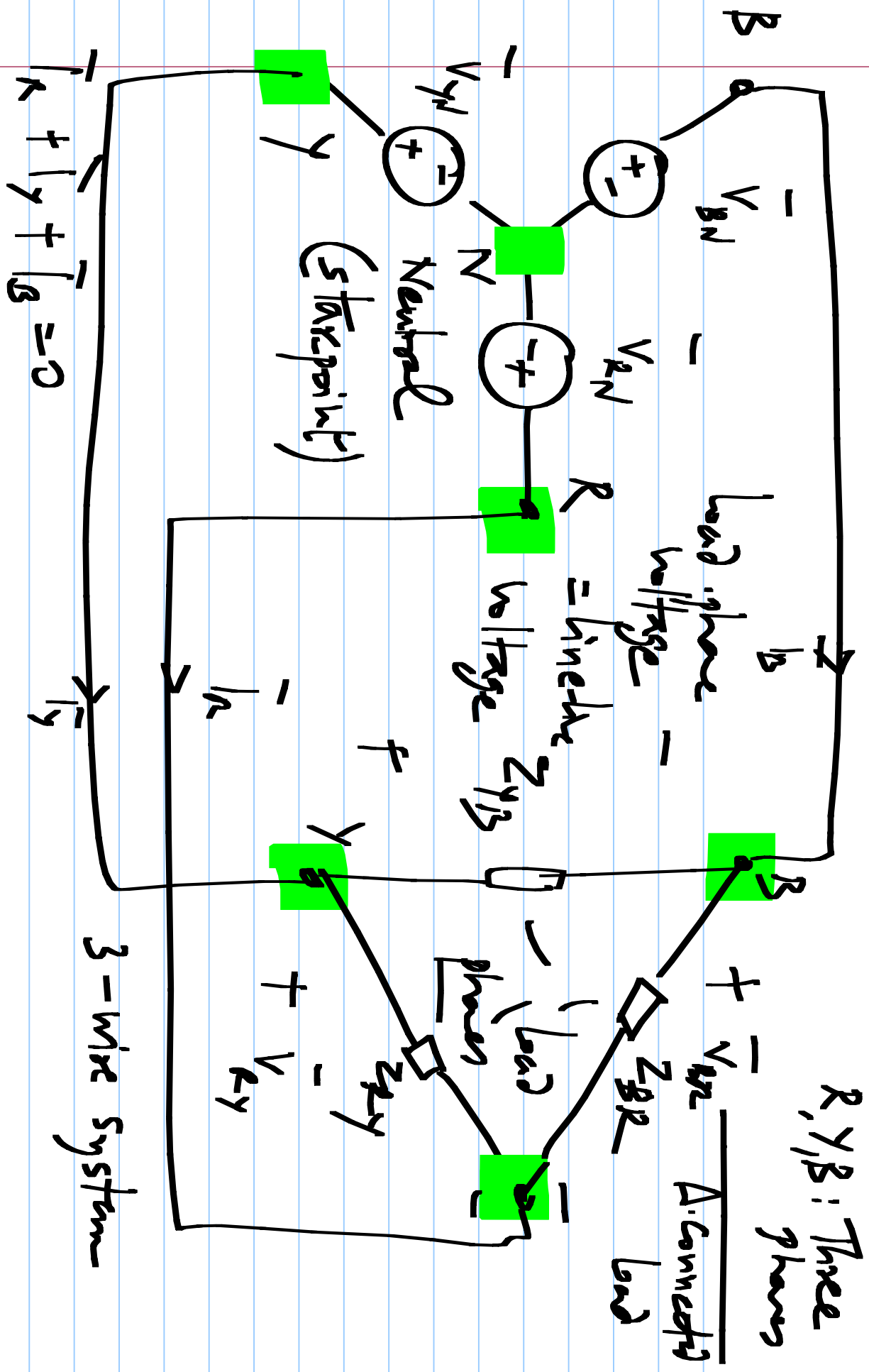


R, Y, B : Three phases

Δ -connected load

3-wire system

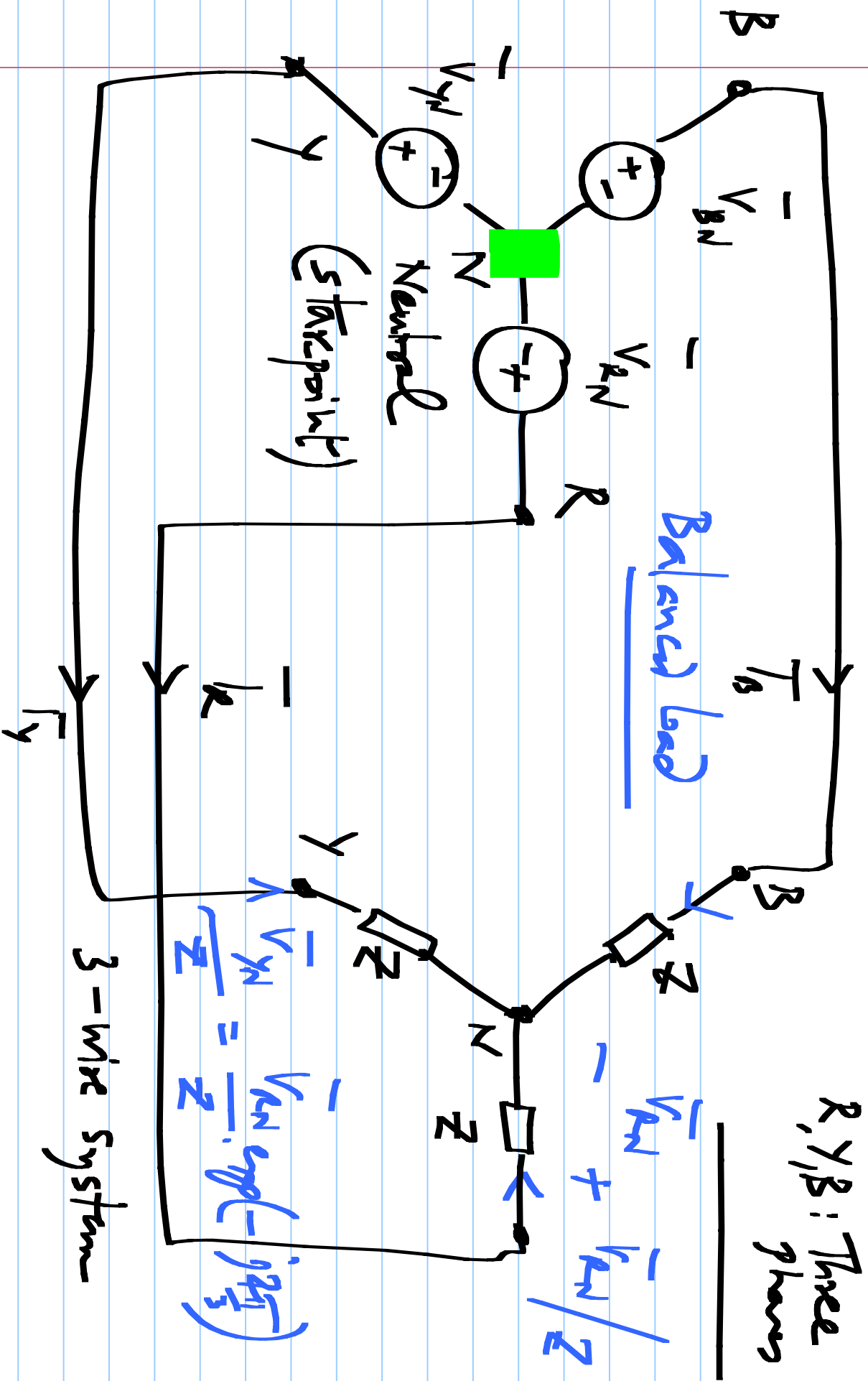

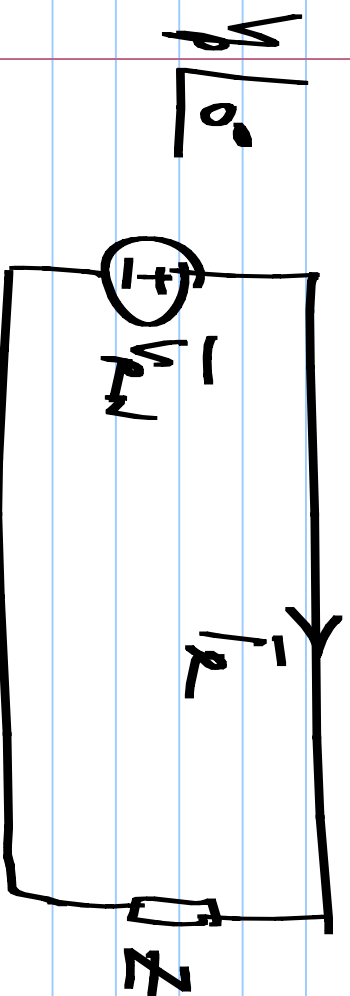
For balanced load: Analyze a single phase



$$\tilde{I}_R = \tilde{V}_R / Z$$

$$\tilde{V}_{RN} = \tilde{V}_R \exp(-j2\pi/3) ; \quad \tilde{V}_{BN} = \tilde{V}_R \exp(-j4\pi/3)$$
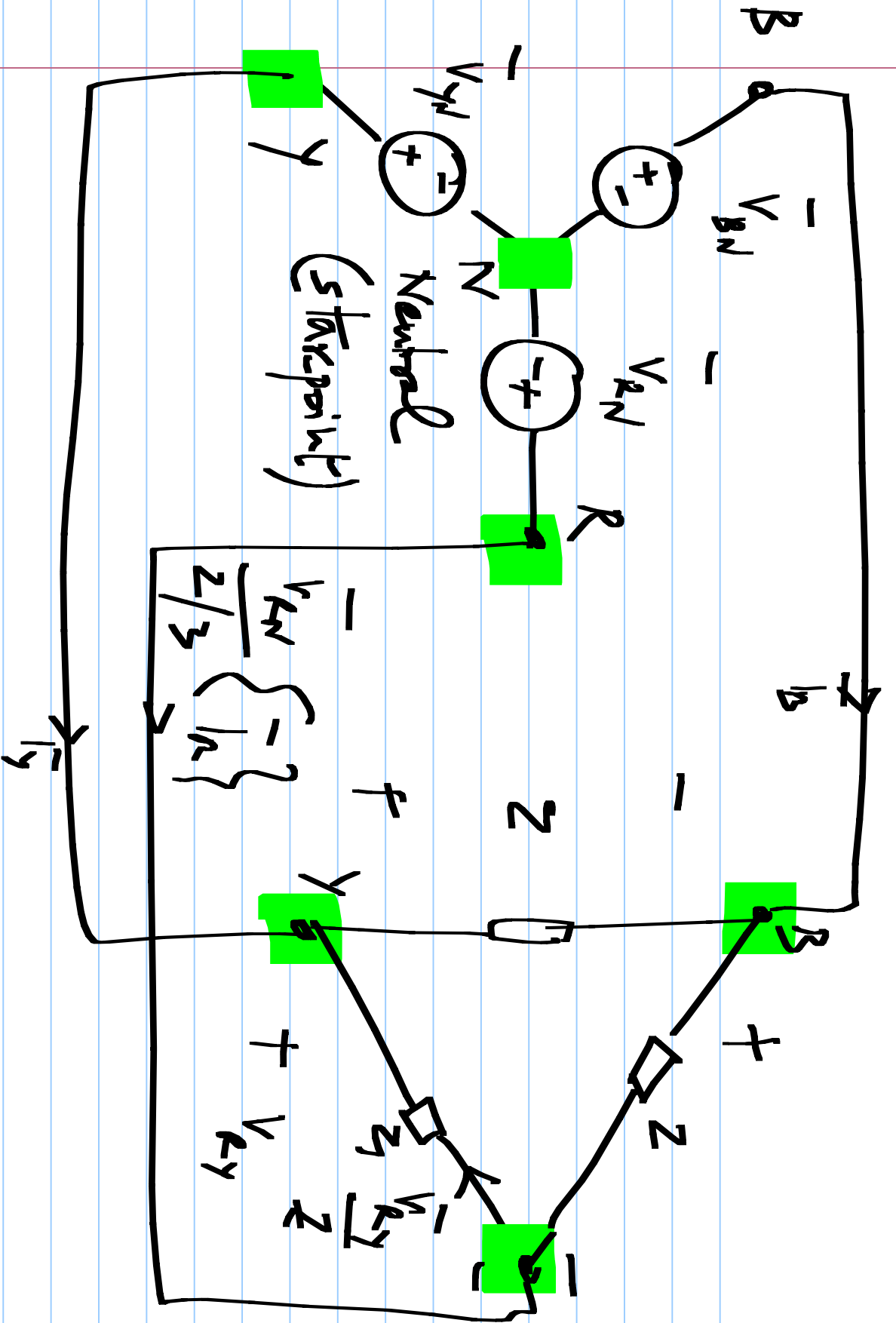
$$\tilde{I}_Y = \tilde{I}_R \exp(-j2\pi/3) ; \quad \tilde{I}_B = \tilde{I}_R \exp(-j4\pi/3)$$



3-phase power transmission in practice

— Constant instantaneous power in rotating machinery

— Efficient (in terms of resources to transmit a given power)

— Balanced source

— Balanced ✓
— Unbalanced