## MOS TRANSISTOR CAPACITANCE.

10 JANUARY 2006

## MOS TRANSISTOR CAPACITANCE.

- Capacitance variations in different operating regions :
  - ♦ In the **TRIODE REGION**  $C_{gs} = C_{gd} = \frac{WLC_{ox}}{2} + C_{ov}W.$
  - ♦ In the **SATURATION REGION**  $C_{gs} = \frac{2}{3}WLC_{ox} + C_{ov}W$  $C_{gd} = C_{ov}W.$
  - ♦ If Transistor is OFF  $C_{gs} = C_{gd} = C_{ov}W$ .
- $\checkmark$  Unity Gain frequency  $f_T$  of MOS transistor

$$I_d(s) = g_m V_{gs}(s) - I_g(s) \frac{C_{gd}}{C_{gd} + C_{gs}}$$
$$V_{gs}(s) = \frac{I_g(s)}{s(C_{as} + C_{ad})}$$



Figure 1: SMALL SIGNAL EQUIVALENT CIRCUIT







Figure 3: TRANSISTOR BIASED IN SATURATION



Figure 4: SMALL SIGNAL EQUIVALENT CIRCUIT

$$\frac{I_d(s)}{I_g(s)} = \frac{g_m - sC_{gd}}{s(C_{gs} + C_{gd})}$$

Since  $C_{gd}$  is small, it is neglected Therefore  $L_{l}(s)$ 

$$\frac{I_d(s)}{I_g(s)} = \frac{g_m}{s(C_{gs} + C_{gd})}$$
$$f_T = \frac{g_m}{2\pi C_{gs}}$$
$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_{th})$$
$$C_{gs} = \frac{2}{3} W L C_{ox}$$
$$f_T = \frac{3}{2} \mu_n \frac{V_{gs} - V_{th}}{L^2}$$



Figure 5: PLOT OF GAIN VERSUS FREQUENCY